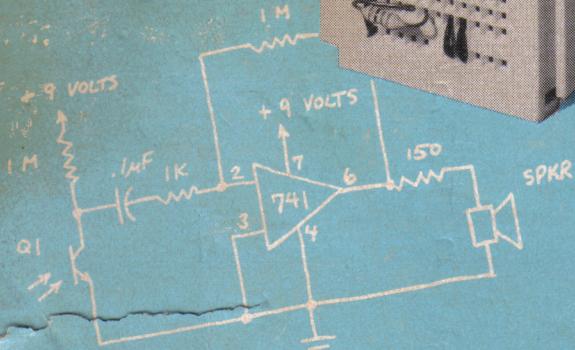



1980 EDITION

Engineer's Notebook


INTEGRATED CIRCUIT APPLICATIONS



PHOTOTRANSISTOR LIGHT RECEIVER

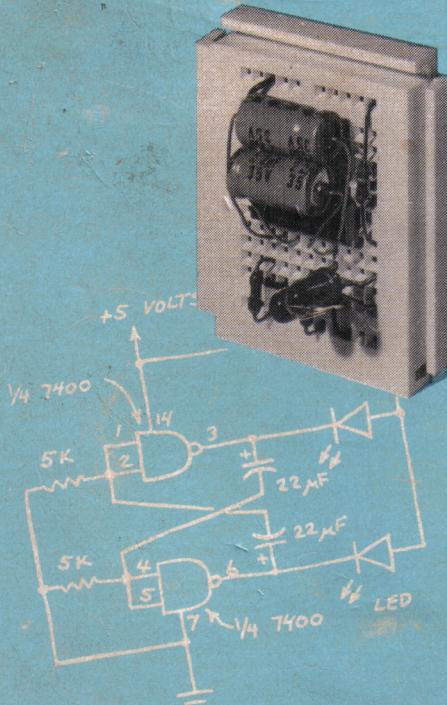


DUAL LED FLASHER

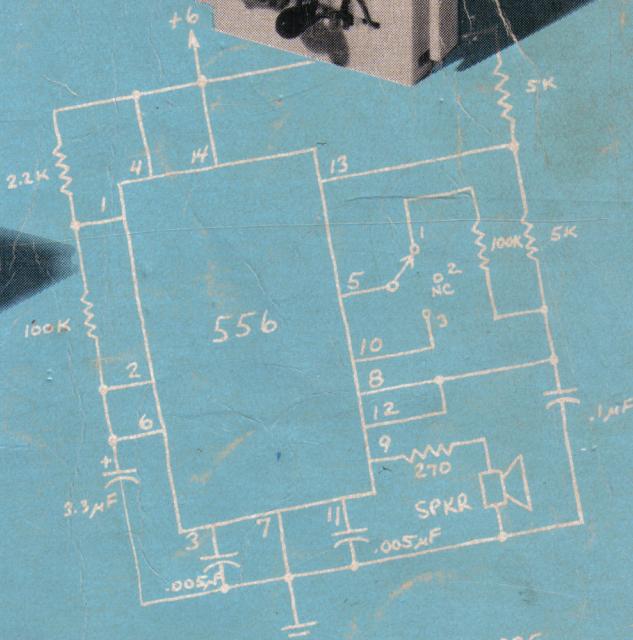

TRI-STATE TONE SOURCE

- 1 - (TWO-TONE)
- 2 - (STEADY)
- 3 - (TONE BURST)

COMMON SCHEMATIC SYMBOLS

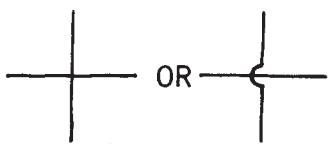


UNCONNECTED
WIRES




CONNECTED
WIRES




GROUND

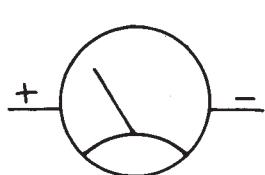


METER

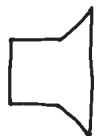

SPEAKER

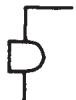

MICROPHONE

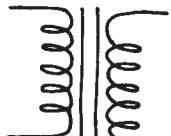


TRANSFORMER




CRYSTAL




SPST TOGGLE
SWITCH

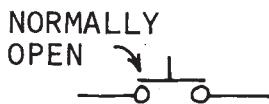

NORMALLY
OPEN
PUSHBUTTON
SWITCH

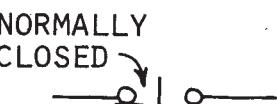

NORMALLY
CLOSED
PUSHBUTTON
SWITCH

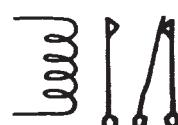


RELAY



RESISTOR



POTENTIOMETER

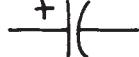

CAPACITOR




VARIABLE
CAPACITOR




DIODE




LIGHT EMITTING
DIODE (LED)

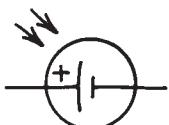


SOLAR CELL

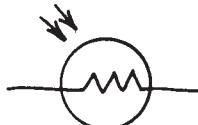


PHOTODIODE

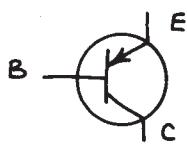

PNP
TRANSISTOR

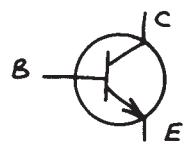

NPN
TRANSISTOR

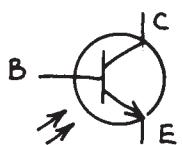

PHOTOTRANSISTOR
(NPN)



LAMP

ENGINEER'S NOTEBOOK

A HANDBOOK OF INTEGRATED CIRCUIT APPLICATIONS

BY

FORREST M. MIMS, III

**CONTRIBUTING EDITOR
POPULAR ELECTRONICS**

FIRST EDITION

SECOND PRINTING--1980

**COPYRIGHT © 1979 BY RADIO SHACK, A DIVISION OF TANDY
CORPORATION. ALL RIGHTS RESERVED. PRINTED IN THE
UNITED STATES OF AMERICA.**

KB3JQQ

READ THIS...

This book is for the entertainment and edification of experimenters and hobbyists. While reasonable care has been exercised with regard to the accuracy of the information in this book, the author and publisher assume no responsibility for errors, omissions or suitability for any application. Neither do we assume any liability for any damages resulting from use of this information. It is your responsibility to determine if use, manufacture or sale of any device incorporating one or more circuits in this book infringes any patents, copyrights or other rights.

Due to the large volume of mail received by Radio Shack and the author, it is impossible to answer letters requesting custom circuit designs, technical advice, troubleshooting assistance, etc. But though we cannot acknowledge individual letters, we will nevertheless be delighted to review carefully your comments, impressions and suggestions about this book. Address your comments to:

Engineer's Notebook
Radio Shack Technical Publications
Dept. DG
1100 One Tandy Center
Fort Worth, TX 76102

Thanks in advance to those who write. And special thanks to Robert Pease, Michael L. Arda, George W. Jehle, B.J. "Stan" Staneslow, Chris Rogers and Desmaret Henri for finding and informing us about a number of errors (all of them minor) in the first printing of this book.

CONTENTS

READ THIS...	2
INTRODUCTION	5
HOW TO USE THIS BOOK	5
REVIEWING THE BASICS	6-9
I. DIGITAL INTEGRATED CIRCUITS	11
A. MOS/CMOS INTEGRATED CIRCUITS (INTRODUCTION)	12-13
GATE PACKAGES	14-21
COMBINATIONAL LOGIC	22-26
SEQUENTIAL LOGIC	27-37
RAMS (MEMORIES)	38-41
MUSIC CHIPS	42-48
B. TTL/LS INTEGRATED CIRCUITS (INTRODUCTION)	51
GATE PACKAGES	52-66
COMBINATIONAL LOGIC	67-73
SEQUENTIAL LOGIC	74-90
II. LINEAR INTEGRATED CIRCUITS (INTRODUCTION)	93
VOLTAGE REGULATORS	94-96
OPERATIONAL AMPLIFIERS	97-107
LED FLASHER	108-109
LED DOT/BAR DISPLAY DRIVER	110-114
TIMERS	115-119
TONE DECODER	120-121
VOLTAGE-TO-FREQUENCY CONVERTER	122-123
VOLTAGE CONTROLLED OSCILLATOR	124
AUDIO AMPLIFIERS	125-127
TEMPERATURE SENSOR/CURRENT SOURCE	128

INTEGRATED CIRCUIT INDEX

TTL/LS

CMOS/MOS

LINEAR

DEVICE	PAGE	DEVICE	PAGE	DEVICE	PAGE
7400/74LS00	52-53	4001	18	555	114-117
7402/74LS02	59	4011	14-15	556	118-119
7404/74LS04	66	4012	17	566	124
7408/74LS08	57	4013	28	567	120-121
74LS10	54	4017	32	723	96
74LS13	62	4020	31	741C	97-100
74LS20	55	4021	30	1458	101
74LS27	60	4023	16	7805	94
74LS30	56	4027	29	7812	94
74LS32	58	4028	26	7815	94
7441	70	4046	36-37	9400	122-123
7447/74LS47	72	4049	20	LF353	102
7448	73	4050	21	LM317	95
74LS51	61	4051	22	LM324	104
7473/74LS73	76	4066	23	LM334	128
7474/74LS74	75	4070	19	LM339	106-107
7475/74LS75	78	4511	24	LM377	127
7476/74LS76	77	4518	33	LM383	126
74LS85	67	4543	25	LM386	125
7490/74LS90	84	MC14553	34-35	LM1877	127
7492/74LS92	85	MM5369	27	LM3900	105
74LS93	86	2102L	38-39	LM3909	108-109
74LS123	74	2114L/4045	40-41	LM3914	110-111
74LS132	63	MM5871	48	LM3915	112-113
74LS151	69	S2688/MM5837	47	TL084	103
74154	71	S50240	46	TDA2002	126
74LS157	68	SAD1024A	44-45		
74LS161	87	SN76477*	42-43		
74LS164	82	SN76478*	42-43		
74LS175	79				
74192/74LS192	88	* I ² L chips.			
74193/74LS193	89				
74LS194	83				
74LS196	90				
74LS367	64				
74LS368	65				
74LS373	80				
74LS374	81				

INTRODUCTION

Though I've kept engineering notebooks for 15 years, the idea for this notebook came from Gary Burkhart, Radio Shack's parts buyer, and Dave Gunzel, manager of Radio Shack's publications division. Gary has long wanted to include in his parts line a no-frills sourcebook of circuits for every Radio Shack IC. He and Dave have invested many hours answering my questions, providing components and technical information and reviewing the circuits. I'm grateful for their assistance.

Unless otherwise acknowledged, the circuits in this notebook are adapted from these sources:

1. Applications information published by the manufacturers of the various ICs.

2. My engineering notebooks.

3. "Experimenter's Corner" and "Project of the Month," two columns I write each month for POPULAR ELECTRONICS magazine.

Many of the circuits were developed specifically for this notebook. I hope you enjoy working with them as much as I have!

Forrest M. Mims, III

HOW TO USE THIS BOOK

To squeeze the maximum number of circuits into this notebook, only essential information is provided. Therefore you will want to use this notebook in conjunction with Radio Shack's "Semiconductor Reference Handbook" and other data books.

For a quickie review of important components and construction tips, read the next few pages. The remainder of the notebook is divided into two major sections: digital and linear. The digital section is further divided into two major IC families: MOS/CMOS and TTL/LS. The chips in each section are organized according to function, not numerical sequence.

Though most circuits in this book can function on their own,

consider them as building blocks you can connect to other circuits to accomplish new applications. Experiment! Change resistors and capacitors in RC circuits to alter frequencies and timing. Add new functions. Above all, work with as many different chips as you can. If you've always used TTL, you'll be impressed with the operating flexibility of CMOS. If your forte is digital logic, you'll be amazed at what you can do with an op-amp. Finally, keep a record of your experiments and circuit designs. A notebook with a grid ruling like this one is best, but a 50¢ spiral notebook is OK.

For beginners only....Be sure to read the next few pages! Begin with simple chips (gate packages, timers, op-amps, etc.), and you'll soon be ready for more advanced circuits and projects. Good luck!

REVIEWING THE BASICS

INTRODUCTION

"Can I use a 0.22 uF capacitor instead of a 0.10 uF unit?"

"Is it OK to substitute a 12,000 ohm resistor for a 10,000 ohm unit?"

This section will tackle these common questions and many others. Master them, and you will be well prepared to tackle the circuits in this book!


RESISTORS

Resistors limit the flow of electrical current. A resistor has a resistance (R) of 1 ohm if a current (I) of 1 ampere flows through it when a potential difference (E) of 1 volt is placed across it. In other words:

$$R = \frac{E}{I} \text{ (or) } I = \frac{E}{R} \text{ (or) } E = IR$$

These handy formulas form Ohm's law. Memorize them! You'll use them often.

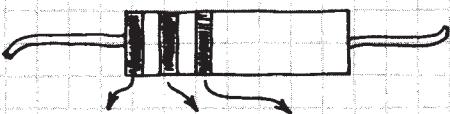Resistors are identified by a color code:



COLOR	1	2	3 (Multiplier)	
BLACK	0	0		1
BROWN	1	1		10
RED	2	2		100
ORANGE	3	3		1000
YELLOW	4	4		10,000
GREEN	5	5		100,000
BLUE	6	6		1,000,000
VIOLET	7	7		10,000,000
GRAY	8	8		100,000,000
WHITE	9	9		(none)

A fourth color band may be present. It specifies the tolerance of the resistor. Gold is $\pm 5\%$ and silver is $\pm 10\%$. No fourth band means $\pm 20\%$.

Since no resistor has a perfect tolerance, it's often OK to substitute resistors. For example, it's almost always OK to use a 1.8K resistor in place of a 2.0K unit. Just try to stay within 10-20% of the specified value.

What does K mean? It's short for 1,000. 20K means $20 \times 1,000$ or 20,000 ohms. M is short for meg-ohm or 1,000,000 ohms. Therefore a 2.2M resistor has a resistance of 2,200,000 ohms.

Resistors which resist lots of current must be able to dissipate the heat that's produced. Always use resistors with the specified power rating! No power rating specified? Then it's usually OK to use 1/4 or 1/2 watt units.


Almost every electronic circuit uses resistors. Here are three of the most important applications for resistors:

1. Limit current to LEDs, transistors, speakers, etc.

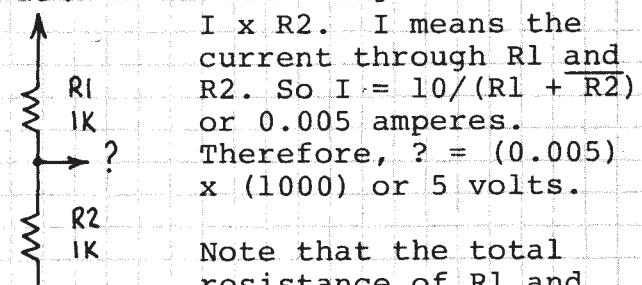2. Voltage division. For instance:


+10V

The voltage at ? is $I \times R_2$. I means the current through R_1 and R_2 . So $I = 10 / (R_1 + R_2)$ or 0.005 amperes. Therefore, $? = (0.005) \times (1000)$ or 5 volts.




Note that the total resistance of R_1 and R_2 is simply $R_1 + R_2$. This rule provides a handy trick for making custom resistances.

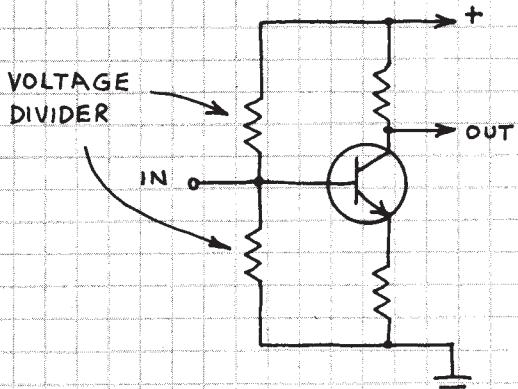Voltage dividers are used to bias transistors:



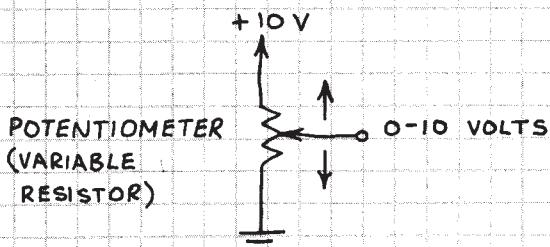They're also a convenient source of variable voltage:



And they're useful in voltage sensing circuits. See the comparator circuits in this notebook.

3. They control the charging time of capacitors. Read on...

CAPACITORS

Capacitors store electrical energy and block the flow of direct current while passing alternating current. Capacitance is specified in farads. One farad represents a huge capacitance so most capacitors have values of small fractions of a farad:

$$1 \text{ microfarad (uF)} = 10^{-6} \text{ farad}$$

$$1 \text{ picofarad (pF)} = 10^{-12} \text{ farad}$$


or

$$1 \text{ uF} = 1,000,000 \text{ pF}$$

The value of a capacitor is usually printed on the component. The uF and pF designations may not be present. Small ones marked 1-1000 are rated in pF; larger ones

marked .001-1000 are rated in uF.

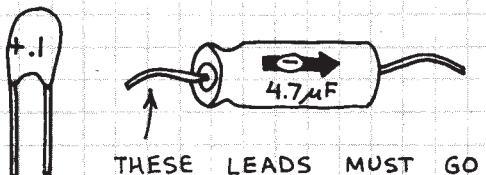Electrolytic capacitors provide high capacity in a small space. Their leads are polarized and must be connected into a circuit in the proper direction.




Capacitors have a voltage rating. It's usually printed under the capacity marking. The voltage rating must be higher than the highest expected voltage (usually the power supply voltage).

Caution: A capacitor can store a charge for a considerable time after power is removed. This charge can be dangerous! A large electrolytic capacitor charged to only 5 or 10 volts can melt the tip of a screwdriver placed across its leads! High voltage capacitors can store a lethal charge! Discharge a capacitor by carefully placing a resistor (1K or more; use Ohm's law) across its leads. Use only one hand to prevent touching both leads of the capacitor.

Important capacitor applications:

1. Remove power supply spikes. (Place 0.01-0.1 uF across power supply pins of digital ICs. Stops false triggering.)

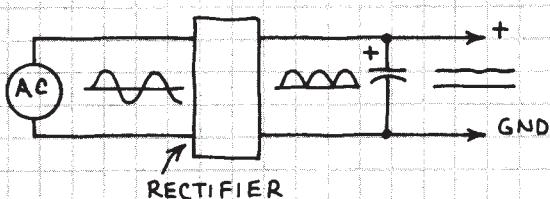2. Smooth rectified AC voltage into steady DC voltage. (Place 100-10,000 uF across rectifier output.)




3. Block DC signal while passing AC signal.


4. Bypass AC signal around a circuit or to ground.

5. Filter out unwanted portions of a fluctuating signal.

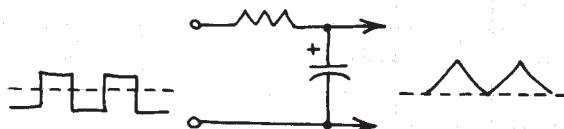
6. Use with resistor to integrate a fluctuating signal:



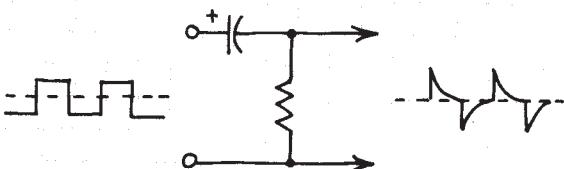7. Or to differentiate a fluctuating signal:



8. Perform a timing function:

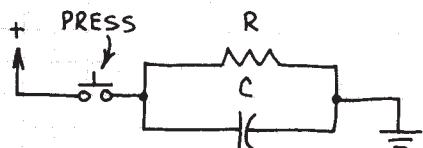

C will quickly charge...then slowly discharge through R.

9. Store a charge to keep a transistor turned off or on.

10. Store a charge to be dumped through a flashtube or LED in a fast and powerful pulse.

Can you substitute capacitors? In most cases changing the value of a capacitor 10% or even 100% will not cause a malfunction, but circuit operation may be affected. In a timing circuit, for example, increasing the value of the timing capacitor will increase the timing period. Changing the capacitors in a filter will change the filter's frequency response. Be sure to use the proper voltage rating. And don't worry about the difference between 0.47 and 0.5 uF.

SEMICONDUCTORS

Usually made from silicon. Be sure to observe all operating restrictions. Brief descriptions of important semiconductor devices:


DIODES

Permit current to flow in but one direction (forward bias). Used to rectify AC, allow current to flow into a circuit but block its return, etc.



ZENER DIODES

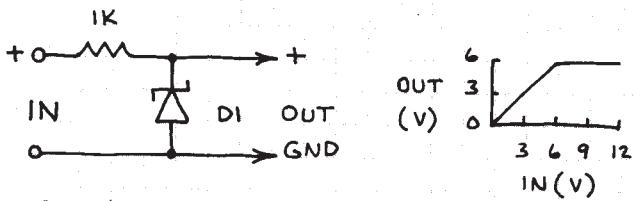
The zener diode is a voltage regulator. In this typical circuit, voltage exceeding the diode's breakdown voltage is shunted to ground:



Zeners can also protect voltage sensitive components and provide a convenient reference voltage.

LIGHT EMITTING DIODES

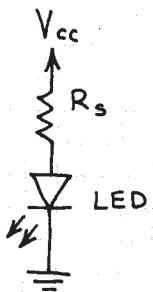LEDs emit green, yellow, red or infrared when forward biased. A series resistor should be used to limit current to less than the maximum allowed:



$$R_s = \frac{V_{CC} - V_{LED}}{LED_I}$$

Example: V_{LED} of red LED is 1.7 volts. For a forward current (LED_I) of 20 mA at $V_{CC} = 5$ volts, $R = 330$ ohms. Don't exceed LED_I !!


Infrared LEDs are much more powerful than visible LEDs, but their radiation is totally invisible. Use them for object detectors and communicators.

TRANSISTORS


In this notebook, transistors are used as simple amplifiers and switches that turn on LEDs. Any general purpose switching transistors will work.

INTEGRATED CIRCUITS

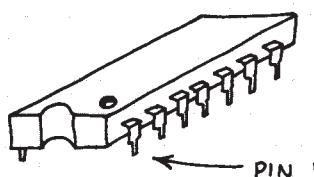Since an IC is a complete circuit on a silicon chip, you must observe all operating restrictions. Reversed polarity, excessive supply voltage and sourcing or sinking too much current can destroy an IC. Be sure to pay close attention to the location of the power supply pins! Most ICs are packaged in 8, 14 or 16 pin plastic DIPs (Dual In-line Packages). A notch or circle is near pin 1:




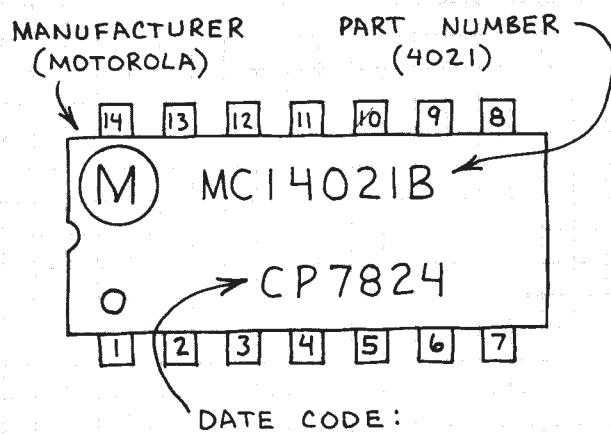When the IC is right side up, pin 1 is at lower left:



78 = 1978
24 = 24th WEEK

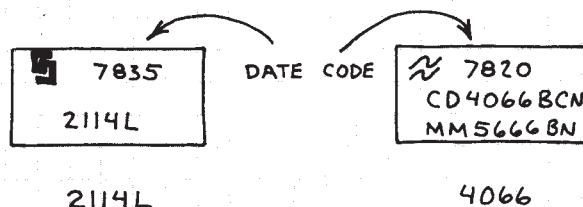Incidentally, a date code may not be present, but other numbers may be...and the date code is not always below the device number:



Store ICs in a plastic cabinet if you can afford one. Or insert them in rows in a styrofoam tray (the kind used for meat in a grocery store). CAUTION: Never store MOS/CMOS ICs in ordinary non-conductive plastic. See p. 12.

CIRCUIT BUILDING

Build your circuits on a solderless breadboard to make changes and find bugs. Then make permanent versions. Radio Shack plastic modular sockets (276-173, etc.) are ideal. They include two socket rows for power supply connections and snap rails for attaching sockets together. Parts and wires can be inserted directly into the holes in the socket.

For permanent circuits, use Radio Shack PC boards. Catalog numbers 276-024 and 276-151 are ideal for simple IC projects. Use larger universal PC boards for more complex projects (276-152 & 276-157). You can cut them into smaller sections with a nibbler tool or small saw.

I prefer to use wrapping wire for IC projects. Insert wrapping sockets in board and make connections with a Wire-Wrapping tool (such as 276-1570). Apply wrapping wire directly to leads of transistors, resistors, etc. and solder in place.



NOTES

DIGITAL INTEGRATED CIRCUITS

INTRODUCTION

DIGITAL ICs ARE 2-STATE DEVICES. ONE STATE IS NEAR 0 VOLTS OR GROUND (LOW OR L) AND THE OTHER IS NEAR THE IC'S SUPPLY VOLTAGE (HIGH OR H). SUBSTITUTE 0 FOR L AND 1 FOR H AND DIGITAL ICs CAN PROCESS INDIVIDUAL BINARY DIGITS (BITS) OR MULTIPLE BIT WORDS. A 4-BIT WORD IS A NIBBLE AND AN 8-BIT WORD IS A BYTE.

THE BINARY SYSTEM

IT'S VERY HELPFUL TO KNOW THE FIRST 16 BINARY NUMBERS. IF 0=L AND 1=H, THEY ARE:

KEY	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0 - LLLL	0	8 - HLLL	8													
1 - LLHL	1	9 - HLLH	9													
2 - LHLH	2	10 - HLHL	A													
3 - LLHH	3	11 - HLHH	B													
4 - LHLL	4	12 - HHLL	C													
5 - LHLH	5	13 - HHHL	D													
6 - LHHL	6	14 - HHHL	E													
7 - LHHH	7	15 - HHHH	F													

NOTE THAT LLLL(0) IS AS MUCH A NUMBER AS ANY OTHER NUMBER.

LOGIC GATES

LOGIC CIRCUITS ARE MADE BY INTER-CONNECTING TWO OR MORE OF THESE BASIC LOGIC GATES:




AND

A	B	OUT
L	L	L
L	H	L
H	L	L
H	H	H



NAND

A	B	OUT
L	L	H
L	H	H
H	L	H
H	H	L

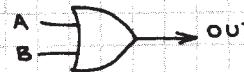


OR

A	B	OUT
L	L	L
L	H	H
H	L	H
H	H	H



NOR

A	B	OUT
L	L	H
L	H	L
H	L	L
H	H	L

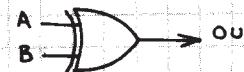

EXCLUSIVE-OR

A	B	OUT
L	L	L
L	H	H
H	L	H
H	H	L



EXCLUSIVE-NOR

A	B	OUT
L	L	H
L	H	L
H	L	L
H	H	H



YES (BUFFER)

A	OUT
L	L
H	H



NOT (INVERTER)

A	OUT
L	H
H	L

3-STATE LOGIC



CONTROL	A	OUT
L	L	L
L	H	H
H	X	HI-Z




CONTROL	A	OUT
L	L	H
L	H	L

HI-Z: OUTPUT IN HIGH IMPEDANCE STATE.

MOS/CMOS INTEGRATED CIRCUITS

INTRODUCTION

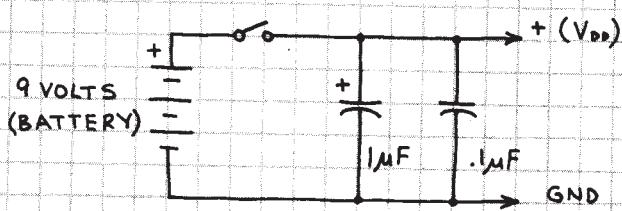MOS ICS CAN CONTAIN MORE FUNCTIONS PER CHIP THAN TTL/LS AND ARE VERY EASY TO USE. MOST CHIPS IN THIS SECTION ARE CMOS (COMPLEMENTARY MOS). THEY CONSUME VERY LITTLE POWER AND OPERATE OVER A +3-15 VOLT RANGE. CMOS CAN BE POWERED BY THIS:



OR YOU CAN USE A LINE POWERED SUPPLY MADE FROM A 7805/7812/7815. SEE THE LINEAR SECTION.


INCIDENTALLY, YOU CAN POWER A CMOS CIRCUIT FROM TWO SERIES CONNECTED PENLIGHT CELLS, BUT A 9-12 VOLT SUPPLY WILL GIVE BETTER PERFORMANCE.

OPERATING REQUIREMENTS

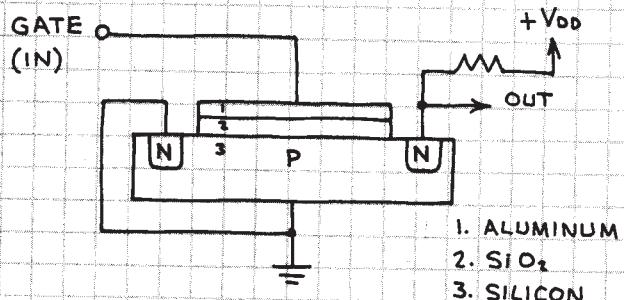
1. THE INPUT VOLTAGE SHOULD NOT EXCEED V_{DD} ! (TWO EXCEPTIONS: THE 4049 AND 4050.)
2. AVOID, IF POSSIBLE, SLOWLY RISING AND FALLING INPUT SIGNALS SINCE THEY CAN CAUSE EXCESSIVE POWER CONSUMPTION. RISETIMES FASTER THAN 15 MICROSECONDS ARE BEST.
3. ALL UNUSED INPUTS MUST BE CONNECTED TO V_{DD} (+) OR V_{SS} (GND). OTHERWISE ERRATIC CHIP BEHAVIOR AND EXCESSIVE CURRENT CONSUMPTION WILL OCCUR.
4. NEVER CONNECT AN INPUT SIGNAL TO A CMOS CIRCUIT WHEN THE POWER IS OFF.
5. OBSERVE HANDLING PRECAUTIONS.

HANDLING PRECAUTIONS

A CMOS CHIP IS MADE FROM PMOS AND NMOS TRANSISTORS. MOS MEANS METAL-OXIDE-SILICON (OR SEMICONDUCTOR). P AND N REFER TO POSITIVE AND NEGATIVE CHANNEL MOS TRANSISTORS. AN NMOS TRANSISTOR LOOKS LIKE THIS:



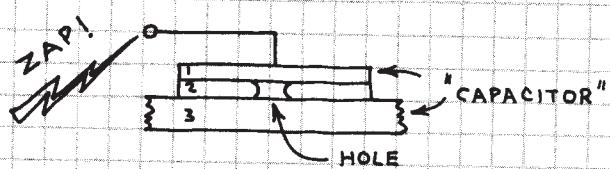A PMOS TRANSISTOR IS IDENTICAL EXCEPT THE P AND N REGIONS ARE EXCHANGED. THE SiO_2 (SILICON DIOXIDE) LAYER IS A GLASSY FILM THAT SEPARATES AND INSULATES THE METAL GATE FROM THE SILICON SUBSTRATE. THIS FILM IS WHY A MOS TRANSISTOR OR IC PLACES PRACTICALLY NO LOAD ON THE SOURCE OF AN INPUT SIGNAL. THE FILM IS VERY THIN AND IS THEREFORE EASILY PUNCTURED BY STATIC ELECTRICITY:





PREVENT STATIC DISCHARGE!



1. NEVER STORE MOS IC'S IN NONCONDUCTIVE PLASTIC "SNOW," TRAYS, BAGS OR FOAM.
2. PLACE MOS IC'S PINS DOWN ON AN ALUMINUM FOIL SHEET OR TRAY WHEN THEY ARE NOT IN A CIRCUIT OR STORED IN CONDUCTIVE FOAM.
3. USE A BATTERY POWERED IRON TO SOLDER MOS CHIPS. DO NOT USE AN AC POWERED IRON.

INTERFACING CMOS

1. IF SUPPLY VOLTAGES ARE EQUAL:

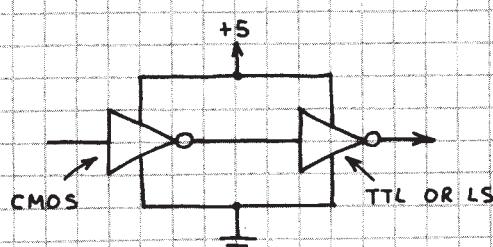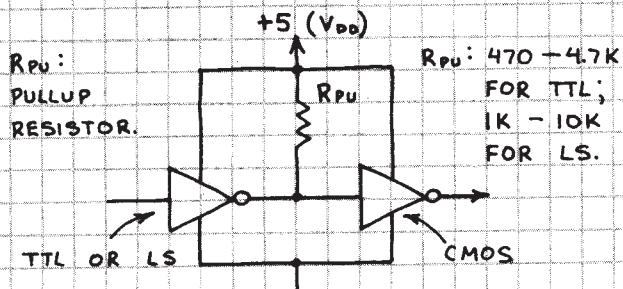


2. DIFFERENT SUPPLY VOLTAGES:

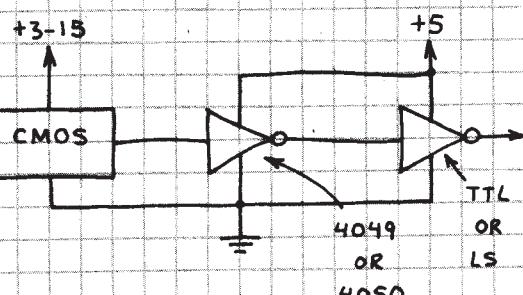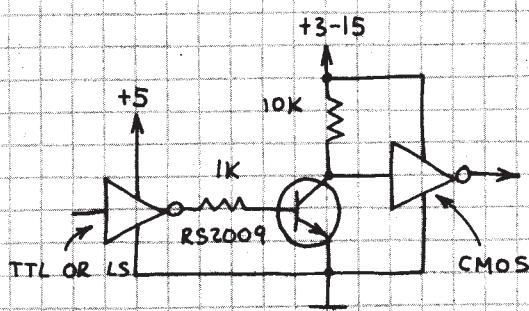


NOTE THAT CMOS MUST BE POWERED BY AT LEAST 5 VOLTS WHEN CMOS IS INTERFACED WITH TTL. OTHERWISE THE CMOS INPUT WILL EXCEED V_{dd} .

3. CMOS LED DRIVERS:

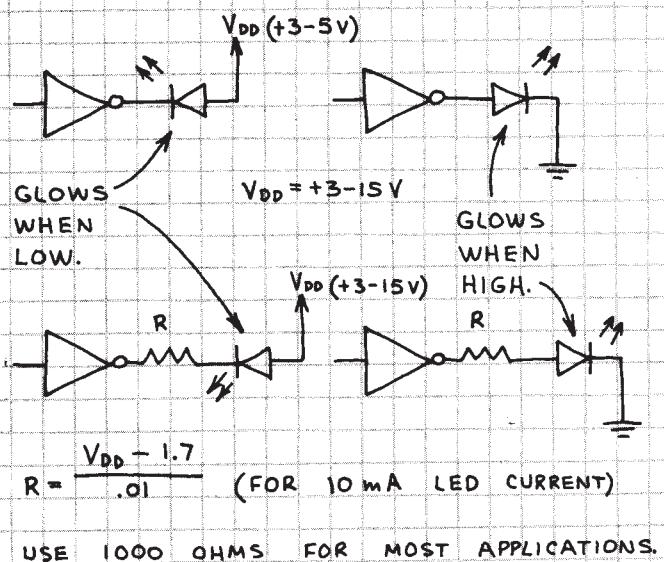

CMOS LOGIC CLOCK

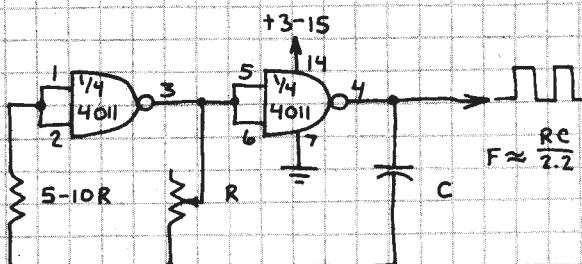MANY CIRCUITS IN THIS SECTION REQUIRE A SOURCE OF PULSES. HERE'S A SIMPLE CMOS CLOCK:



TYPICAL VALUES: $R = 100K$, $C = 0.01 - 0.1 \mu F$

OK TO USE 4049... BUT MUCH MORE CURRENT WILL BE REQUIRED.

CMOS TROUBLESHOOTING


1. DO ALL INPUTS GO SOMEWHERE?
2. ARE ALL IC PINS INSERTED INTO THE BOARD OR SOCKET?
3. IS THE IC HOT? IF SO, SEE 1-2 ABOVE AND MAKE SURE THE OUTPUT IS NOT OVERLOADED.
4. DOES THE CIRCUIT OBEY ALL CMOS OPERATING REQUIREMENTS?
5. HAVE YOU FORGOTTEN A CONNECTION?

QUAD NAND GATE

4011


THE BASIC CMOS BUILDING BLOCK CHIP. MORE APPLICATIONS THAN TTL
7400/74LS00 QUAD NAND GATE.

V_{DD} (+3-15V)

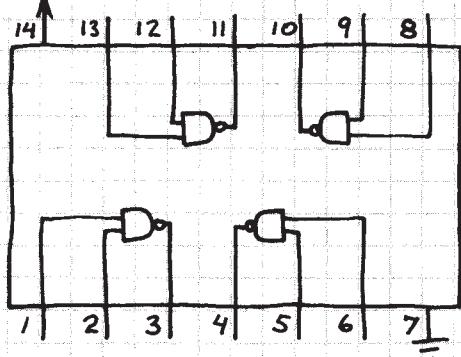

CONTROL GATE


A B | OUT

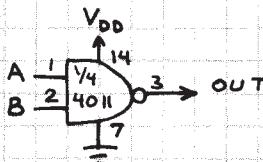


LL	H
LH	H
HH	L

IMPORTANT: CONNECT ALL UNUSED INPUTS TO PIN 7 OR 14!

INVERTER

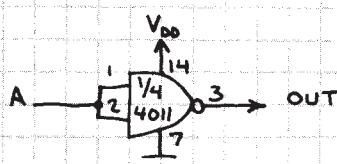


A	OUT
L	H
H	L

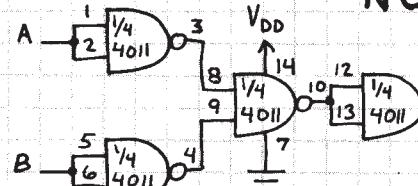


A	B	OUT
L	L	H
L	H	L
H	L	L
H	H	L

AND GATE

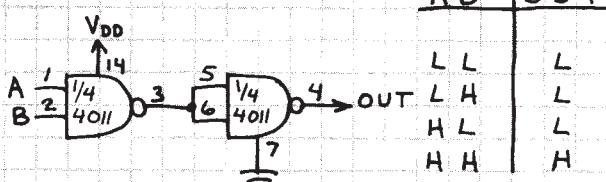


A	B	OUT
L	L	L
L	H	L
H	L	L
H	H	H

4-INPUT NAND GATE

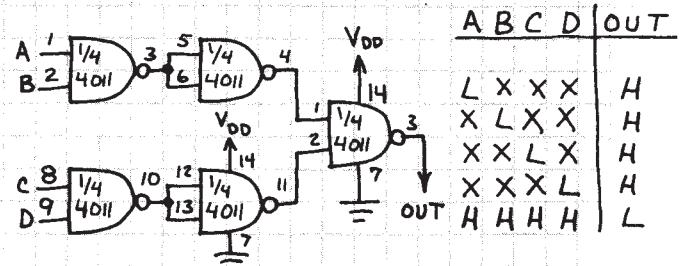


A	B	C	D	OUT
L	X	X	X	H
X	L	X	X	H
X	X	L	X	H
X	X	X	L	H
H	H	H	H	L

OR GATE

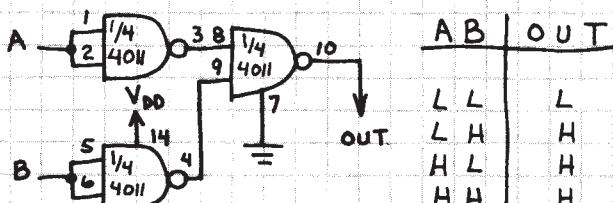


A	B	OUT
L	L	L
L	H	H
H	L	H
H	H	H

EXCLUSIVE-OR GATE

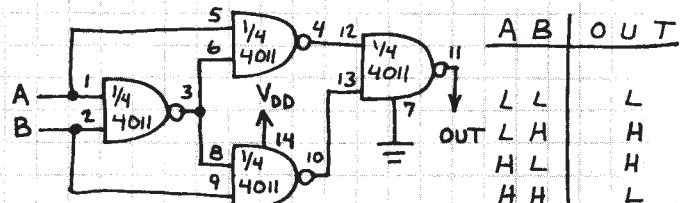


A	B	OUT
L	L	L
L	H	H
H	L	H
H	H	H

AND-OR GATE

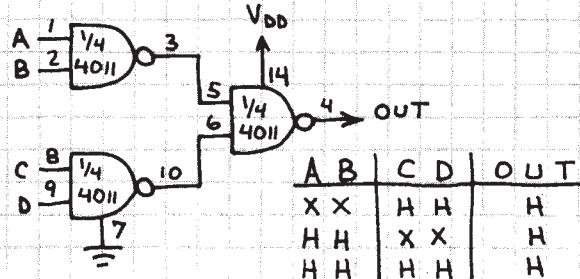

A	B	C	D	OUT
X	X	H	H	H
H	H	X	X	H
H	H	H	H	H

EXCLUSIVE-NOR GATE

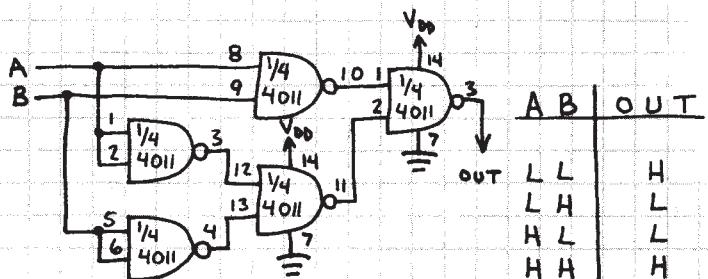


A	B	OUT
L	L	H
L	H	L
H	L	L
H	H	H

QUAD NAND GATE (CONTINUED)


4011

GATED OSCILLATOR

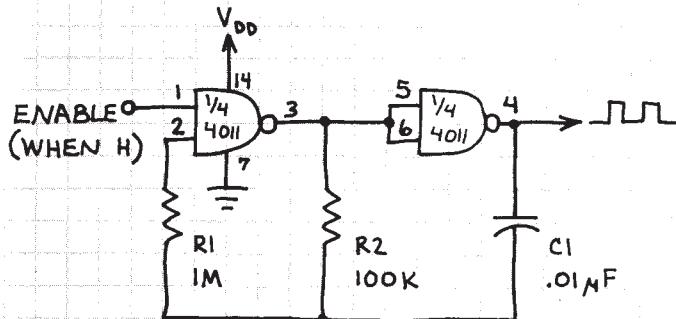


OUTPUT FREQUENCY IS
1 KHz SQUARE WAVE.

TOUCH SWITCH

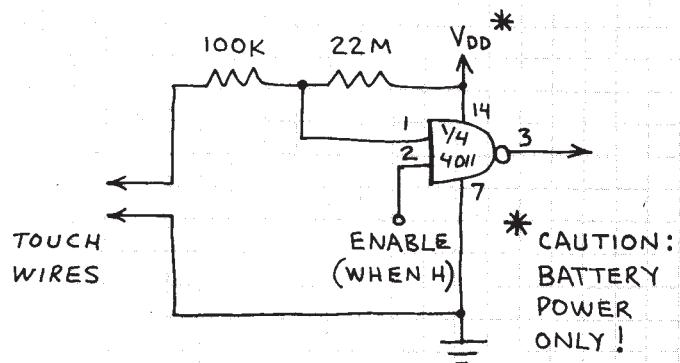


OUTPUT GOES HIGH WHEN
TOUCH WIRES ARE BRIDGED
BY A FINGER.

SIMPLE OSCILLATOR

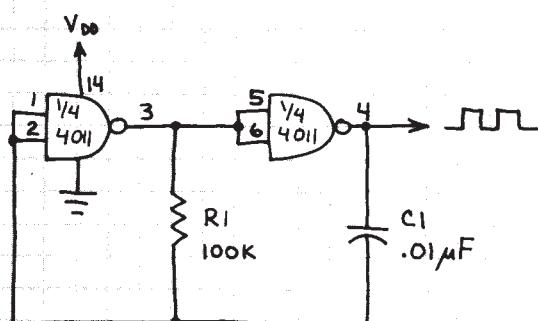


OUTPUT NOT AS SYMMETRICAL
AS ABOVE CIRCUIT.

ONE-SHOT TOUCH SWITCH

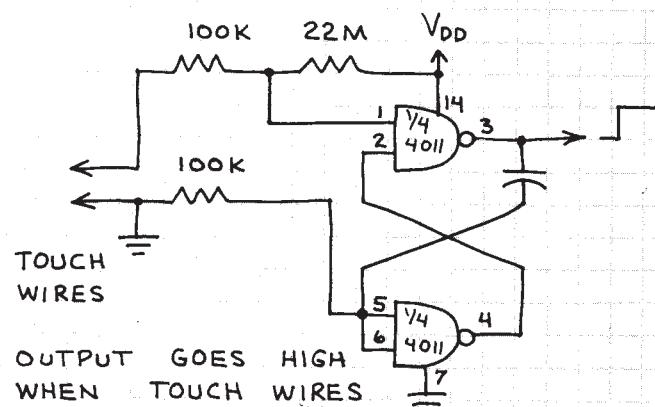


OUTPUT GOES HIGH
WHEN TOUCH WIRES
ARE BRIDGED BY A
FINGER. OUTPUT THEN RETURNS LOW
AFTER ABOUT 1 SECOND.

GATED FLASHER

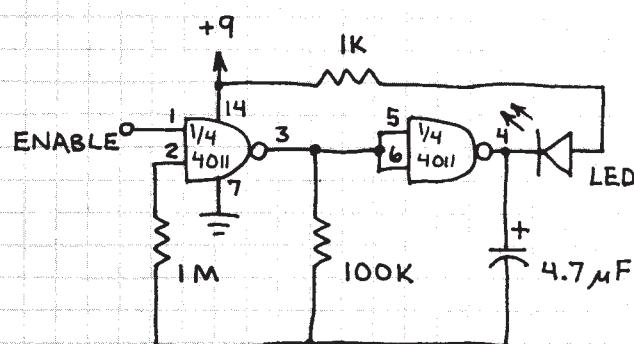


LED FLASHES 1-2 Hz
WHEN ENABLE IS HIGH.
LED STAYS ON WHEN
ENABLE IS LOW.

INCREASED OUTPUT DRIVE

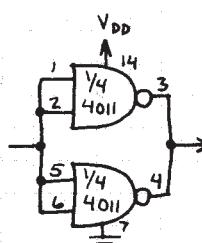

INVERTER

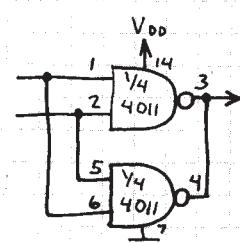

NAND GATE


USE THIS METHOD TO INCREASE
CURRENT THE 4011 CAN SOURCE
OR SINK. OK TO ADD MORE GATES.

TRIPLE 3-INPUT NAND GATE

4023


HANDY FOR MAKING CUSTOM DECODERS,
CONVERTERS AND MULTIPLE INPUT GATES.

6-INPUT OR GATE

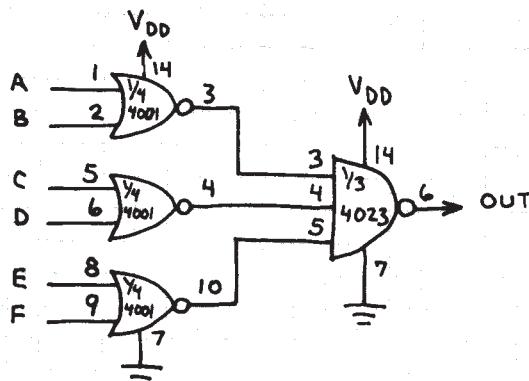

IMPORTANT: CONNECT ALL UNUSED INPUTS TO PIN 7 OR 14.


9-INPUT NAND GATE

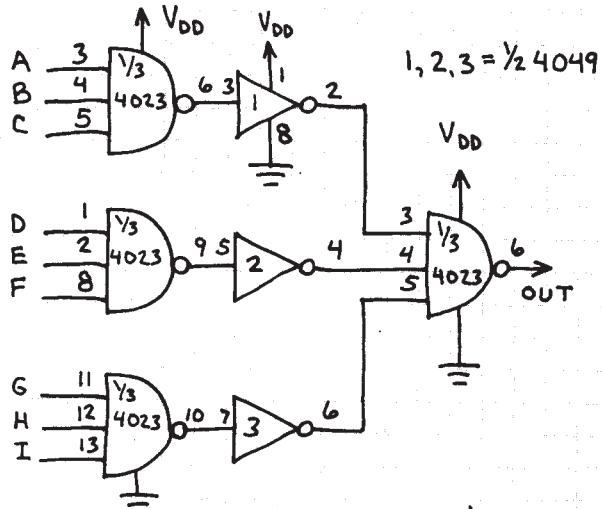


ALL UNUSED 'INPUTS
MUST BE GROUNDED.

DECIMAL-TO-BCD CONVERTER

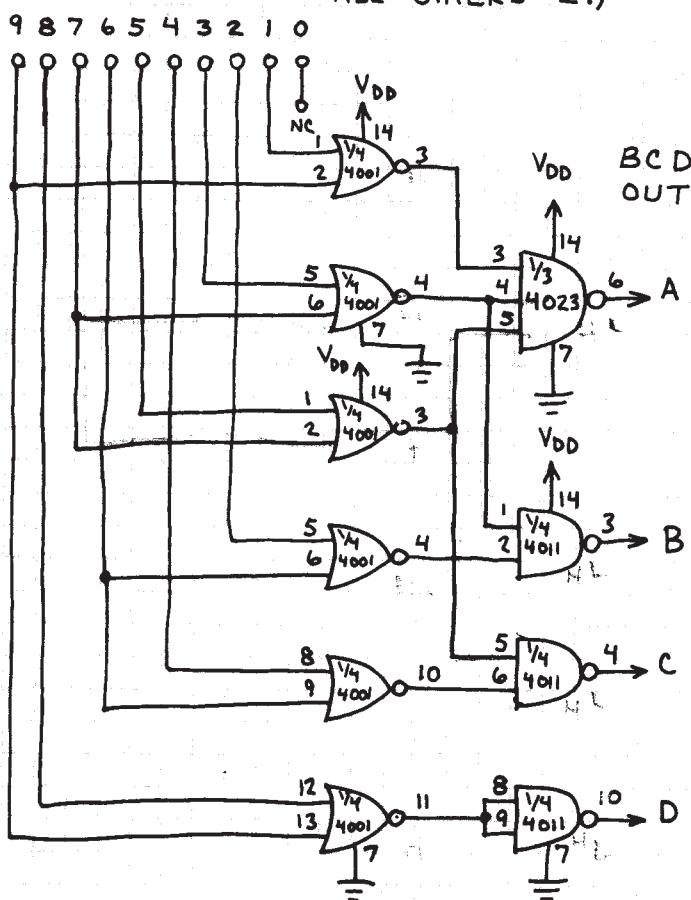DECIMAL IN (SELECTED DIGIT 4,
ALL OTHERS L.)




1-OF-4 DECODER

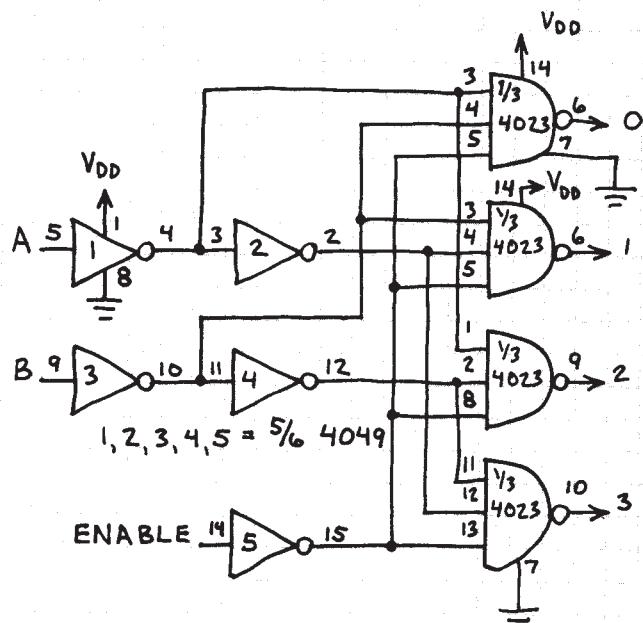


DUAL 4-INPUT NAND GATE 4012

VERY USEFUL IN MAKING DECODERS. ALSO CAN BE USED TO ADD ONE OR MORE ENABLE INPUTS TO VARIOUS CIRCUITS.


V_{DD} (+3-15V)

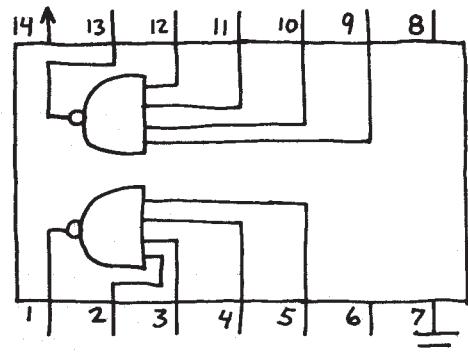

ENABLE INPUT

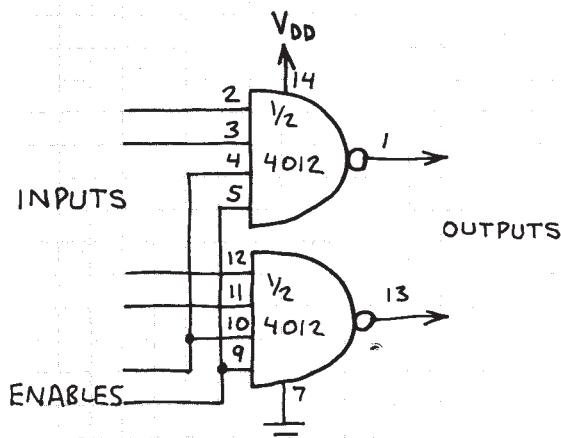


1-OF-4 DECODER

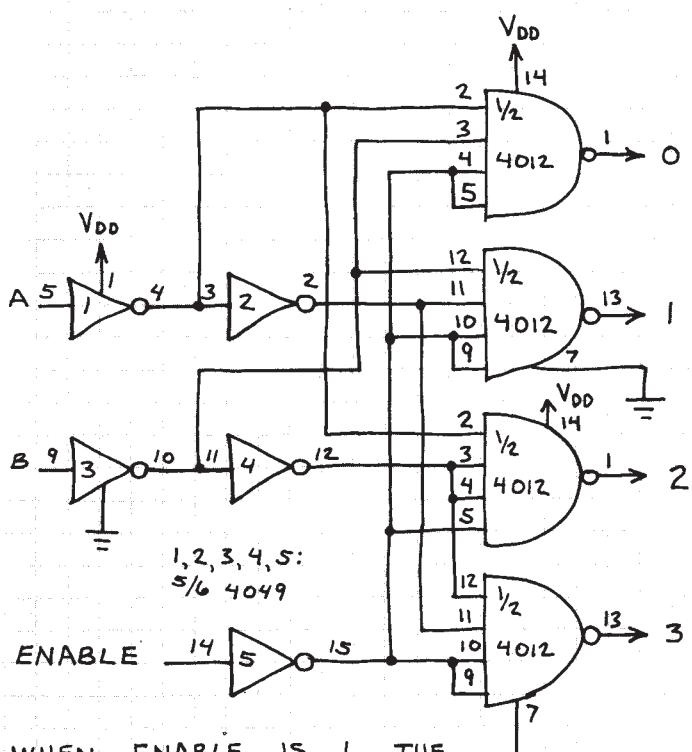


WHEN ENABLE IS L, THE OUTPUT CORRESPONDING TO THE BA BINARY INPUTS GOES LOW. ALL OTHER OUTPUTS GO HIGH WHEN ENABLE IS H.

BCD DECODERS


DECIMAL 0

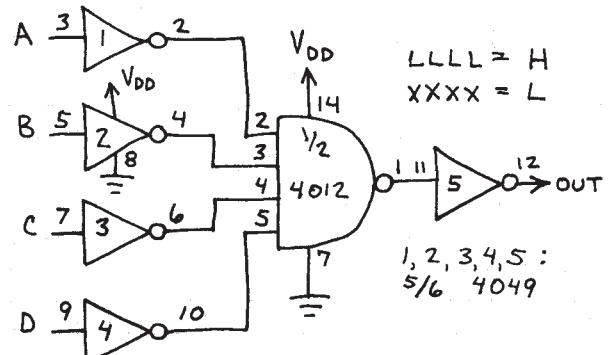

DECIMAL 1

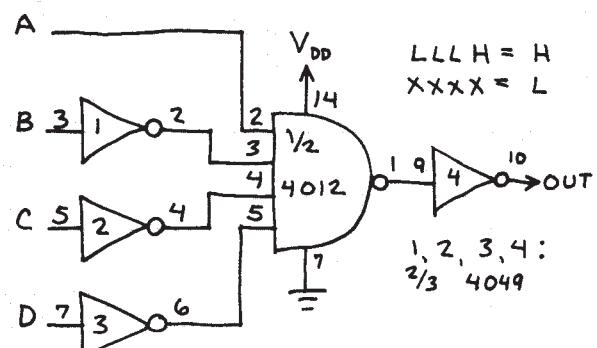

DECIMAL 9

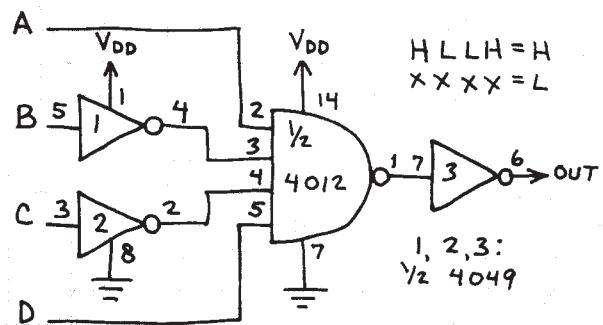


QUAD NOR GATE


4001

AN IMPORTANT CMOS BUILDING BLOCK CHIP. ITS HIGH IMPEDANCE INPUT MAKES POSSIBLE MORE APPLICATIONS THAN THE TTL 7402/74LS02 QUAD NOR GATE.


V_{DD} (+3-15 V)

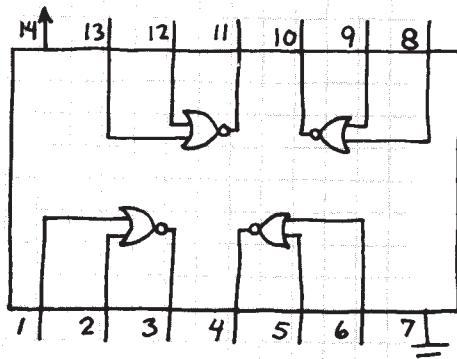

BOUNCELESS SWITCH

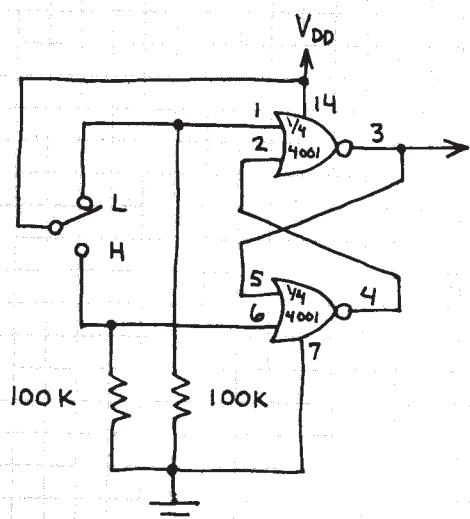


GATED TONE SOURCE

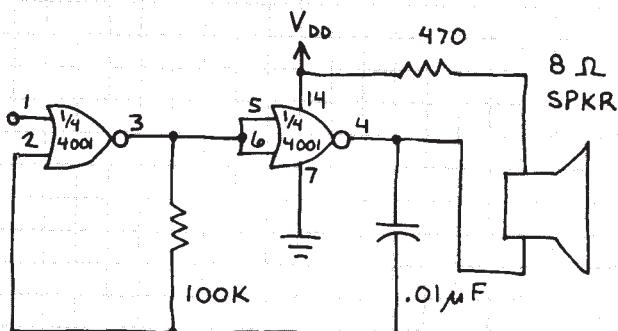

TONE FREQUENCY IS ABOUT 1KHz.



RS LATCH

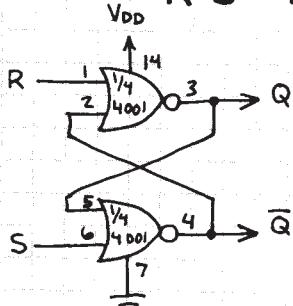

R	S	Q	\bar{Q}
L	L	NO CHANGE	
L	H	H	L
H	L	L	H
H	H	NOT ALLOWED	

IMPORTANT: CONNECT ALL UNUSED INPUTS TO PIN 7 OR 14.

INCREASED OUTPUT DRIVE

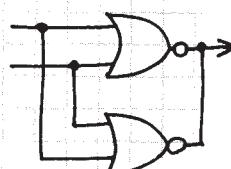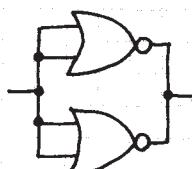


INVERTER

NOR GATE


USE THIS METHOD TO INCREASE CURRENT. THE 4001 CAN SOURCE OR SINK. OK TO ADD MORE GATES.

LED FLASHER

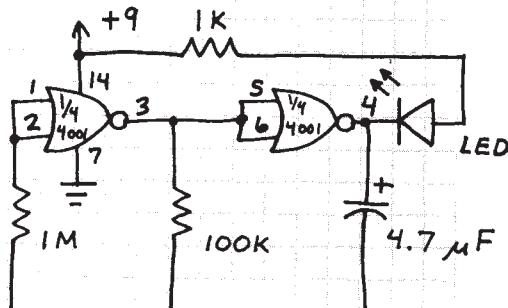

LED FLASHES 1-2 TIMES/SECOND.

OR GATE

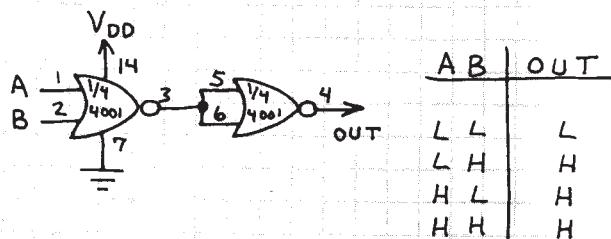

A	B	OUT	AB
L	L	L	L
L	H	H	H
H	L	H	H
H	H	H	H


QUAD EXCLUSIVE-OR GATE

4070

THE OUTPUT OF EACH GATE GOES LOW WHEN BOTH INPUTS ARE EQUAL. THE OUTPUT GOES HIGH IF THE INPUTS ARE UNEQUAL. MANY APPLICATIONS INCLUDING BINARY ADDITION, COMPARING BINARY WORDS AND PHASE DETECTION.


IMPORTANT: CONNECT UNUSED INPUTS TO PIN 7 OR 14.

V_{DD} (+3-15V)

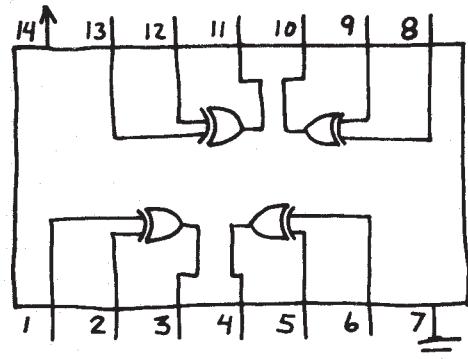


1-BIT COMPARATOR

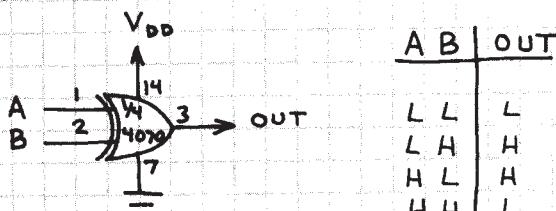THIS CIRCUIT IS ALSO A HALF-ADDER WITHOUT A CARRY OUTPUT.




CONTROLLED INVERTER

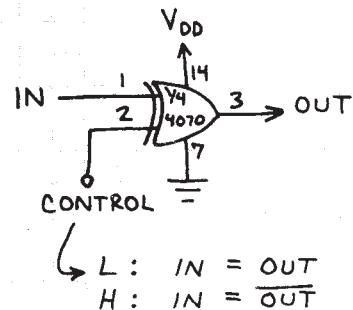


BINARY FULL ADDER

4-BIT COMPARATOR


DETERMINES IF TWO 4-BIT WORDS ARE EQUAL.

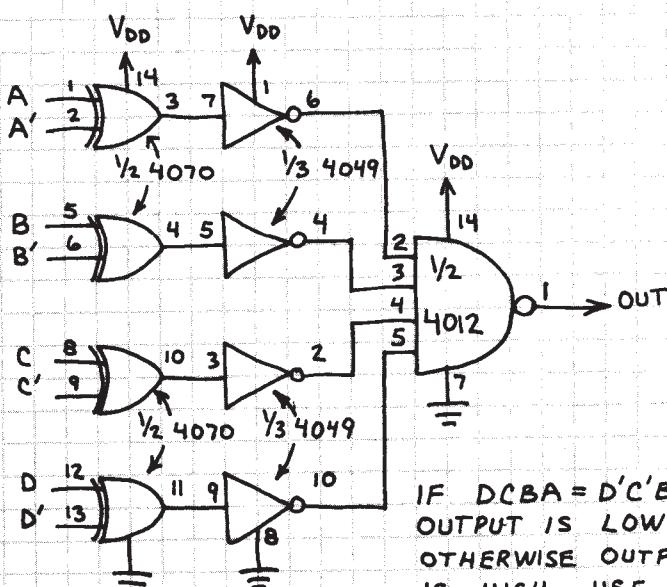

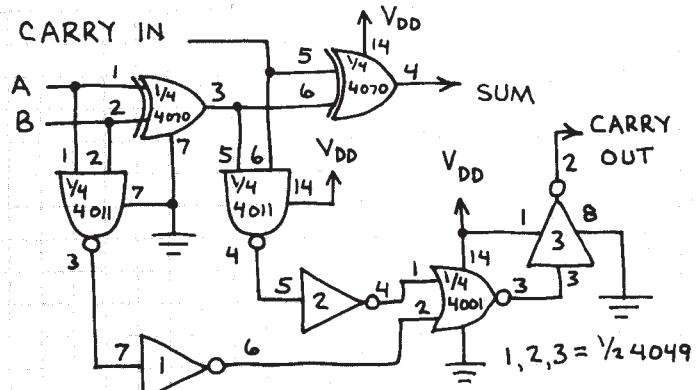IF DCBA = D'C'B'A'
OUTPUT IS LOW.
OTHERWISE OUTPUT IS HIGH. USE
SECOND HALF OF
4012 AS INVERTER TO REVERSE OPERATION.




PHASE DETECTOR

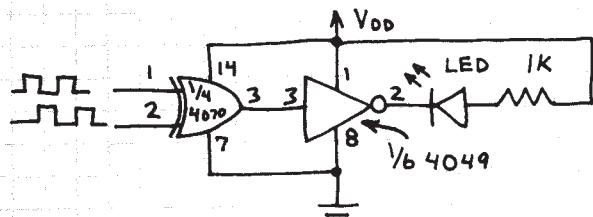


LED STOPS GLOWING WHEN THE INPUT FREQUENCIES ARE EQUAL.

HEX INVERTING BUFFER 4049

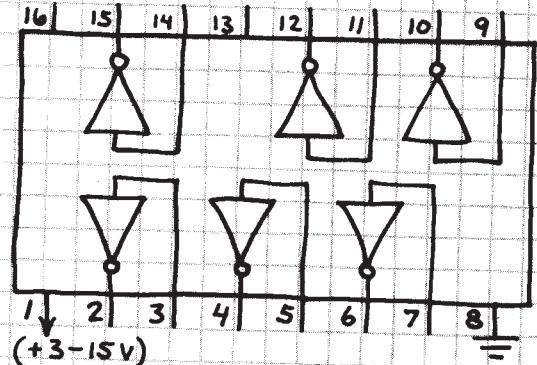IN ADDITION TO STANDARD LOGIC AND CMOS TO TTL INTERFACING, OFTEN USED IN OSCILLATORS AND PULSE GENERATORS. FOR LOW CURRENT APPLICATIONS, USE 4011 CONNECTED AS INVERTER. (OK TO USE 4011 FOR CIRCUITS ON THIS PAGE.)




CLOCK PULSE GENERATOR

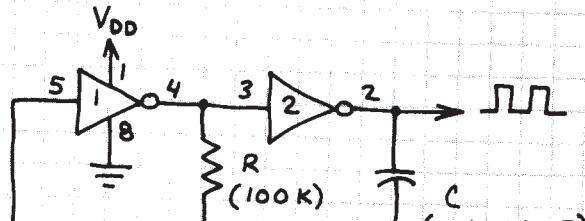


$$1,2 = \frac{1}{3} \text{ 4049 PULSE RATE} = \frac{1}{1.4RC}$$

PHASE SHIFT OSCILLATOR

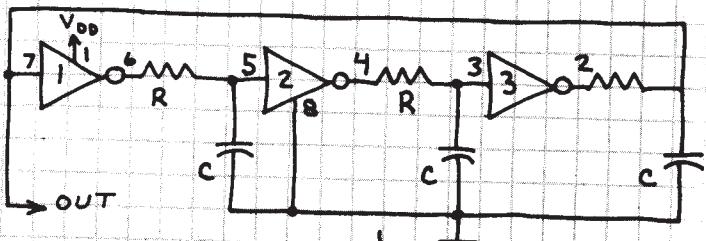


$$\text{OUTPUT FREQUENCY} = \frac{1}{3.3RC} = 1.2, 3 = \frac{1}{2} \text{ 4049}$$

BOUNCELESS SWITCH

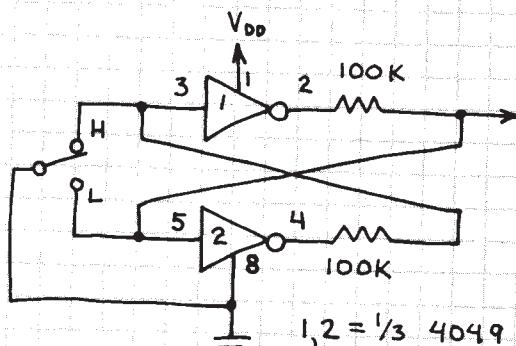


$$1,2 = \frac{1}{3} \text{ 4049}$$

TRIANGLE WAVE SOURCE

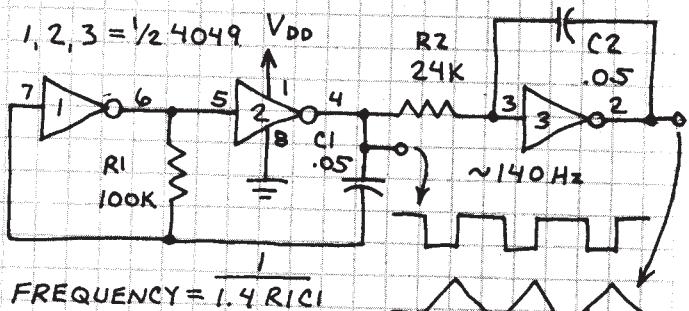


SQUARE WAVE GENERATOR

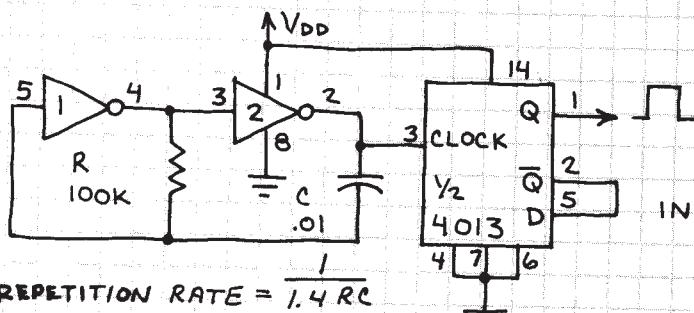

$$\text{REPETITION RATE} = \frac{1}{1.4RC}$$

$$1,2 = \frac{1}{3} \text{ 4049}$$

LINEAR 10X AMPLIFIER

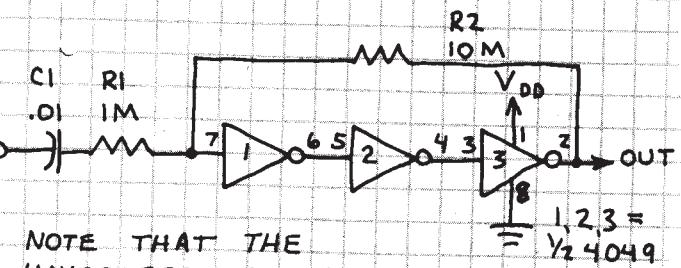


NOTE THAT THE INVERTERS ARE USED IN A LINEAR MODE. GAIN = R_2/R_1 .

HEX NON-INVERTING BUFFER

4050


PRIMARILY INTENDED FOR
INTERFACING CMOS TO TTL.
SUPPLIES MORE CURRENT
THAN STANDARD CMOS.

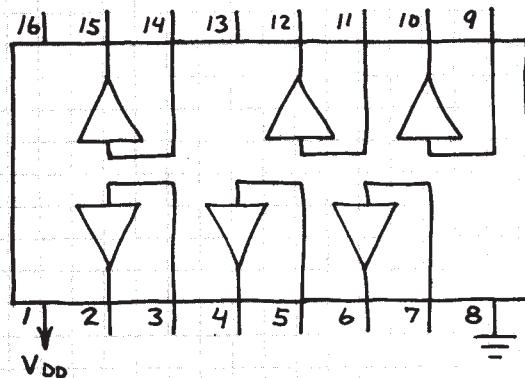IMPORTANT: ALL UNUSED INPUTS
MUST GO TO PIN 1 OR 8.




NOTE UNUSUAL LOCATION
OF POWER SUPPLY PINS.


OUTPUT EXPANDER

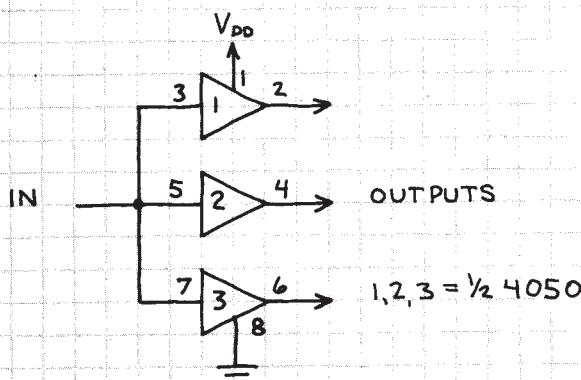


OUTPUT BUFFER

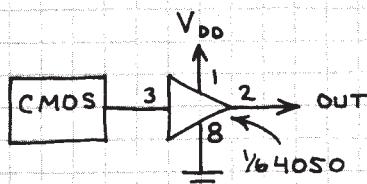


CMOS TO CMOS AT LOWER V_{DD}

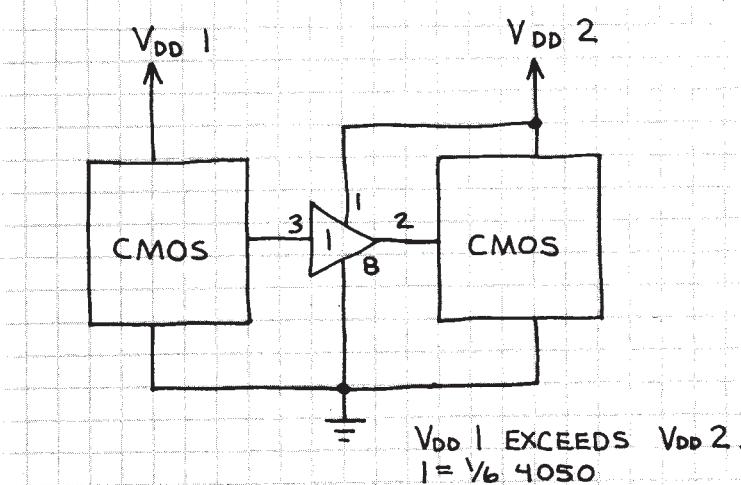


LOGIC PROBE

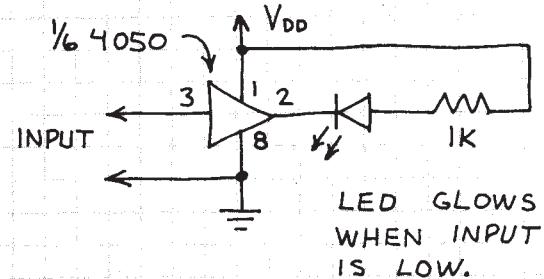

INCREASED OUTPUT DRIVE

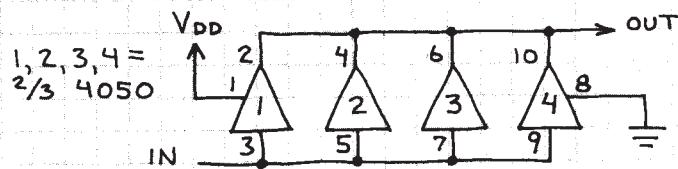


CMOS TO TTL/LS AT LOWER V_{CC}

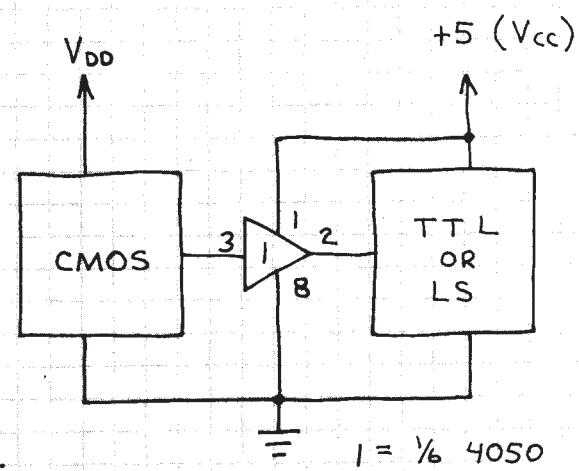


ANALOG MULTIPLEXER

4051

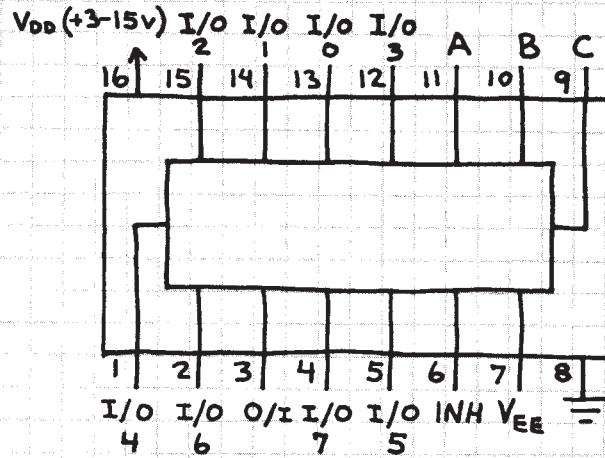
INPUT ADDRESS AT CBA SELLECTS 1-OF-8 ANALOG SWITCHES. SIGNAL AT SELECTED SWITCH I/O (INPUT/OUTPUT) IS THEN APPLIED TO COMMON O/I (OUTPUT/INPUT). THE INPUT SIGNAL MUST NOT EXCEED V_{DD}. THE INHIBIT (INH) INPUT SHOULD BE GROUNDED FOR NORMAL OPERATION. ALL SWITCHES ARE OPEN WHEN INH IS HIGH.



1-OF-8 MULTIPLEXER


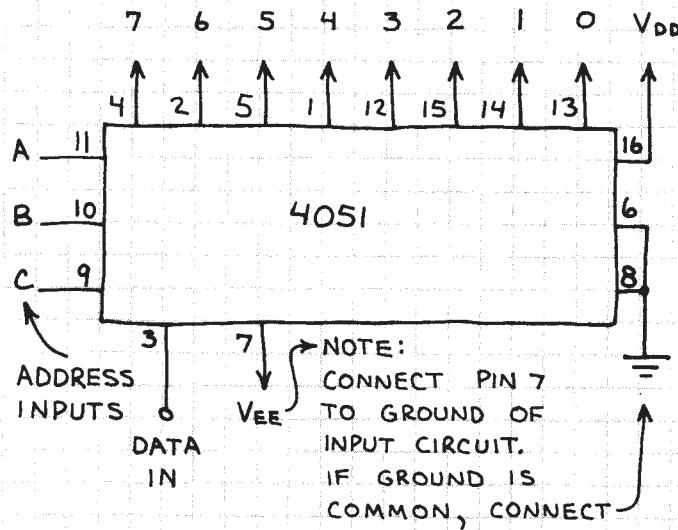


1-OF-8 DATA SELECTOR (DEMULTIPLEXER)

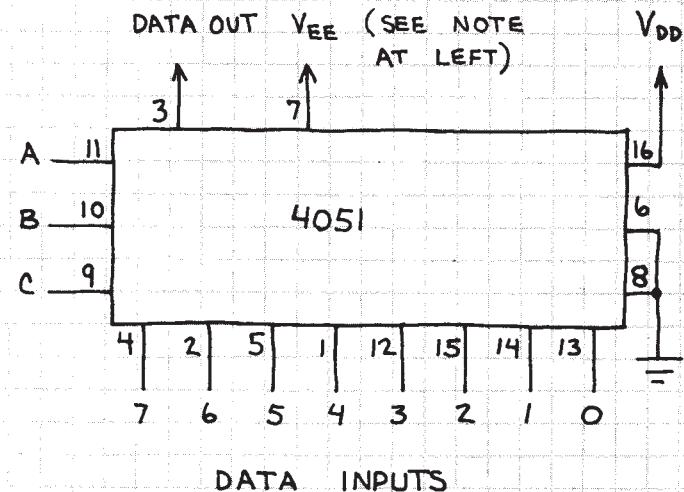

TONE SEQUENCER

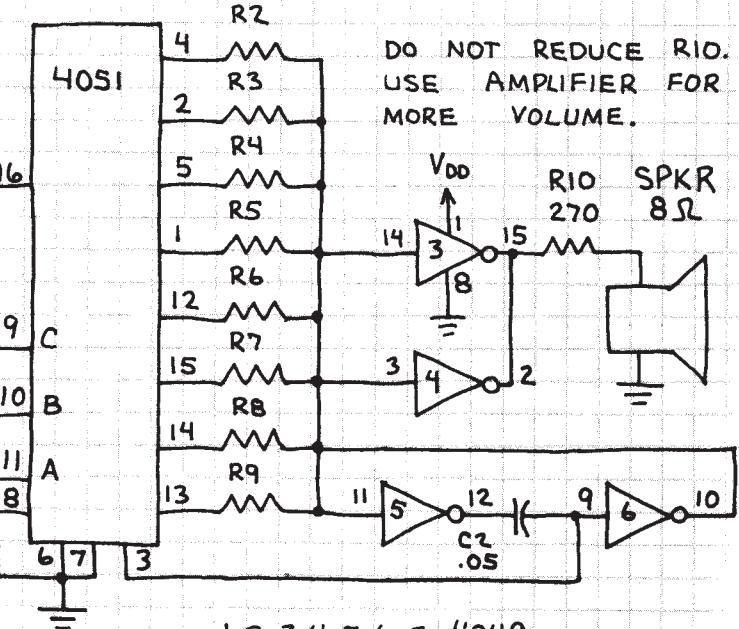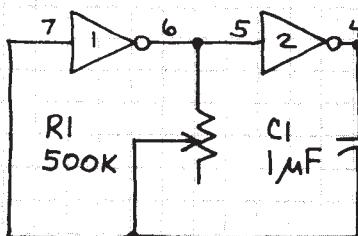CYCLES THROUGH 8 TONES AND REPEATS. R1 CONTROLS TEMPO. R2-R9 ARE INDIVIDUAL TONE RESISTORS. USE 1K-100K EACH.




1, 2, 3, 4, 5, 6 = 4049

QUAD BILATERAL SWITCH


4066

ONE OF THE MOST VERSATILE CMOS CHIPS. PINS A, B, C AND D CONTROL FOUR ANALOG SWITCHES. CLOSE A SWITCH BY CONNECTING ITS CONTROL PIN TO V_{DD} . ON RESISTANCE = $80 - 250$ OHMS. OPEN A SWITCH BY CONNECTING ITS CONTROL PIN TO GROUND (PIN 7). OFF RESISTANCE = 10^9 OHMS. I/O (INPUT/OUTPUT) AND O/I PINS ARE REVERSIBLE.

V_{DD} (+3-15 V)

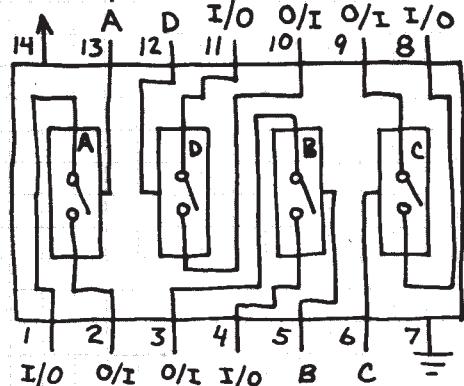


DATA BUS CONTROL

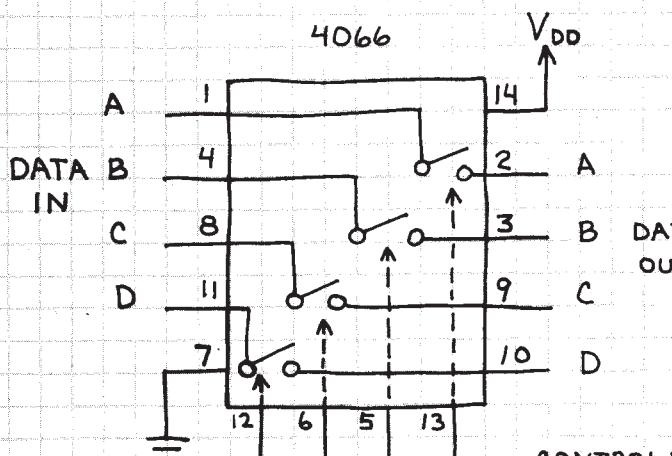


CONTROL:
L = OFF
H = LOAD

DATA SELECTOR

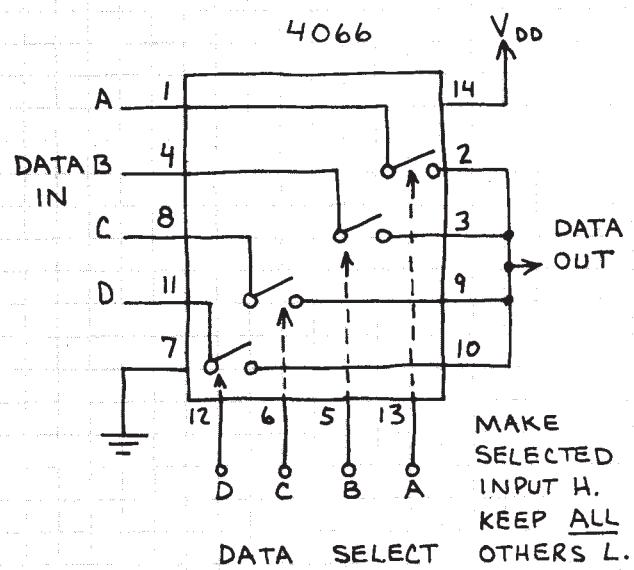

MAKE
SELECTED
INPUT H.
KEEP ALL
OTHERS L.

DIGITAL TO ANALOG (D/A) CONVERTER

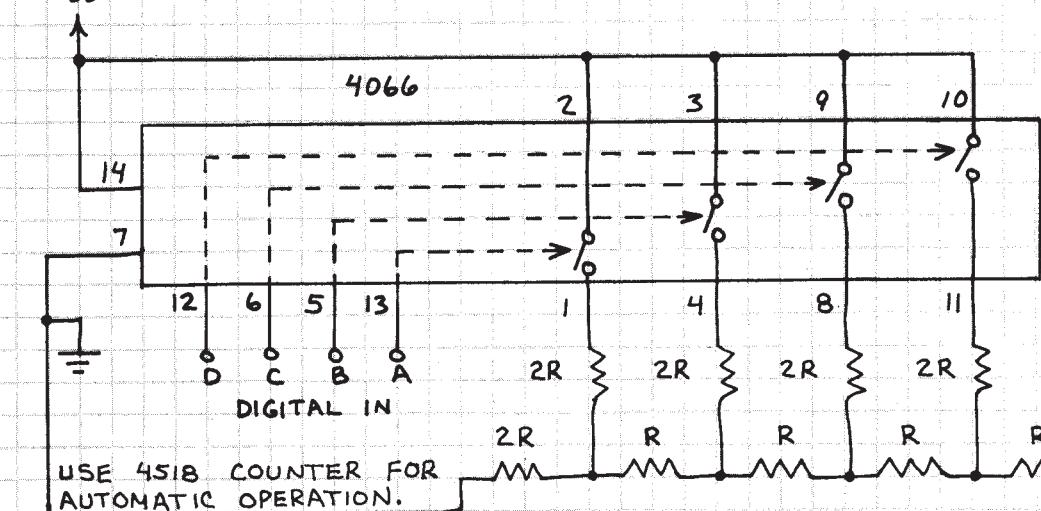


THIS IS NOT A LINEAR D/A CONVERTER. INSTEAD IT PRODUCES A PSEUDO-RANDOM OUTPUT THAT RANGES FROM 3.06 - 5.62 VOLTS ($V_{DD} = 9$ V). USE TO DRIVE 4046 VCO OR PRODUCE UNUSUAL WAVEFORMS. $R = 47K$ AND $2R = 100K$.

ANALOG VOLTAGE OUT

BCD-TO-7-SEGMENT LATCH/DECODER/DRIVER 4511

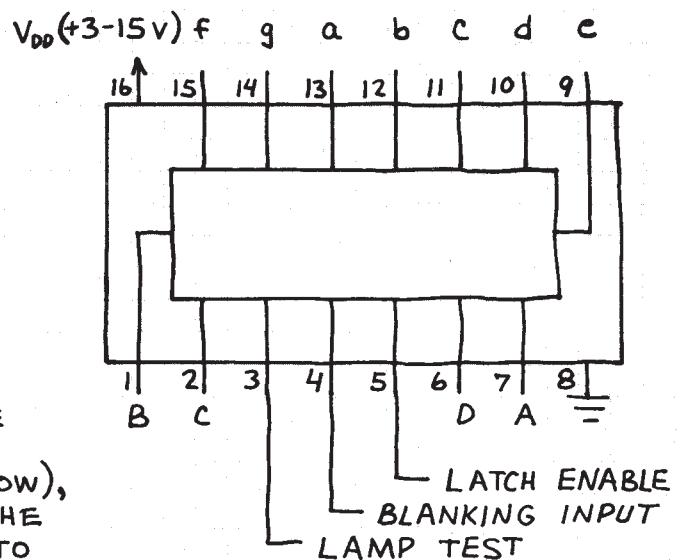
CONVERTS BCD DATA INTO FORMAT SUITABLE FOR PRODUCING DECIMAL DIGITS ON 7-SEGMENT LED DISPLAY. INCLUDES BUILT-IN 4-BIT LATCH TO STORE DATA TO BE DISPLAYED (WHEN PIN 5 IS HIGH). WHEN LATCH IS NOT USED (PIN 5 LOW), THE 7-SEGMENT OUTPUTS FOLLOW THE BCD INPUTS. MAKE PIN 4 LOW TO EXTINGUISH THE DISPLAY AND HIGH FOR NORMAL OPERATION. MAKE PIN 3 LOW TO TEST THE DISPLAY AND HIGH FOR NORMAL OPERATION.




DISPLAY FLASHER

DISPLAY FLASHES ONCE PER SECOND WHEN E IS HIGH.

E	DISPLAY
H	FLASHES OFF
L	

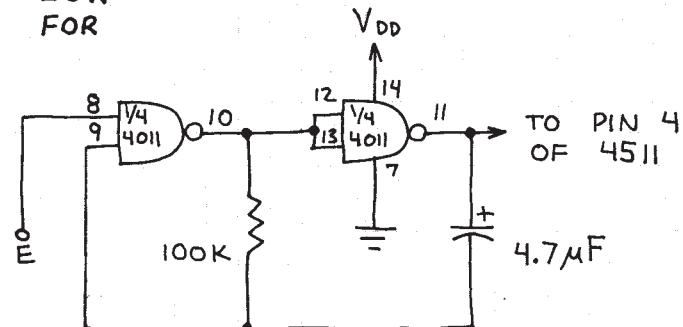


DECIMAL COUNTING UNIT (DCU)

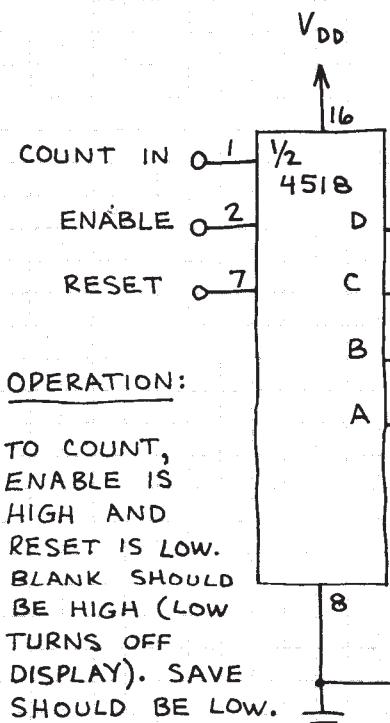


OPERATION:

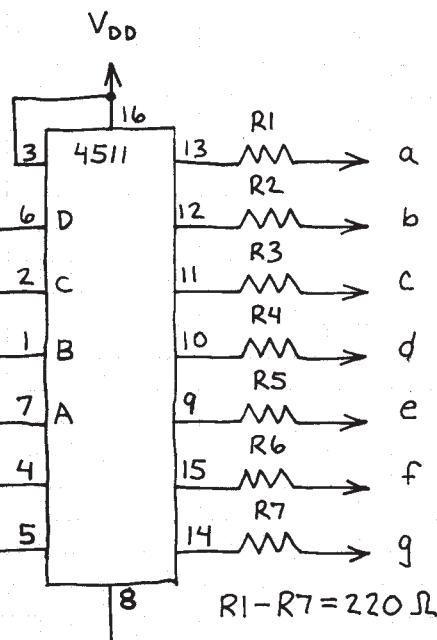TO COUNT, ENABLE IS HIGH AND RESET IS LOW. BLANK SHOULD BE HIGH (LOW TURNS OFF DISPLAY). SAVE SHOULD BE LOW. MAKE SAVE HIGH TO STORE INTERIM COUNT WITHOUT AFFECTING COUNTER.



IMPORTANT: ALL INPUTS MUST GO SOMEWHERE!

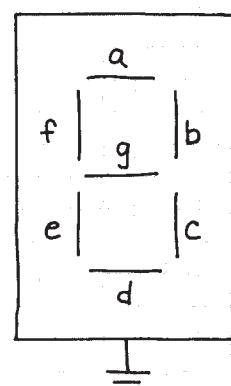


$$R_1 - R_7 = 220\Omega$$

$$V_{DD} = +5-9V$$


COMMON
CATHODE
LED DISPLAY

BCD-TO-7-SEGMENT LATCH/DECODER/DRIVER 4543 (14543)

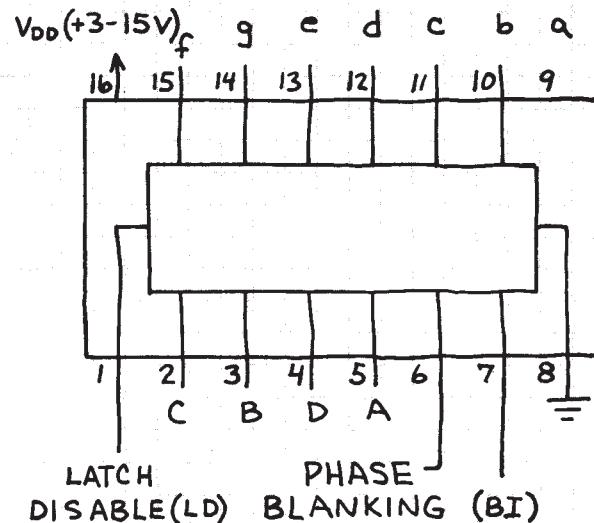
DESIGNED TO DRIVE LIQUID CRYSTAL (LC) DISPLAYS BUT WILL DRIVE OTHER DISPLAYS ALSO. INCLUDES BUILT-IN 4-BIT LATCH TO STORE DATA TO BE DISPLAYED (WHEN PIN 1 IS LOW). WHEN LATCH IS NOT USED (PIN 1 HIGH), THE 7-SEGMENT OUTPUTS FOLLOW THE BCD INPUTS. MAKE PIN 7 HIGH TO BLANK THE DISPLAY AND LOW FOR NORMAL OPERATION.



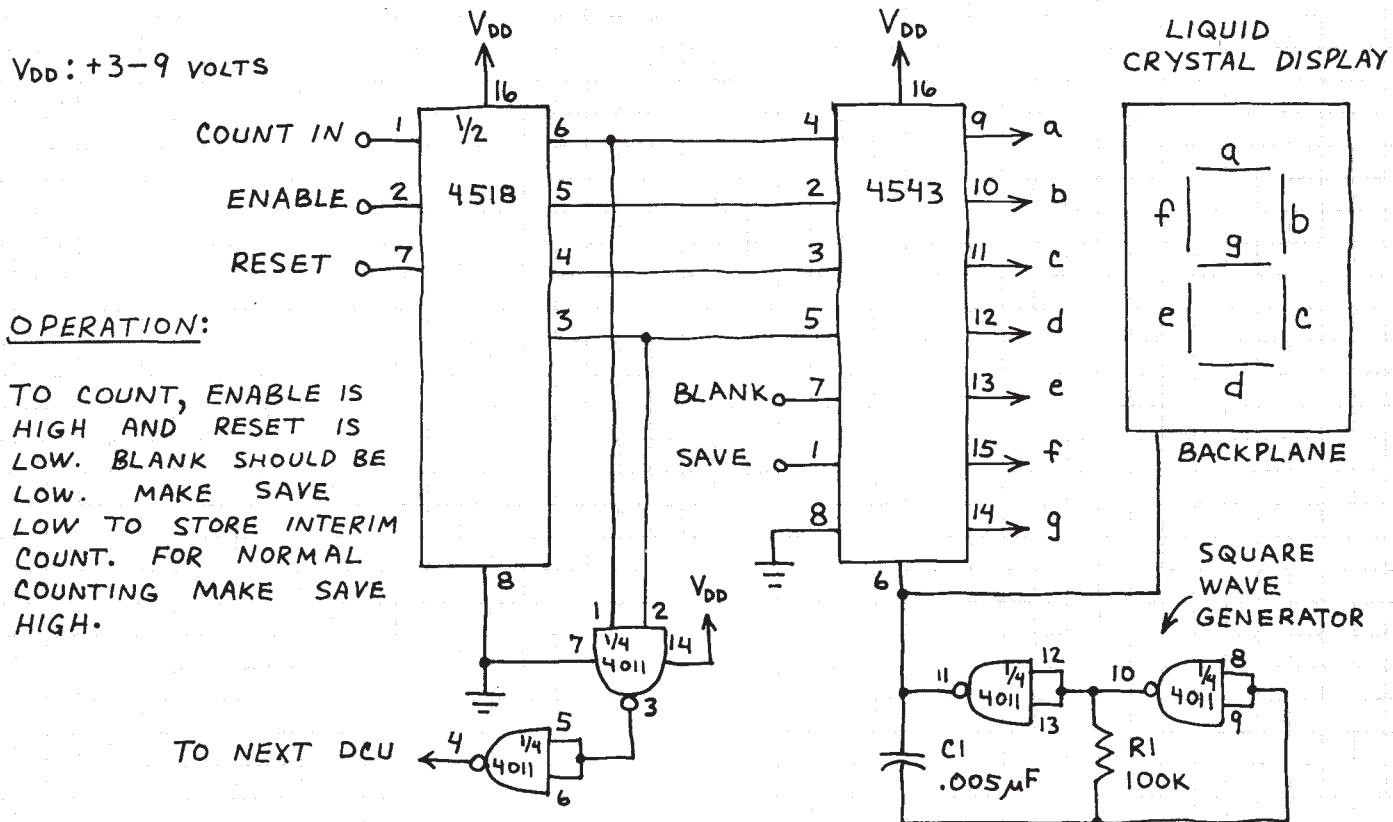LIQUID CRYSTAL DISPLAY DECIMAL COUNTING UNIT




DISPLAY FLASHER

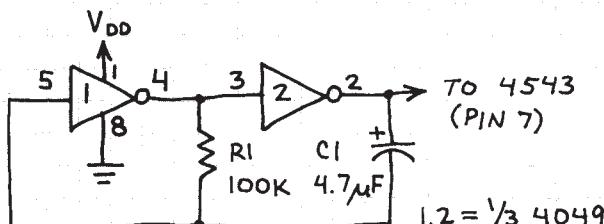

$$1,2 = \frac{1}{3} 4049$$


DRIVING LED DISPLAYS

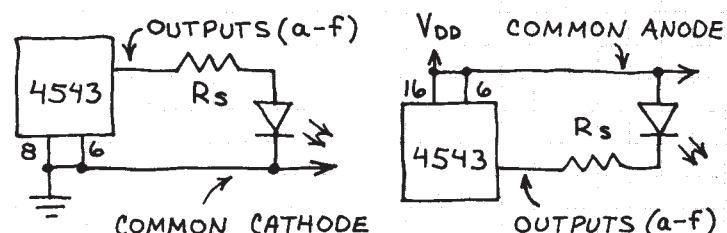


BCD-TO-DECIMAL DECODER

4028

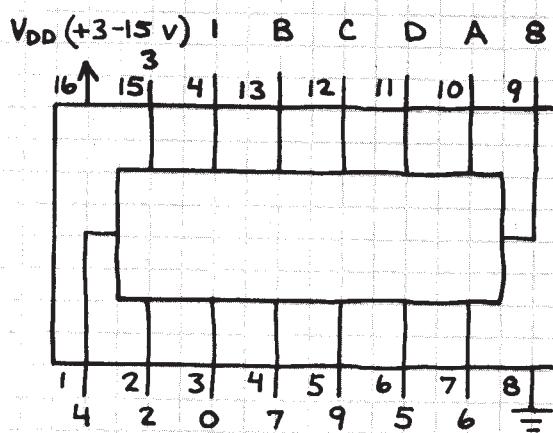DECODES 4-BIT BCD INPUT INTO 1-OF-10 OUTPUTS. SELECTED OUTPUT GOES HIGH; ALL OTHERS STAY LOW. USE FOR DECIMAL READOUTS, SEQUENCERS, PROGRAMMABLE COUNTERS, ETC.




0-9 SECOND TIMER

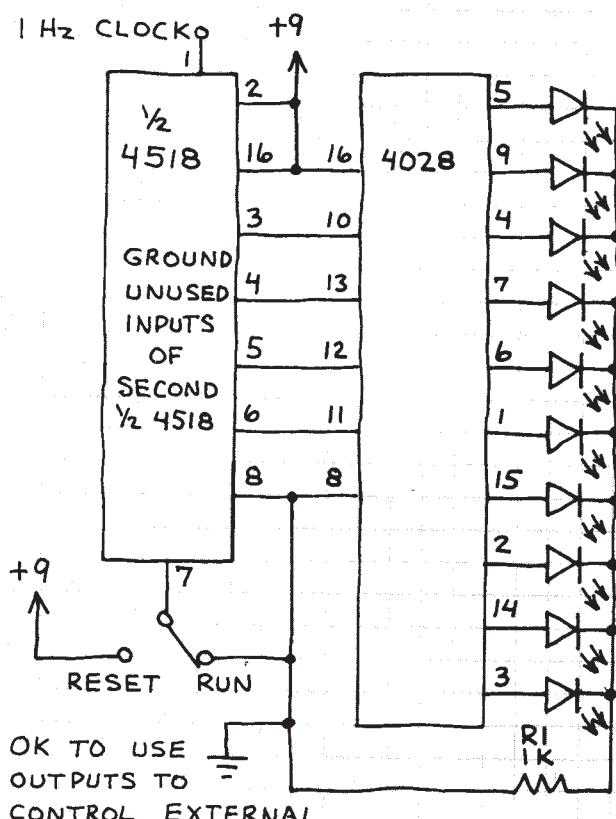


COUNT TO N AND RECYCLE

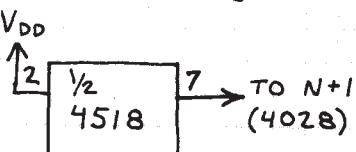USE THE ADJACENT CIRCUIT WITH THESE CHANGES:




1. OMIT 4049
2. MAKE PIN 2 HIGH
3. USE PIN 7 AS CONTROL INPUT.

1-OF-8 DECODER

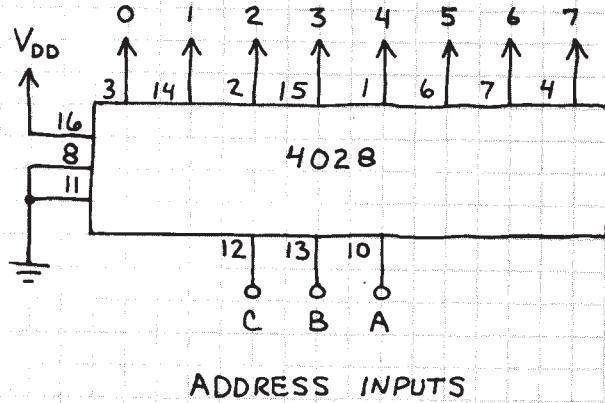


ADDRESS INPUTS

COUNT TO N AND HALT

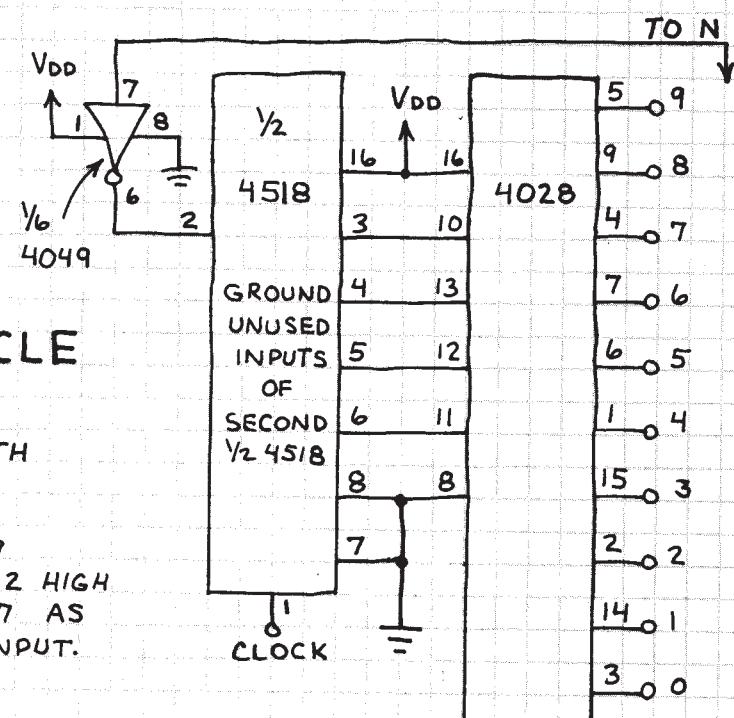


60-Hz TIMEBASE MM5369 (276-1769)

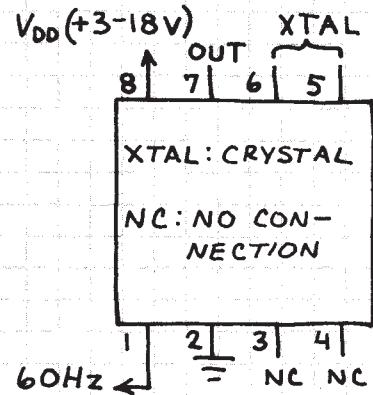PROVIDES PRECISE 60 Hz SQUARE WAVE WHEN USED WITH 3.579545 MHz COLOR TV CRYSTAL. USE FOR MOST DO-IT-YOURSELF TIMERS, CLOCKS, CONTROLLERS, FUNCTION GENERATORS. INSTALL IN SMALL CABINET FOR WORKBENCH PRECISION CLOCK.




60-Hz TIMEBASE

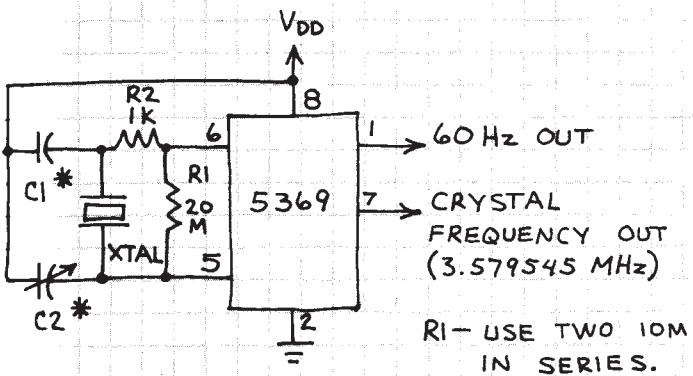


* MOTOROLA SPECIFIES THAT $C_1 = 30\text{ pF}$ AND $C_2 = 6.36\text{ pF}$. OK TO USE SIX 4.7 pF CAPACITORS IN PARALLEL OR 47 pF CAPACITOR FOR C_1 . TRY TUNABLE CAPACITOR (e.g. $5-50\text{ pF}$) FOR C_2 . TO TUNE, CONNECT FREQUENCY METER TO PIN 7. TUNE C_2 UNTIL FREQUENCY IS 3,579,545 Hz. ACCURACY FAIRLY GOOD EVEN IF YOU DON'T TUNE C_2 .


10-Hz TIMEBASE

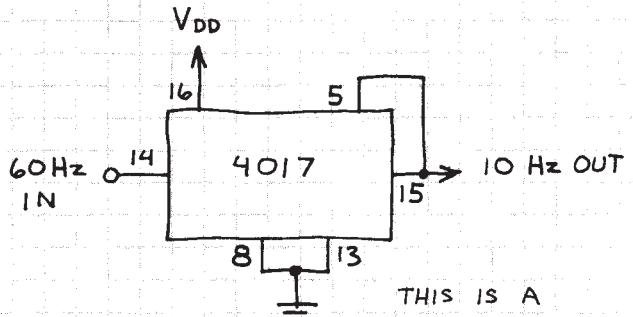

1-Hz TIMEBASE

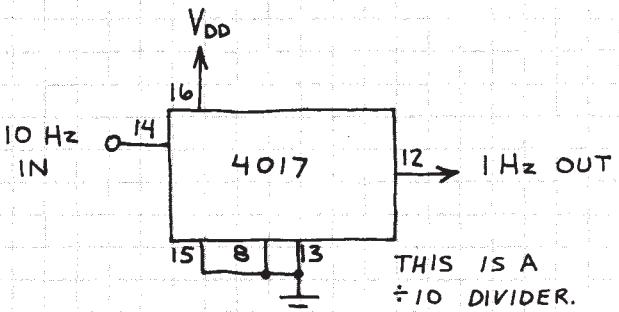

DIGITAL STOPWATCH

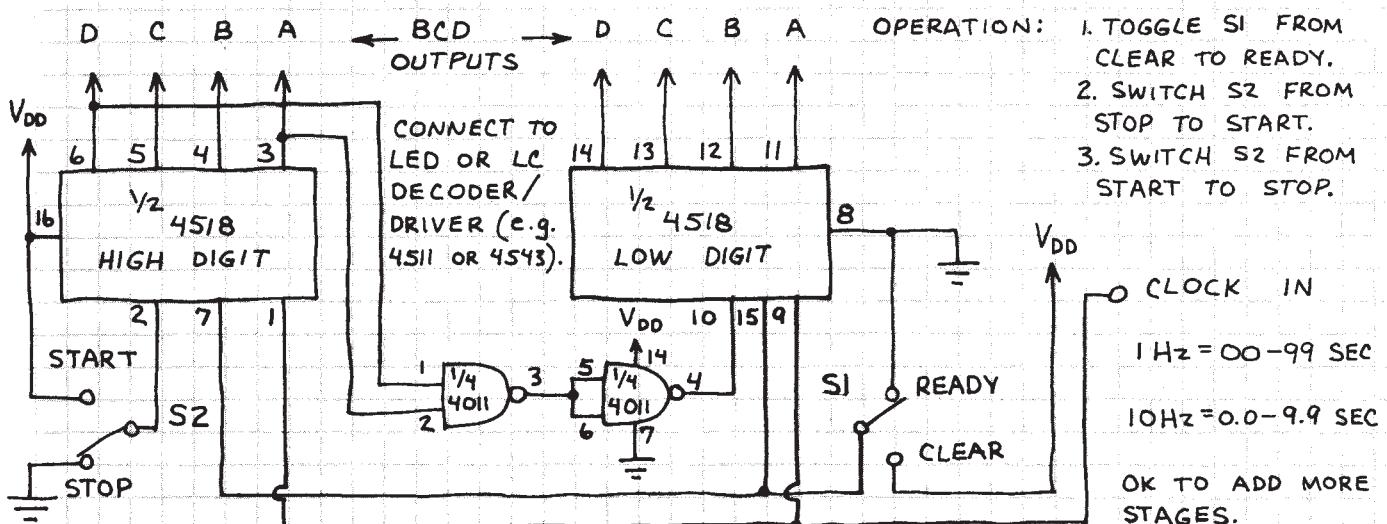


1. TOGGLE SI FROM CLEAR TO READY.
2. SWITCH S2 FROM STOP TO START.
3. SWITCH S2 FROM START TO STOP.

DUAL D FLIP-FLOP


4013

VERY VERSATILE PAIR OF D-TYPE FLIP-FLOPS. GROUND UNUSED INPUTS.


1-OF-4 SEQUENCER

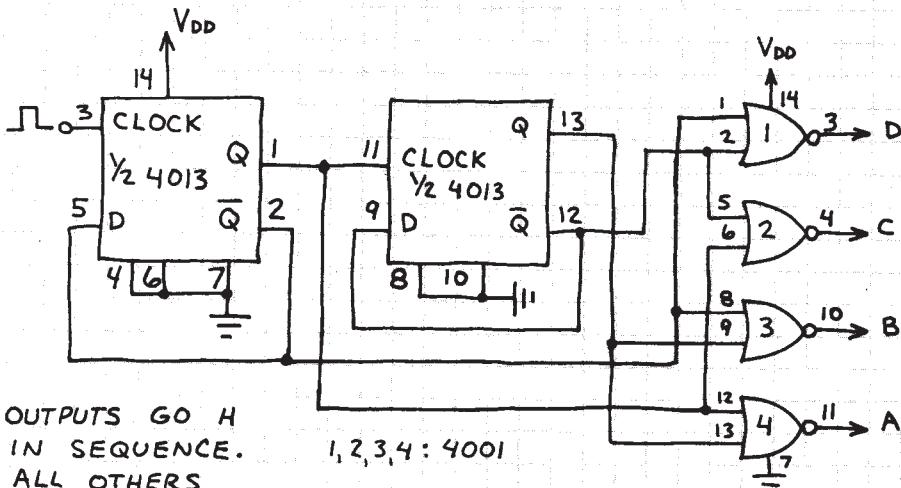

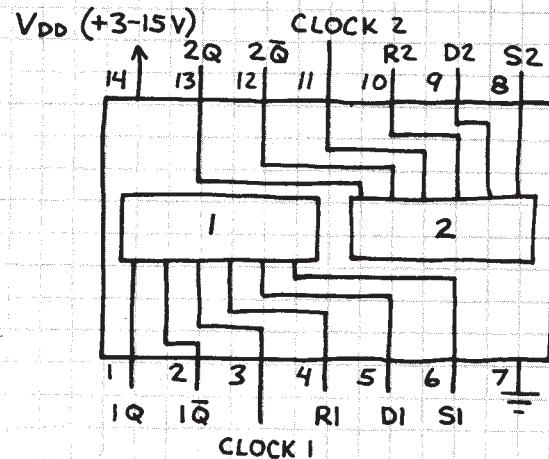
OUTPUTS GO H
IN SEQUENCE.
1, 2, 3, 4 : 4001
ALL OTHERS
STAY L.




DIVIDE-BY-2

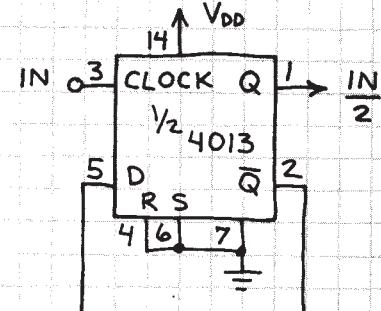

MODULO-8 COUNTER

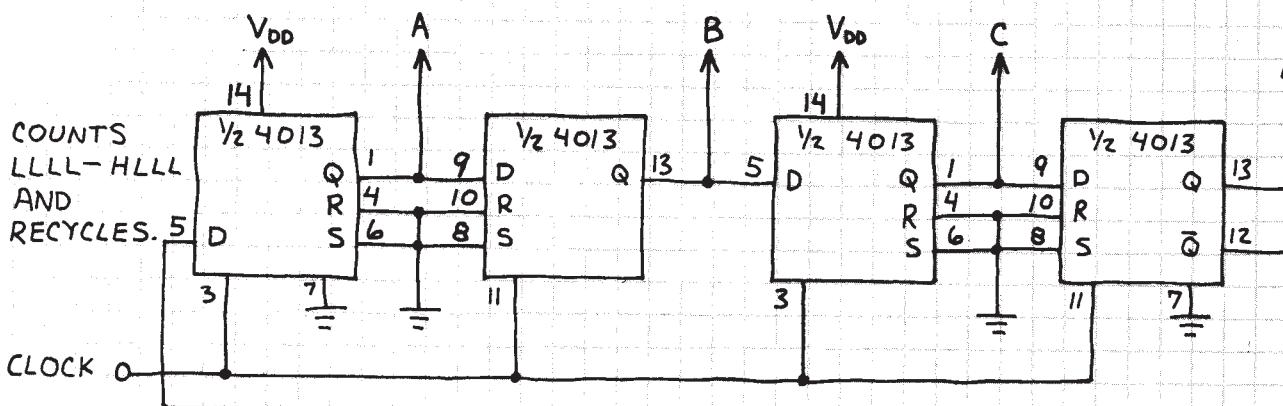

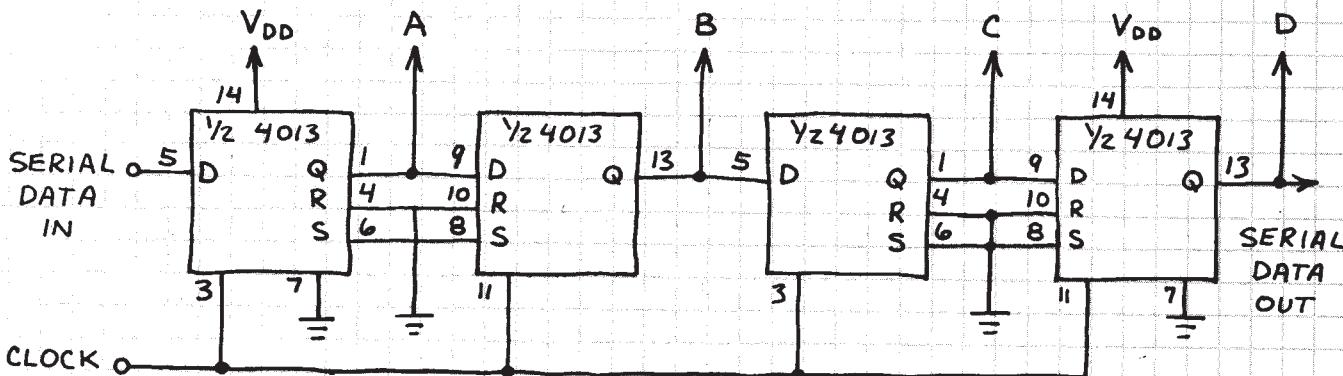
SERIAL IN/OUT, PARALLEL OUT SHIFT REGISTER




DUAL JK FLIP FLOP

4027

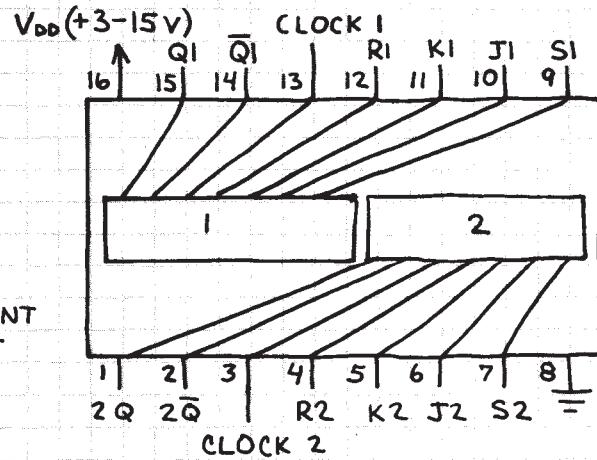
USE FOR DIVIDERS, COUNTERS AND REGISTERS. S (SET) AND R (RESET) INPUTS MUST BE LOW FOR CLOCKING TO OCCUR. MAKING S OR R HIGH SETS OR RESETS FLIP-FLOP INDEPENDENT OF CLOCK. IMPORTANT: ALL INPUTS MUST GO SOMEWHERE!




DIVIDE-BY-2 COUNTER

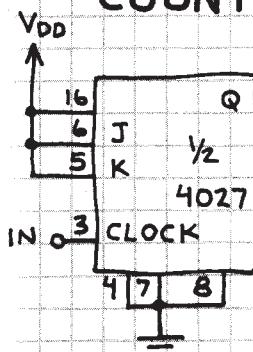


DIVIDE-BY-5 COUNTER

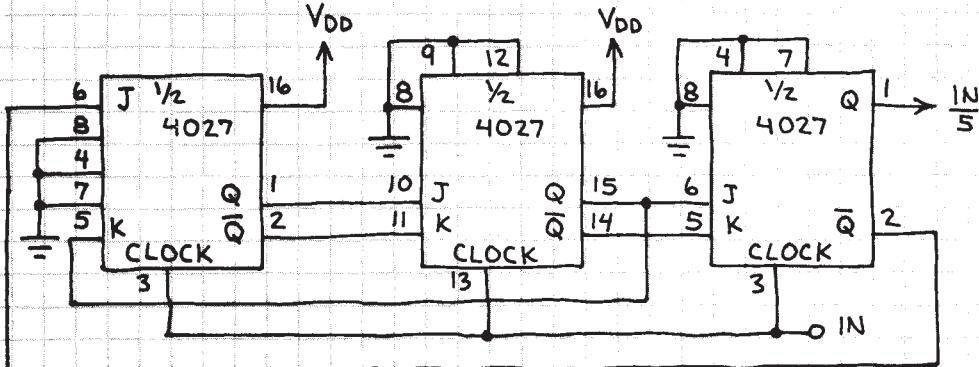


DIVIDE-BY-3 COUNTER

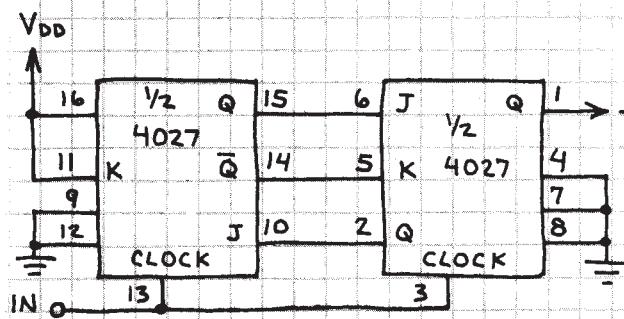

DIVIDE-BY-4 COUNTER

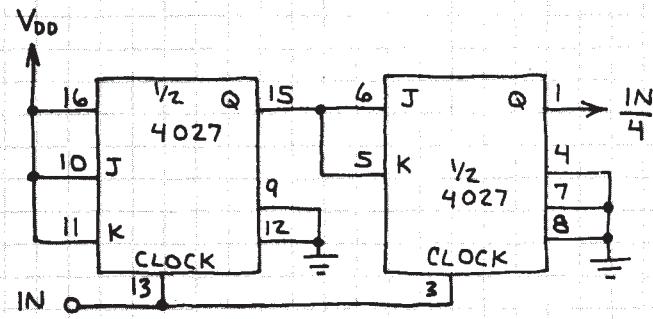


4-BIT SERIAL SHIFT REGISTER

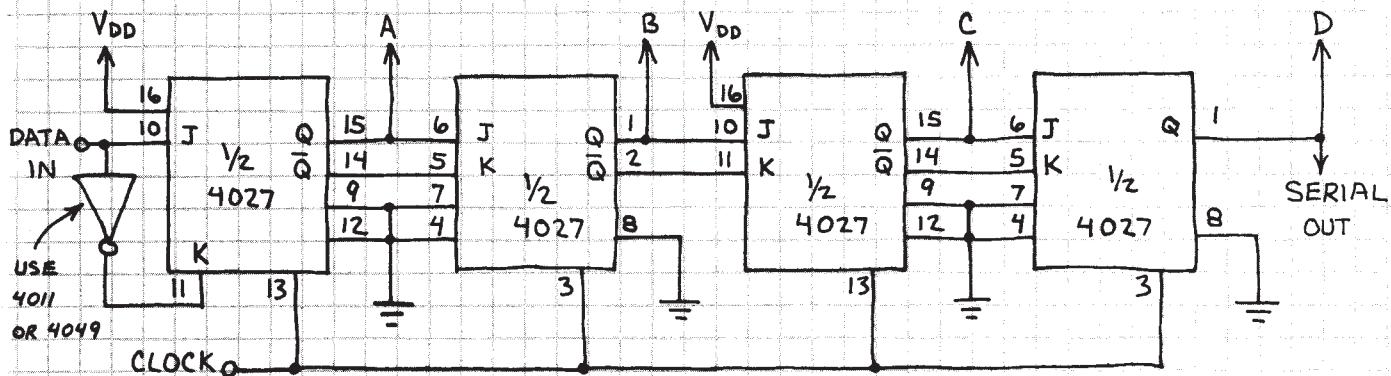

8-STAGE SHIFT REGISTER


4021

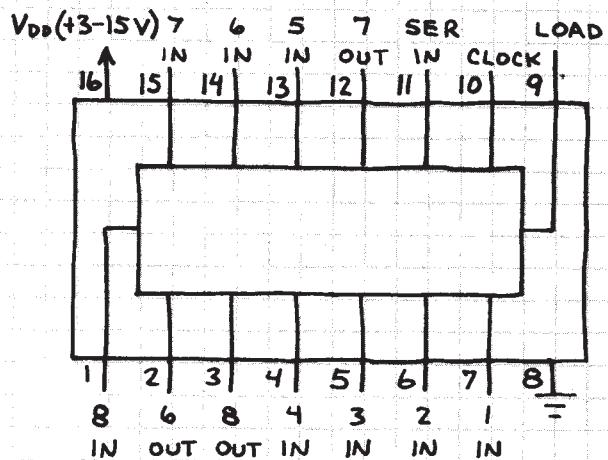PARALLEL INPUT / SERIAL OUTPUT SHIFT REGISTER. ALSO SERIAL INPUT. DATA AT PARALLEL INPUTS IS FORCED INTO THE REGISTER IRRESPECTIVE OF THE CLOCK STATUS WHEN PIN 9 IS MADE HIGH. KEEP PIN 9 LOW FOR NORMAL OPERATION.




PARALLEL-TO-SERIAL DATA CONVERTER

PARALLEL DATA IN

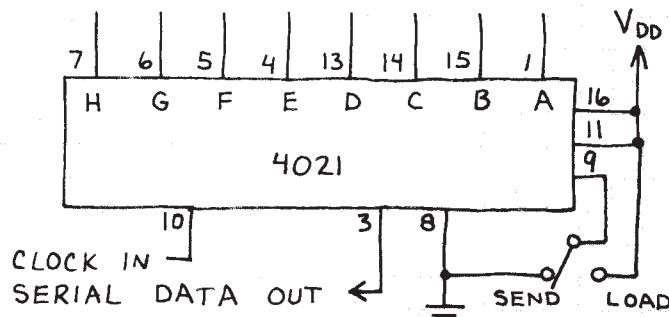


ALL 1's (H's) ARE SENT AFTER THE 8-BIT WORD IS TRANSMITTED.

8-STAGE DELAY LINE

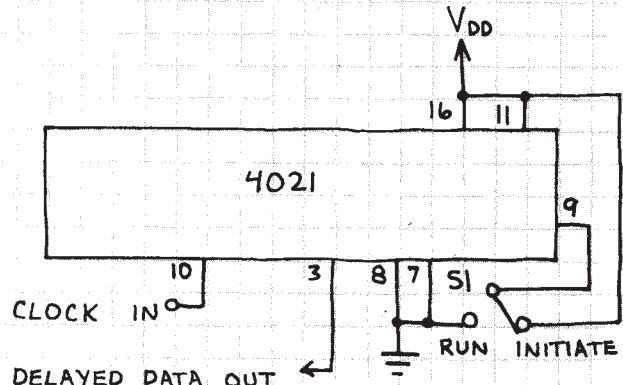


THE FIRST PARALLEL INPUT (PIN 7) IS GROUNDED. THIS LOADS A SINGLE L WHEN SI IS SWITCHED TO INITIATE. THE SINGLE L BIT REACHES THE OUTPUT AFTER 8 CLOCK PULSES.

PSEUDO-RANDOM SEQUENCER

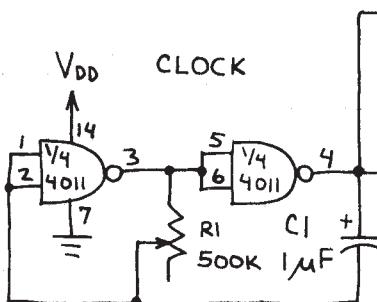

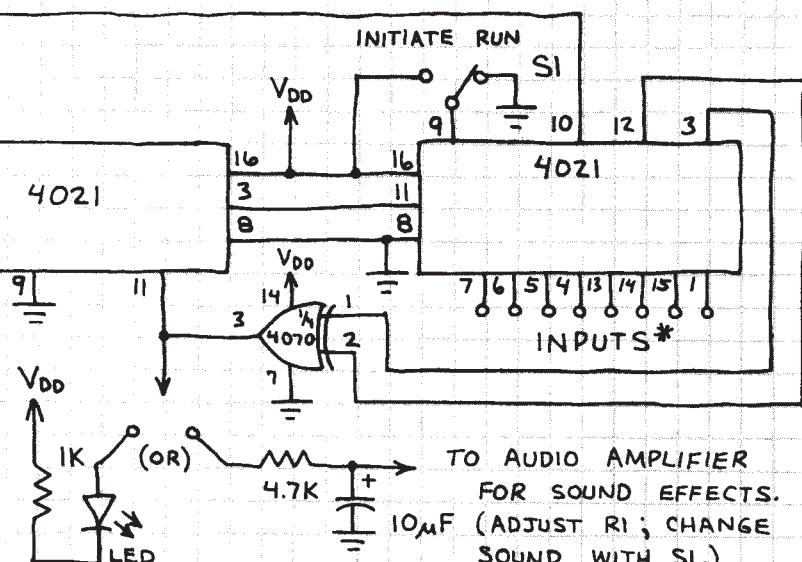
THIS CIRCUIT GENERATES A PSEUDO-RANDOM BIT SEQUENCE AND RECYCLES.* TO CHANGE BIT PATTERN, CONNECT DIFFERENT PATTERNS OF INPUTS OF SECOND 4021 TO V_{DD} OR GROUND.



14-STAGE BINARY COUNTER



4020

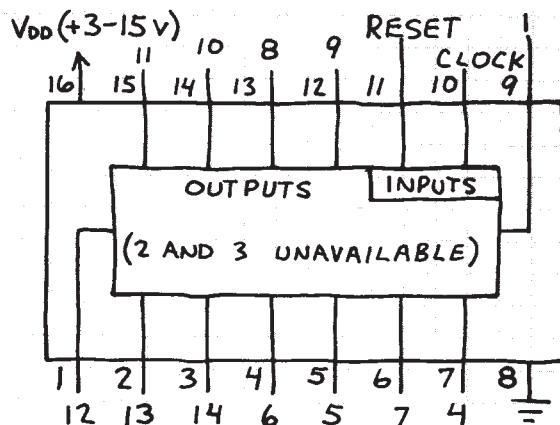A RIPPLE COUNTER WITH CARRY OUTPUT. THE 14-STAGE BINARY COUNT IS COMPLETED IN 16,384 CLOCK PULSES. THIS MAKES POSSIBLE VERY LONG DURATION TIMERS, ASSUMING THE OUTPUTS ARE DECODED. THE OUTPUTS REQUIRE A BRIEF SETTLING TIME AFTER EACH CLOCK PULSE.




14-BIT BINARY COUNTER

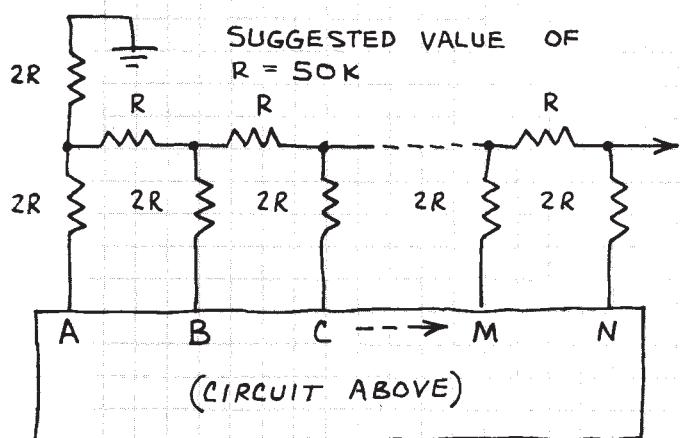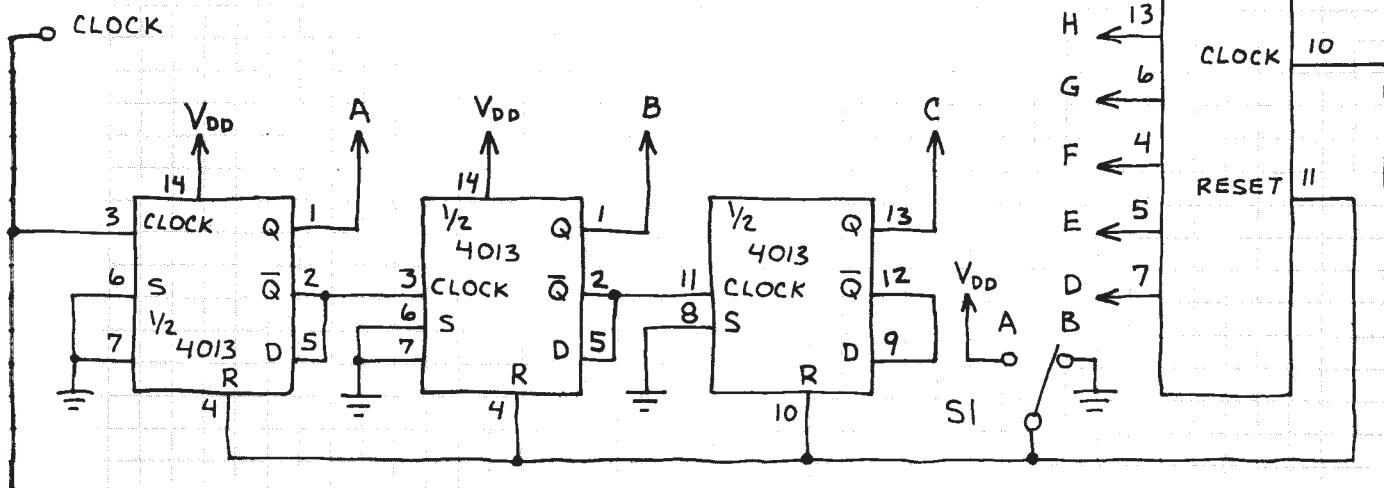THE SECOND AND THIRD OUTPUTS ($\frac{1}{4}$ AND $\frac{1}{8}$) OF THE 4020 ARE NOT AVAILABLE. THIS CIRCUIT INCLUDES A 3-BIT COUNTER TO SUPPLY THE MISSING OUTPUTS. A IS THE LOWEST ORDER OUTPUT.



STAIRCASE GENERATOR

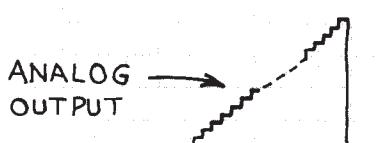


OUTPUT IS A STEPPED VOLTAGE. APPLICATIONS INCLUDE ANALOG-TO-DIGITAL CONVERSION AND WAVEFORM SYNTHESIS.

DECADE COUNTER/DECODER


4017

SEQUENTIALLY MAKES 1-OF-10 OUTPUTS HIGH (OTHERS STAY LOW) IN RESPONSE TO CLOCK PULSES. MANY APPLICATIONS. COUNT TAKES PLACE WHEN PINS 13 AND 15 ARE LOW.



RANDOM NUMBER GENERATOR

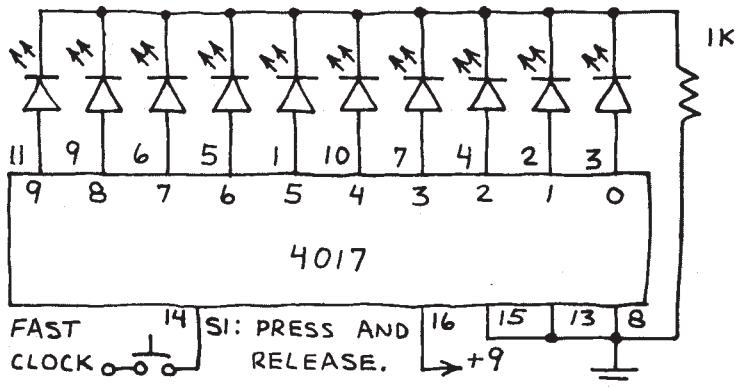


COUNT TO N AND HALT

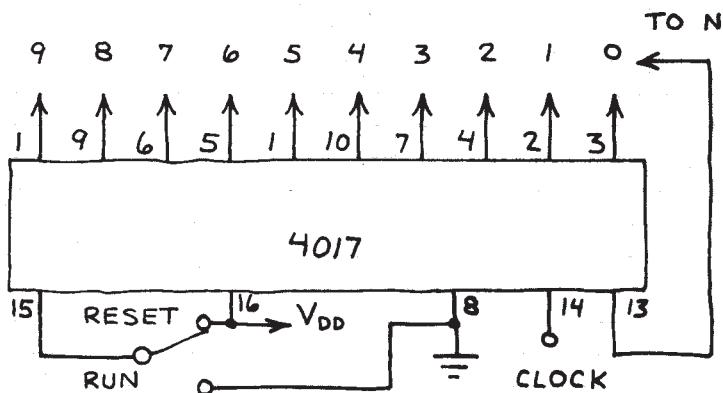

COUNT TO N AND RECYCLE

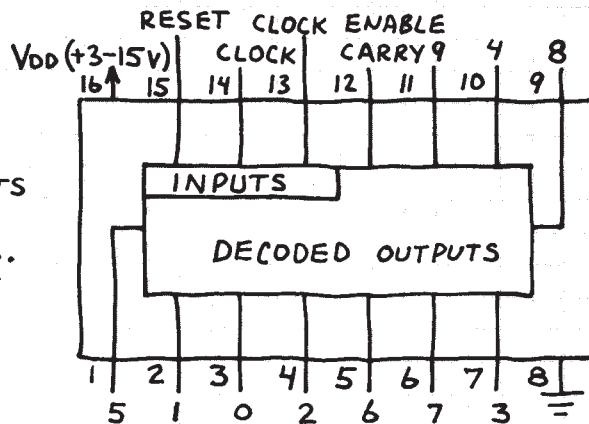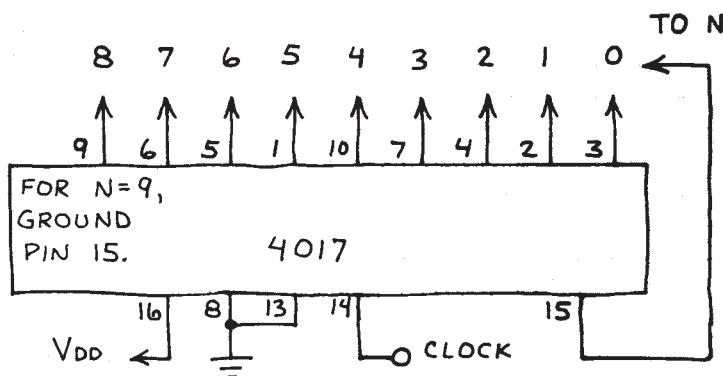

0-99 COUNTER

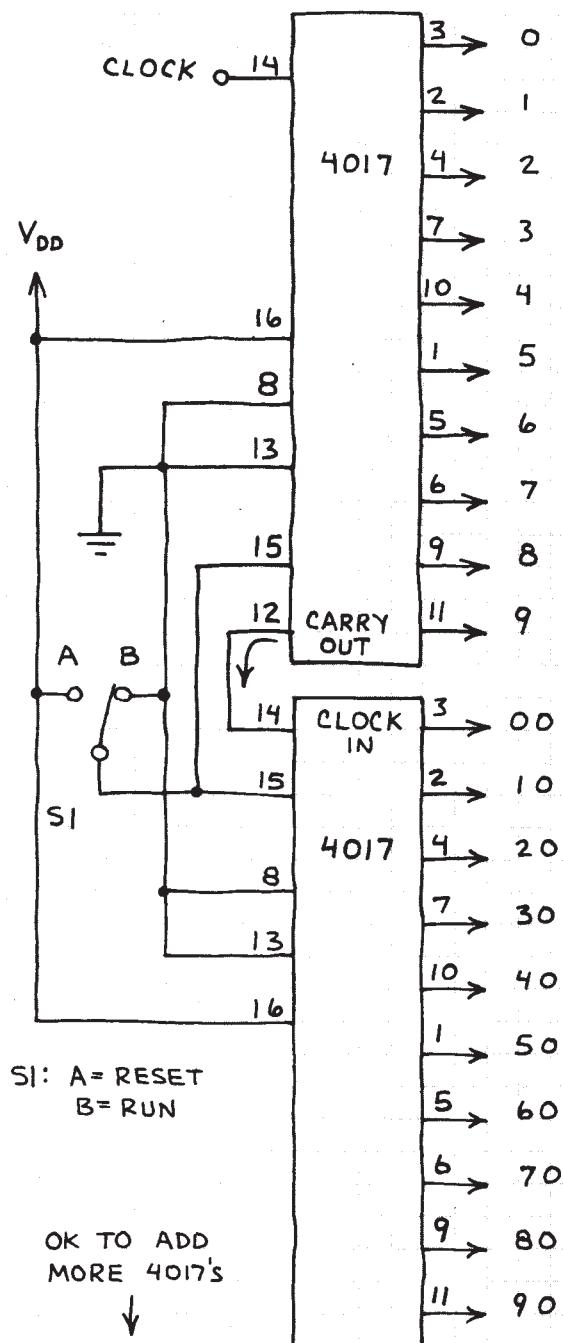


SI: A = RESET
B = RUN

OK TO ADD
MORE 4017'S



DUAL BCD COUNTER

4518

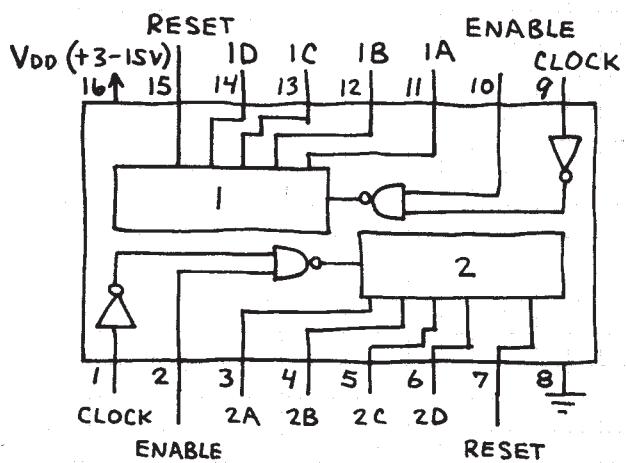TWO SYNCHRONOUS DECADE COUNTERS IN ONE PACKAGE. WHEN ENABLE IS HIGH AND RESET IS LOW, EACH COUNTER ADVANCES ONE COUNT PER CLOCK PULSE.



CASCADED BCD COUNTERS

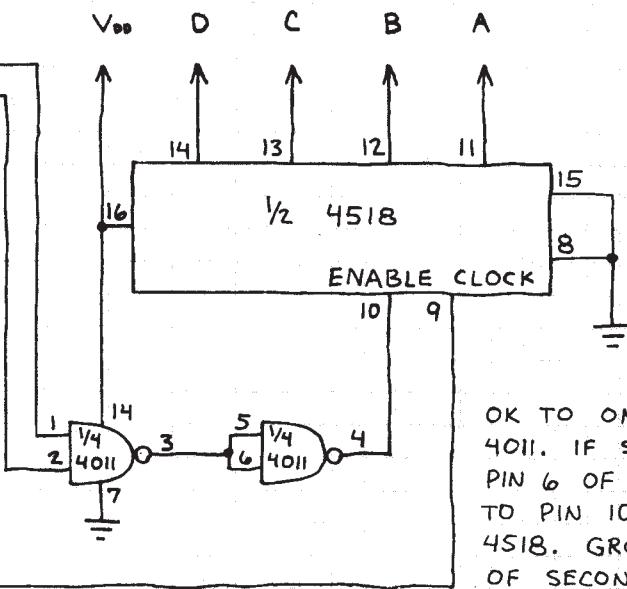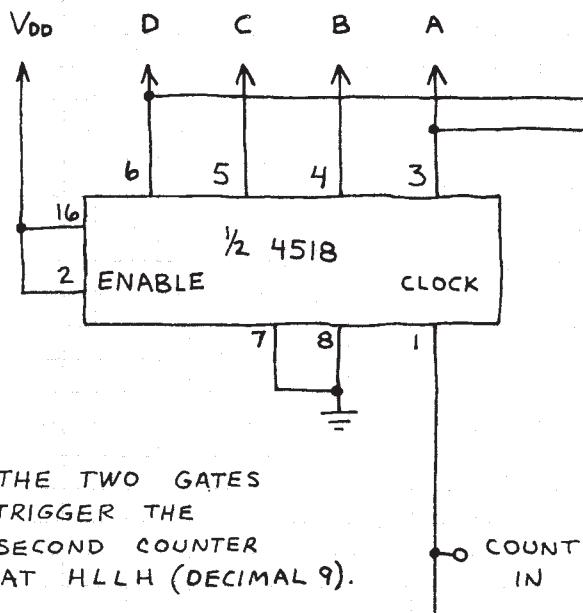


OK TO OMIT THE 4011. IF SO, CONNECT PIN 6 OF FIRST 4518 TO PIN 10 OF SECOND 4518. GROUND PIN 9 OF SECOND 4518 AND APPLY INPUT TO PIN 1 OF FIRST 4518.

BCD KEYBOARD ENCODER


PRESS S0-S9, THEN TOGGLE RESET SWITCH S10 TO VDD AND BACK TO GROUND.

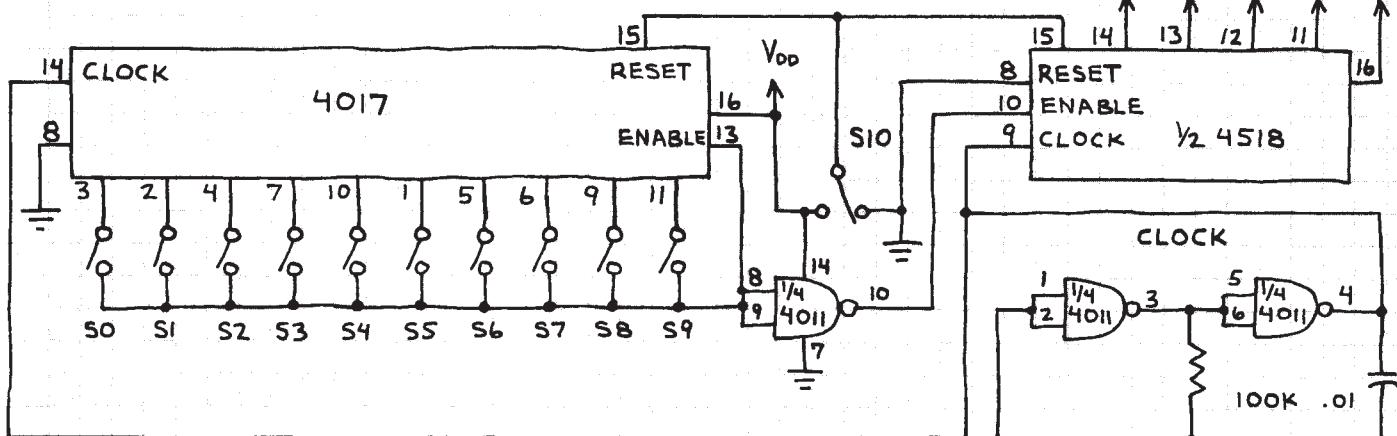BCD EQUIVALENT OF SELECTED KEY (S0-S9) APPEARS → D C B A V_{DD}




3-DIGIT BCD COUNTER MC14553

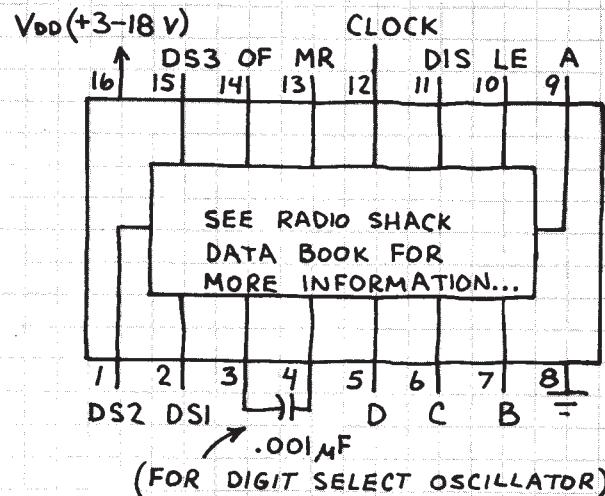
COMPLETE 3-DIGIT COUNTER. USE FOR DO-IT-YOURSELF EVENT AND FREQUENCY COUNTERS. BEGINNERS: GET SOME PRACTICAL CIRCUIT EXPERIENCE BEFORE USING THIS CHIP. PIN EXPLANATIONS: DS (DIGIT SELECT) 1, 2, 3 - SEQUENTIALLY STROBES READOUTS. LE - LATCH ENABLE (WHEN H). DIS - INHIBITS INPUT WHEN H. CLOCK - INPUT. MR - MASTER RESET (WHEN H). OF - OVERFLOW. A, B, C, D - BCD OUTPUTS.



3-DIGIT EVENT COUNTER

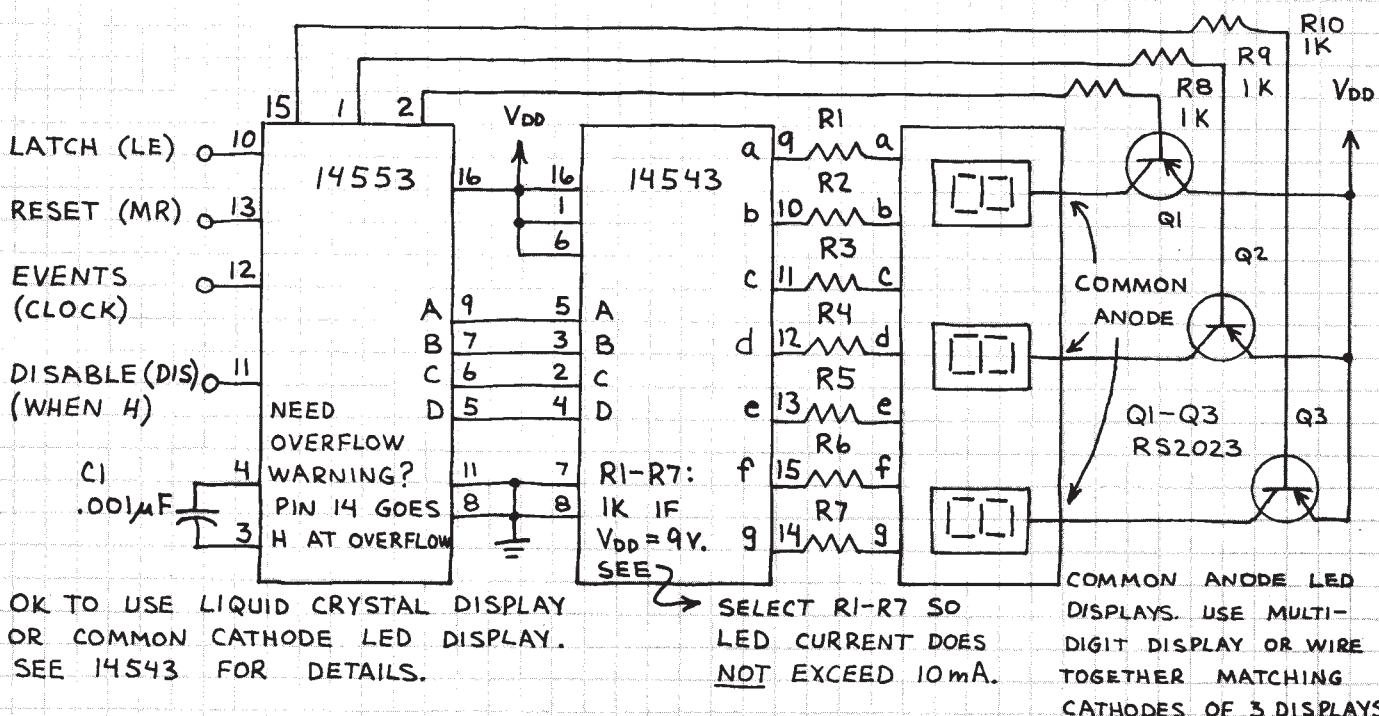


6-DIGIT FREQUENCY COUNTER

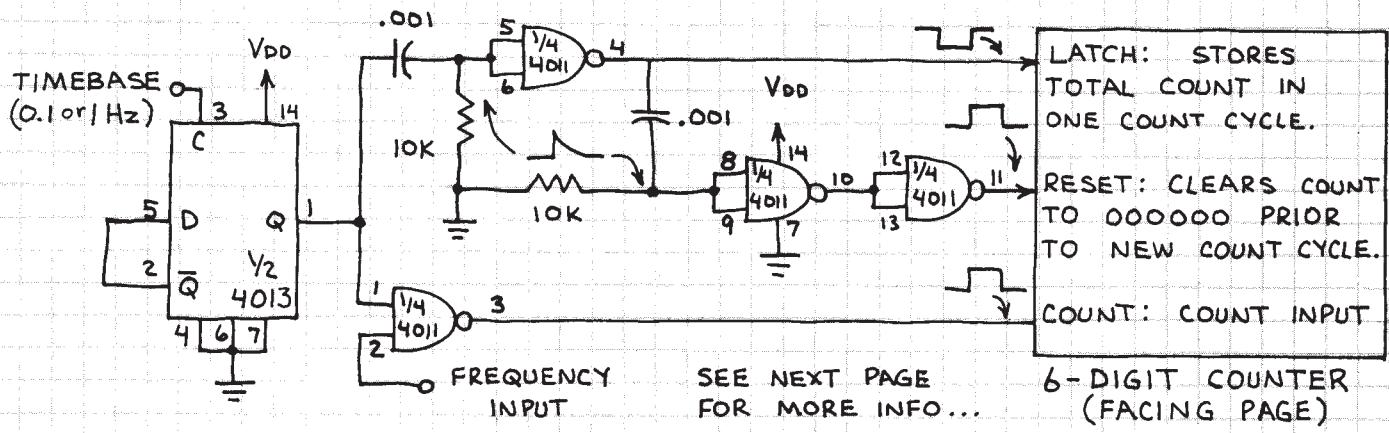

3-DIGIT BCD COUNTER (CONTINUED)

MC14553

6-DIGIT COUNTER

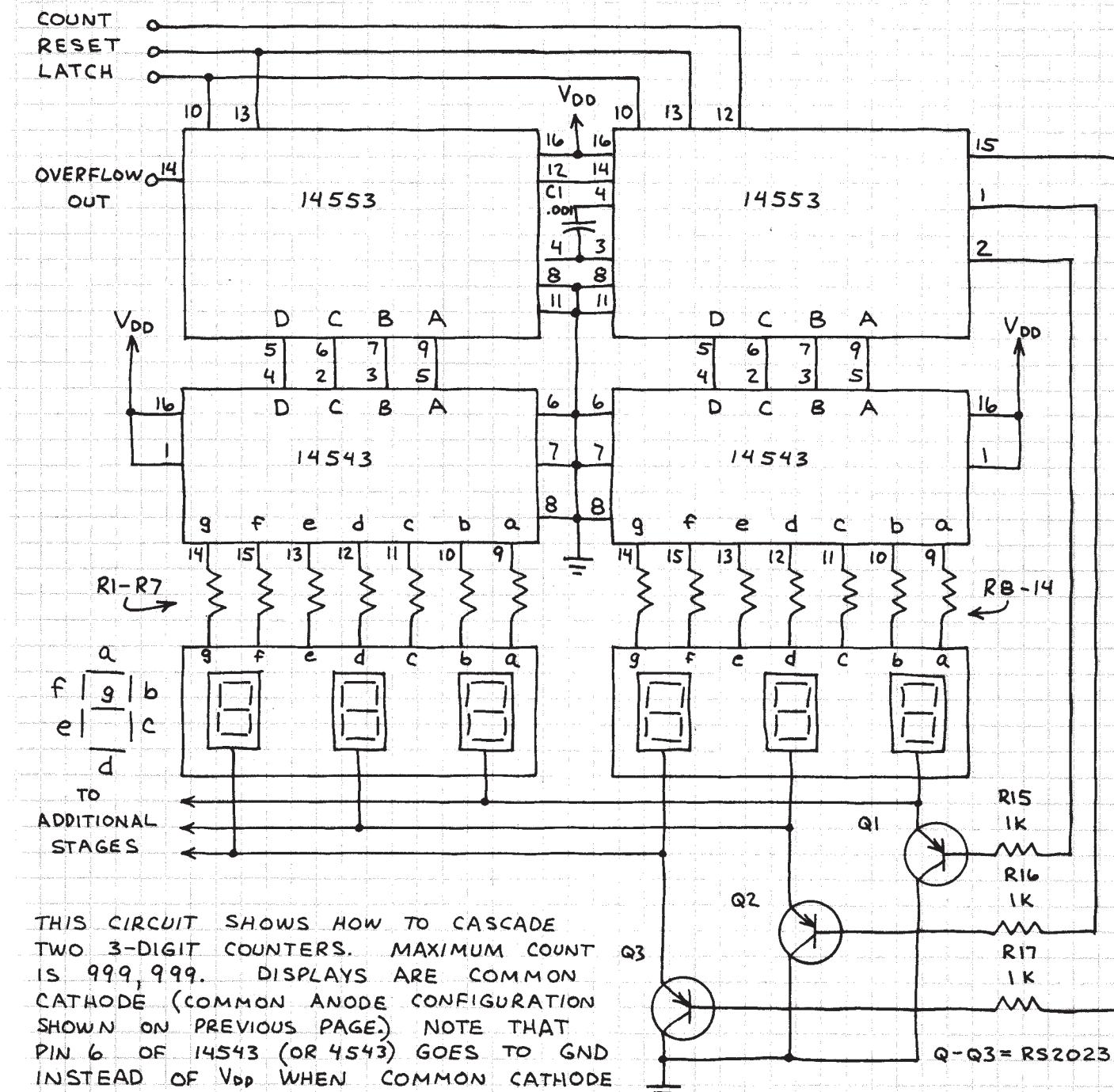


THIS CIRCUIT SHOWS HOW TO CASCADE TWO 3-DIGIT COUNTERS. MAXIMUM COUNT Q3 IS 999,999. DISPLAYS ARE COMMON CATHODE (COMMON ANODE CONFIGURATION SHOWN ON PREVIOUS PAGE). NOTE THAT PIN 6 OF 14543 (OR 4543) GOES TO GND INSTEAD OF V_{DD} WHEN COMMON CATHODE DISPLAY IS USED.

FREQUENCY COUNTER:


USE INPUT AND CONTROL CIRCUIT ON PREVIOUS PAGE. INPUT FREQUENCY SHOULD NOT EXCEED V_{DD}. NON-SQUARE WAVE INPUTS MAY REQUIRE INPUT TAILORING. USE COMPARATOR TO SHARPEN SLOW RISING WAVES.

INPUT BUFFER

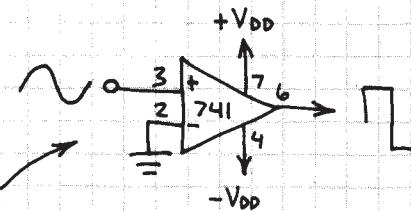


PHASE-LOCKED LOOP (PLL) 4046

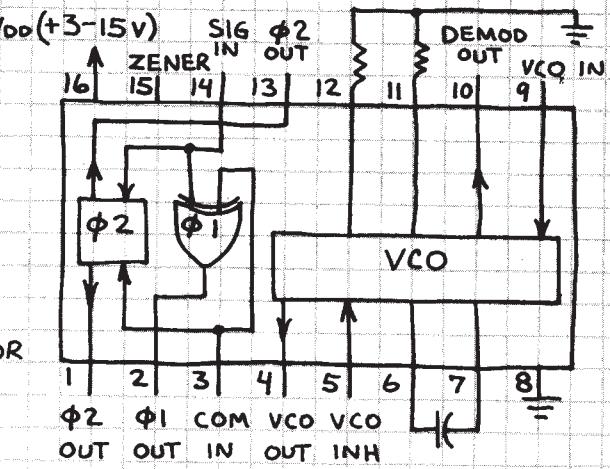
EXCEPTIONALLY VERSATILE CHIP. CONTAINS TWO PHASE COMPARATORS AND VOLTAGE CONTROLLED OSCILLATOR (VCO). USE VCO AND ONE PHASE COMPARATOR TO MAKE PLL. CIRCUITS ON THIS PAGE USE VCO ONLY. SEE RADIO SHACK SEMICONDUCTOR REFERENCE HANDBOOK FOR MORE INFORMATION.




SPEAKER AMPLIFIER*

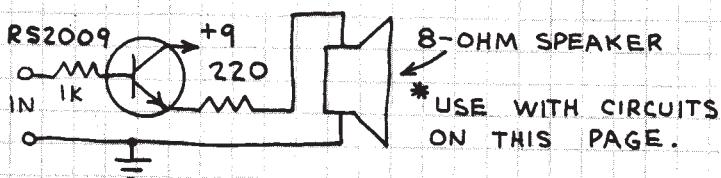

TUNABLE OSCILLATOR

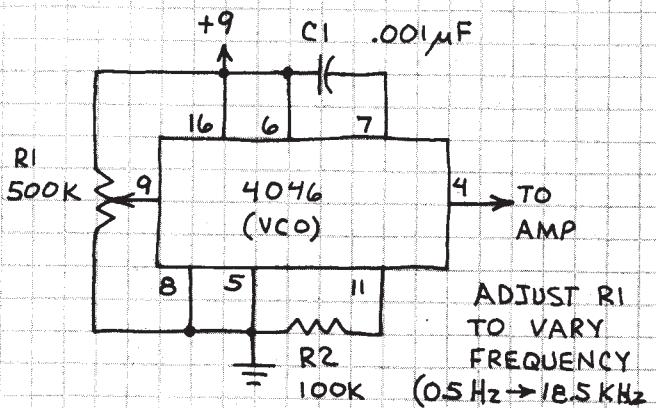


CHIRP BURST SEQUENCER

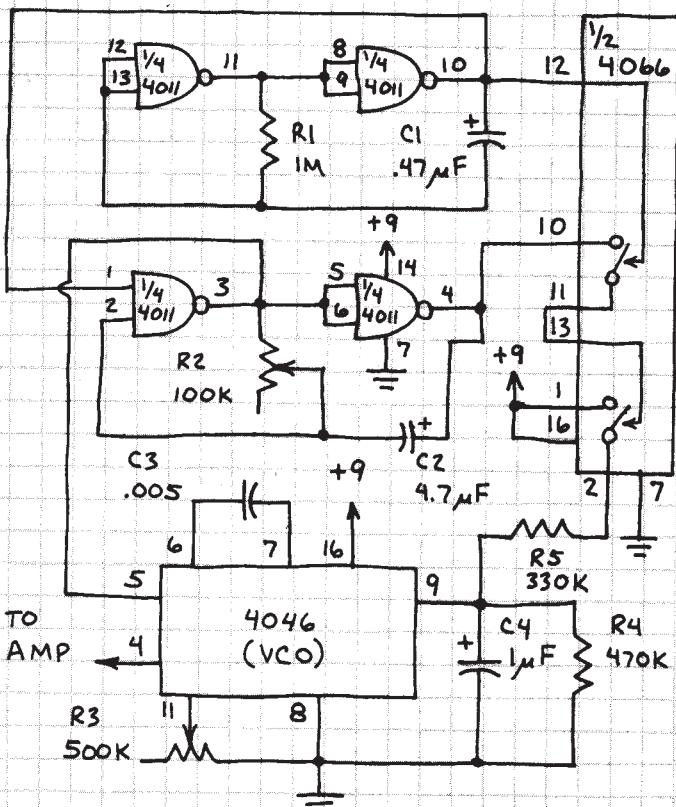

R2: ADJUST FOR 1-4 CHIRPS PER CYCLE.
CHIRPS WILL HAVE DIFFERENT FREQUENCIES.

R3: CONTROLS PITCH OF CHIRPS.
FOR TONES INSTEAD OF CHIRPS,
CONNECT TO PIN 12 INSTEAD OF PIN 11.

SIREN

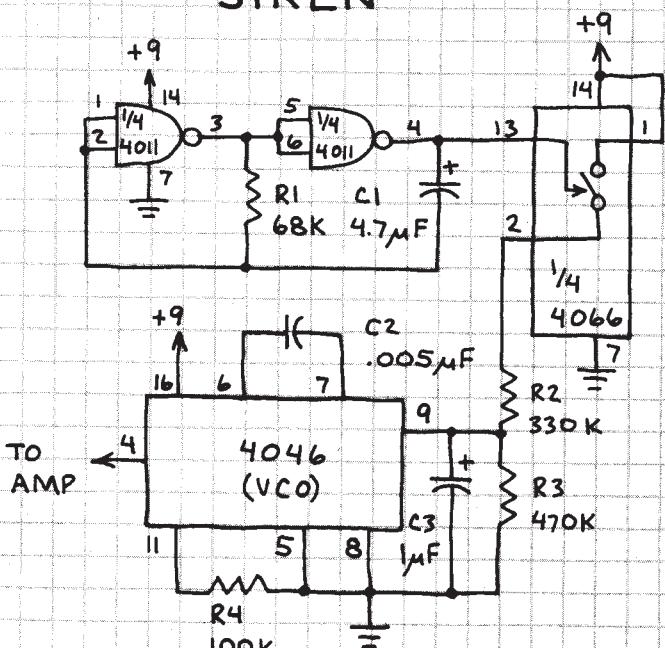


CHANGE R1 OR C1 TO ALTER CYCLE TIME.
CHANGE R4 OR C2 TO ALTER FREQUENCY.
CHANGE R3 OR C3 TO ALTER WAIL.

PHASE LOCKED LOOP (CONTINUED)


4046

SOUND EFFECTS GENERATOR

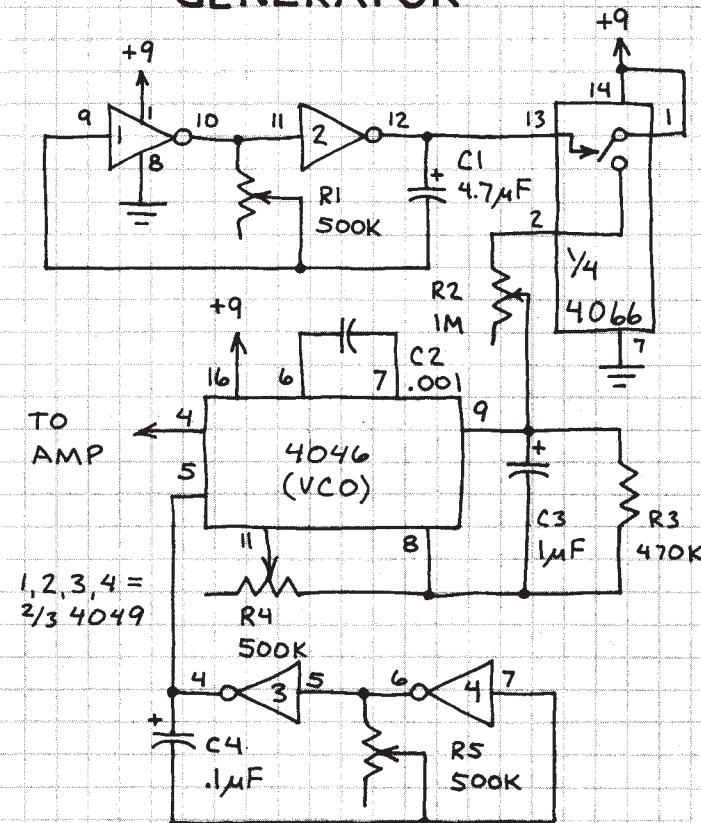

PRODUCES FASCINATING VARIETY OF UNDULATING AND CHOPPED TONES.
R1 CONTROLS CYCLE TIME. R2 CONTROLS DELAY TIME. R4 CONTROLS FREQUENCY RANGE. R5 CONTROLS CHOPPING RATE. CHANGING R5's SETTING GIVES MOST DRAMATIC RESULTS.


FREQUENCY SYNTHESIZER

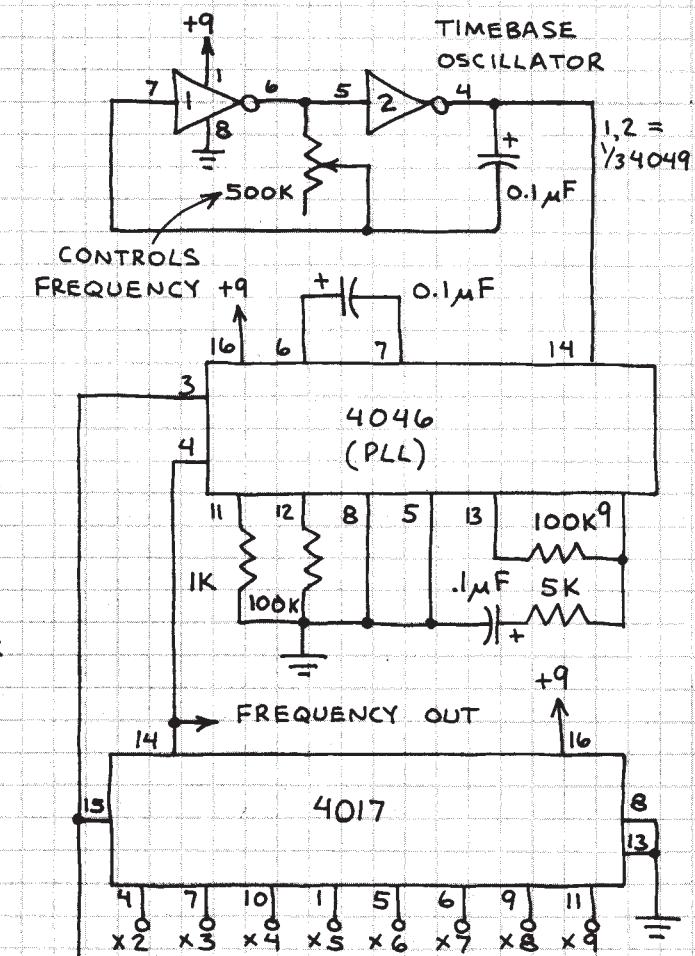


SELECT TIMEBASE FREQUENCY MULTIPLICATION FACTOR. SET TIMEBASE TO ~ 100 Hz.

TONE BURST GENERATOR

LOCK INDICATOR *

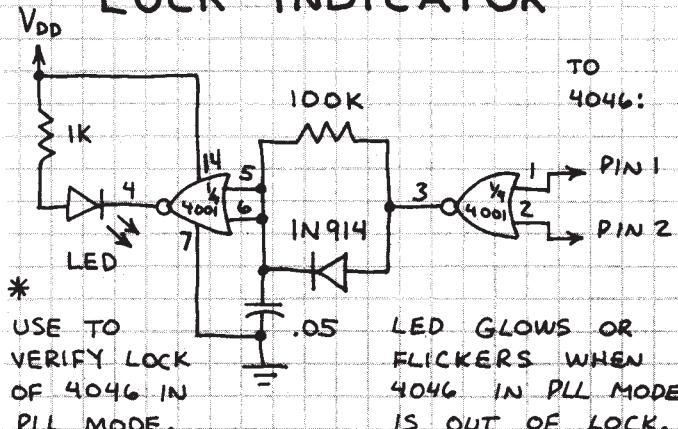

USE TO VERIFY LOCK OF 4046 IN PLL MODE.

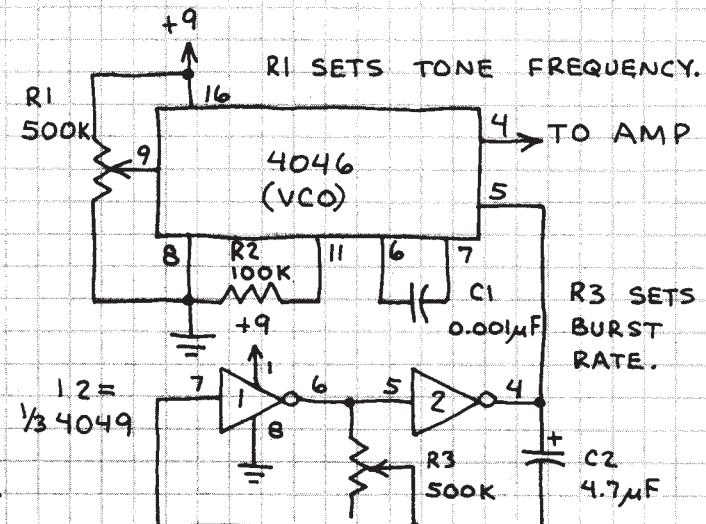


1024-BIT STATIC RAM

2102L



1024 1-BIT STORAGE LOCATIONS ADDRESSED BY PINS A0-A9. TTL/LS COMPATIBLE.
CE (CHIP ENABLE) INPUT CONTROLS R/W (READ/WRITE) OPERATIONS. 3-STATE OUTPUTS.

CE | R/W | OPERATION

L	L	WRITE (LOADS BIT AT PIN 11)
L	H	READ (OUTPUTS BIT AT PIN 12)
H	X	HIZ (OUTPUT ENTERS THIRD STATE)

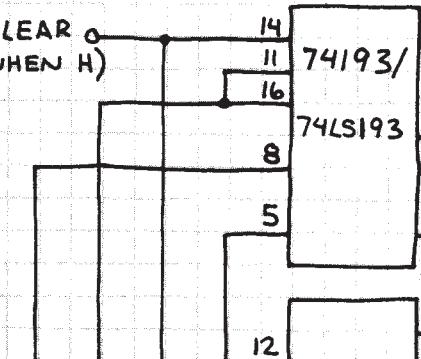

2102L ADDRESSING CIRCUIT

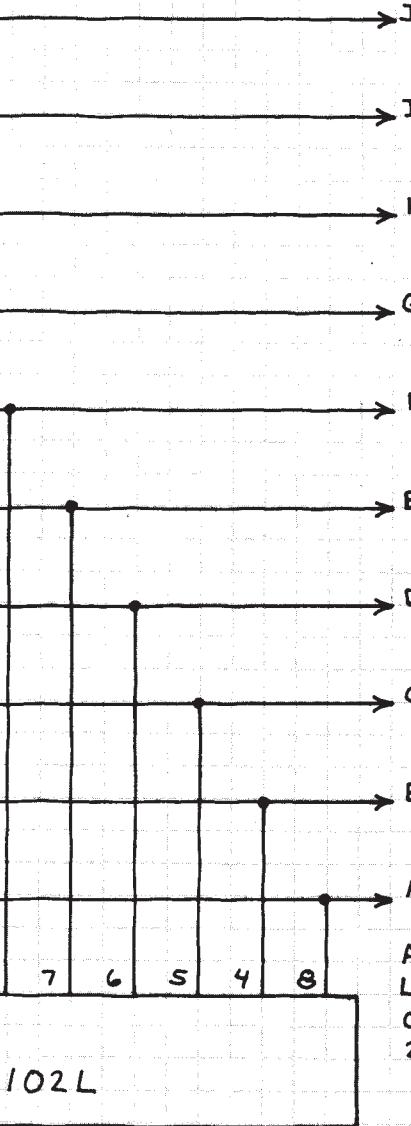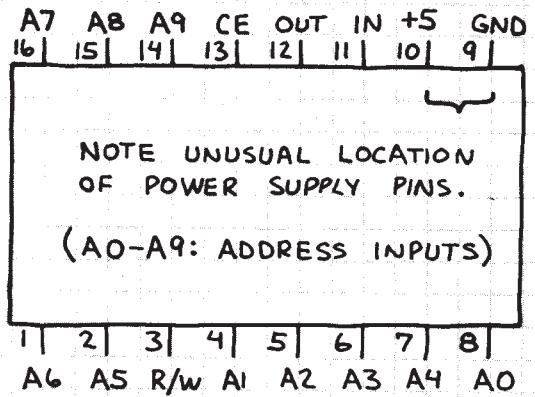

THE ADDRESS INPUTS MUST BE STABLE DURING R/W OPERATIONS.


1024-BIT STATIC RAM (CONTINUED)

2102L

ADDING PROGRAMMED OR MANUAL JUMP


ADD THESE CONNECTIONS TO THE ADDRESSING CIRCUIT ON FACING PAGE.

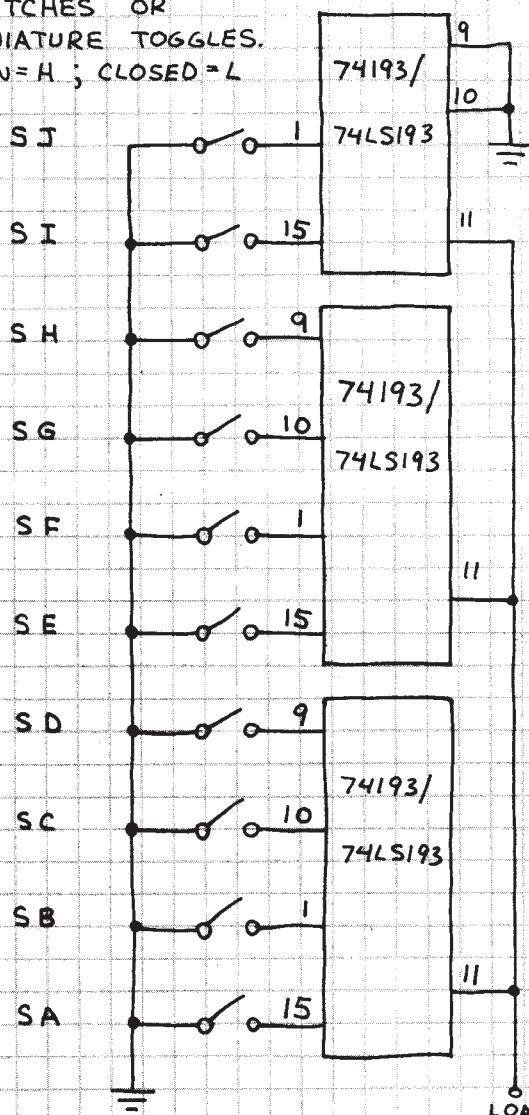SA-SJ: USE
8-POSITION DIP
SWITCHES OR
MINIATURE TOGGLERS.
OPEN = H; CLOSED = L




NORMALLY THE LOAD INPUT IS HIGH.
MAKING LOAD LOW LOADS THE
ADDRESS PROGRAMMED IN SWITCHES
SA-SJ INTO THE 74193'S. THIS
PERMITS A PROGRAMMED JUMP
OR A MANUAL JUMP TO ANY
ADDRESS.

SINGLE I/O PORT

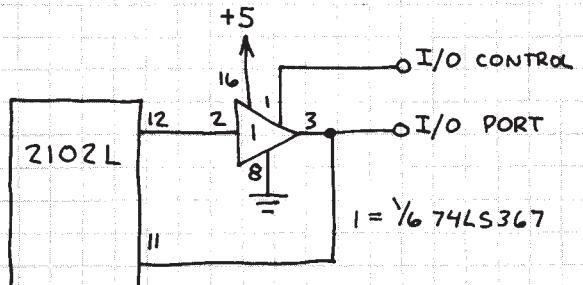

ADD THIS CIRCUIT TO THE ADDRESSING CIRCUIT ON FACING PAGE. WHEN I/O (INPUT/OUTPUT) CONTROL IS H, PIN 3 OF THE 74LS367 ENTERS THIRD STATE (HI-Z) AND I/O PORT ACCEPTS INPUT DATA. WHEN PIN 3 OF THE 74LS367 IS L, I/O PORT OUTPUTS DATA. BOTH THESE OPERATIONS ARE DEPENDENT UPON THE STATUS OF THE 2102L CONTROL INPUTS.

CASCADING 2102L'S

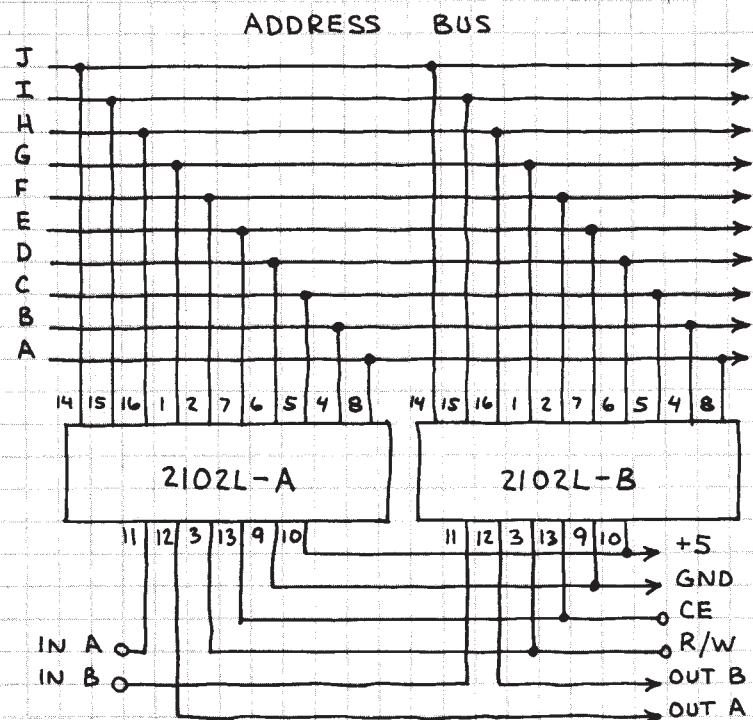


1024 x 4-BIT RAM


2114L / 4045

1024-4-BIT STORAGE LOCATIONS ADDRESSED BY PINS A0-A9. TTL/LS COMPATIBLE.

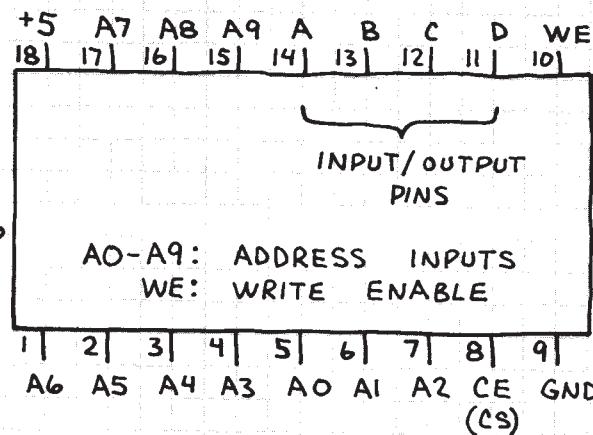FOR READ/WRITE OPERATIONS, CE (CHIP ENABLE, ALSO CALLED CHIP SELECT) MUST BE LOW. WE INPUT MUST BE LOW TO WRITE (LOAD) DATA INTO CHIP. WHEN WE IS HIGH, DATA IN ADDRESSED LOCATION APPEARS AT INPUT/OUTPUT PINS. IDEAL CHIP FOR DO-IT-YOURSELF MICROCOMPUTERS AND CONTROLLERS.



2114L ADDRESSING CIRCUIT

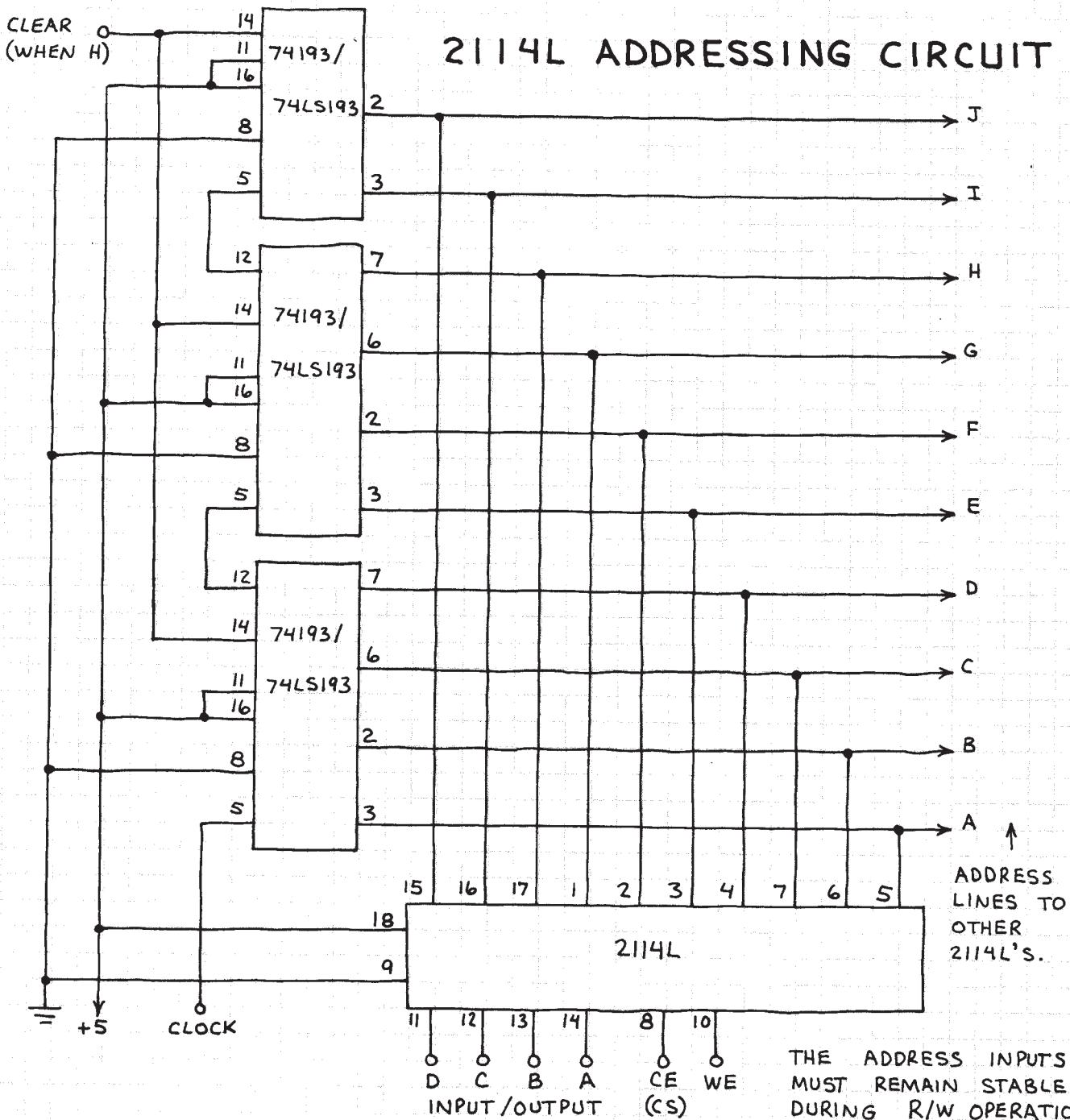

1024 x 4-BIT RAM (CONTINUED)


2114L/4045

1024-NIBBLE

DATA LOADING CIRCUIT

(NIBBLE = 4-BIT WORD OR $\frac{1}{2}$ 8-BIT WORD)

SI-CLEAR

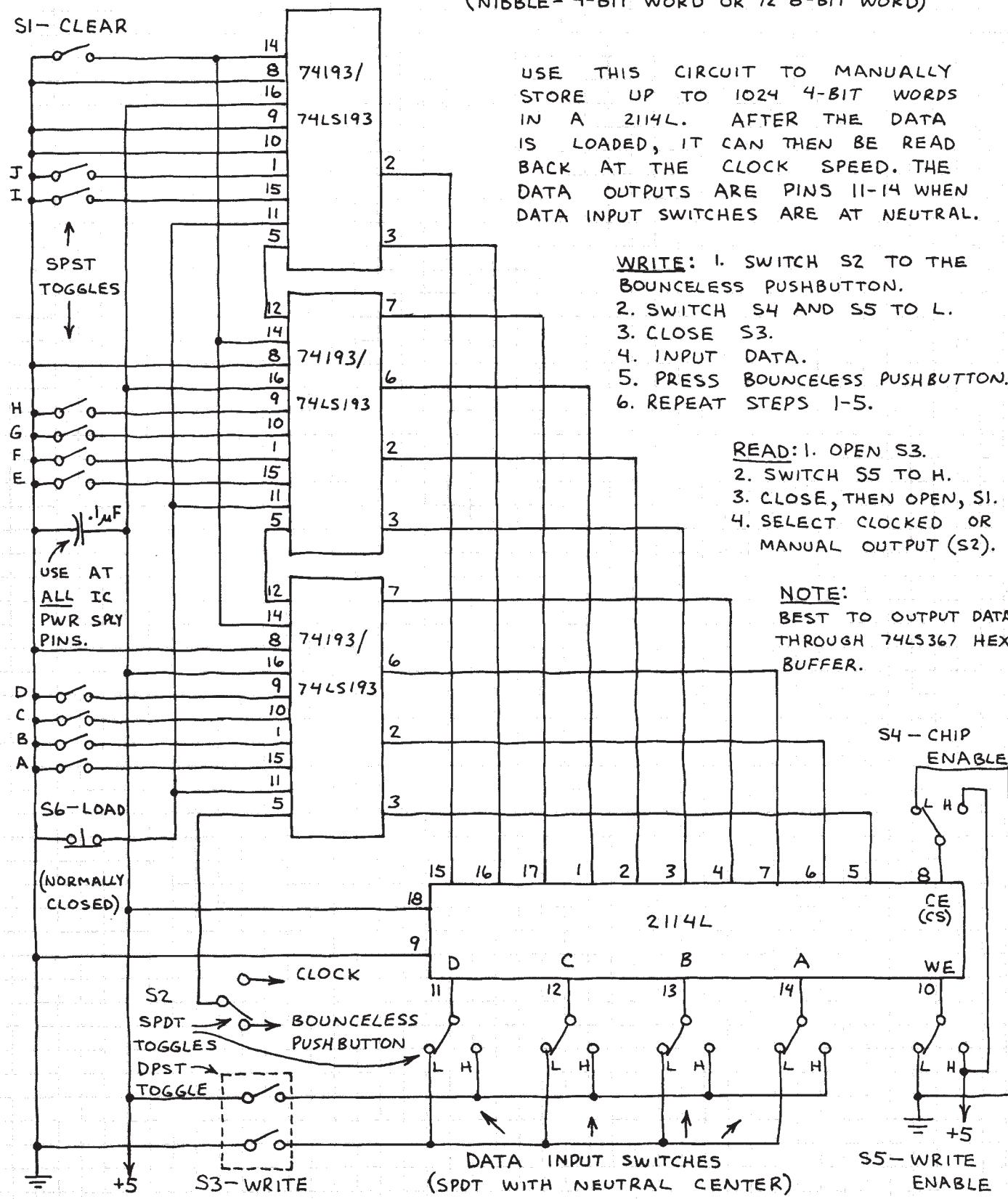


USE THIS CIRCUIT TO MANUALLY STORE UP TO 1024 4-BIT WORDS IN A 2114L. AFTER THE DATA IS LOADED, IT CAN THEN BE READ BACK AT THE CLOCK SPEED. THE DATA OUTPUTS ARE PINS 11-14 WHEN DATA INPUT SWITCHES ARE AT NEUTRAL.

WRITE: 1. SWITCH S2 TO THE BOUNCELESS PUSHBUTTON.
2. SWITCH S4 AND S5 TO L.
3. CLOSE S3.
4. INPUT DATA.
5. PRESS BOUNCELESS PUSHBUTTON.
6. REPEAT STEPS 1-5.

READ: 1. OPEN S3.
2. SWITCH S5 TO H.
3. CLOSE, THEN OPEN, S1.
4. SELECT CLOCKED OR MANUAL OUTPUT (S2).

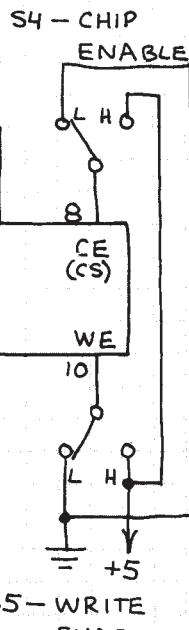NOTE:
BEST TO OUTPUT DATA THROUGH 74LS367 HEX BUFFER.



COMPLEX SOUND GENERATOR

SN76477N / SN76488N


NOTE: THE SN76488 INCLUDES BUILT-IN SPEAKER AMPLIFIER. THE SN76477 DOES NOT.

INCORPORATES S.L.F. ENVELOPE SELECT 1 (SUPER LOW FREQUENCY OSCILLATOR), VCO (VOLTAGE CONTROLLED OSCILLATOR), NOISE GENERATOR AND A MIXER THAT ALLOWS THE OUTPUTS FROM ONE OR MORE OF THE ABOVE TO BE COMBINED. CAN BE OPERATED TOGETHER WITH APPROPRIATE RESISTORS AND CAPACITORS TO PRODUCE MANY KINDS OF SOUNDS. CAN BE CONTROLLED BY EXTERNAL LOGIC. SEE DATA SHEET INSTRUCTIONS. SUPPLIED WITH CHIP FOR MORE INFO. SN76477 AND SN76488 ARE INTERCHANGEABLE... BUT SN76488 DOES NOT NEED OUTPUT AMPLIFIER. NOTE: THIS CHIP IS EASY +4.5-12V (9V BEST) TO USE IF YOU FOLLOW DATA SHEET INSTRUCTIONS.

ENVELOPE SELECT 1
GROUND 2
EXTERNAL NOISE CLOCK 3
NOISE CLOCK 4
NOISE FILTER 5
NOISE FILTER 6
DECAY 7
ATTACK/DECAY 8
SYSTEM ENABLE 9
ATTACK 10
AMPLITUDE 11
FEEDBACK 12
AUDIO OUTPUT 13
14

PINOUTS FOR BOTH CHIPS ARE IDENTICAL EXCEPT:	28 ENVELOPE SELECT 2
SN76488 - PIN 12 IS AN AUDIO INPUT.	27 MIXER SELECT C
	26 MIXER SELECT A
	25 MIXER SELECT B
	24 ONE-SHOT
	23 ONE-SHOT
	22 VCO SELECT
SN76477 REQUIRES SIMPLE OUTPUT AMPLIFIER.	21 S.L.F.
	20 S.L.F.
	19 PITCH CONTROL
SN76488 OUTPUT:	18 VCO
	17 VCO
	16 EXTERNAL VCO
	15 VREG


PERCUSSION SYNTHESIZER

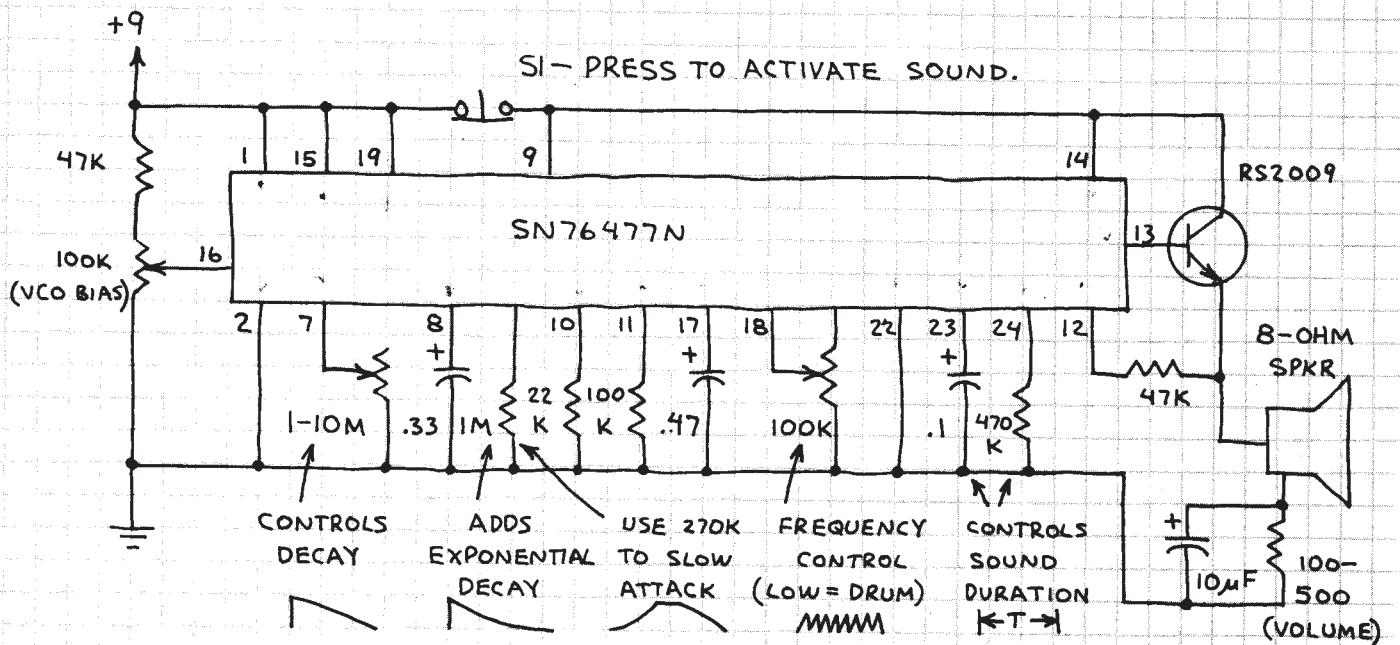

COMPLEX SOUND GENERATOR (CONTINUED)


SN76477N / SN76488N

NOISE GENERATOR

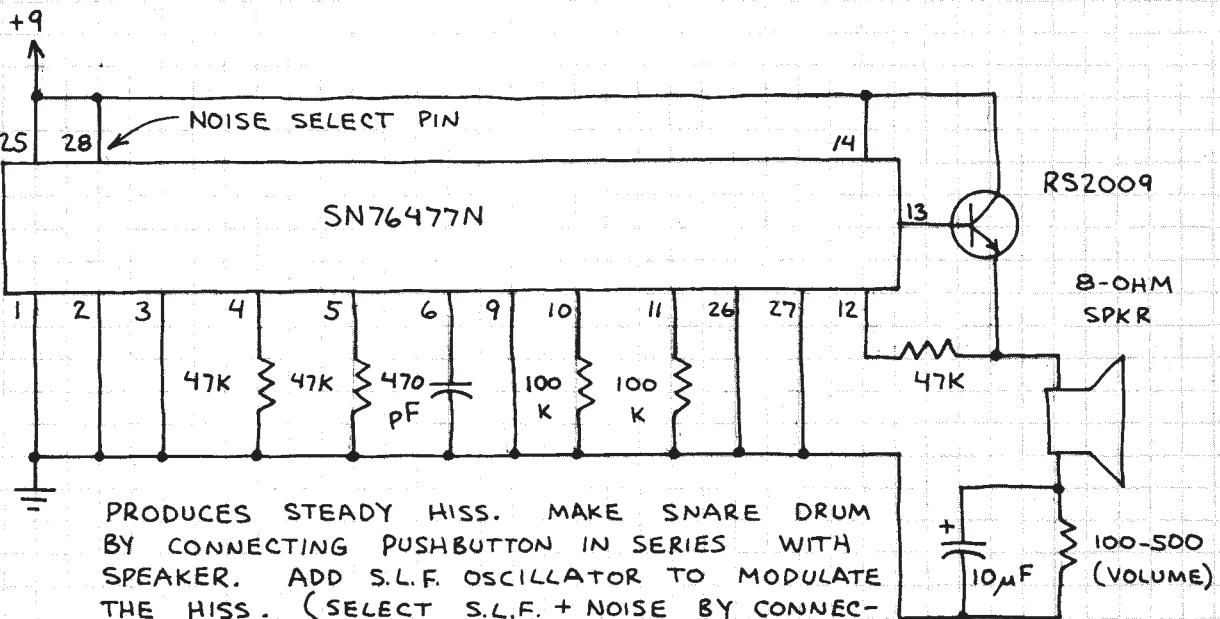

PRODUCES STEADY HISS. MAKE SNARE DRUM BY CONNECTING PUSHBUTTON IN SERIES WITH SPEAKER. ADD S.L.F. OSCILLATOR TO MODULATE THE HISS. (SELECT S.L.F. + NOISE BY CONNECTING PINS 25 AND 26 TO GND AND PIN 27 TO +9V. ADD 1M POT FROM PIN 20 TO GND AND 1μF CAPACITOR FROM PIN 21 TO GND.) SOUNDS LIKE STEAM TRAIN OR PROPELLER AIRCRAFT DEPENDING ON ADJUSTMENT OF 1M POT.

UNIVERSAL UP-DOWN TONE GENERATOR

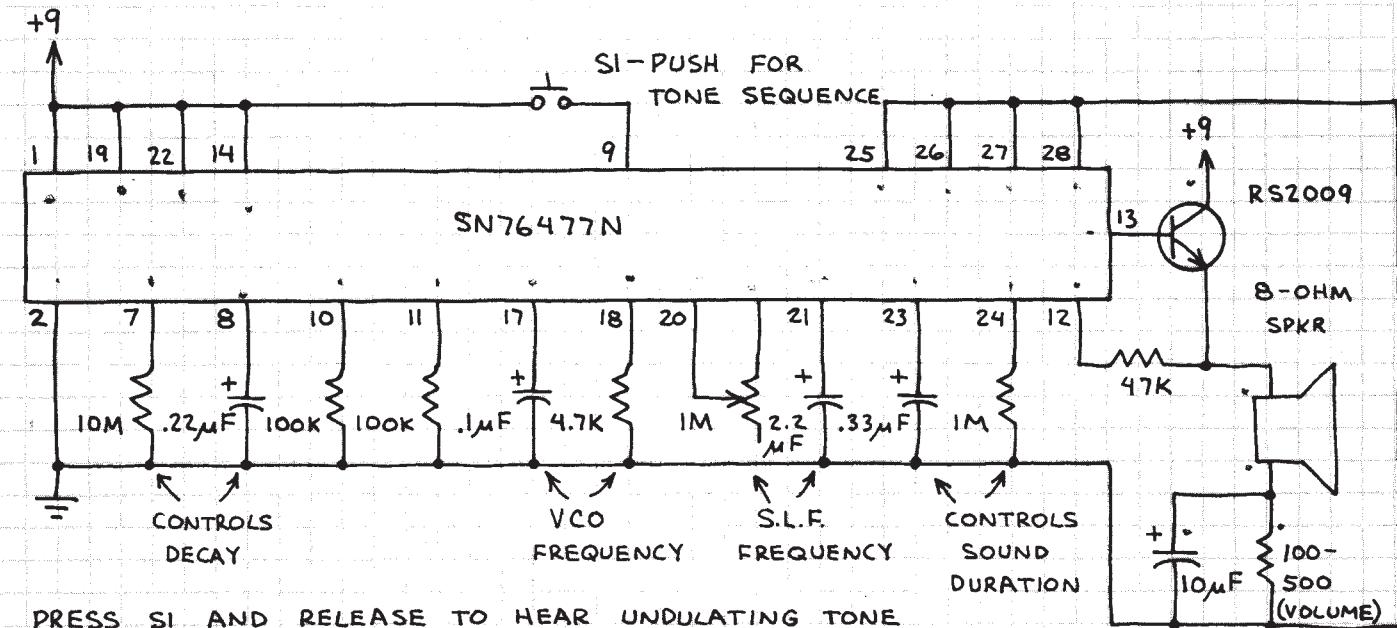


PRESS SI AND RELEASE TO HEAR UNDULATING TONE THAT GRADUALLY DECAYS AND STOPS. CHANGE VCO AND S.L.F. COMPONENTS FOR MANY DIFFERENT SOUND EFFECTS RANGING FROM SIREN TO SCIENCE FICTION MOVIE SOUNDS. FOR CONTINUOUS SOUND, OMIT COMPONENTS AT PINS 7, 8, 23, 24 AND GROUND PIN 9.

DUAL ANALOG DELAY LINE


SAD-1024A

CONTAINS TWO INDEPENDENT 512 STAGE SERIAL ANALOG DELAY (SAD) LINES (ALSO CALLED ANALOG SHIFT REGISTERS). OK TO USE EACH 512 STAGE SAD SEPARATELY OR IN SERIES. ANALOG DELAYS OF UP TO $\frac{1}{2}$ SECOND CAN BE ACHIEVED. A 2-PHASE CLOCK IS REQUIRED TO DRIVE INPUTS ϕ_1 AND ϕ_2 . INPUT DATA RIDES THROUGH THE SAD ON ALTERNATING CLOCK PULSES AND APPEAR AT THE TWO OUTPUTS AFTER PASSING THROUGH ALL 512 STAGES. CONNECT V_{bb} TO V_{dd} (PIN 7) OR, FOR OPTIMUM RESULTS, TO 1 VOLT BELOW V_{dd} . THIS CHIP CAN BE TRICKY TO USE SINCE SEVERAL EXTERNAL ADJUSTMENTS ARE REQUIRED. CIRCUITS ON THIS PAGE EXPLAIN OPERATING REQUIREMENTS WHILE A COMPLETE CIRCUIT IS SHOWN ON FACING PAGE.



SAD IN/OUT CONTROLS

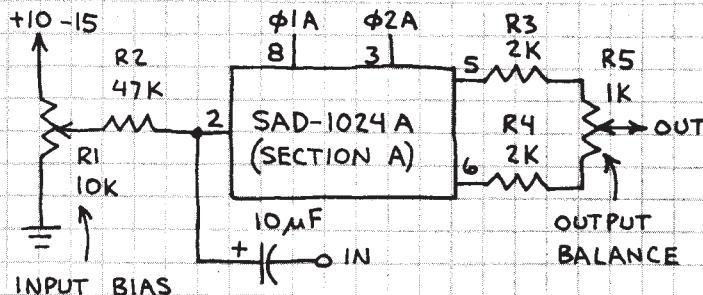

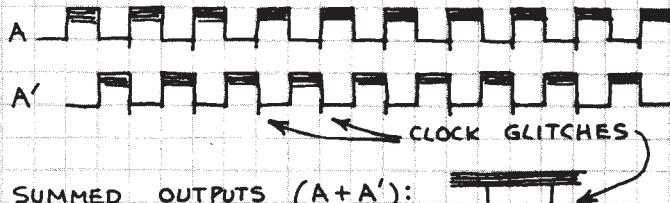ADJUST R_1 (INPUT BIAS) FOR OPTIMUM AUDIO OUTPUT. OUTPUTS APPEAR LIKE THIS ON A SCOPE:




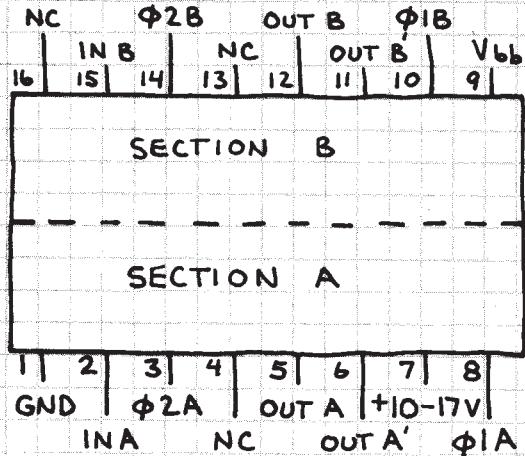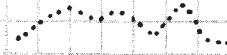SET SCOPE TO VISUALIZE INPUT SIGNAL (COMPRESSING CLOCK RATE):




CAUTION: THIS NMOS CHIP IS VULNERABLE TO DAMAGE FROM STATIC DISCHARGE! FOLLOW CMOS HANDLING PROCEDURES.

SERIAL OPERATION

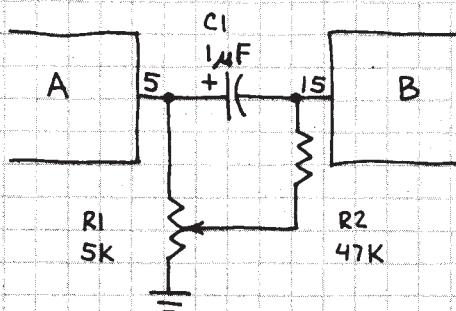

R_1 CONTROLS BIAS TO SECTION B. NOTE THAT ONLY ONE OUTPUT OF A IS CONNECTED TO INPUT OF B.

OUTPUT SUMMER

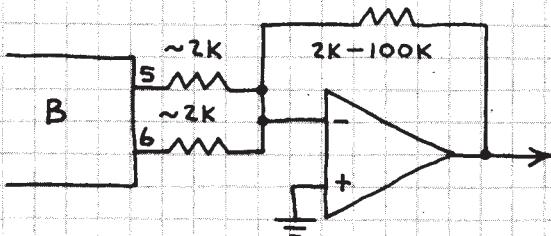


ANY OP-AMP CAN BE USED, BUT LOW NOISE FET INPUT TYPES ARE BEST.

DUAL ANALOG DELAY LINE (CONTINUED)


SAD-1024A

ADJUSTABLE FLANGER OR PHASER

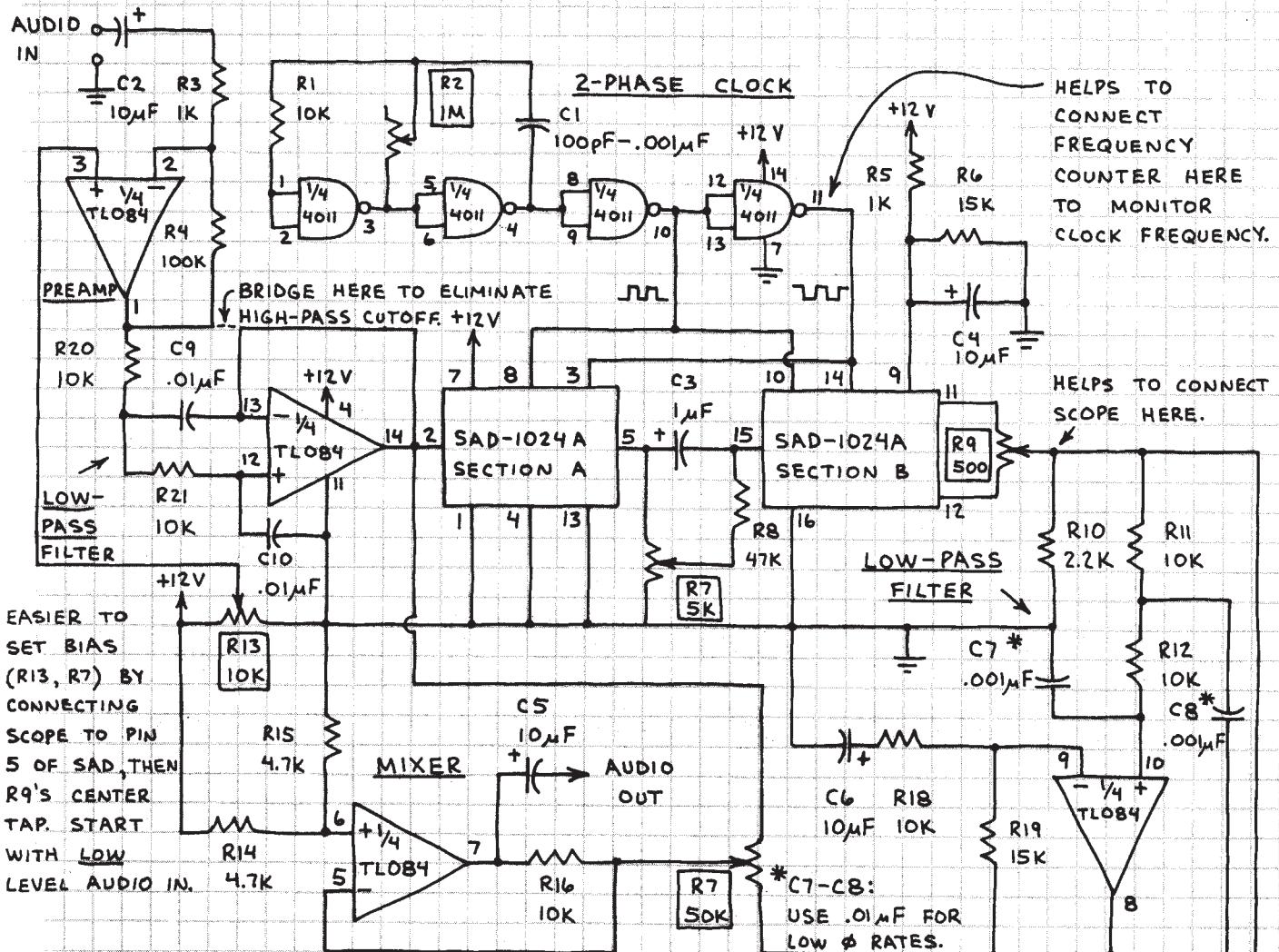

ADJUST CIRCUIT FOR DESIRED EFFECT BY CONNECTING TRANSISTOR RADIO TO AUDIO INPUT. TUNE RADIO TO A TALK SHOW FOR BEST RESULTS. R13 AND R7 CONTROL BIAS TO SECTIONS A AND B OF THE SAD. R9 BALANCES THE SAD OUTPUTS. R2 CONTROLS THE CLOCK RATE. R17 IS THE MAIN BALANCE CONTROL. IT CONTROLS THE RELATIVE AMPLITUDES OF THE ORIGINAL AND DELAYED SIGNAL APPLIED TO THE MIXER. CONNECT THE OUTPUT TO A POWER AMPLIFIER. YOU MUST ADJUST BIAS CONTROLS PROPERLY FOR BEST RESULTS. SET R2 FOR LOW FREQUENCIES (3-8kHz) FOR SINGLE ECHO. USE HIGHER CLOCK FREQUENCIES (20-100kHz) FOR HOLLOW, SWISHY SOUNDS. NOTE: THIS CIRCUIT IS NOT FOR BEGINNERS.


REVERBERATOR

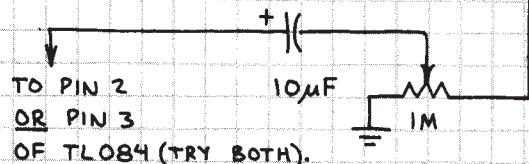

ADD THIS FEEDBACK CIRCUIT FOR UNUSUAL REVERBERATION EFFECTS. SLOW CLOCK FREQUENCIES GIVE MOST STRIKING REVERBERATIONS. TRY 5-20 kHz. FASTER CLOCK (20-100 kHz) AND CAREFUL ADJUSTMENT GIVES ROBOT-LIKE SOUND USED IN SOME SCIENCE FICTION MOVIES.


TOP OCTAVE SYNTHESIZER S50240

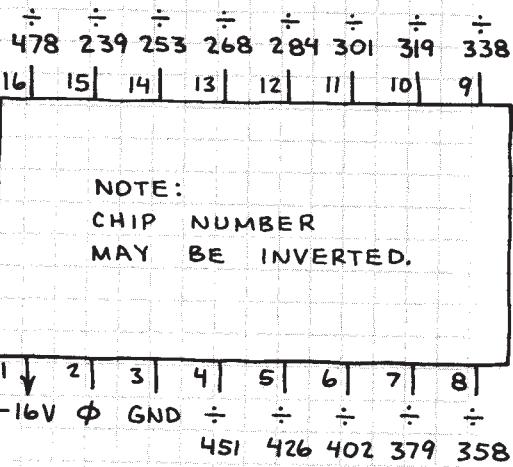THIS PMOS CHIP ACCEPTS AN INPUT FREQUENCY (ϕ) AND THEN DIVIDES IT INTO A FULL OCTAVE PLUS ONE NOTE ON THE EQUALLY TEMPERED SCALE. THIS CHIP IS IDEAL FOR MUSIC SYNTHESIZERS, ORGANS, ETC. FOR TOP OCTAVE OPERATION, ϕ SHOULD BE 2.00024 MHz; LOWER FREQUENCIES GIVE LOWER OCTAVES.




NOTE:
CHIP NUMBER
MAY BE INVERTED.



ADJUSTABLE OCTAVE SYNTHESIZER

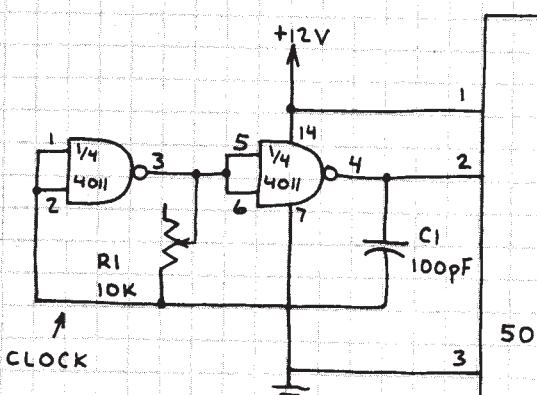

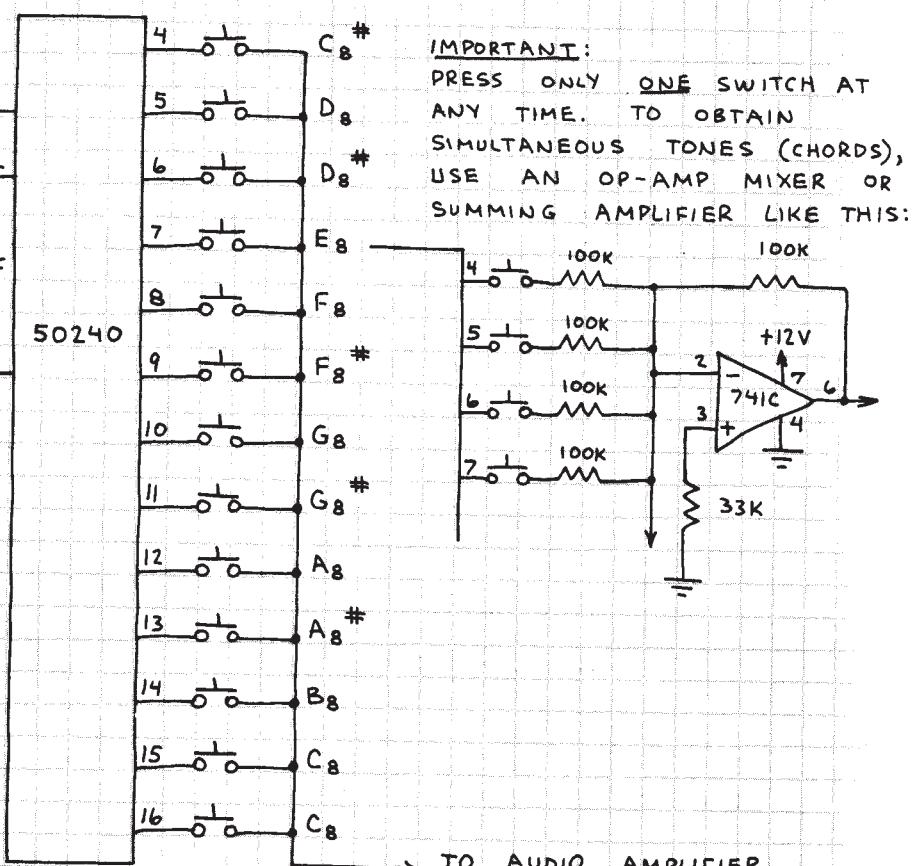FOR TOP OCTAVE, ADJUST R1 FOR CLOCK FREQUENCY OF 2.00024 MHz. FOR NEXT LOWER OCTAVE, USE 1.00012 MHz CLOCK FREQUENCY.




SPECIAL EFFECTS

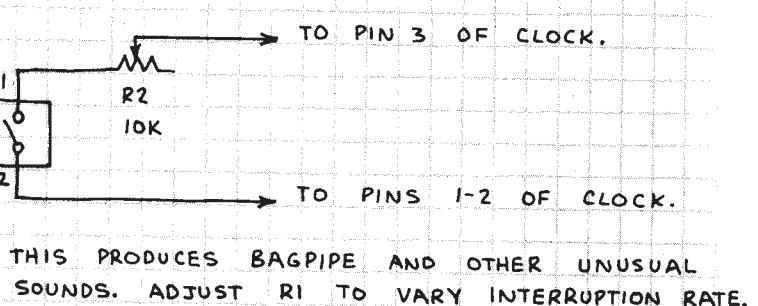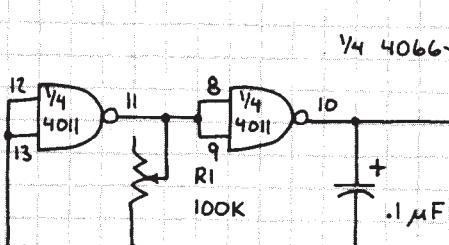


NOISE GENERATOR S2688 / MM5837N

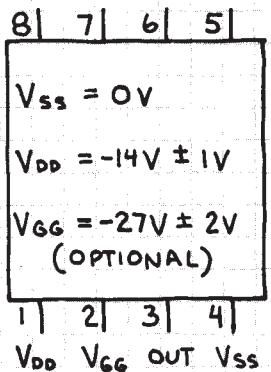PRODUCES BROADBAND WHITE NOISE FOR AUDIO AND OTHER APPLICATIONS. THE NOISE QUALITY IS VERY UNIFORM. IT IS PRODUCED BY A 17-BIT SHIFT REGISTER WHICH IS CLOCKED BY AN INTERNAL OSCILLATOR.




WHITE NOISE SOURCE

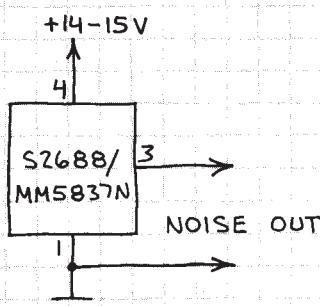


CONNECT OUTPUT TO AUDIO AMPLIFIER TO HEAR NOISE.
USE 7815 VOLTAGE REGULATOR TO OBTAIN +15 VOLTS.

PINK NOISE SOURCE

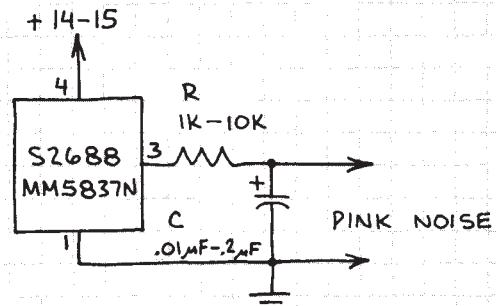


CHANGE R AND C TO ALTER NOISE SPECTRUM.
ALSO, TRY LOWER SUPPLY VOLTAGES TO CHANGE SPECTRUM.

COIN TOSSE

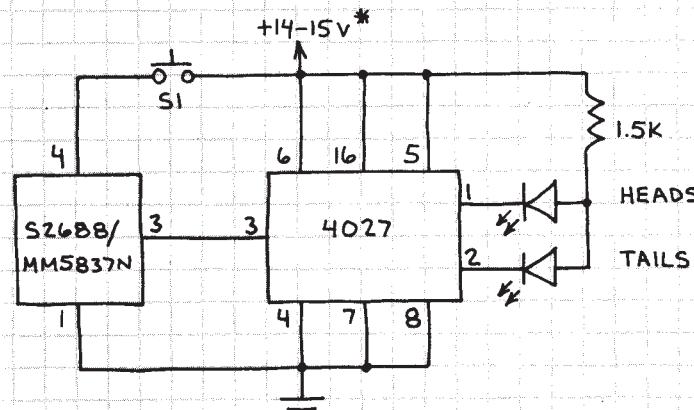

PRESS S1; BOTH LEDS GLOW. RELEASE S1 AND ONLY ONE GLOWS. GROUND INPUTS OF UNUSED HALF OF 4027 (PINS 9, 10, 11, 12 AND 13).*(OK TO USE 9-VOLT BATTERY AS POWER SUPPLY.)

SNARE / BRUSH NOISE

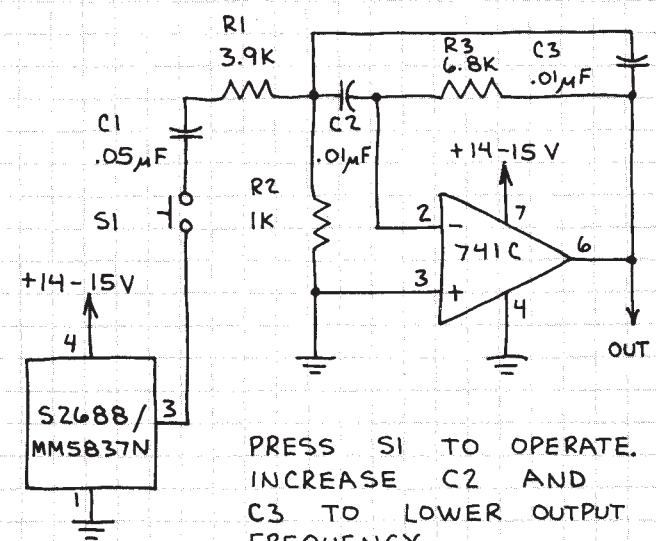


PRESS S1 TO OPERATE.
INCREASE C2 AND C3 TO LOWER OUTPUT FREQUENCY.

RHYTHM PATTERN GENERATOR MM5871

PRODUCES SIX DIFFERENT RHYTHM PATTERNS AND TRIGGERS FIVE DIFFERENT INSTRUMENTS.
ADJUSTABLE TEMPO. COMPlicated TO USE, BUT WELL WORTH THE EFFORT.

RHYTHM BOX

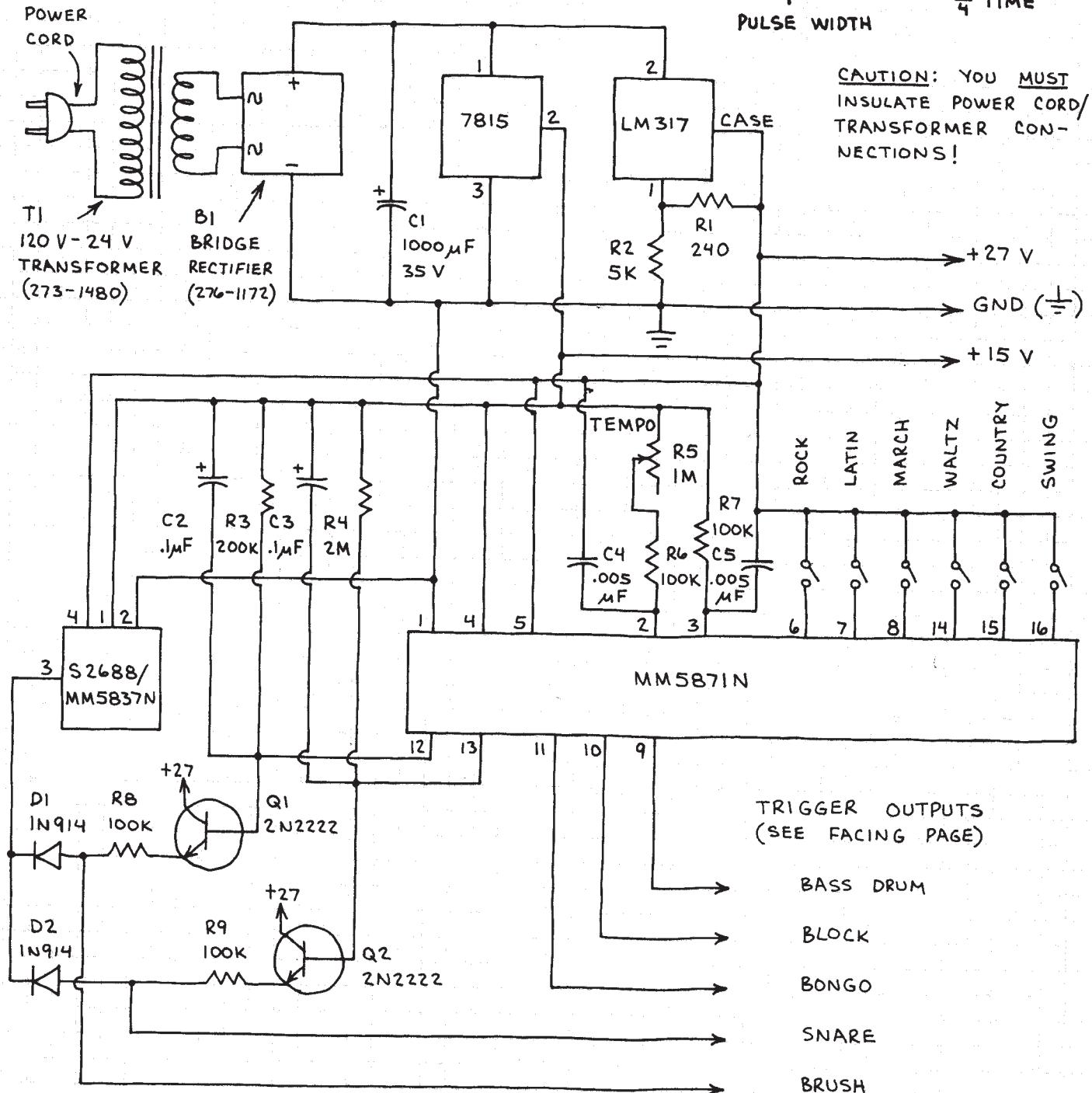


RHYTHM PATTERN GENERATOR (CONTINUED)

MM5871


PERCUSSION SYNTHESIZERS:

OK TO TUNE BY MAKING SLIGHT CHANGES TO RC COMPONENTS.


BASS DRUM

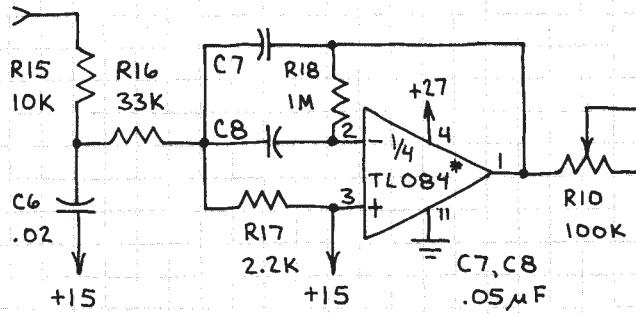


BLOCK

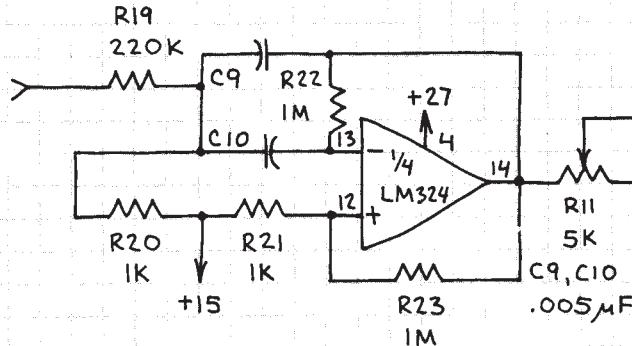


BONGO

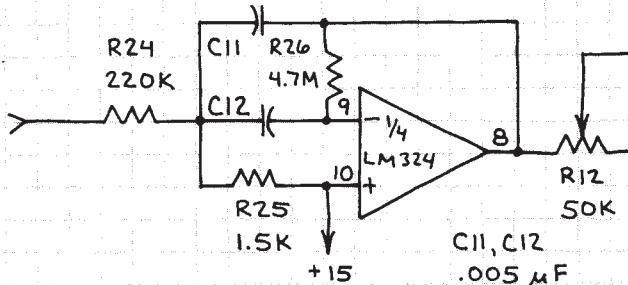

SNARE

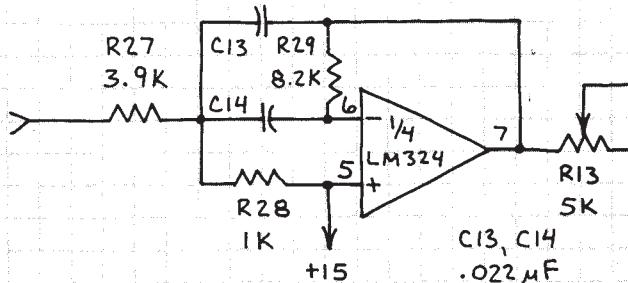

BRUSH

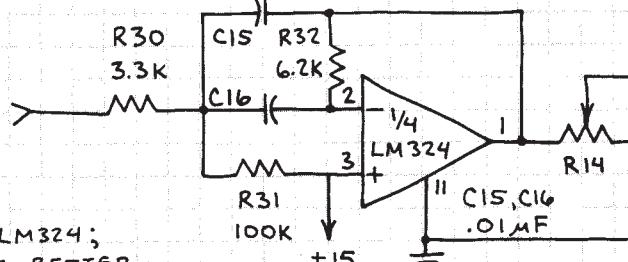

* OK TO USE LM324;
TLO84 WORKS BETTER.

MM5871 PIN EXPLANATIONS:

- 1 - V_{GG} (-27V ± 2V)
- 2 - TEMPO CONTROL (RC NETWORK)
- 3 - TRIGGER OUTPUT PULSE WIDTH CONTROL (RC NETWORK)
- 4 - V_{DD} (-14V ± 2V)
- 5 - V_{SS} (0V)

PATTERN SELECT INPUTS—
6 - ROCK 8 - MARCH 15 - C/W
7 - LATIN 14 - WALTZ 16 - SWING


TRIGGER OUTPUTS—
9 - BASS 11 - BONGO 13 - SNARE
10 - BLOCK 12 - BRUSH

RHYTHM BOX OPERATION:

POTS R10-R14 CONTROL VOLUME OF EACH INSTRUMENT. EXPERIMENT WITH SETTINGS FOR BEST RESULTS. OK TO SELECT TWO OR MORE PATTERNS SIMULTANEOUSLY!

SUMMING AMPLIFIER / PREAMPLIFIER

AUDIO POWER AMPLIFIER

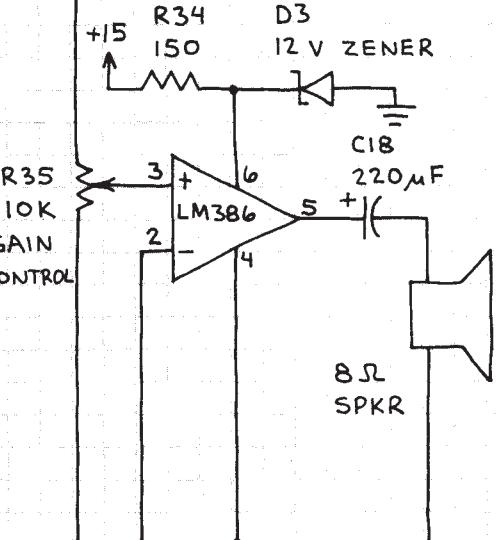


NOTES

TTL/LS INTEGRATED CIRCUITS

INTRODUCTION

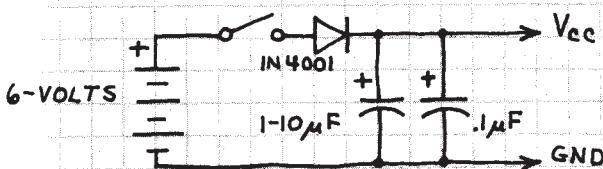TTL IS THE BEST ESTABLISHED AND MOST DIVERSIFIED IC FAMILY. LS IS FUNCTIONALLY IDENTICAL TO TTL BUT IS SLIGHTLY FASTER AND USES 80% LESS POWER. TTL/LS CHIPS REQUIRE A REGULATED 4.75-5.25 VOLT POWER SUPPLY. HERE'S A SIMPLE BATTERY SUPPLY:



THE DIODE DROPS THE BATTERY VOLTAGE TO A SAFE LEVEL. BOTH CAPACITORS SHOULD BE INSTALLED ON THE TTL/LS CIRCUIT BOARD. CIRCUITS WITH LOTS OF TTL/LS CHIPS CAN USE LOTS OF CURRENT. USE A COMMERCIAL 5 VOLT LINE POWERED SUPPLY TO SAVE BATTERIES. OR MAKE YOUR OWN. (SEE THE 7805 ON PAGE 94.)

OPERATING REQUIREMENTS

1. V_{CC} MUST NOT EXCEED 5.25 VOLTS.
2. INPUT SIGNALS MUST NEVER EXCEED V_{CC} AND SHOULD NOT FALL BELOW GND.
3. UNCONNECTED TTL/LS INPUTS USUALLY ASSUME THE H STATE... BUT DON'T COUNT ON IT! IF AN INPUT IS SUPPOSED TO BE FIXED AT H, CONNECT IT TO V_{CC}.
4. IF AN INPUT IS SUPPOSED TO BE FIXED AT L, CONNECT IT TO GND.
5. CONNECT UNUSED AND/NAND/OR INPUTS TO A USED INPUT OF THE SAME CHIP.
6. FORCE OUTPUTS OF UNUSED GATES H TO SAVE CURRENT (NAND—ONE INPUT H; NOR—ALL INPUTS L).


7. USE AT LEAST ONE DECOUPLING CAPACITOR (0.01-0.1 μF) FOR EVERY 5-10 GATE PACKAGES, ONE FOR EVERY 2-5 COUNTERS AND REGISTERS AND ONE FOR EACH ONE-SHOT. DECOUPLING CAPACITORS NEUTRALIZE THE HEFTY POWER SUPPLY SPIKES THAT OCCUR WHEN A TTL/LS OUTPUT CHANGES STATES. THEY MUST HAVE SHORT LEADS AND BE CONNECTED FROM V_{CC} TO GND AS NEAR THE TTL/LS ICs AS POSSIBLE.

8. AVOID LONG WIRES WITHIN CIRCUITS

9. IF THE POWER SUPPLY IS NOT ON THE CIRCUIT BOARD, CONNECT A 1-10μF CAPACITOR ACROSS THE POWER LEADS WHERE THEY ARRIVE AT THE BOARD.

INTERFACING TTL/LS

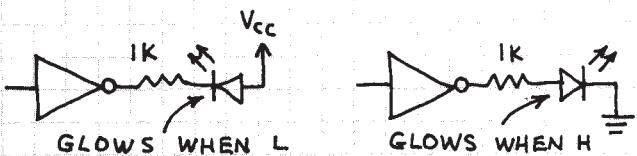1. 1 TTL OUTPUT WILL DRIVE UP TO 10 TTL OR 20 LS INPUTS.
2. 1 LS OUTPUT WILL DRIVE UP TO 5 TTL OR 10 LS INPUTS.
3. TTL/LS LED DRIVERS:




TTL/LS TROUBLESHOOTING

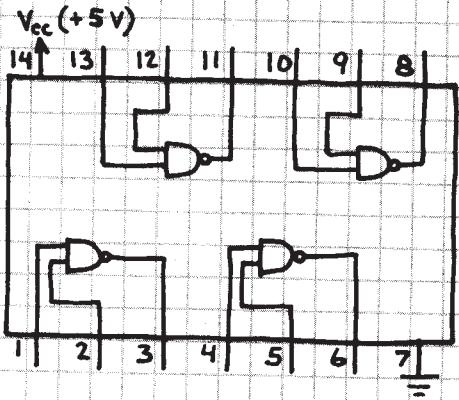
1. DO ALL INPUTS GO SOMEWHERE?
2. ARE ALL IC PINS INSERTED INTO THE BOARD OR SOCKET?
3. DOES THE CIRCUIT OBEY ALL TTL/LS OPERATING REQUIREMENTS?
4. HAVE YOU FORGOTTEN A CONNECTION?
5. HAVE YOU USED ENOUGH DECOUPLING CAPACITORS? ARE THEIR LEADS SHORT?
6. IS V_{CC} AT EACH CHIP WITHIN RANGE?

QUAD NAND GATE 7400 / 74LS00


THE BASIC BUILDING BLOCK CHIP FOR THE ENTIRE TTL FAMILY. VERY EASY TO USE. HUNDREDS OF APPLICATIONS.




CONTROL GATE

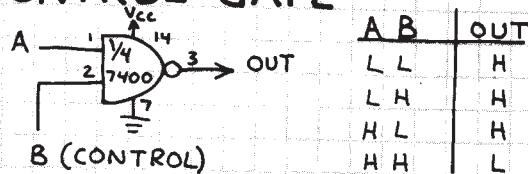


INVERTER

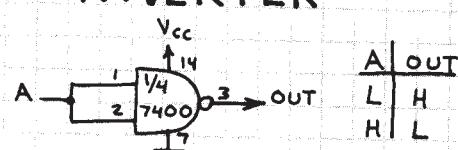


AND GATE

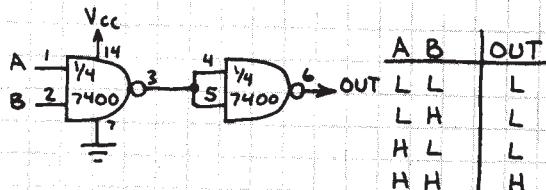

OR GATE

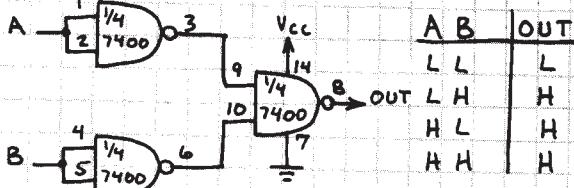


AND-OR GATE

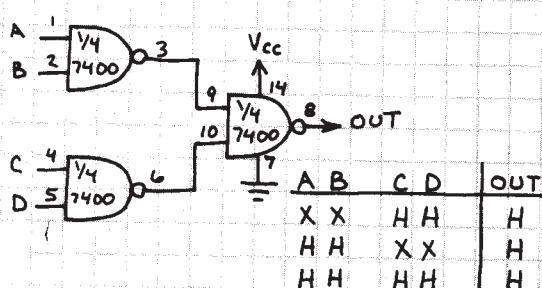


NOTE: PIN NUMBERS CAN BE REARRANGED IF DESIRED.


NOR GATE

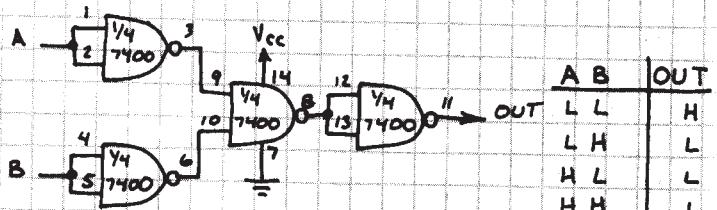


4-INPUT NAND GATE

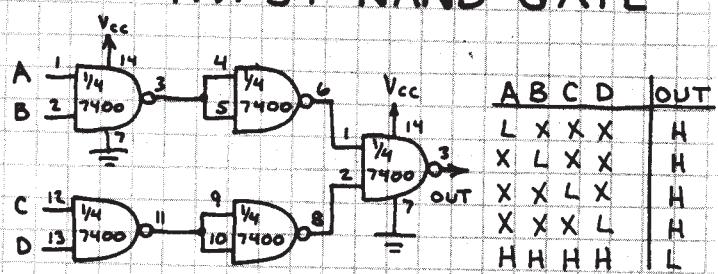

EXCLUSIVE-OR GATE

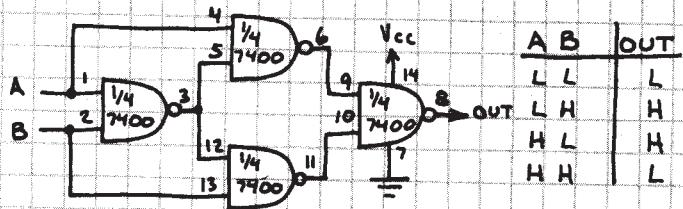


EXCLUSIVE-NOR GATE

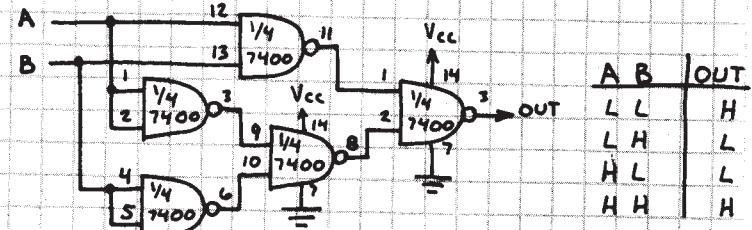


QUAD NAND GATE 7400/74LS00 (CONTINUED)


HALF ADDER

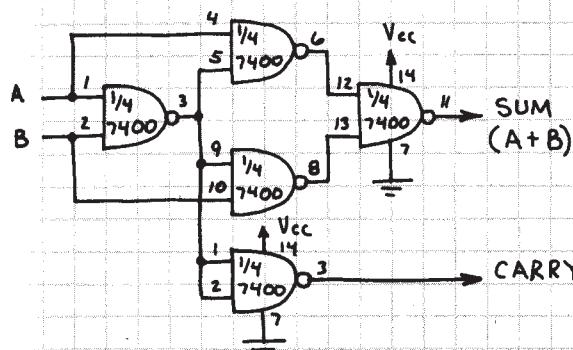

RS LATCH

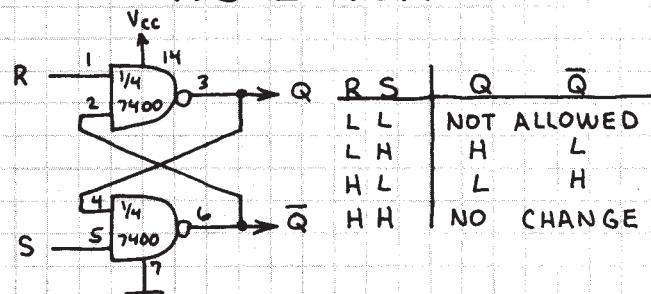


D FLIP-FLOP

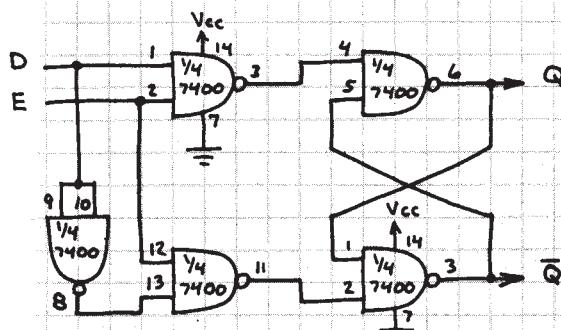


WHEN ENABLE (E) INPUT IS HIGH,
Q OUTPUT FOLLOWS D INPUT. NO
CHANGE WHEN E IS LOW.

GATED RS LATCH

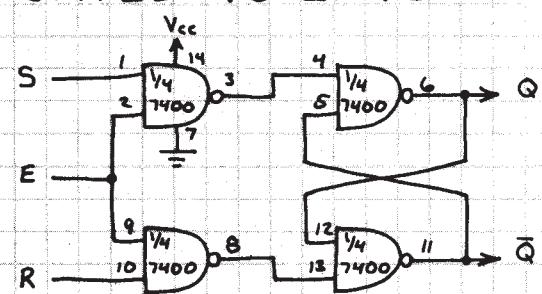


FUNCTIONS AS RS LATCH
WHEN ENABLE (E) INPUT IS
HIGH. IGNORES RS INPUTS
WHEN E IS LOW.

LED DUAL FLASHER

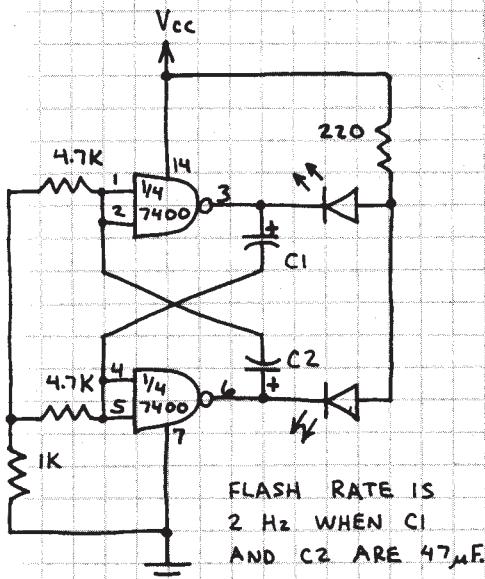

FLASH RATE IS
2 Hz WHEN C1
AND C2 ARE $47\mu F$.


SWITCH DEBOUNCER

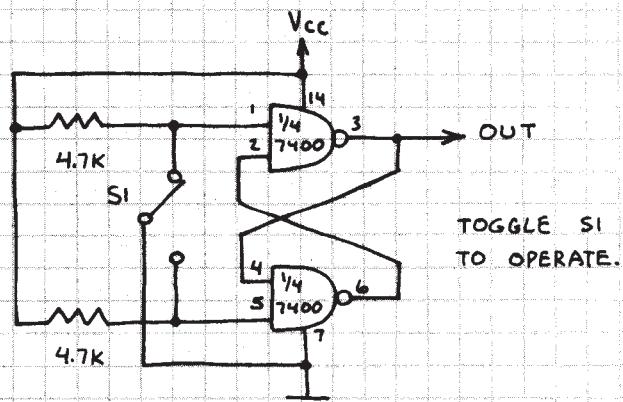


TOGGLE S1
TO OPERATE.
PROVIDES NOISE FREE OUTPUT FROM
STANDARD SPDT TOGGLE SWITCH.

TRIPLE 3-INPUT NAND GATE 74LS10

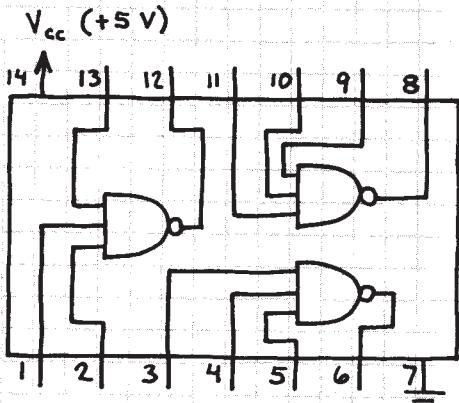VERY USEFUL IN DO-IT-YOURSELF DECODERS. ALSO VERY HANDY FOR ADDING ENABLE CONTROL TO DIGITAL CIRCUITS.




1-OF-4 DECODER

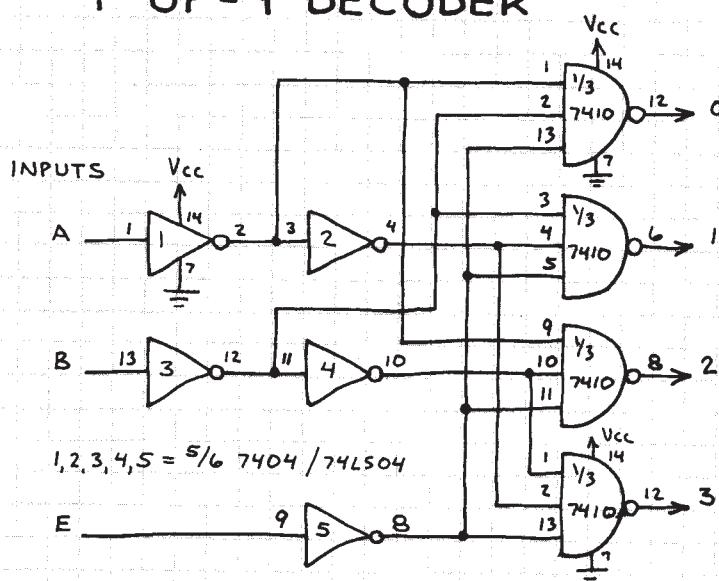


FOR EACH OF 4 POSSIBLE BINARY INPUTS (LL, LH, HL AND HH) ONE INPUT GOES LOW WHILE ALL OTHERS STAY HIGH. E SHOULD BE H.

ENABLE INPUT

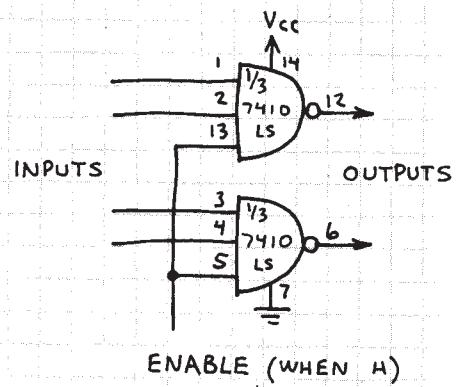

TYPICAL ENABLE INPUT CIRCUIT. USE THIS METHOD TO CONTROL ONE OR MORE GATES.

1-OF-8 DECODER

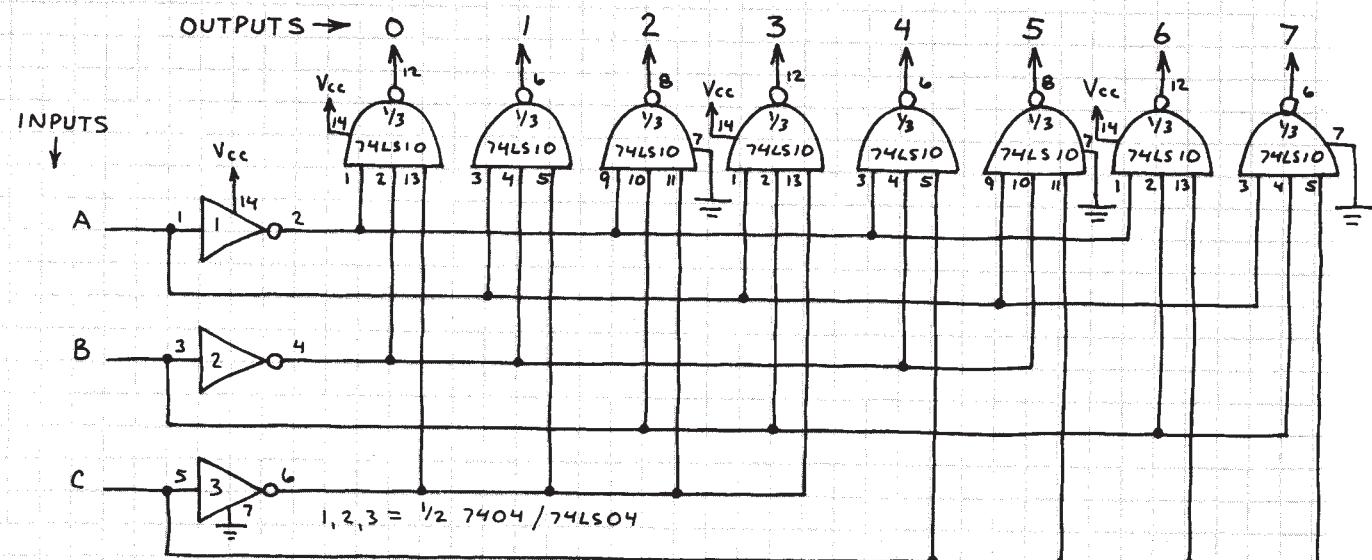


FOR EACH OF 8 POSSIBLE BINARY INPUTS (LLL, LLH, LHL...HHH), ONE OUTPUT GOES LOW WHILE ALL OTHERS STAY HIGH.



DUAL 4-INPUT NAND GATE

74LS20

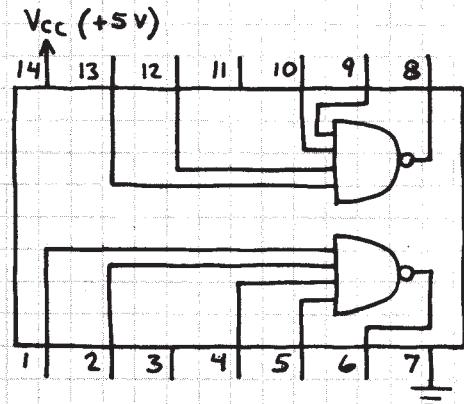MANY DECODER AND ENCODER APPLICATIONS CAN BE USED AS DUAL 3-INPUT NAND GATE WITH ENABLE (CONTROL) INPUT FOR EACH GATE.




BCD DECODERS

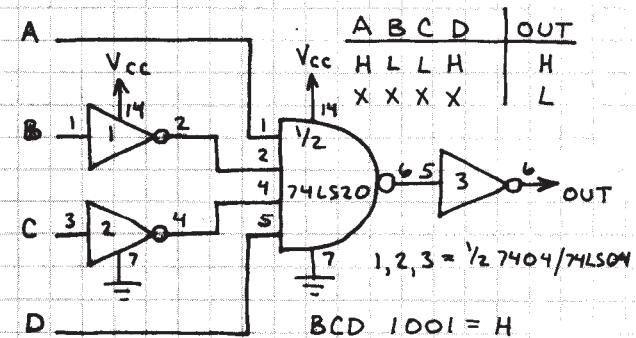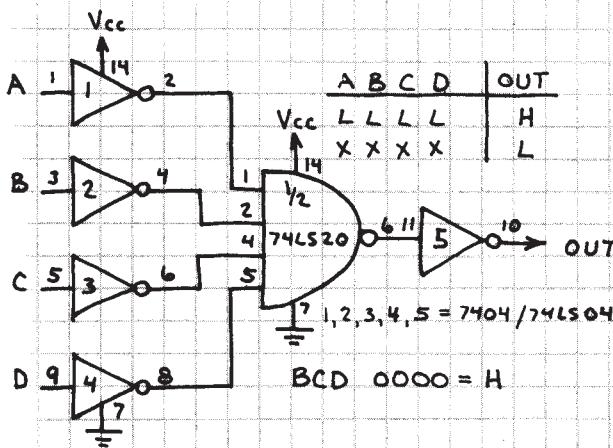

OUTPUTS GO HIGH WHEN APPROPRIATE BCD WORD APPEARS AT INPUTS DCBA. OUTPUTS STAY LOW FOR ALL OTHER INPUTS. (OMIT FINAL INVERTER TO PROVIDE ACTIVE LOW OUTPUT.) USE THIS METHOD TO DECODE ANY 4-BIT NIBBLE.

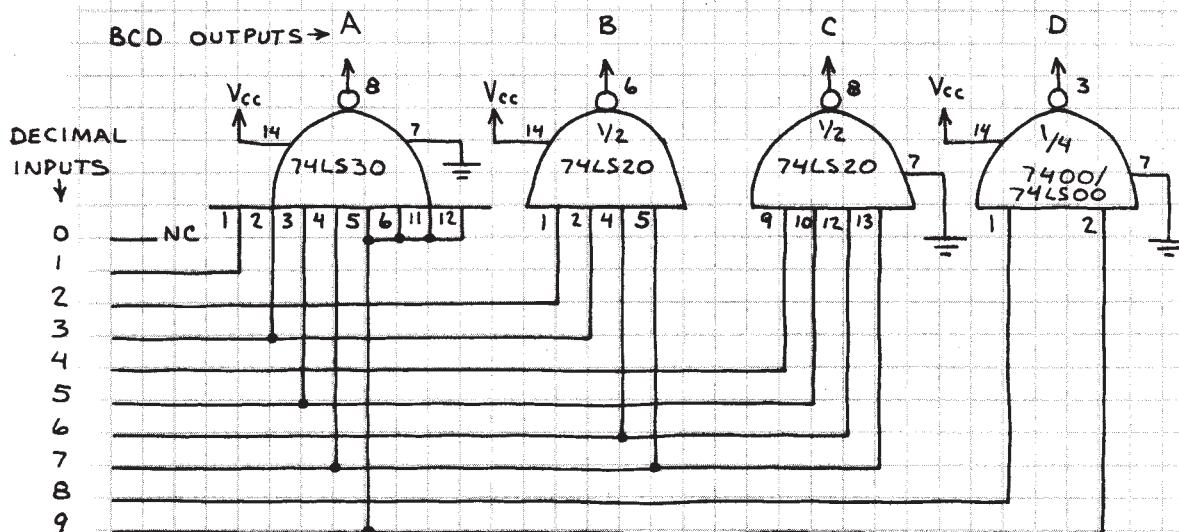DECIMAL-TO-BINARY CODED DECIMAL (BCD) ENCODER




SELECTED INPUT SHOULD BE LOW AND ALL OTHER INPUTS SHOULD BE HIGH. BCD EQUIVALENT WILL APPEAR AT THE OUTPUTS.


8-INPUT NAND GATE

74LS30

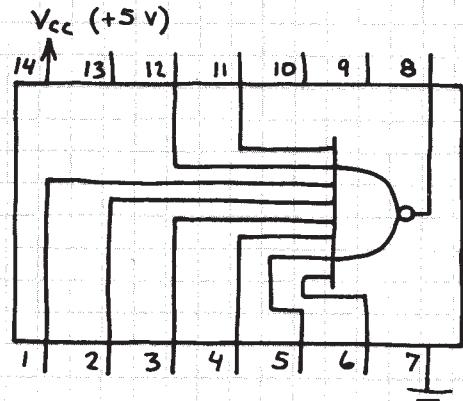HANDY FOR BYTE-SIZE (8-BIT) DECODING APPLICATIONS. CAN DECODE UP TO 2^8 INPUT COMBINATIONS. ALSO USEFUL AS PROGRAMMABLE NAND GATE.




8-BIT DECODER

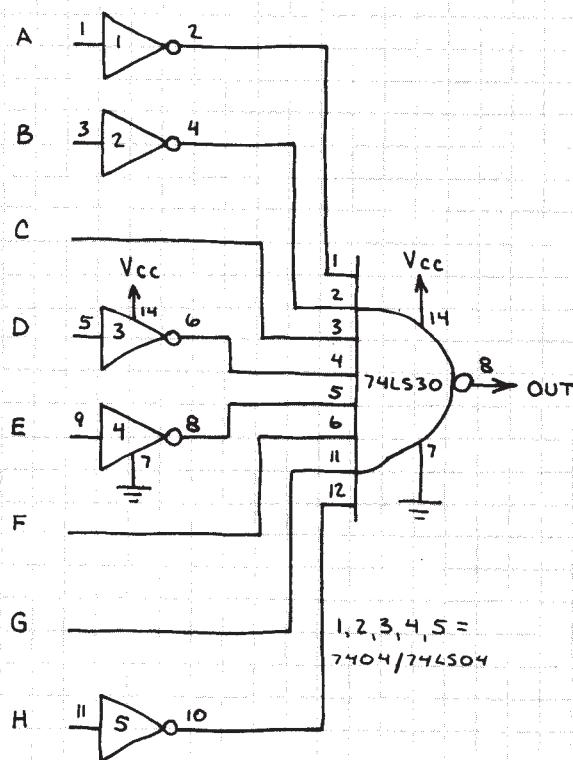


OUTPUT GOES LOW ONLY WHEN INPUT IS LHHLLHLL (DECIMAL 100). UP TO 2^8 INPUTS CAN BE DECODED BY REARRANGING UP TO 8 INPUT INVERTERS.

UNANIMOUS VOTE DETECTOR

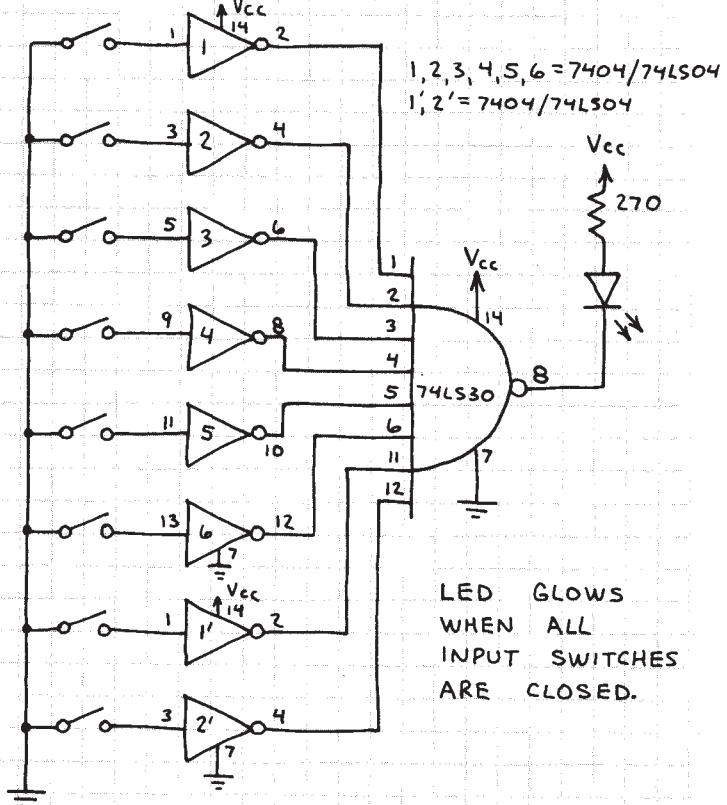


PROGRAMMABLE NAND GATES


5-INPUT

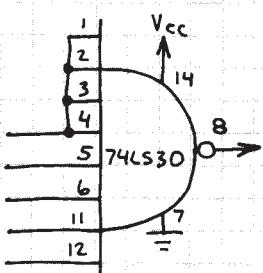

6-INPUT

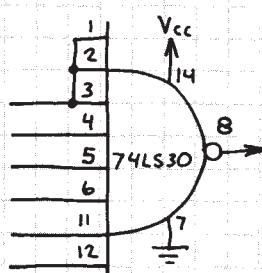


7-INPUT

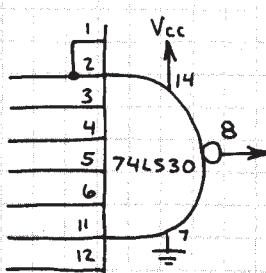


QUAD AND GATE

7408 / 74LS08

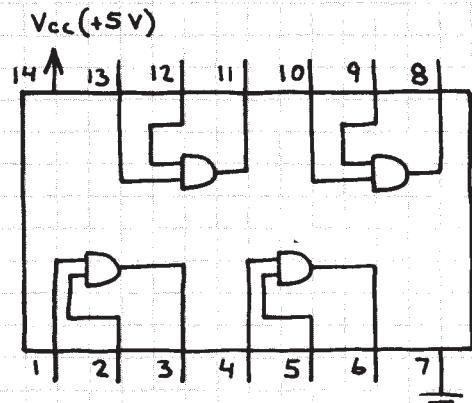ONE OF THE BASIC BUILDING BLOCK CHIPS. NOT AS VERSATILE, HOWEVER, AS THE 7400 / 74LS00 QUAD NAND GATE.




AND GATE BUFFER

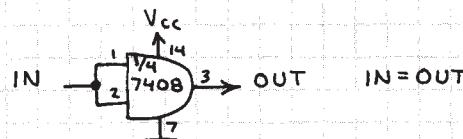

USE FOR INTERFACING WITHOUT CHANGING LOGIC STATES.


DIGITAL TRANSMISSION GATE

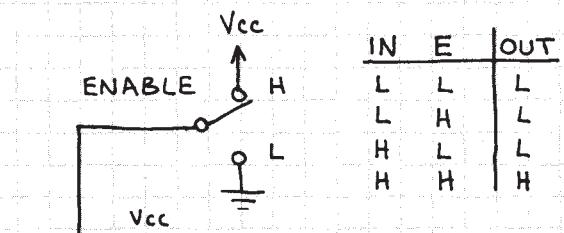

IN	E	OUT
L	L	L
L	H	L
H	L	L
H	H	H


E = ENABLE

NAND GATE

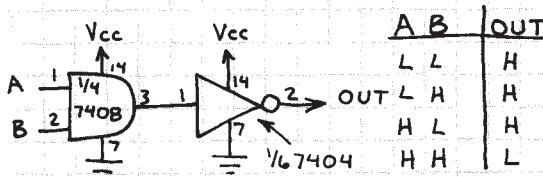


A	B	OUT
L	L	H
L	H	H
H	L	H
H	H	L

NOR GATE

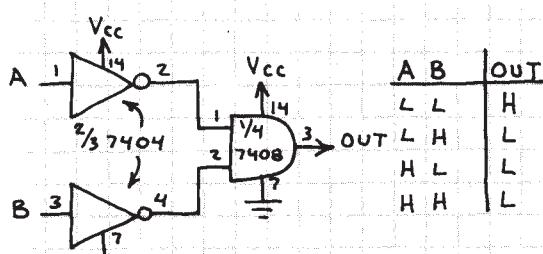


A	B	OUT
L	L	H
L	H	L
H	L	L
H	H	L

AND-OR-INVERT GATE

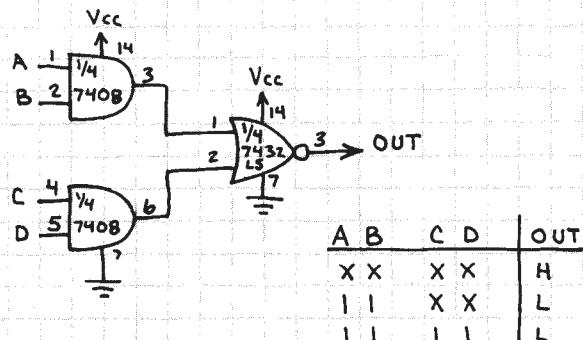


A	B	C	D	OUT
X	X	X	X	H
1	1	X	X	L
1	1	1	1	L

4-INPUT NAND GATE

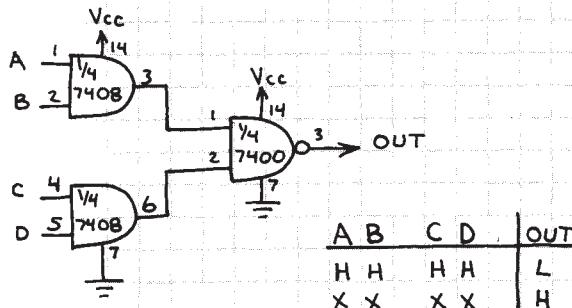

A	B	C	D	OUT
H	H	H	L	L
X	X	X	H	H

4-INPUT AND GATE

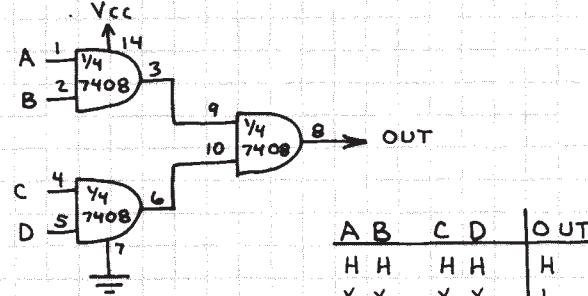


A	B	C	D	OUT
H	H	H	H	H
X	X	X	X	L

QUAD OR GATE


74LS32

FOUR 2-INPUT OR GATES.
NOT AS VERSATILE AS 7402/
74LS02 QUAD NOR GATE,
BUT VERY USEFUL IN SIMPLE
DATA SELECTORS.

V_{cc} (+5 V)

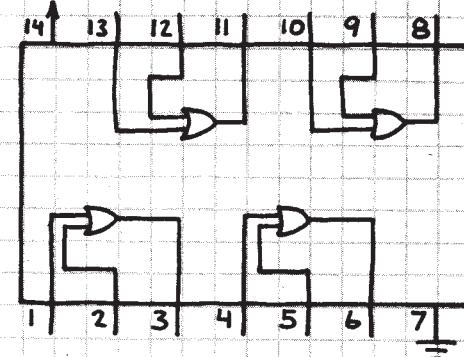


AND-OR CIRCUIT

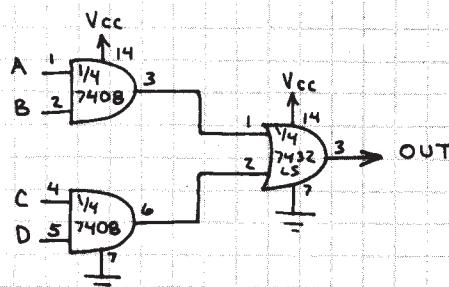


OUTPUT GOES HIGH WHEN BOTH INPUTS OF EITHER OR BOTH AND GATES ARE HIGH; OTHERWISE THE OUTPUT IS LOW. THIS BASIC CIRCUIT IS USED TO MAKE DATA SELECTORS... AS SHOWN BELOW

NOR GATE

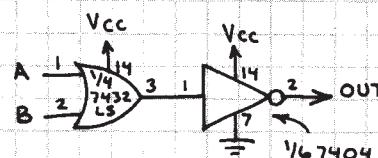

A	B	OUT
L	L	H
L	H	L
H	L	L
H	H	L


NAND GATE

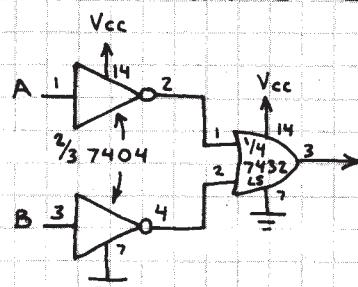

A	B	OUT
L	L	H
L	H	H
H	L	H
H	H	L

2-INPUT DATA SELECTOR

DATA IN

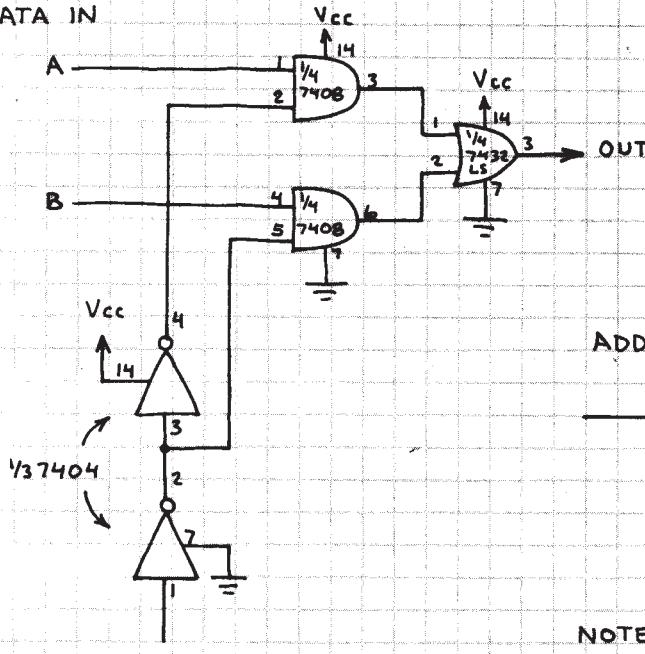

SELECTS 1-OF-2 INPUTS
AND TRANSMITS ITS
LOGIC STATE TO THE
OUTPUT.


ADDRESS	DATA IN		OUT
	A	B	
L	X	L	L
L	X	H	H
H	L	X	L
H	H	X	H

NOTE: FOR 3-INPUT DATA SELECTOR,
USE 74LS27 NOR GATE FOLLOWED
BY INVERTER AND PRECEDED BY
74LS10 3-INPUT AND GATES.


ADDRESS (DATA SELECT)

QUAD NOR GATE 7402/74LS02

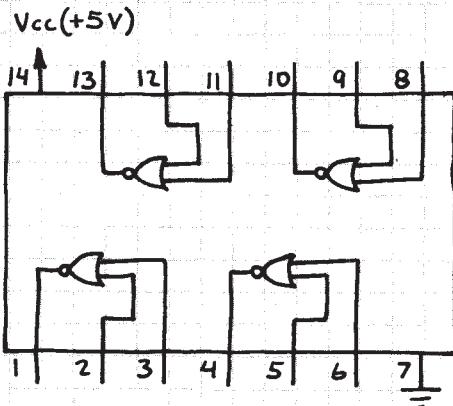JUST AS VERSATILE AS THE
7400/74LS00 QUAD NAND GATE...
BUT NOT USED AS OFTEN.
ADD INVERTER (7404/74LS04)
TO BOTH INPUTS OF A NOR
GATE AND AN AND GATE IS
FORMED.




EXCLUSIVE-OR GATE

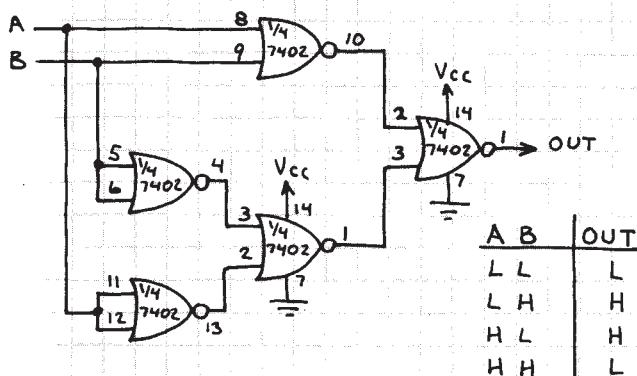


THIS CIRCUIT IS EQUIVALENT
TO A BINARY HALF-ADDER.

ONE-SHOT

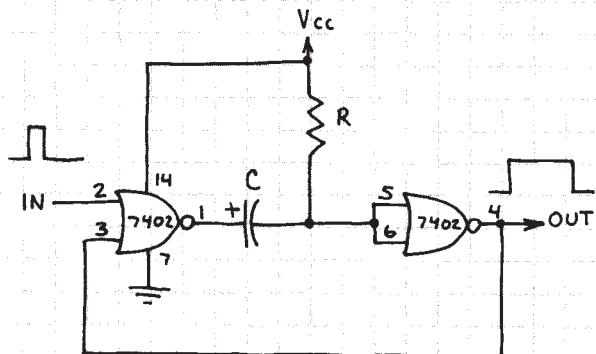


THIS CIRCUIT IS A MONOSTABLE
MULTIVIBRATOR OR PULSE STRETCHER.
AN INPUT PULSE TRIGGERS AN
OUTPUT PULSE WITH A DURATION
DETERMINED BY R AND C. OUTPUT
PULSE WIDTH IS APPROXIMATELY 0.8 RC.


RS LATCH

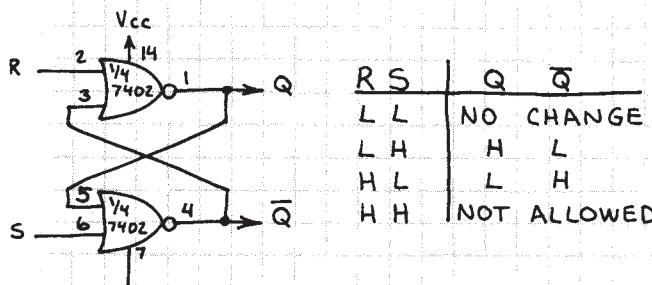


AND GATE

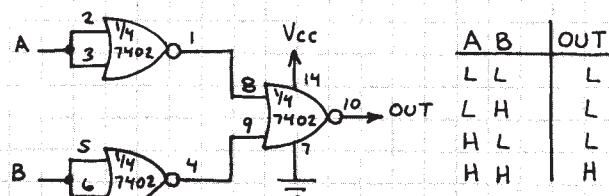

4-INPUT NOR GATE

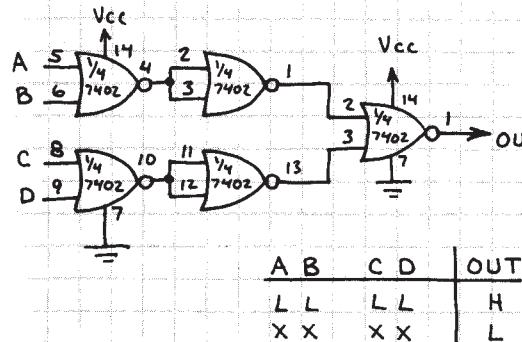


OR GATE

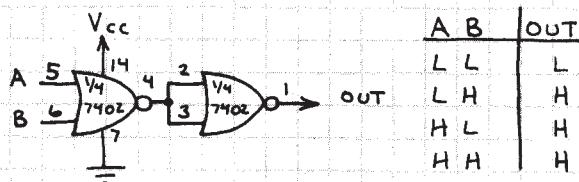


TRIPLE 3-INPUT NOR GATE

74LS27

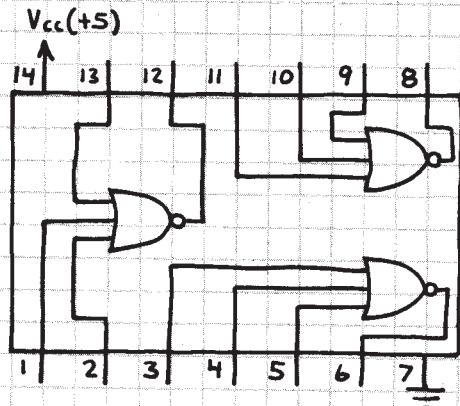
USEFUL FOR DATA SELECTORS
AND NOR GATE FLIP-FLOPS
THAT REQUIRE CLEAR AND
PRESET INPUTS.



GATED RS LATCH

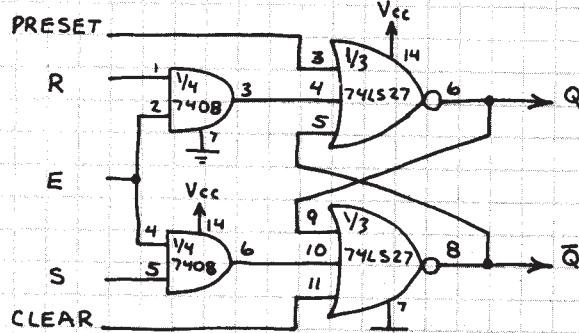


3-INPUT OR GATE

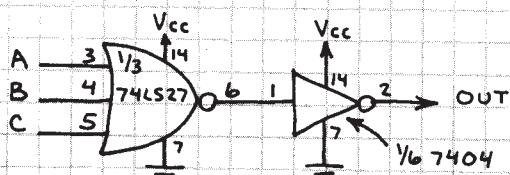

FUNCTIONS AS RS LATCH WHEN
E (ENABLE) INPUT IS HIGH. IGNORES
RS INPUTS WHEN E IS LOW.

DATA IN

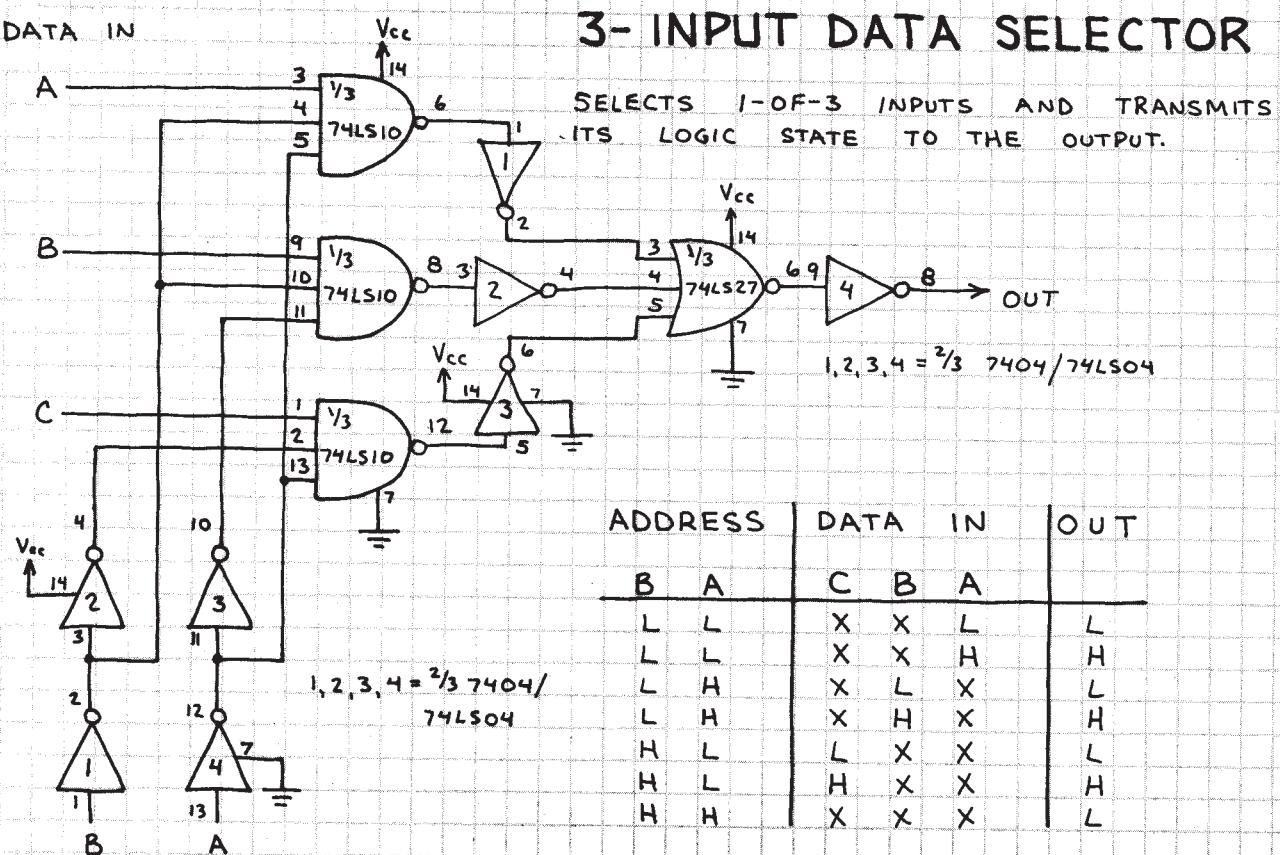


ADDRESS	DATA IN	OUT			
B	A	C	B	A	
L	L	X	X	L	L
L	L	X	X	H	H
L	H	X	L	X	L
L	H	X	H	X	H
H	L	L	X	X	X
H	L	H	H	X	X
H	H	X	X	X	X

ADDRESS (DATA SELECT)


DUAL AND-OR-INVERT GATE

74LS51

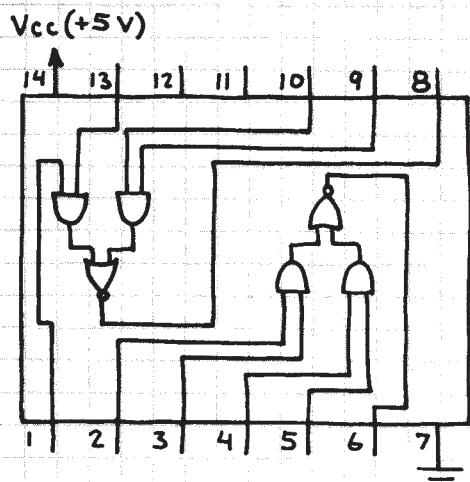VERY VERSATILE BUILDING BLOCK CHIP. IDEAL FOR CUSTOMIZED DATA SELECTORS, LATCHES AND EXPANSION OF A SINGLE INPUT TO AN AND-OR INPUT.




LATCH WITH ENABLE INPUT

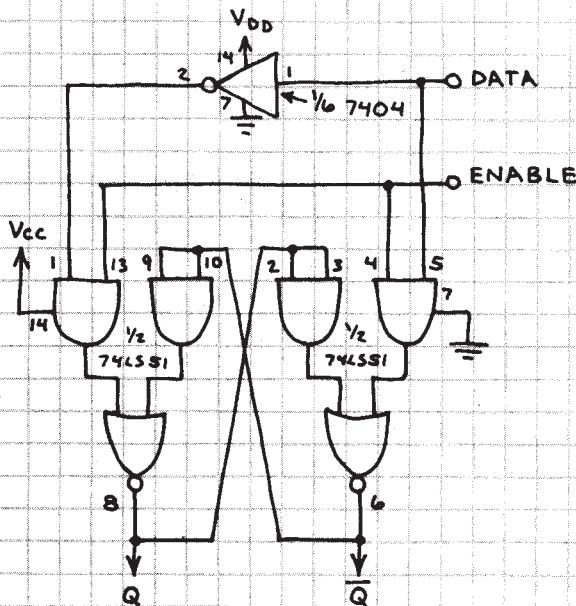

Q OUTPUT FOLLOWS DATA INPUT WHEN ENABLE INPUT IS HIGH. NO CHANGE WHEN ENABLE IS LOW.


TYPICAL AND-OR INPUT

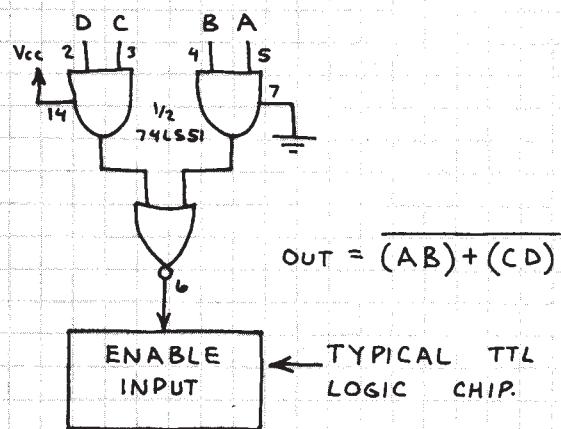

THIS CIRCUIT SELECTS 1-OF-2 4-BIT WORDS.

NOTE THAT THE SELECTED WORD IS INVERTED AT THE OUTPUTS. THE CIRCUIT REQUIRES TWO 74LS51 CHIPS.


INPUT	OUT
X X	H
H X	L
H X	L
L X	H
L H X	L

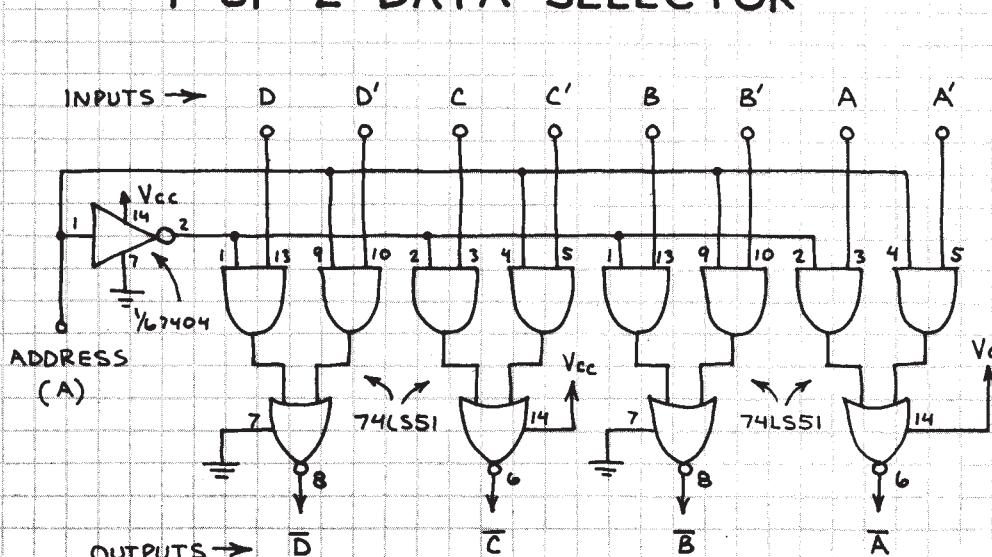


DUAL NAND SCHMITT TRIGGER

74LS13

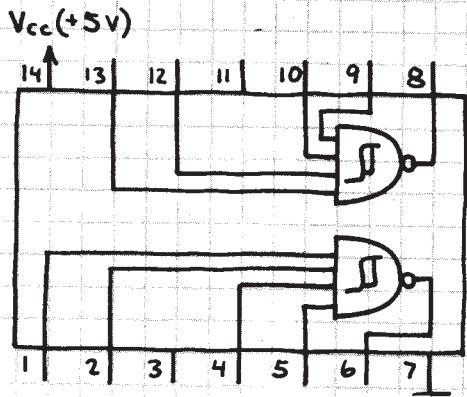
TWO 4-INPUT NAND GATES WITH A SWITCHING THRESHOLD. OUTPUTS GO LOW WHEN INPUTS EXCEED 1.7 VOLTS. OUTPUTS GO HIGH WHEN INPUTS FALL TO 0.9 VOLT. IF ANY INPUT IS LOW, THE RESPECTIVE OUTPUT WILL STAY HIGH AND THE GATE WILL NOT TRIGGER.




GATED THRESHOLD DETECTOR

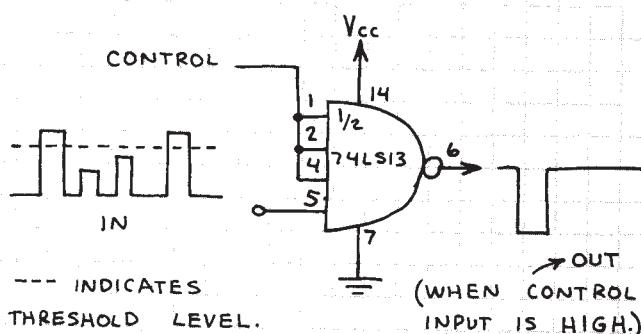

PHOTOTRANSISTOR RECEIVER

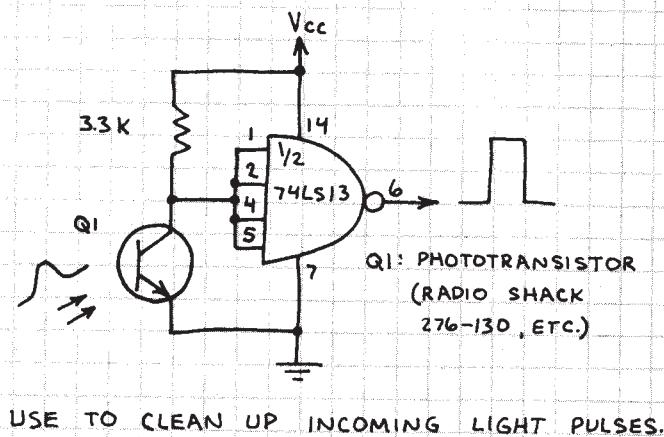


GATED OSCILLATOR

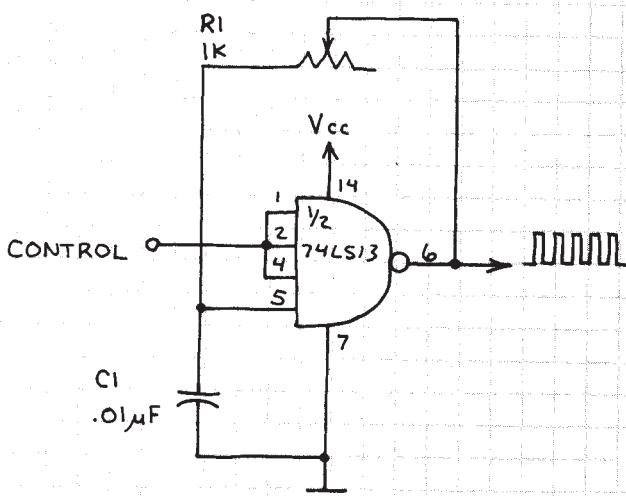

OSCILLATES WHEN CONTROL IS HIGH.
CHANGE RI AND CI TO CHANGE FREQUENCY. OK TO USE THIS CIRCUIT AS GATED CLOCK FOR LOGIC CIRCUITS.

TWO-STATE LED FLASHER

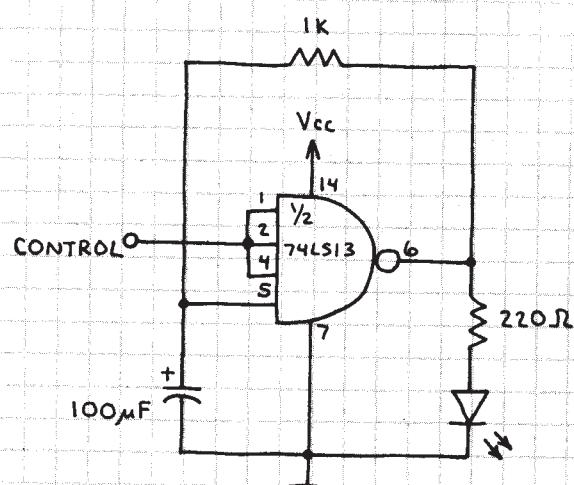


LED FLASHES TWICE EACH SECOND WHEN CONTROL INPUT IS HIGH.
LED STAYS ON AND DOES NOT FLASH WHEN CONTROL IS LOW.


QUAD NAND SCHMITT TRIGGER

74LS132

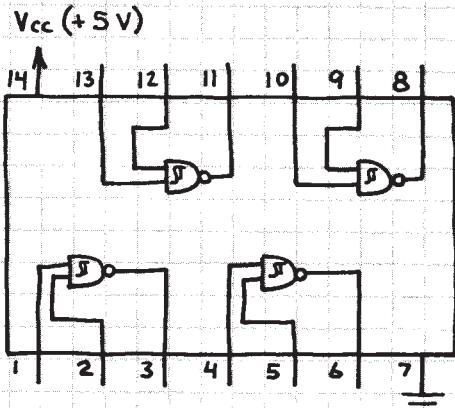
NAND GATES WITH A SWITCHING THRESHOLD. OUTPUTS GO LOW WHEN INPUTS EXCEED 1.7 VOLTS. OUTPUTS GO LOW WHEN INPUTS FALL TO 0.9 VOLT. VERY USEFUL FOR CLEANING UP DIGITAL SIGNALS BEFORE THEY ARE ALLOWED TO ENTER A LOGIC CIRCUIT.




WAVE SHAPER

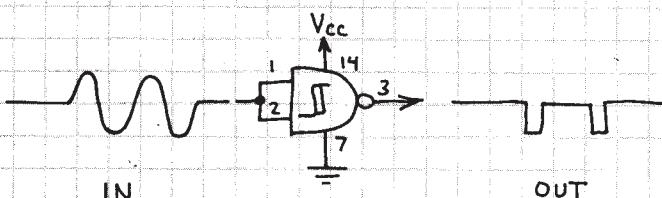


PULSE RESTORER

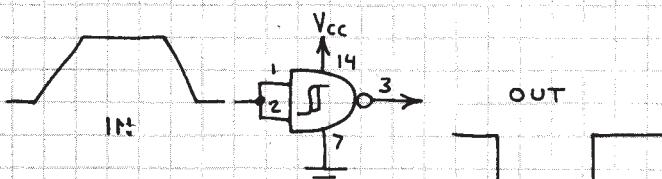

NOISE ELIMINATOR

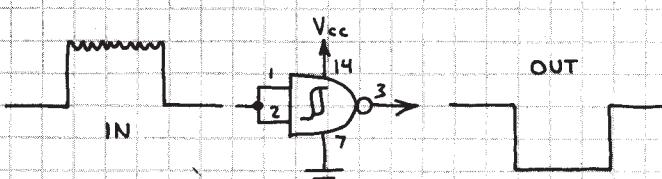


THRESHOLD DETECTOR

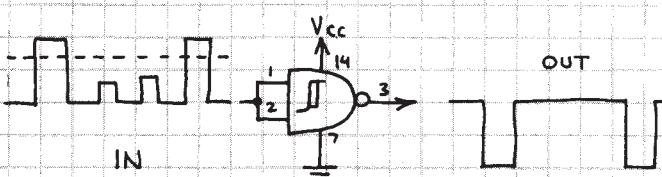

--- INDICATES THRESHOLD LEVEL.


LED FLASHER

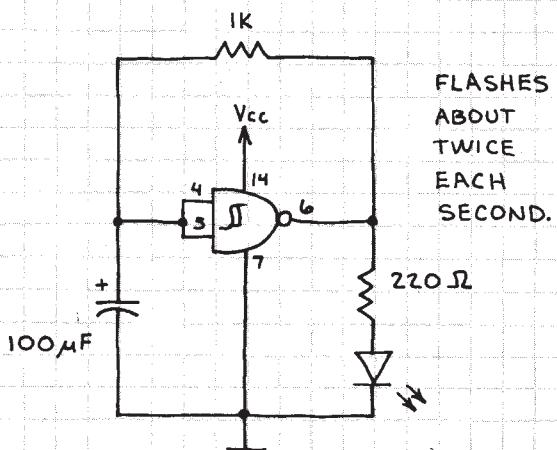


FLASHES ABOUT TWICE EACH SECOND.

ADDING ENABLE INPUT

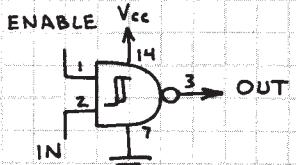TRIGGERS WHEN ENABLE INPUT IS HIGH. OUTPUT HIGH WHEN ENABLE LOW.



BOUNCELESS PUSHBUTTON

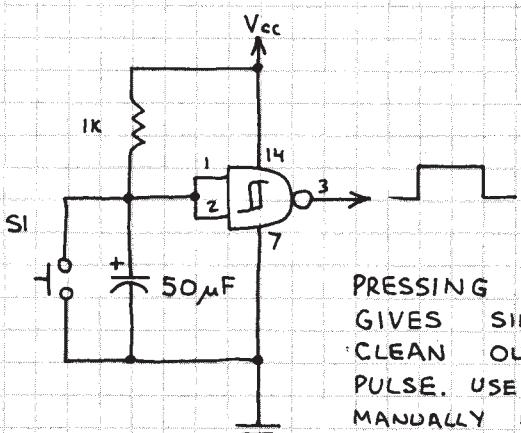


PRESSING SI GIVES SINGLE, CLEAN OUTPUT PULSE. USE FOR MANUALLY INJECTING LOGIC SIGNALS, ETC.

HEX 3-STATE BUS DRIVER 74LS367

EACH GATE FUNCTIONS AS A NON-INVERTING BUFFER WHEN ITS ENABLE INPUT (G1 OR G2) IS LOW. OTHERWISE EACH GATE'S OUTPUT ENTERS THE HIGH IMPEDANCE (HI-Z) STATE.


HERE'S THE TRUTH TABLE:

G	IN	OUT
H	X	HI-Z
L	L	L
L	H	H

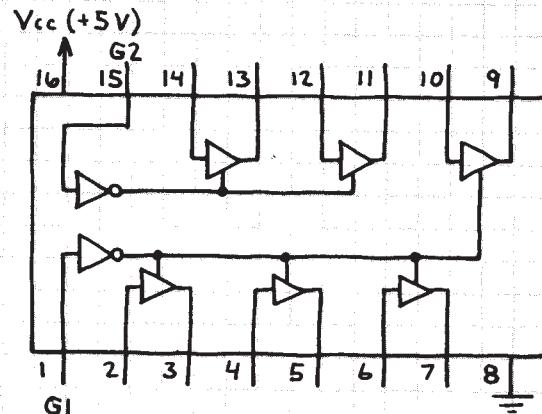


ADDING 3-STATE OUTPUT TO TTL


1-OF-2 DATA SELECTOR

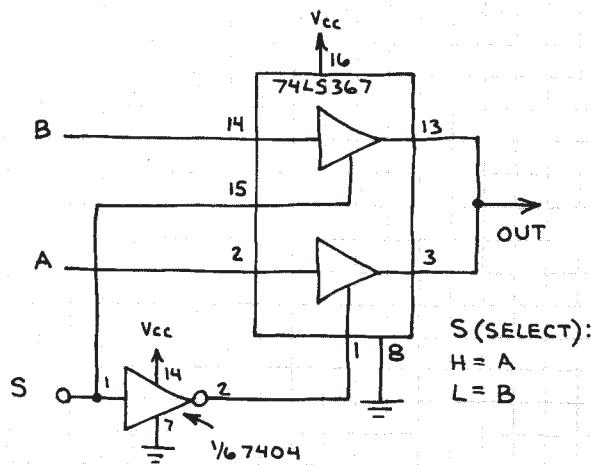

1-OF-2 DATA SELECTOR

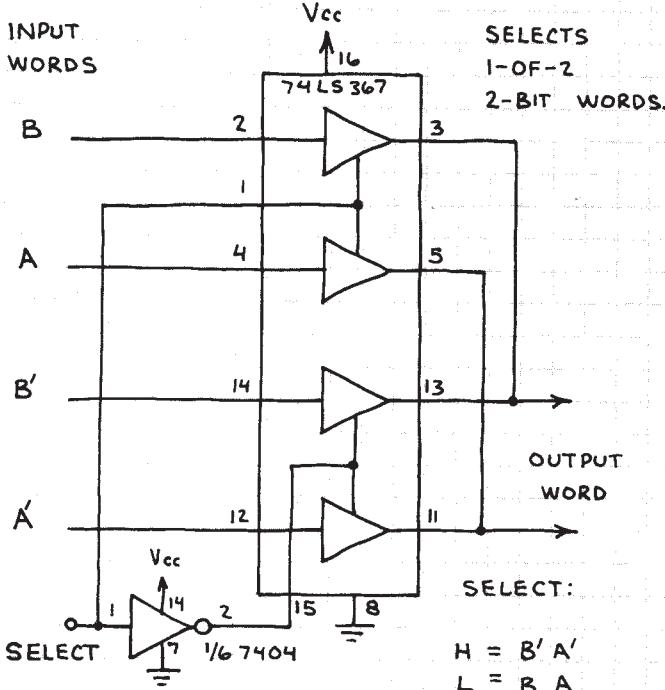

BIDIRECTIONAL DATA BUS

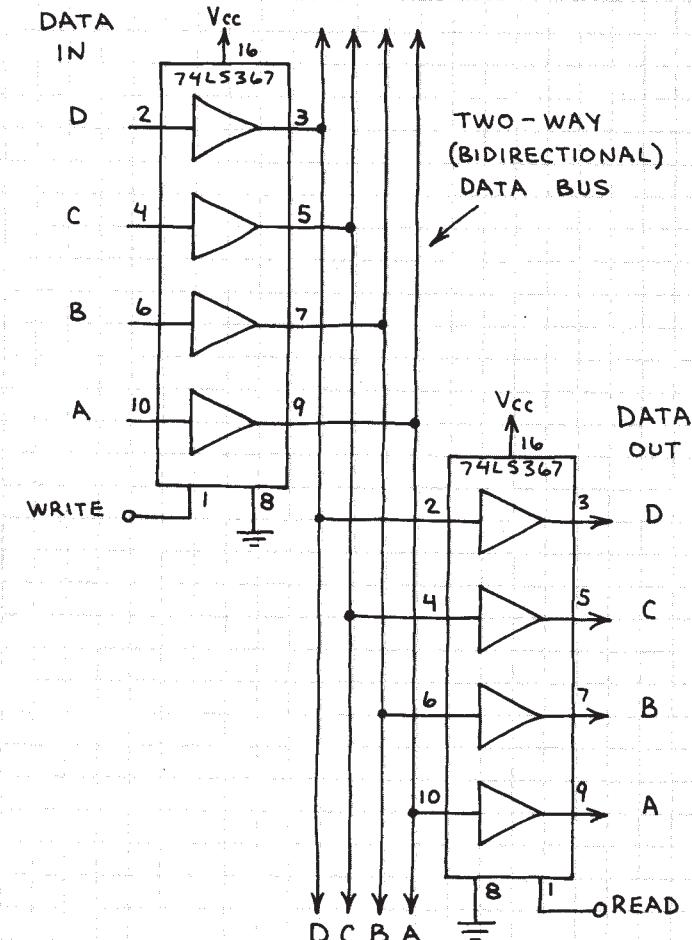


HEX 3-STATE BUS DRIVER 74LS368


EACH GATE FUNCTIONS AS AN INVERTER WHEN ITS ENABLE INPUT (G1 OR G2) IS LOW. OTHERWISE EACH GATE'S OUTPUT ENTERS THE HIGH IMPEDANCE (HI-Z) STATE.

HERE'S THE TRUTH TABLE:


G	IN	OUT
H	X	HI-Z
L	L	H
L	H	L

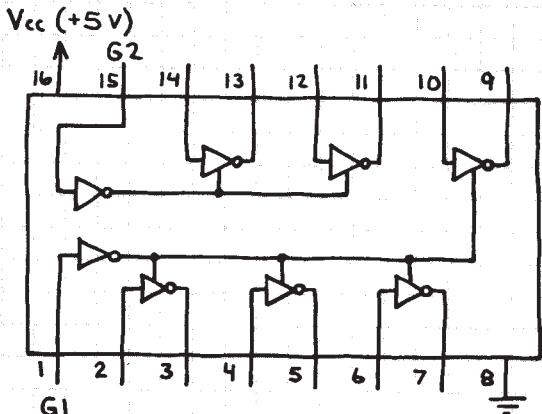


BIDIRECTIONAL DATA BUS

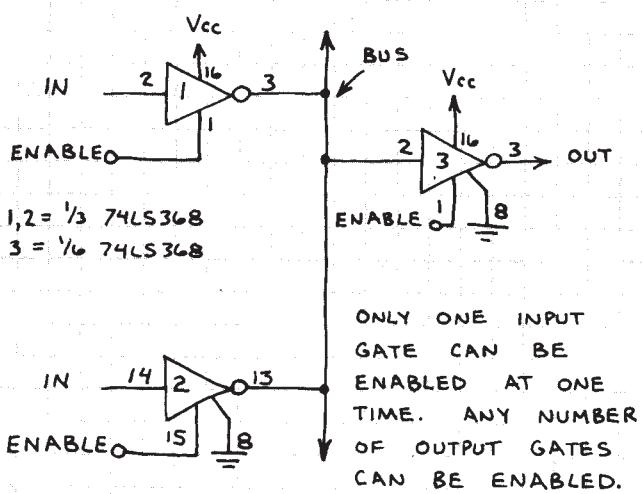


GATED TONE SOURCE

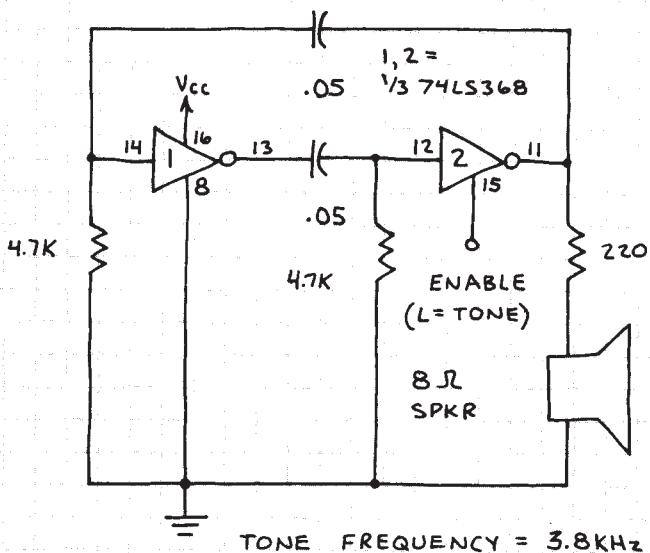

GATED LED FLASHER

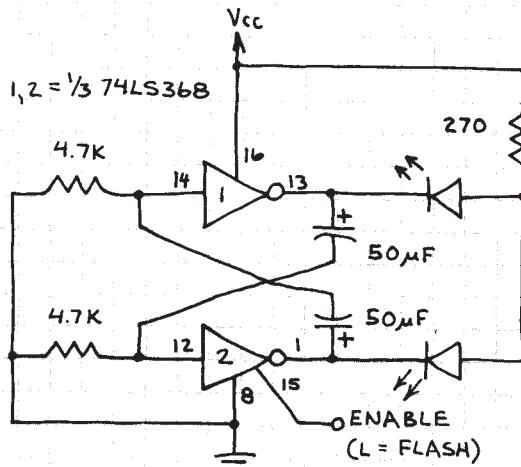


BOUNCELESS SWITCH (WITH ENABLE)

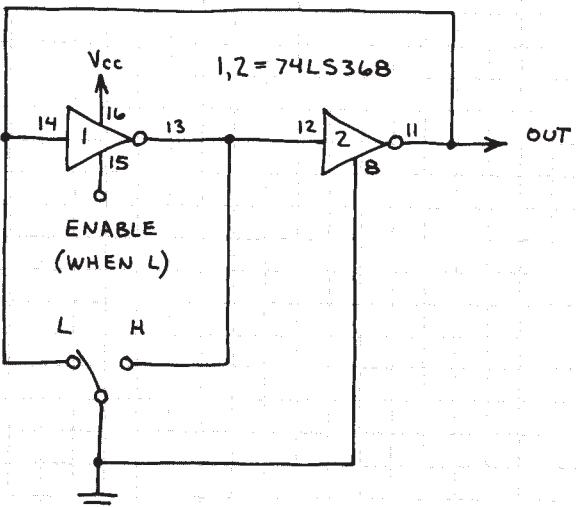


HEX INVERTER 7404/74LS04

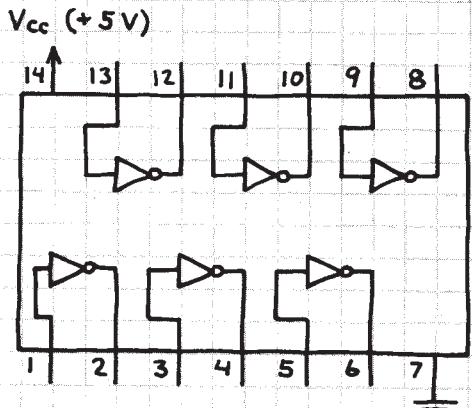
VERY IMPORTANT IN ALMOST ALL LOGIC CIRCUITS. CHANGES AN INPUT TO ITS COMPLEMENT (i.e. H → L AND L → H).




BOUNCEFREE SWITCH

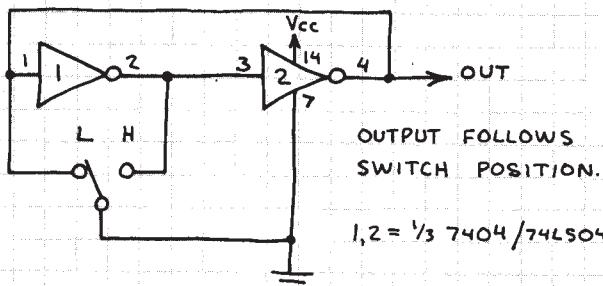


AUDIO OSCILLATOR

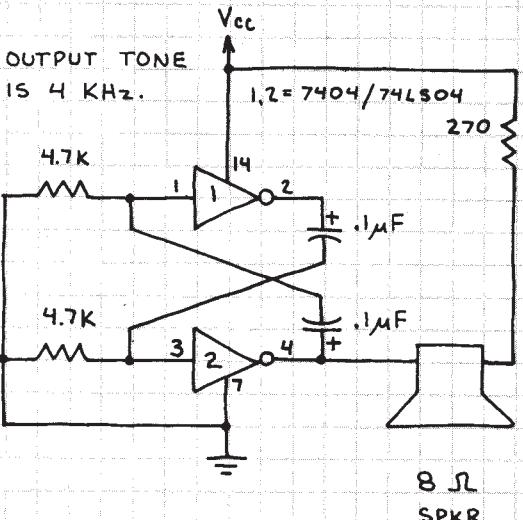

UNIVERSAL EXPANDER

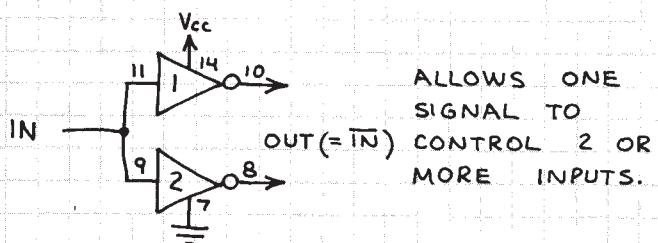

1-OF-2 DEMULTIPLEXER

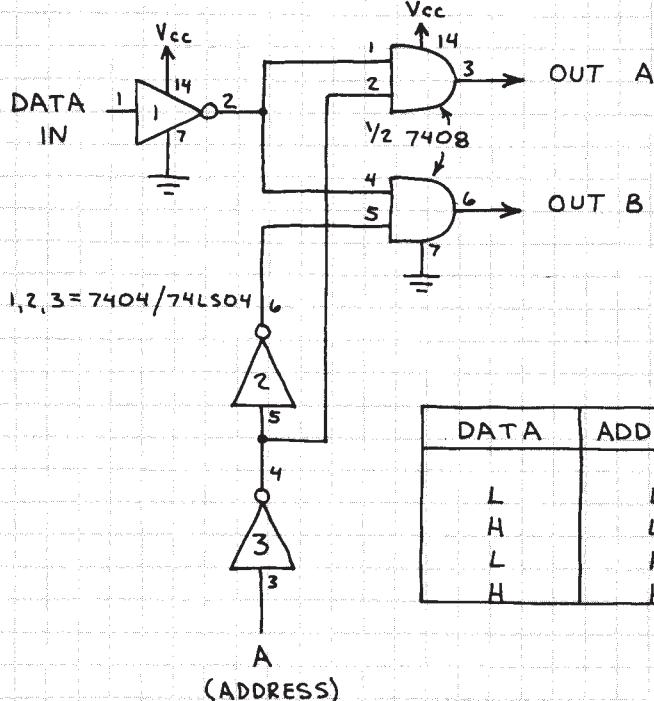


THIS CIRCUIT STEERS THE INPUT BIT TO THE OUTPUT SELECTED BY THE ADDRESS.

THIS TECHNIQUE CAN BE USED TO MAKE MULTIPLE OUTPUT DEMULTIPLEXERS.

DATA	ADDRESS	OUT A	OUT B
L	L	L	H
H	L	H	H
L	H	H	H
H	H	H	H


4-BIT MAGNITUDE COMPARATOR 74LS85

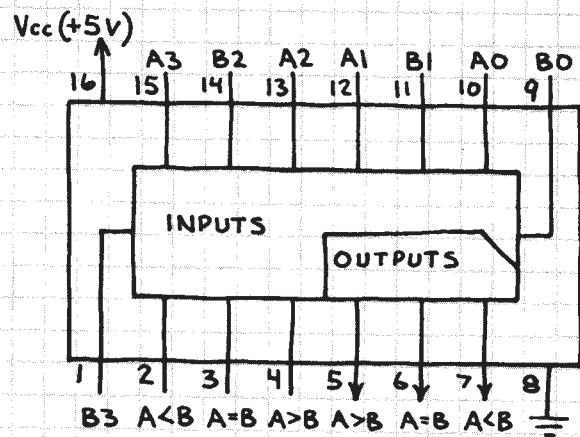COMPARES TWO 4-BIT WORDS. INDICATES WHICH IS LARGER OR IF THEY ARE EQUAL.




8-BIT COMPARATOR


HIGH EQUAL LOW

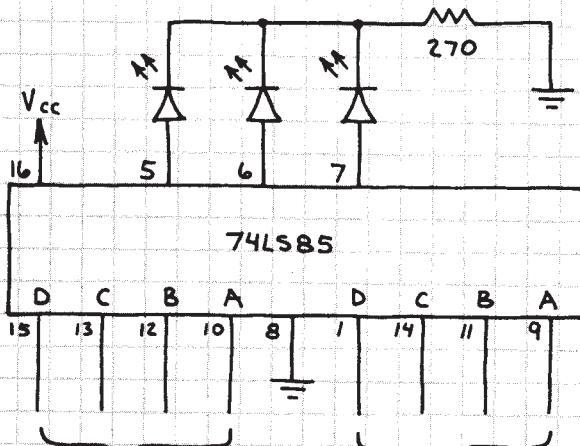

(OUTPUT LEDs ARE OPTIONAL.)

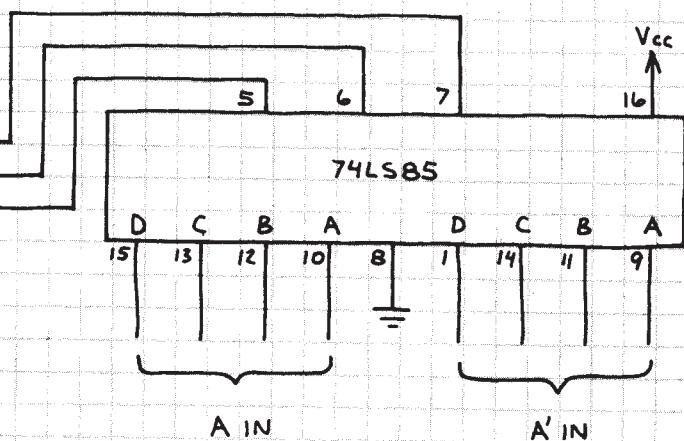


BINARY HI-LO GAME

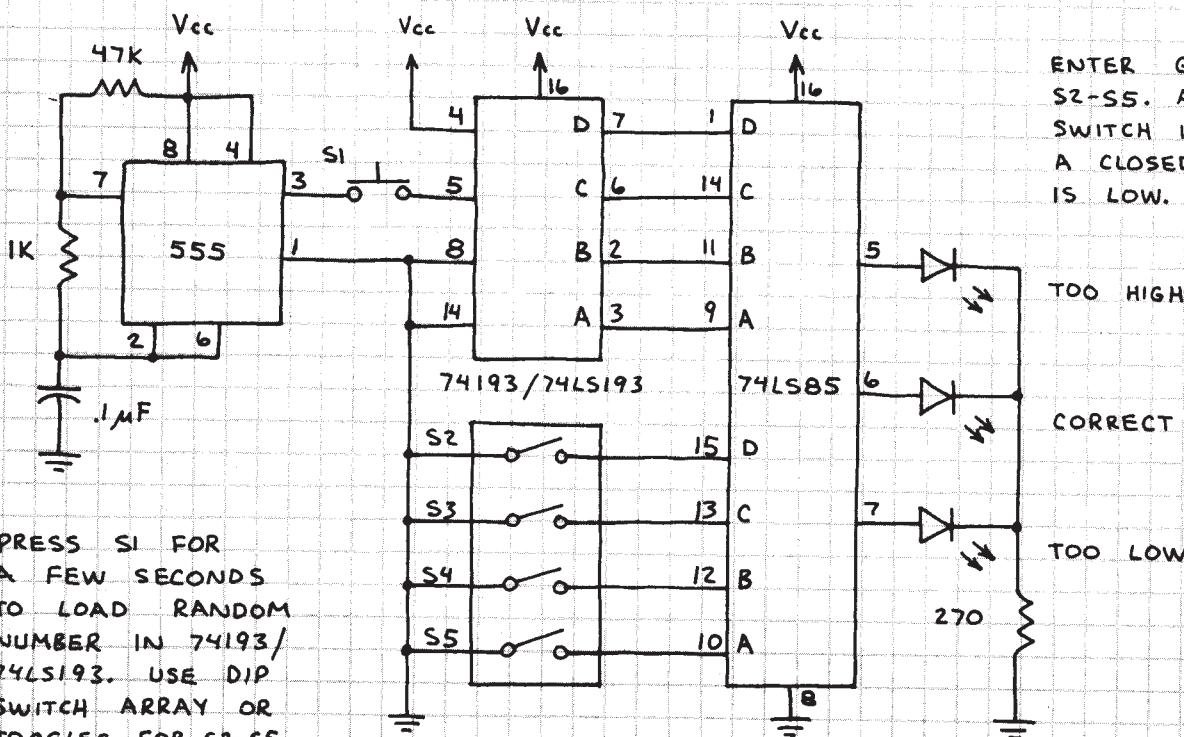


QUAD 1-OF-2 DATA SELECTOR

74LS157

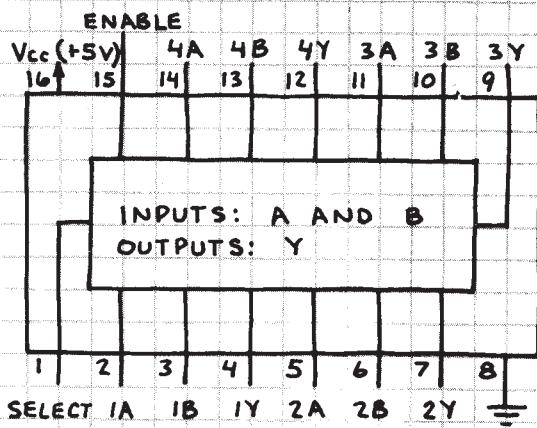
FOUR 2-LINE TO 1-LINE MULTIPLEXERS.
MANY USES IN ROUTING DATA. ALL
4 DATA SELECTORS ARE ENABLED
WHEN PIN 15 IS LOW.




DOUBLE DUTY DISPLAY

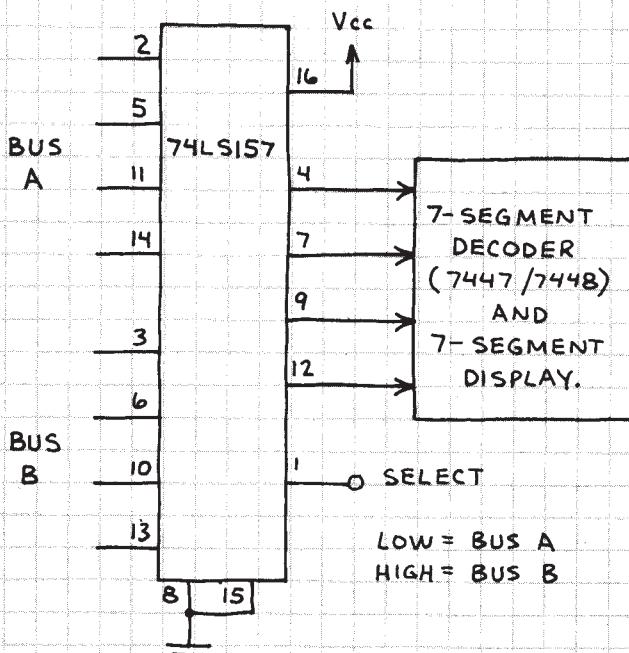

BUS SELECTOR

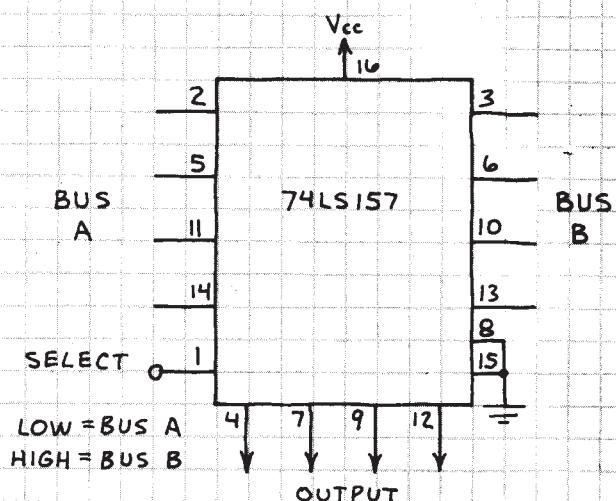

WORD SORTER

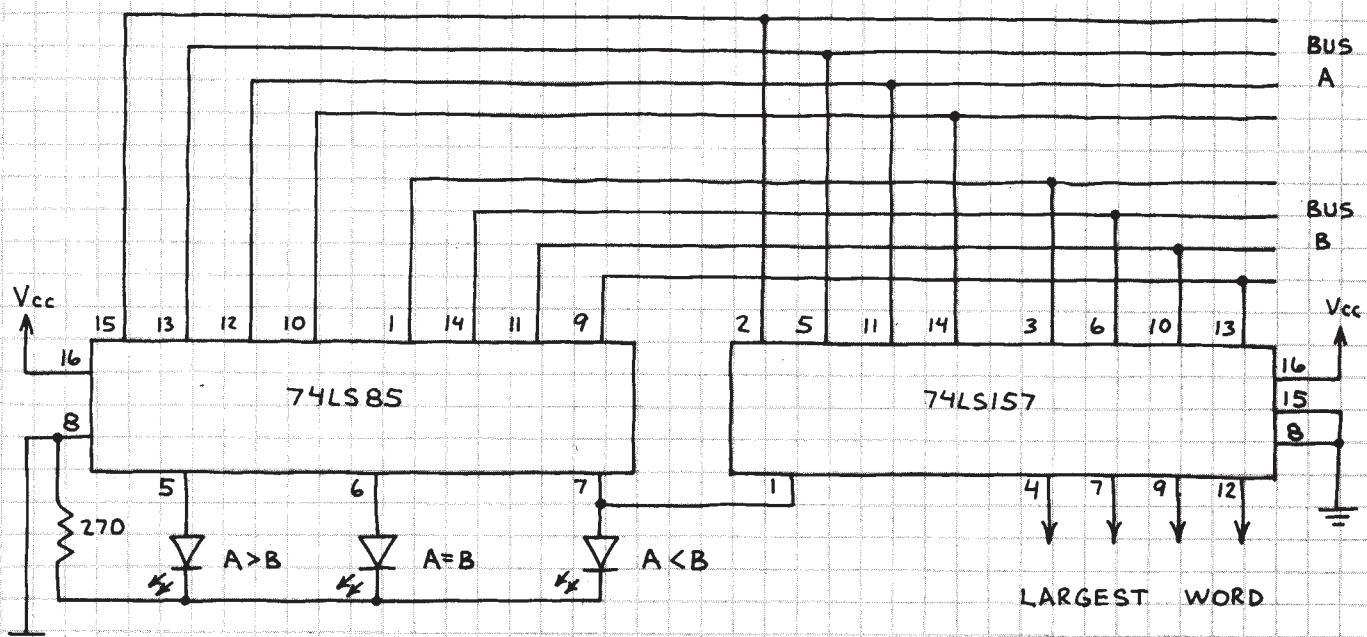

THIS CIRCUIT CONTINUALLY MONITORS TWO DATA BUSES. BUS WITH HIGHEST MAGNITUDE DATA WORD IS ROUTED AUTOMATICALLY TO OUTPUT.



I-OF-8 DATA SELECTOR

74LS151


EQUIVALENT TO 8-LINE TO 1-LINE MULTIPLEXER.

PROGRAMMABLE GATE

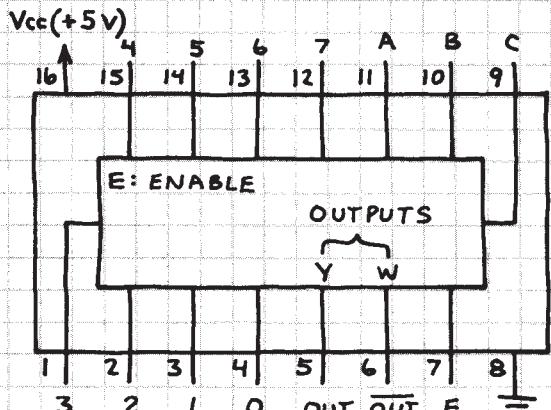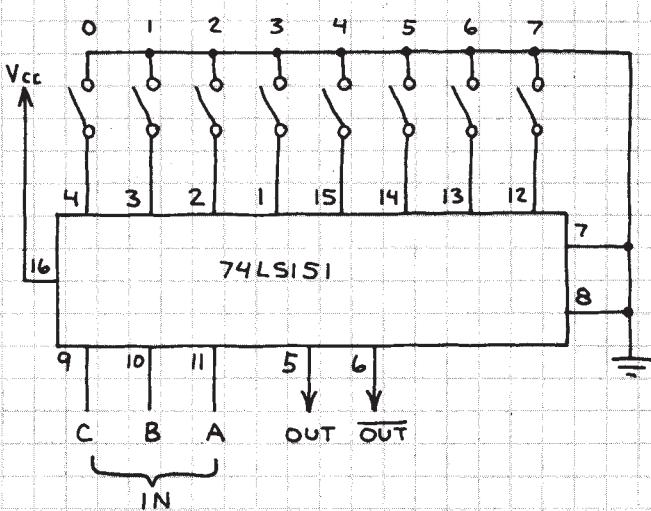3-BIT ADDRESS SELLECTS ONE SWITCH AND APPLIES ITS STATUS (OPEN = HIGH AND CLOSED = LOW) TO THE OUTPUT. ANY 3-INPUT LOGIC FUNCTION CAN BE PROGRAMMED IN SECONDS.




PATTERN GENERATOR

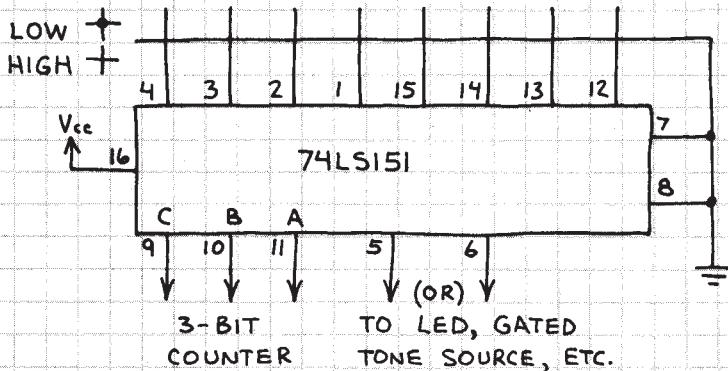


PROGRAM ANY DESIRED LOW-HIGH BIT PATTERN. THEN PLAY IT BACK.

OCTAL KEYBOARD ENCODER

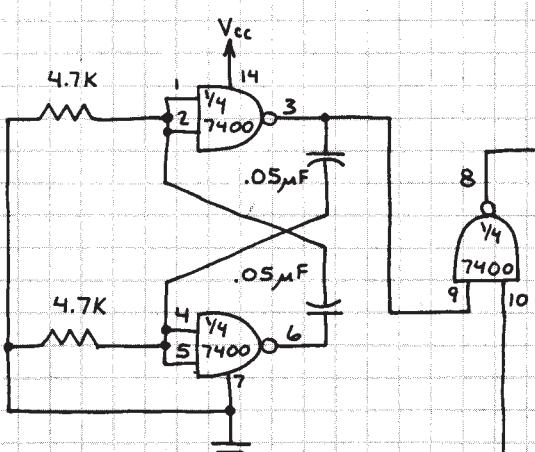

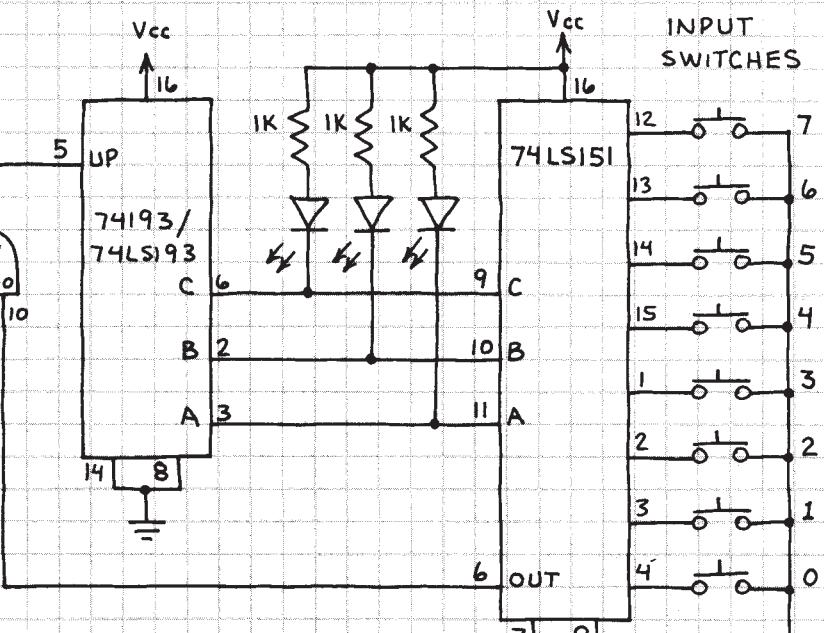PRESS NUMBERED SWITCH AND ITS BINARY EQUIVALENT APPEARS ON THE READOUT LEDs. THE LEDs ARE OPTIONAL.




READOUT LEDs:
ON = LOW (0)
OFF = HIGH (1)


BCD-TO-DECIMAL DECODER

7441

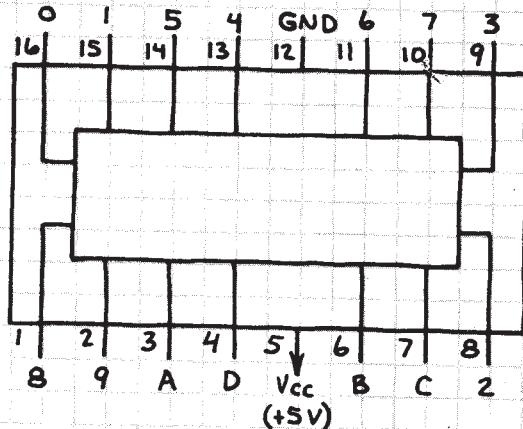DECODES 4-BIT BCD INPUT INTO 1-OF-10 OUTPUTS. SELECTED OUTPUT GOES LOW; ALL OTHERS STAY HIGH. ORIGINALLY DESIGNED TO DRIVE GASEOUS GLOW DISCHARGE TUBES. ALL OUTPUTS GO HIGH FOR BINARY INPUTS EXCEEDING HLLH (1001).




1-OF-10 DECODED COUNTER

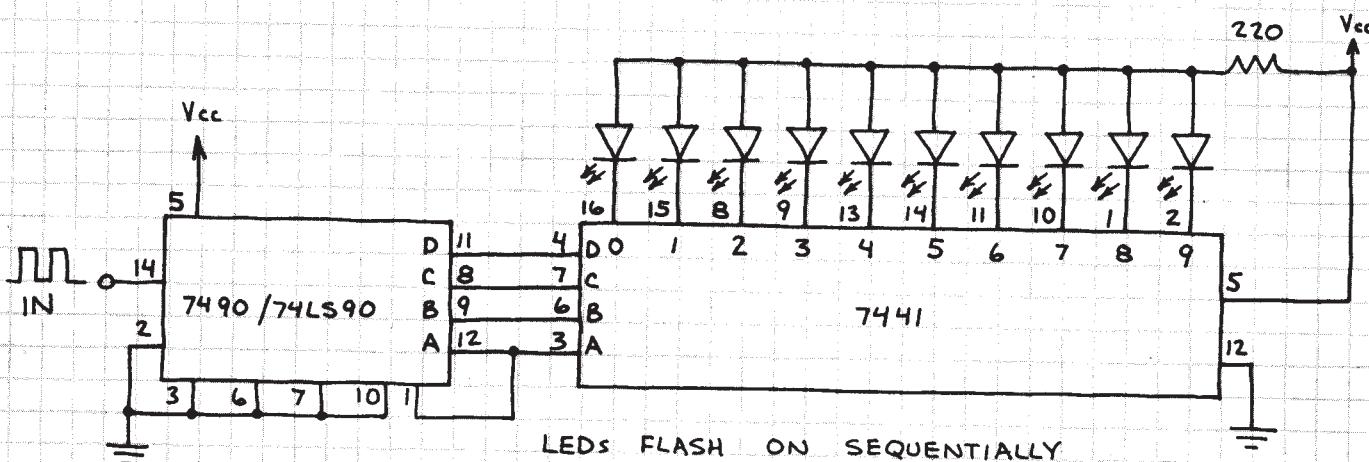

LEDS FLASH ON SEQUENTIALLY IN RESPONSE TO DECODED COUNT. ONLY ONE LED SERIES RESISTOR IS REQUIRED.

10-NOTE TONE SEQUENCER

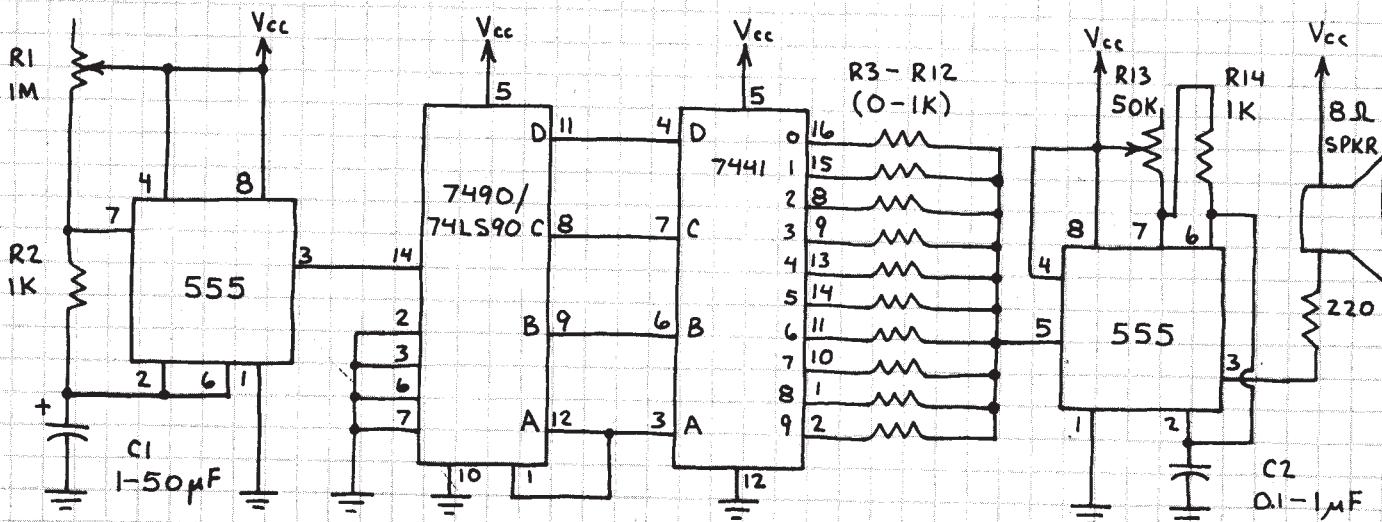


INCREASE CI TO DECREASE TEMPO. INCREASE C2 TO INCREASE TONE FREQUENCIES. TONES ARE DETERMINED BY R3-R12.

4-LINE TO 16-LINE


DECODER

74154

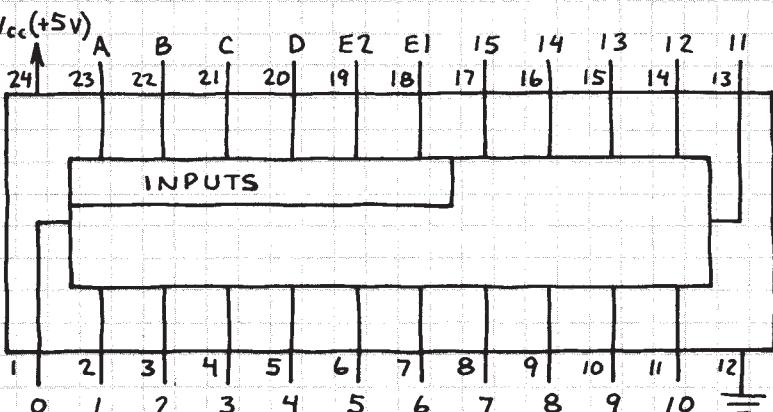
EACH 4-BIT ADDRESS DRIVES ONE OUTPUT LOW. ALL OTHERS STAY HIGH. ENABLE INPUTS (E1 AND E2) MUST BE LOW. IF ONE OR BOTH ARE HIGH, ALL OUTPUTS GO LOW.




1-TO-16 DEMULTIPLEXER

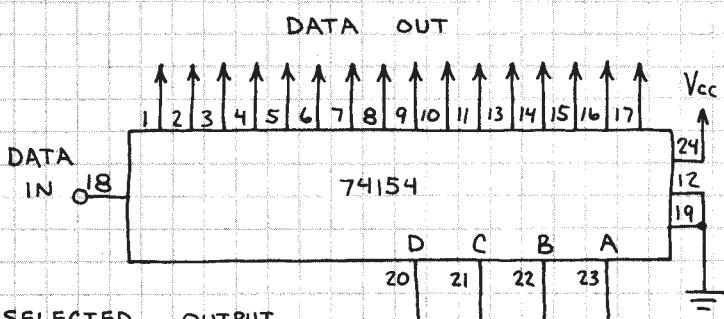

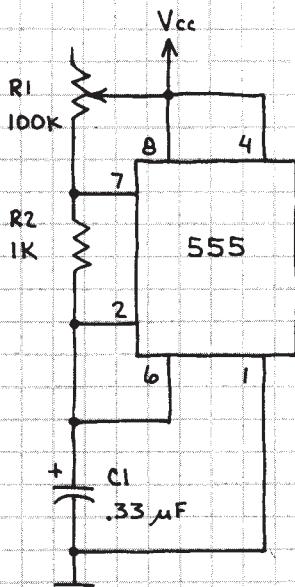SELECTED OUTPUT IS LOW WHEN DATA IN IS LOW. IF DATA IN IS HIGH, SELECTED OUTPUT IS HIGH.



BACK AND FORTH FLASHER

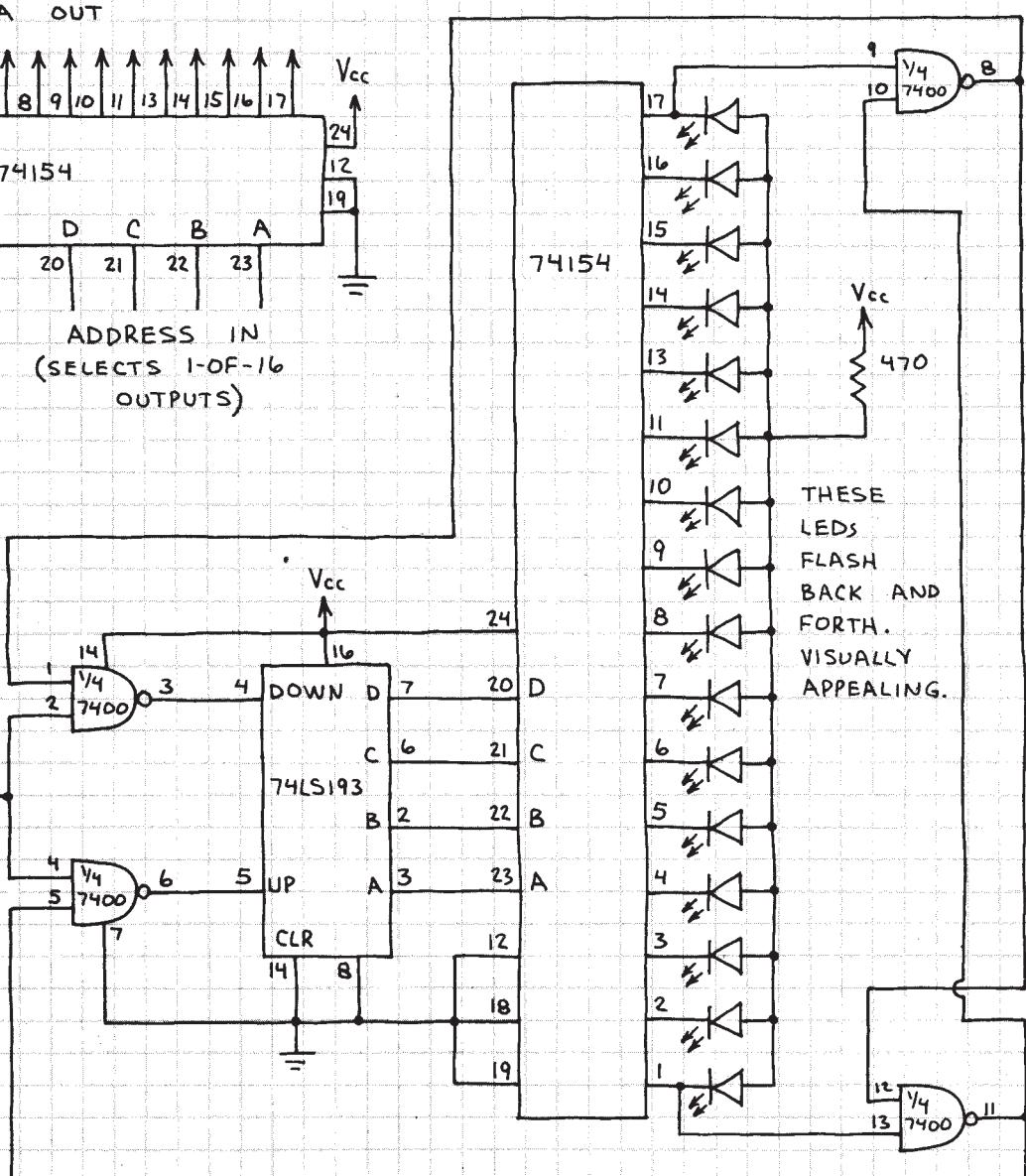


INCREASE R1 TO SLOW FLASH RATE.


BCD-TO-7 SEGMENT DECODER/DRIVER

7447 / 74LS47

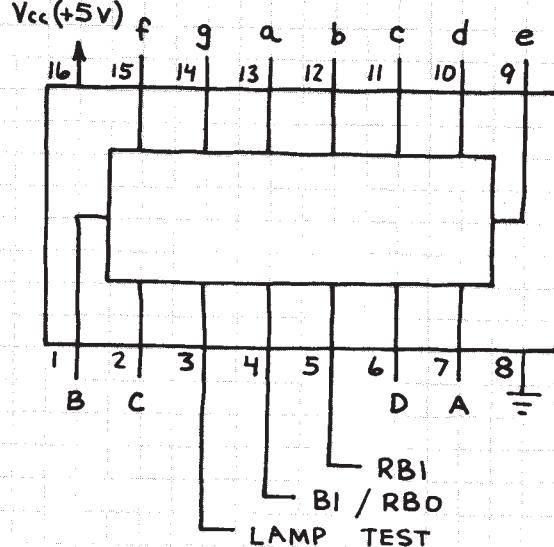
CONVERTS BCD DATA INTO FORMAT SUITABLE FOR PRODUCING DECIMAL DIGITS ON COMMON ANODE LED 7-SEGMENT DISPLAY. WHEN LAMP TEST INPUT IS LOW, ALL OUTPUTS ARE LOW (ON). WHEN BI/RBO (BLANKING INPUT) IS LOW, ALL OUTPUTS ARE HIGH (OFF). WHEN DCBA INPUT IS LLLL (DECIMAL 0) AND RBI (RIPPLE BLANKING INPUT) IS LOW, ALL OUTPUTS ARE HIGH (OFF). THIS PERMITS UNWANTED LEADING 0's IN A ROW OF DIGITS TO BE BLANKED.




MANUALLY SWITCHED DISPLAY

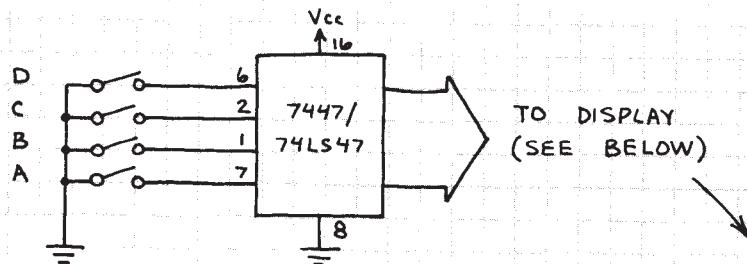

DISPLAY FLASHER

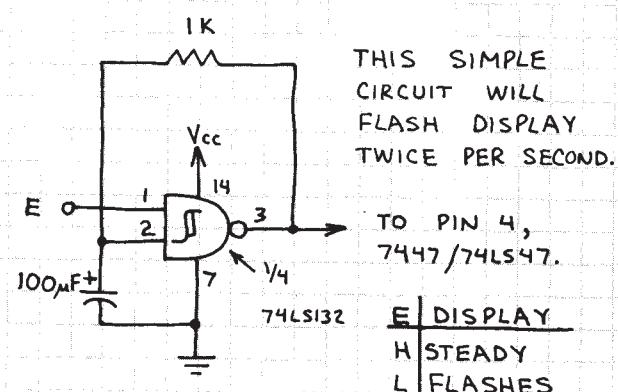


0-9 SECOND / MINUTE TIMER

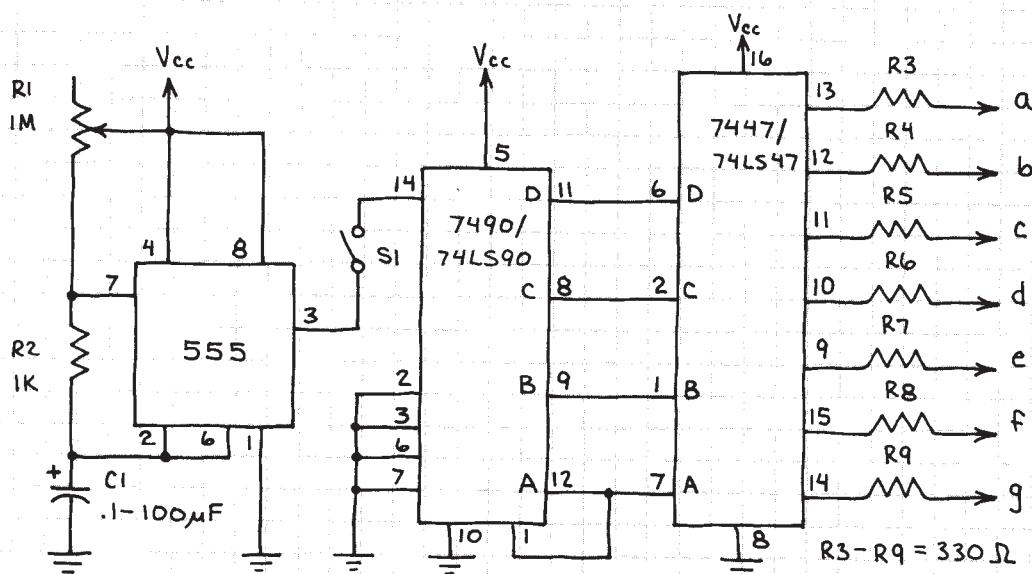


BCD-TO-7-SEGMENT DECODER / DRIVER 7448

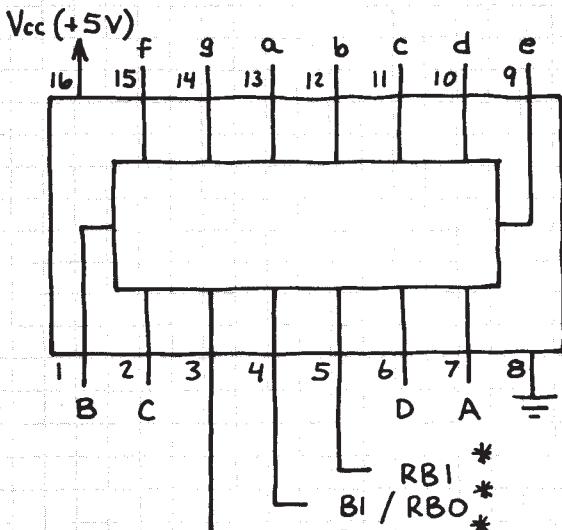CONVERTS BCD DATA INTO
FORMAT SUITABLE FOR PRODUCING
DECIMAL DIGITS ON COMMON
CATHODE LED 7-SEGMENT DISPLAY.




*SEE 7447 FOR
EXPLANATIONS.

DISPLAY DIMMER

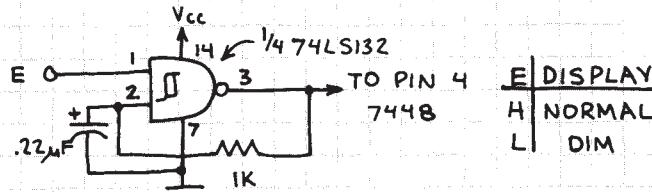


O-99 TWO DIGIT COUNTER



LOWEST ORDER DISPLAY

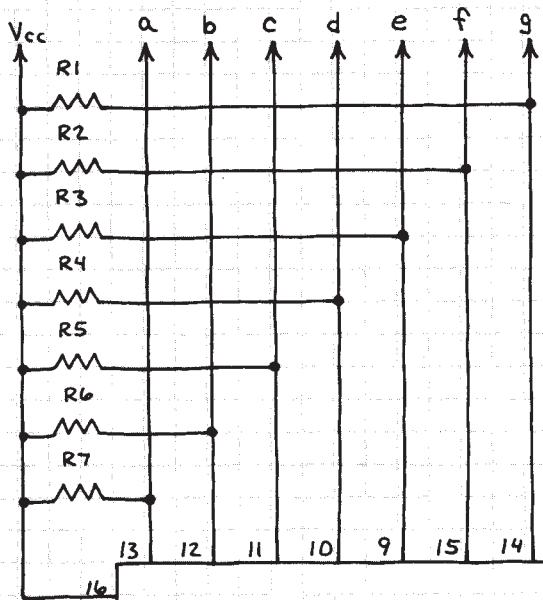

HIGHEST ORDER DISPLAY

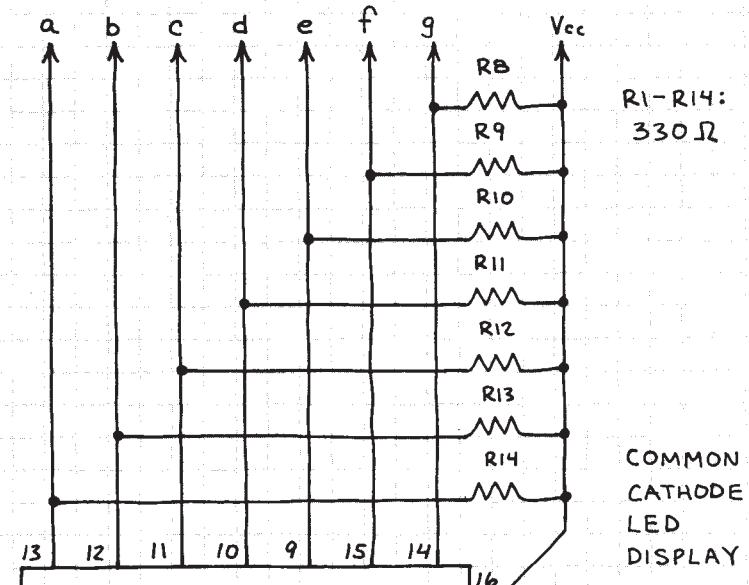


COMMON
CATHODE
LED
DISPLAY

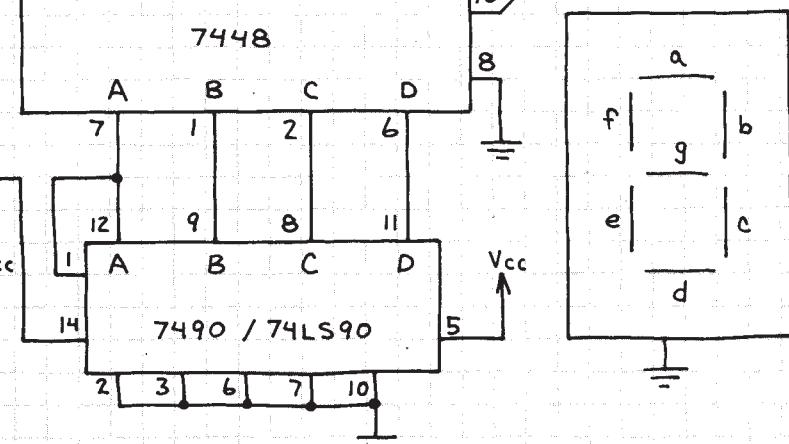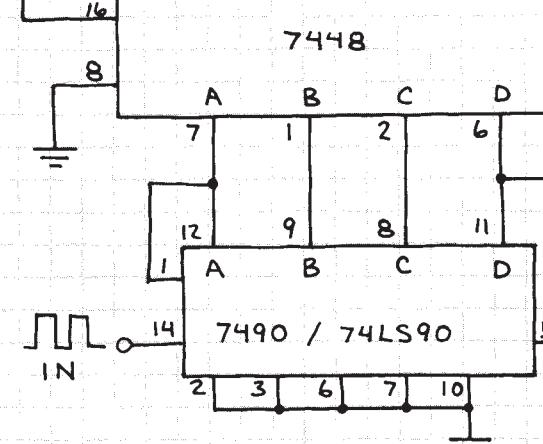

DUAL ONE-SHOT


74LS123

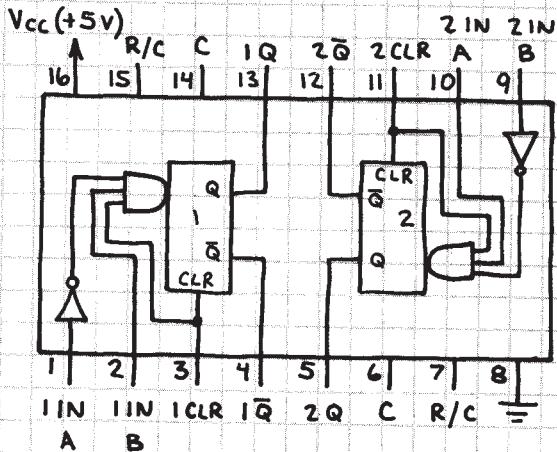TWO FULLY INDEPENDENT MONOSTABLE MULTIVIBRATORS. BOTH ARE RETRIGGERABLE. PINS DESIGNATED R AND R/C ARE FOR EXTERNAL TIMING RESISTOR AND CAPACITOR. SEE RADIO SHACK DATA BOOK FOR INFORMATION ABOUT R AND C.



BASIC ONE-SHOT

MISSING PULSE DETECTOR

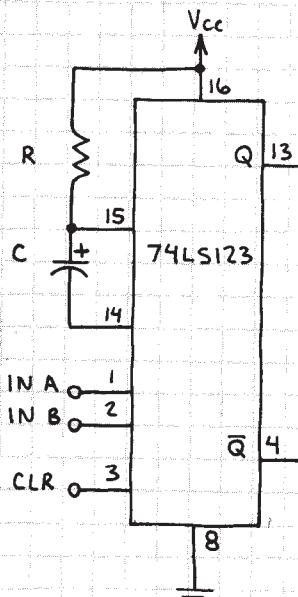


TWO WAYS TO TRIGGER:

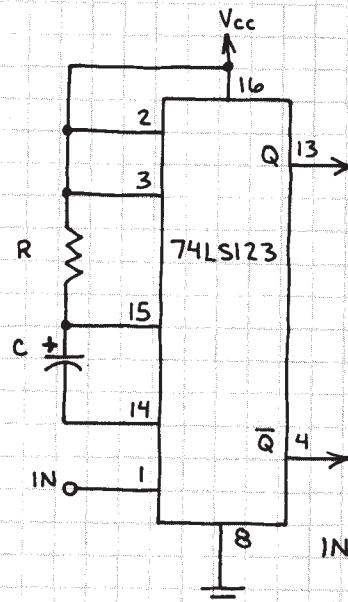1. KEEP INPUTS A AND B LOW; THEN MAKE B HIGH.
2. KEEP INPUTS A AND B HIGH; THEN MAKE A LOW.

TO CLEAR:


MAKE PIN 3 LOW.
THIS ALSO INITIATES TRIGGERING.





Q OUTPUT STAYS HIGH SO LONG AS INCOMING PULSES ARRIVE BEFORE ONE-SHOT TIMING PERIOD RUNS OUT.

ADJUST R AND C TO GIVE TIMING PERIOD ABOUT $\frac{1}{3}$ LONGER THAN THE INTERVAL BETWEEN INCOMING PULSES.

OPERATION:

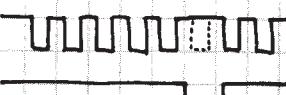

TONE STEPPER

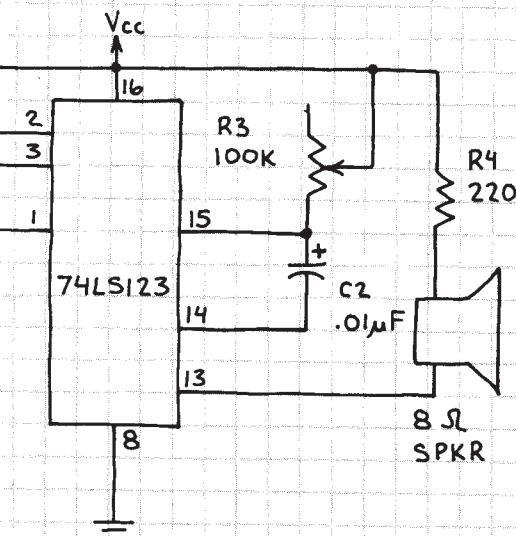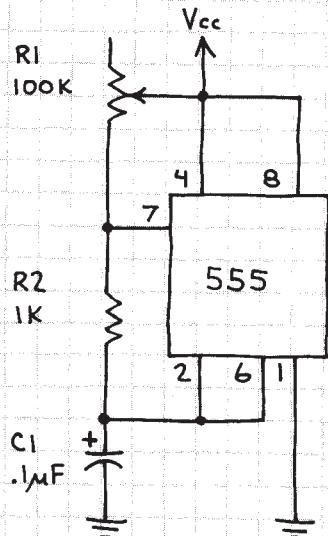

THIS CIRCUIT STEPS ACROSS A RANGE OF TONES WHEN R1 AND/OR R3 ARE ADJUSTED. VERY UNUSUAL SOUND EFFECTS.


CHANGE C1 AND C2 FOR OTHER TONE RANGES. ALSO, TRY PHOTORESISTORS FOR R1 AND R3.

DUAL D FLIP-FLOP

7474 / 74LS74

TWO D (DATA) FLIP-FLOPS IN A SINGLE PACKAGE. DATA AT D INPUT IS STORED AND MADE AVAILABLE AT Q OUTPUT WHEN CLOCK PULSE (ϕ) GOES HIGH. HERE'S THE TRUTH TABLE:


PRESET	CLEAR	CLOCK	D	Q	\bar{Q}
L	H	X	X	H	L
H	L	X	X	L	H
H	H	↑	H	H	L
H	H	↑	L	L	H

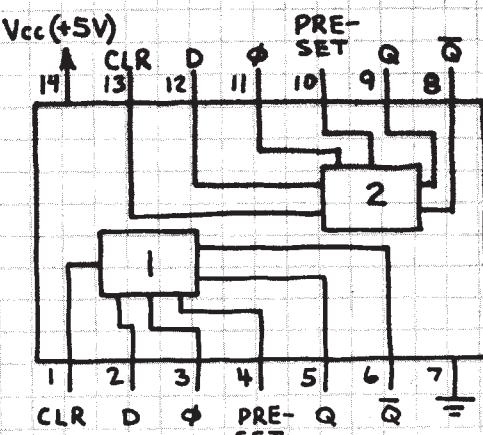

ϕ IS CLOCK INPUT.


↑ IS RISING EDGE OF CLOCK PULSE.

2-BIT STORAGE REGISTER

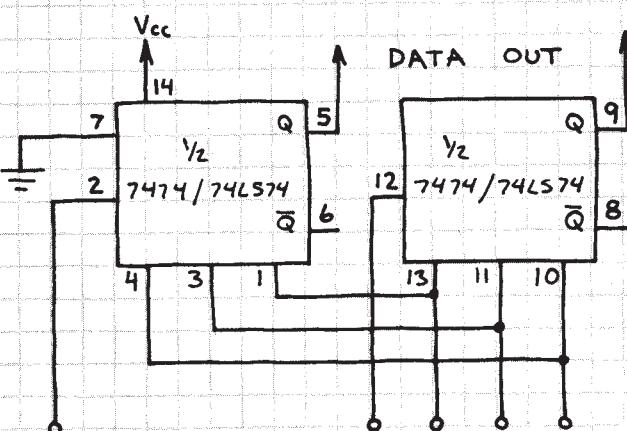


D ← DATA IN → D CLR ϕ PRESET

PHASE DETECTOR

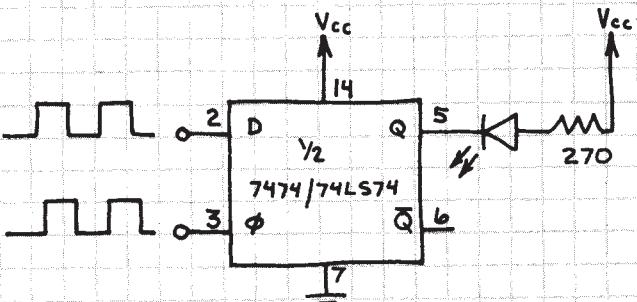


THE LED GLOWS WHEN INPUT FREQUENCIES F_1 AND F_2 ARE UNEQUAL OR OUT OF PHASE. F_1 AND F_2 SHOULD BE SQUARE WAVES.

WAVE SHAPER

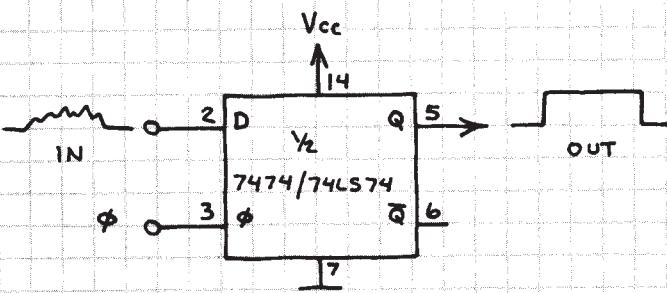

DIVIDE-BY-TWO COUNTER

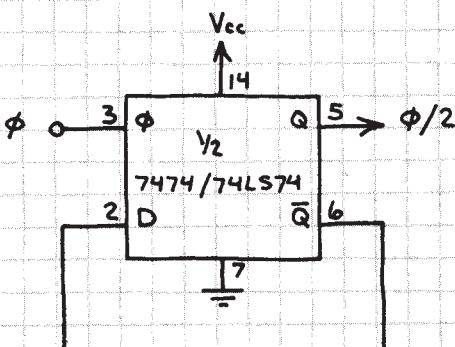


DUAL J-K FLIP-FLOP

7473 / 74LS73



TWO JK FLIP-FLOPS IN A SINGLE PACKAGE. NOTE THE CLEAR INPUTS. THESE FLIP-FLOPS WILL TOGGLE (SWITCH OUTPUT STATES) IN RESPONSE TO INCOMING CLOCK PULSES WHEN BOTH J AND K INPUTS ARE HIGH. HERE'S THE TRUTH TABLE:

CLEAR	CLOCK	J	K	Q	\bar{Q}
L	X	X	X	L	H
H	X	H	L	H	L
H	X	L	H	L	H
H	X	H	H	TOGGLE	

DIVIDE-BY-TWO

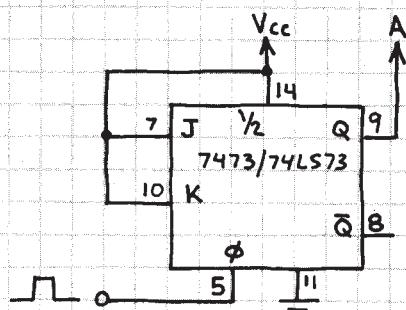

DIVIDE-BY-THREE

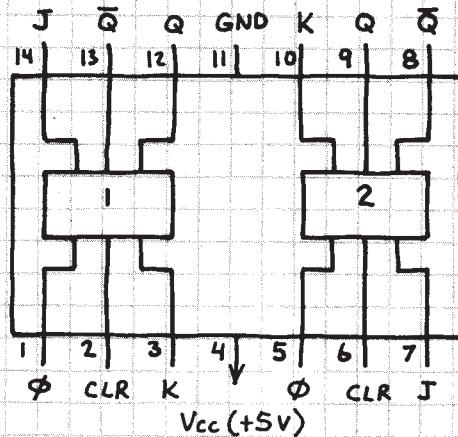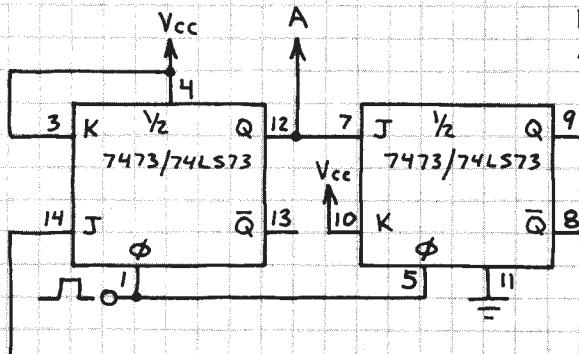


ϕ IS CLOCK INPUT.

BINARY COUNTERS

THE THREE CIRCUITS ON THIS PAGE ARE BINARY COUNTERS THAT COUNT UP TO THE MAXIMUM COUNT AND AUTOMATICALLY RECYCLE. CONNECT A DECODER TO OUTPUT OF DIVIDE-BY-THREE AND DIVIDE-BY-FOUR COUNTERS TO OBTAIN ONE-OF-THREE AND ONE-OF-FOUR OPERATION. THIS TRUTH TABLE SUMMARIZES OPERATION OF THESE COUNTERS:

DIVIDE-BY: TWO OUTPUTS:		A	B	A	B	A	B
L	L	L	L	L	L	L	L
H	L	L	H	L	H	L	H
H	H	H	L	H	L	H	H

DIVIDE-BY-FOUR

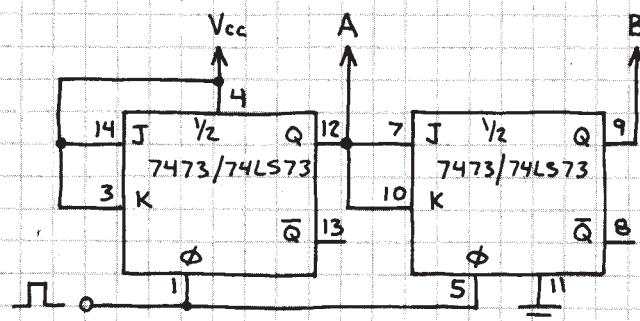


DUAL J-K FLIP-FLOP

7476 / 74LS76

TWO JK FLIP-FLOPS IN A SINGLE PACKAGE. SIMILAR TO 7473 / 74LS73 BUT HAS BOTH PRESET AND CLEAR INPUTS. FLIP-FLOPS WILL TOGGLE (SWITCH OUTPUT STATES) IN RESPONSE TO INCOMING CLOCK PULSES WHEN BOTH J AND K INPUTS ARE HIGH. HERE'S THE TRUTH TABLE:

PRE	CLR	CLK	J	K	Q	\bar{Q}
L	H	X	X	X	H	L
H	L	X	X	X	L	H
H	H	↓	H	L	H	L
H	H	↓	L	H	L	H
H	H	↓	H	H	TOGGLE	

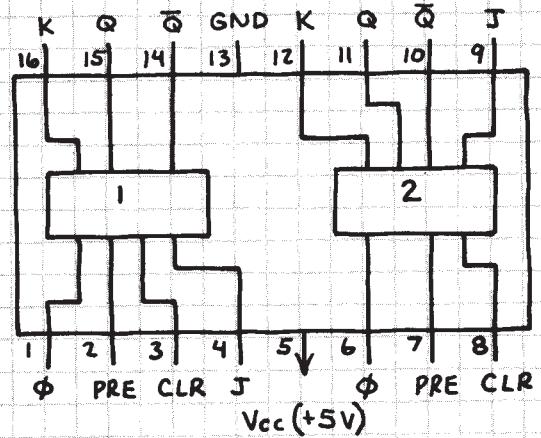


PRE = PRESET

CLR = CLEAR


φ = CLOCK (OR CLK)

TOGGLE = FLIP-FLOP SWITCHES OUTPUT STATES IN RESPONSE TO CLOCK PULSES.

4-BIT SERIAL SHIFT REGISTER

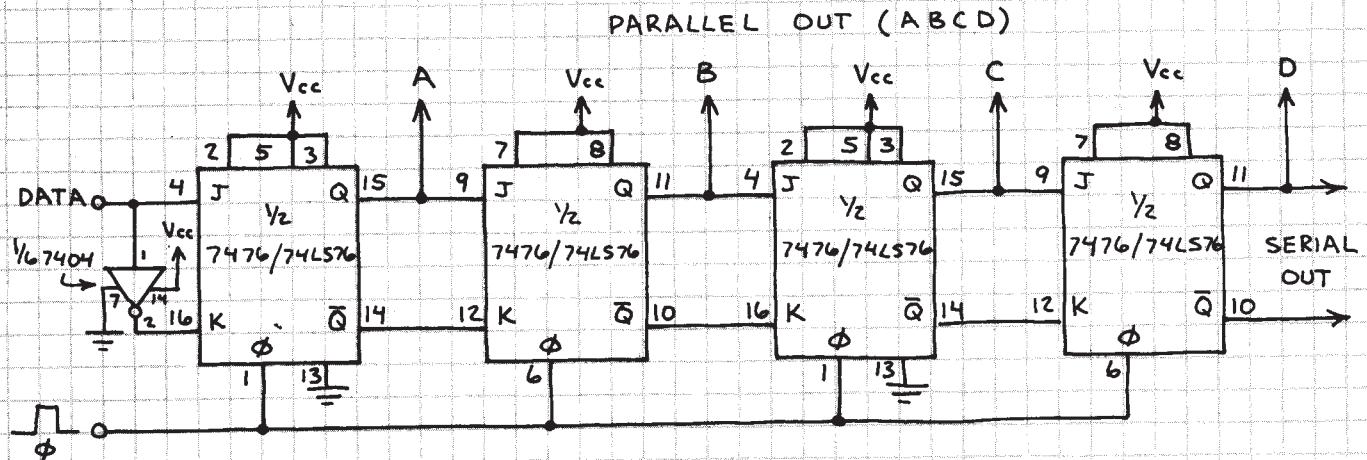


4-BIT BINARY UP COUNTER

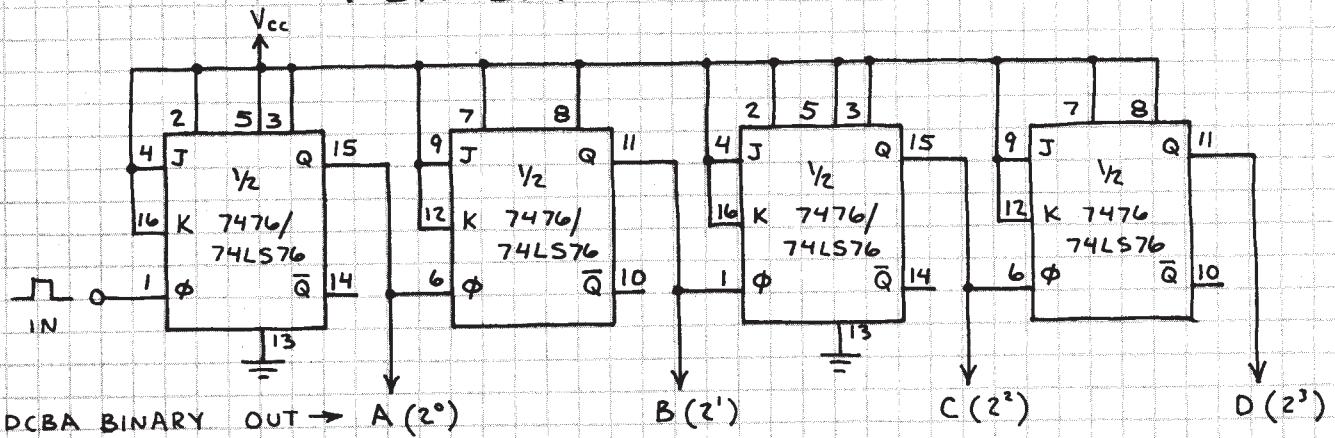


QUAD LATCH 7475/74LS75

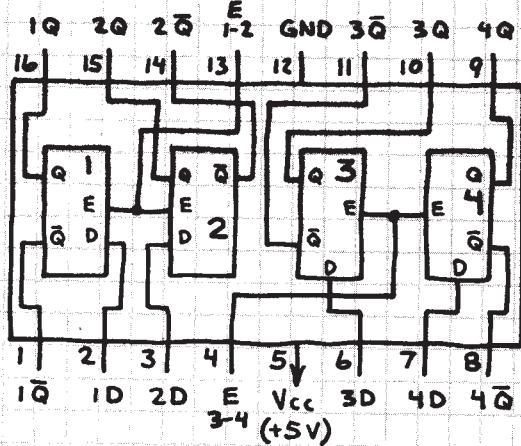A 4-BIT BISTABLE LATCH. PRIMARILY USED TO STORE THE COUNT IN DECIMAL COUNTING UNITS. NOTE THAT BOTH Q AND \bar{Q} OUTPUTS ARE PROVIDED. ALSO NOTE THE E (ENABLE) INPUTS. WHEN E IS HIGH, Q FOLLOWS D.




4-BIT DATA LATCH

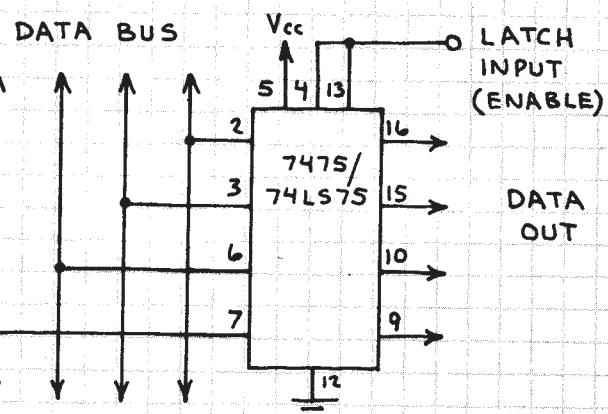DATA ON BUS APPEARS AT OUTPUTS WHEN LATCH INPUT IS HIGH. DATA ON BUS WHEN LATCH INPUT GOES LOW IS STORED UNTIL LATCH INPUT GOES HIGH. (LATCH INPUT CONTROLS BOTH ENABLE INPUTS.) TWO QUAD LATCHES CAN BE USED AS AN 8-BIT DATA LATCH.



DECIMAL COUNTING UNIT

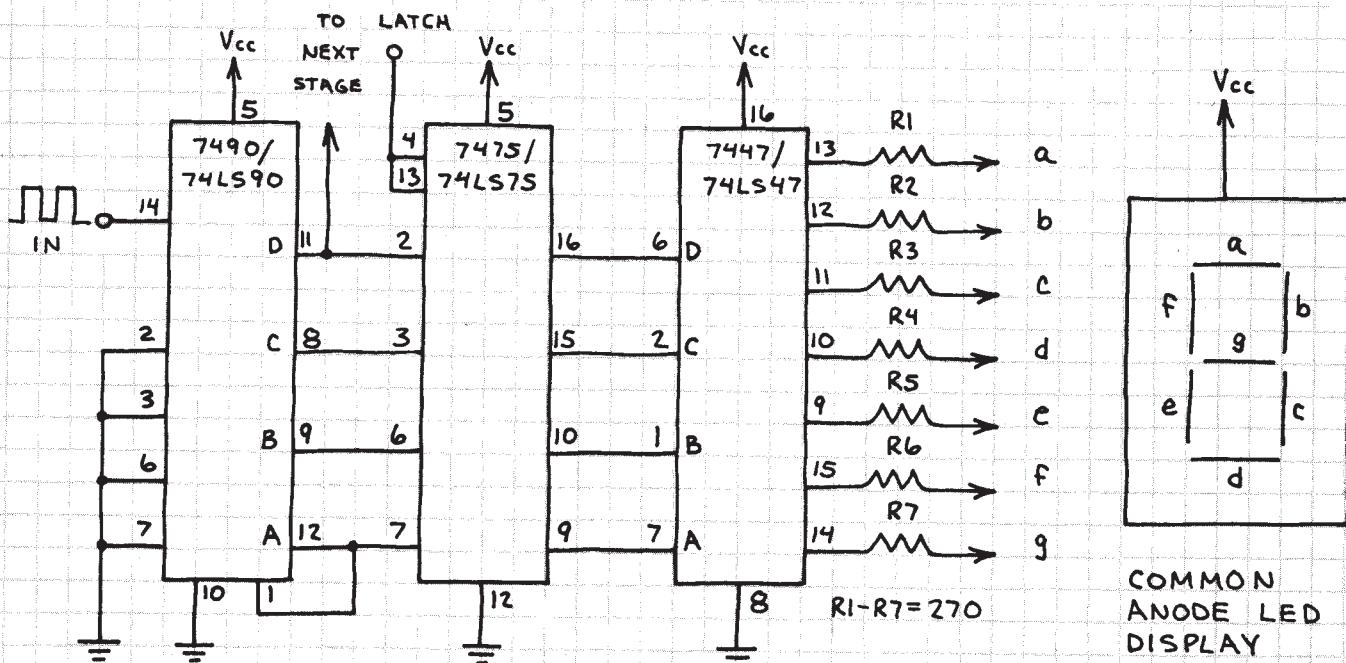


EXPANDABLE DECADE COUNTER. OF 7490/74LS90 OF FIRST UNIT TO INPUT OF SECOND UNIT. A LOW AT THE LATCH INPUT FREEZES THE DATA BEING DISPLAYED.

FOR TWO DIGIT COUNT, CONNECT PIN 11


QUAD D FLIP-FLOP

74LS175

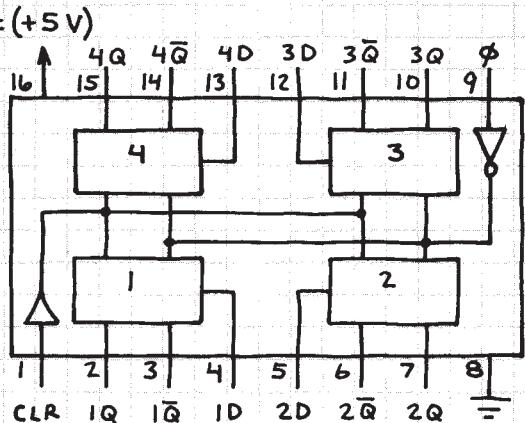HANDY PACKAGE OF FOUR D-TYPE FLIP-FLOPS. DATA AT D-INPUTS IS LOADED WHEN CLOCK GOES HIGH. MAKING CLEAR INPUT LOW MAKES ALL Q OUTPUTS LOW AND \bar{Q} OUTPUTS HIGH.




DATA BUS

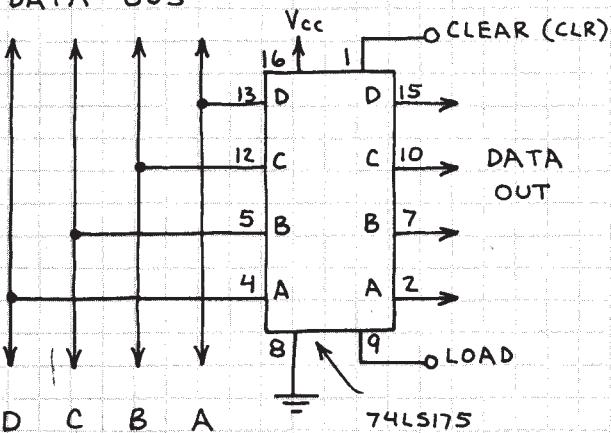


4-BIT DATA REGISTER

DATA ON BUS IS LOADED INTO 74LS175 WHEN LOAD INPUT GOES HIGH. DATA IS THEN STORED AND MADE AVAILABLE AT OUTPUTS UNTIL NEW LOAD PULSE ARRIVES.

MODULO-8 COUNTER

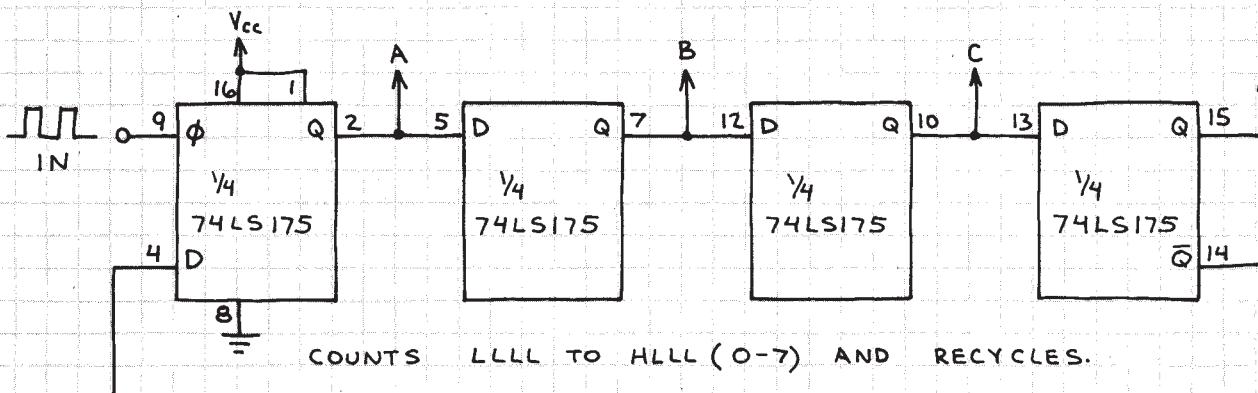

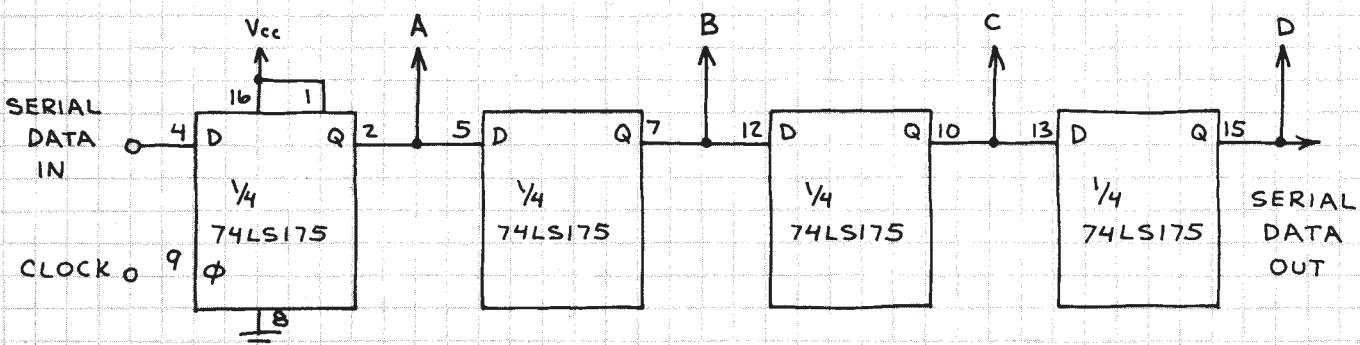
SERIAL IN/OUT, PARALLEL OUT SHIFT REGISTER




OCTAL D-TYPE LATCH

74LS373

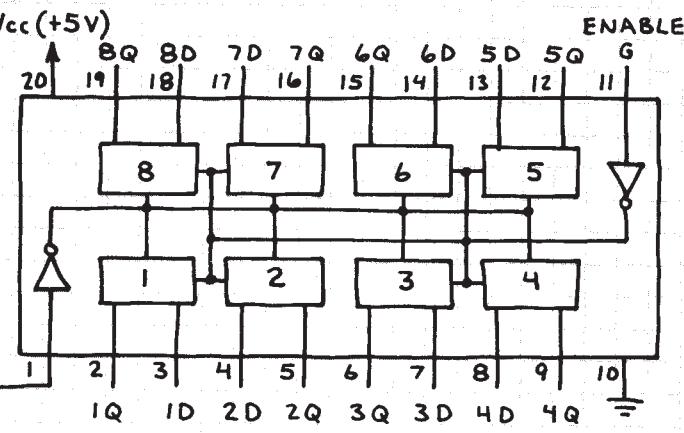EIGHT "TRANSPARENT" D-TYPE LATCHES. OUTPUT FOLLOWS INPUT WHEN ENABLE IS HIGH. THE DATA AT THE INPUTS IS LOADED WHEN THE ENABLE INPUT IS LOW. THIS CHIP HAS 3-STATE OUTPUTS WHICH ARE CONTROLLED BY PIN 1. SEE TRUTH TABLE BELOW.



3-STATE REGISTER

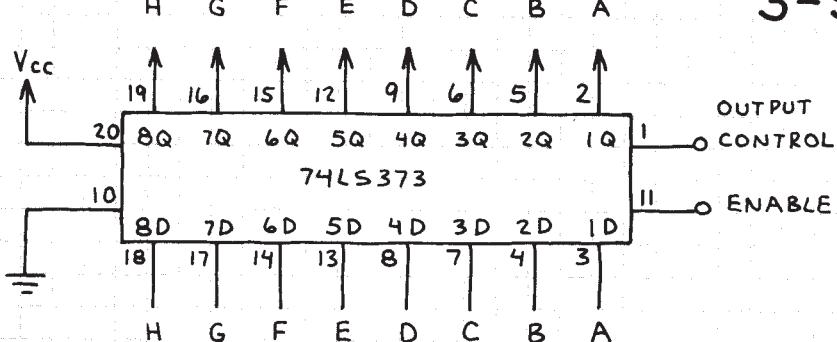



THIS IS A GENERAL PURPOSE 8-BIT STORAGE REGISTER. HERE'S THE TRUTH TABLE:

OUTPUT CONTROL	ENABLE	D	Q
L	H	H	H
L	H	L	L
L	L	X	Q
H	X	X	HI-Z

DATA BUS REGISTERS

H: PLACES OUTPUTS IN HI-Z MODE
L: MAKES DATA AVAILABLE

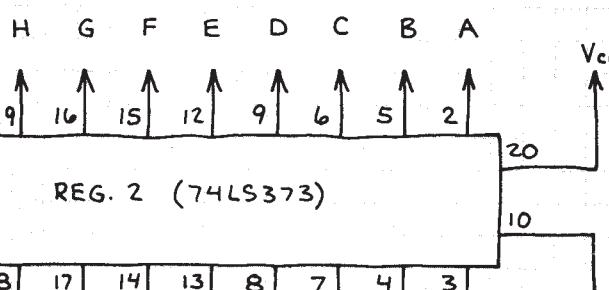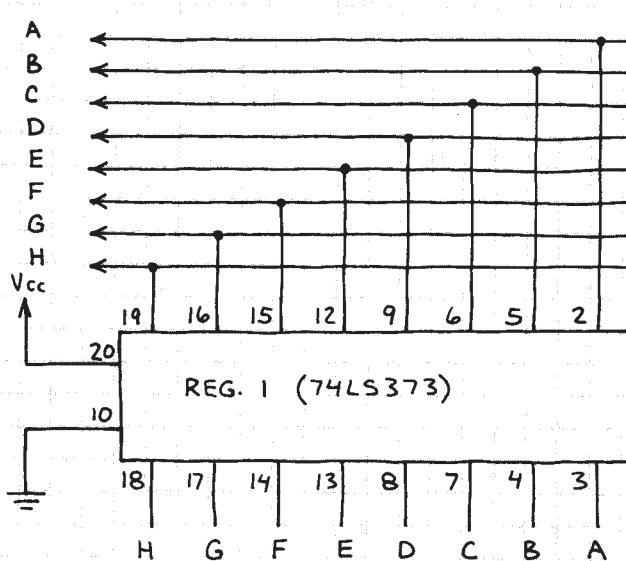H: OUTPUTS FOLLOW DATA ON BUS
L: LOAD DATA FROM BUS



H: DISCONNECTS REG. 1 FROM BUS.
L: CONNECTS REG. 1 TO BUS.


H: OUTPUTS FOLLOW INPUTS.
L: INPUT DATA (ON BUS) LOADED.

AT ANY INSTANT ONLY ONE 74LS373 CAN WRITE DATA ON THE BUS. ANY NUMBER CAN READ DATA FROM BUS.

OCTAL D FLIP-FLOP


74LS374

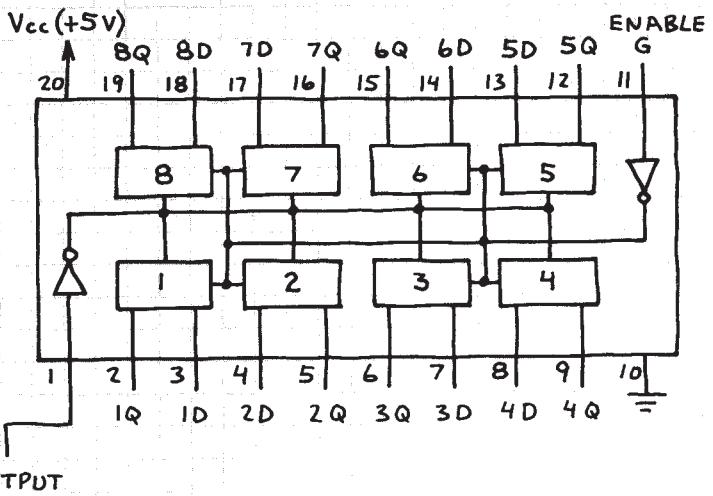EIGHT D-TYPE EDGE TRIGGERED FLIP-FLOPS. UNLIKE 74LS373, OUTPUTS DO NOT FOLLOW INPUTS. INSTEAD, A RISING CLOCK PULSE AT PIN 11 LOADS DATA APPEARING AT INPUTS. THIS CHIP HAS 3-STATE OUTPUTS WHICH ARE CONTROLLED BY PIN 1.



CLOCKED

3-STATE REGISTER

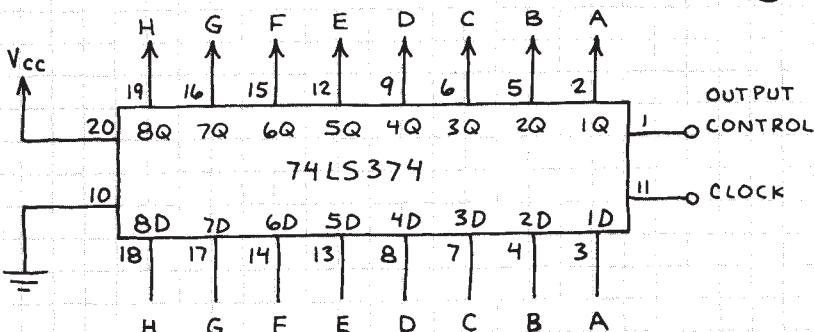


GENERAL PURPOSE CLOCKED REGISTER.
HERE'S THE TRUTH TABLE:

OUTPUT CONTROL	CLOCK	D	Q
L	↑	H	H
L	↑	L	L
L	H	X	Q
H	X	X	HI-Z

COMMON INPUT/OUTPUT BUS REGISTER

← BIDIRECTIONAL DATA BUS →

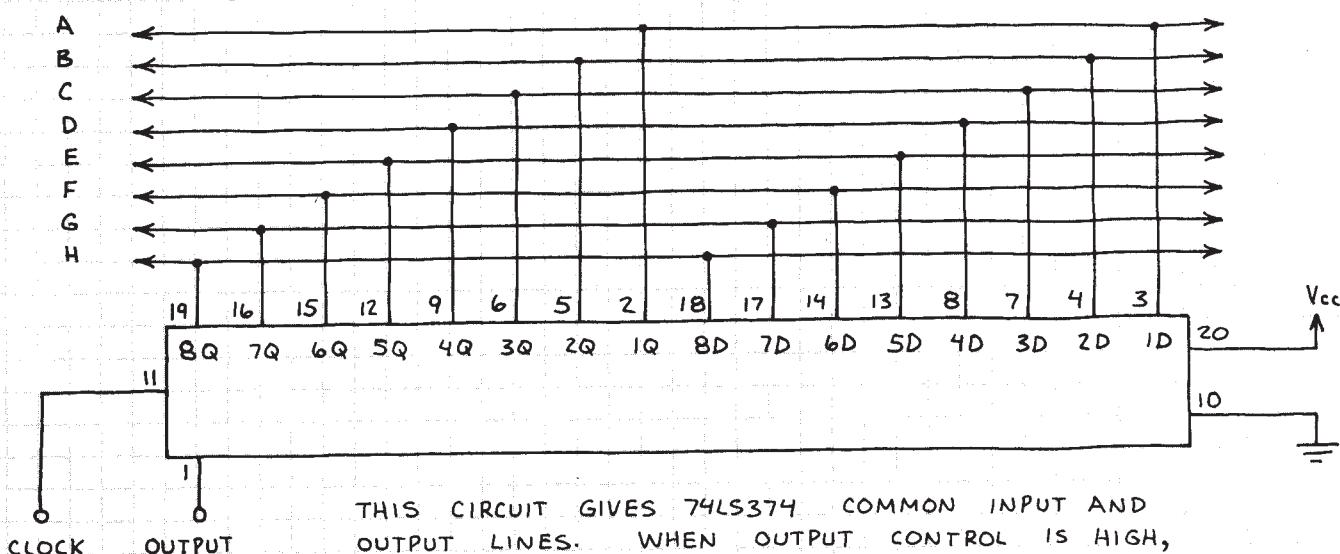


THIS CIRCUIT GIVES 74LS374 COMMON INPUT AND OUTPUT LINES. WHEN OUTPUT CONTROL IS HIGH, DATA ON BUS IS LOADED INTO THE 74LS374 ON THE RISING EDGE (↑) OF THE CLOCK PULSE. WHEN OUTPUT CONTROL IS LOW, DATA IN THE 74LS374 IS WRITTEN ONTO THE BUS.

8-BIT SHIFT REGISTER



74LS164

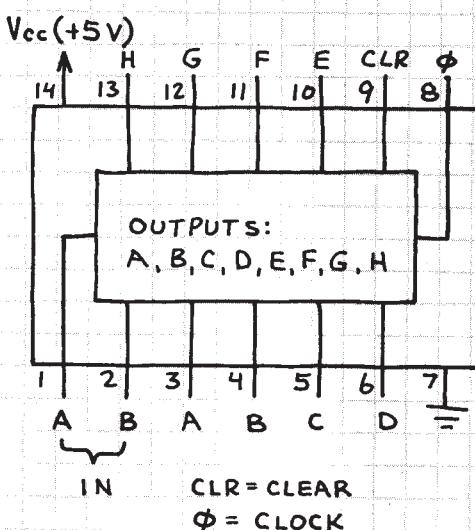DATA AT ONE OF THE TWO SERIAL INPUTS IS ADVANCED ONE BIT FOR EACH CLOCK PULSE. DATA CAN BE EXTRACTED FROM THE 8 PARALLEL OUTPUTS OR IN SERIAL FORM AT ANY SINGLE OUTPUT. ENTER DATA AT EITHER INPUT. THE UNUSED INPUT MUST BE HELD HIGH OR CLOCKING WILL BE INHIBITED. MAKING PIN 9 LOW CLEARS THE REGISTER TO LLLL.




8-BIT SERIAL-TO-PARALLEL DATA CONVERTER

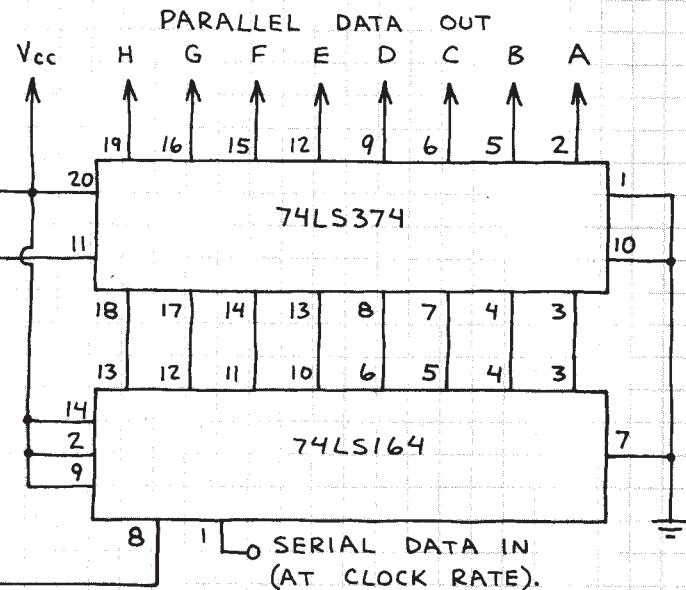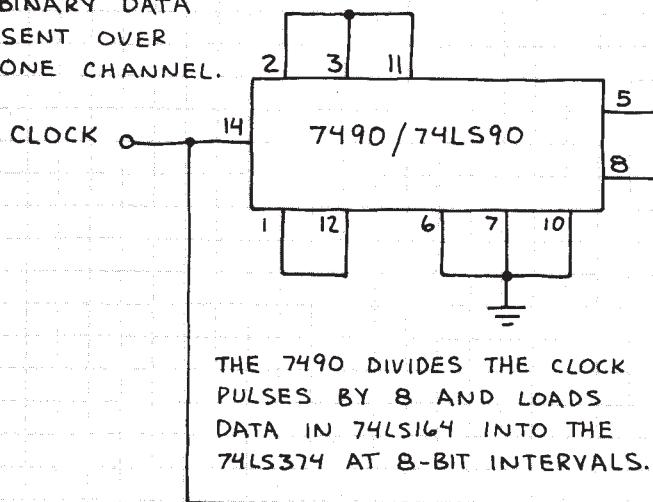USE FOR RECEIVING BINARY DATA SENT OVER ONE CHANNEL.




PSEUDO-RANDOM VOLTAGE GENERATOR

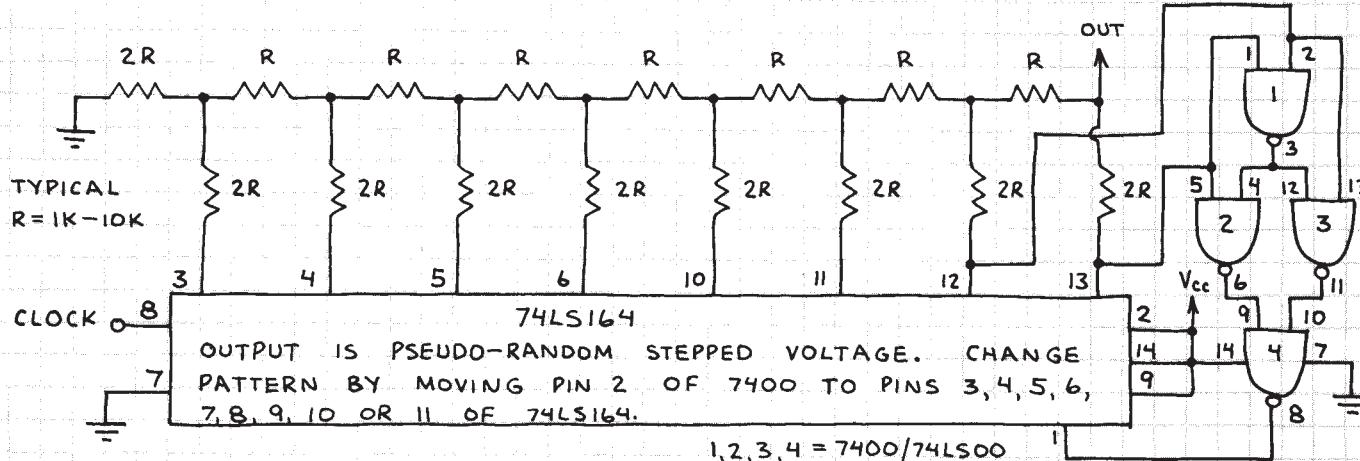


4-BIT SHIFT REGISTER

74LS194

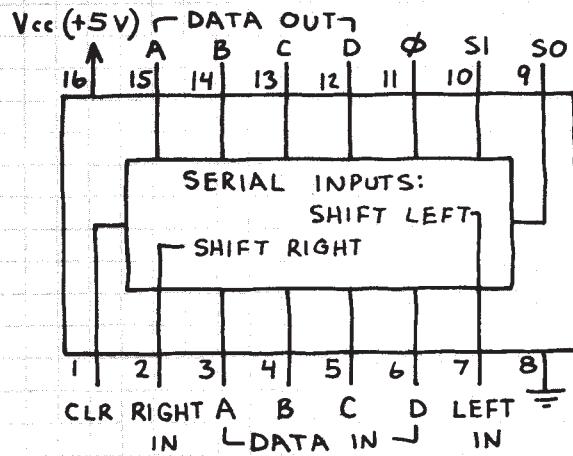
BIDIRECTIONAL UNIVERSAL SHIFT REGISTER. SHIFTS RIGHT WHEN SO IS HIGH AND SI IS LOW. SHIFTS LEFT WHEN SO IS LOW AND SI IS HIGH. SHIFTS ONE POSITION PER CLOCK PULSE. LOADS DATA AT INPUTS WHEN SO AND SI ARE HIGH. IMPORTANT: BYPASS POWER SUPPLY PINS WITH $0.1\mu F$ CAPACITOR!



SEQUENCE GENERATOR

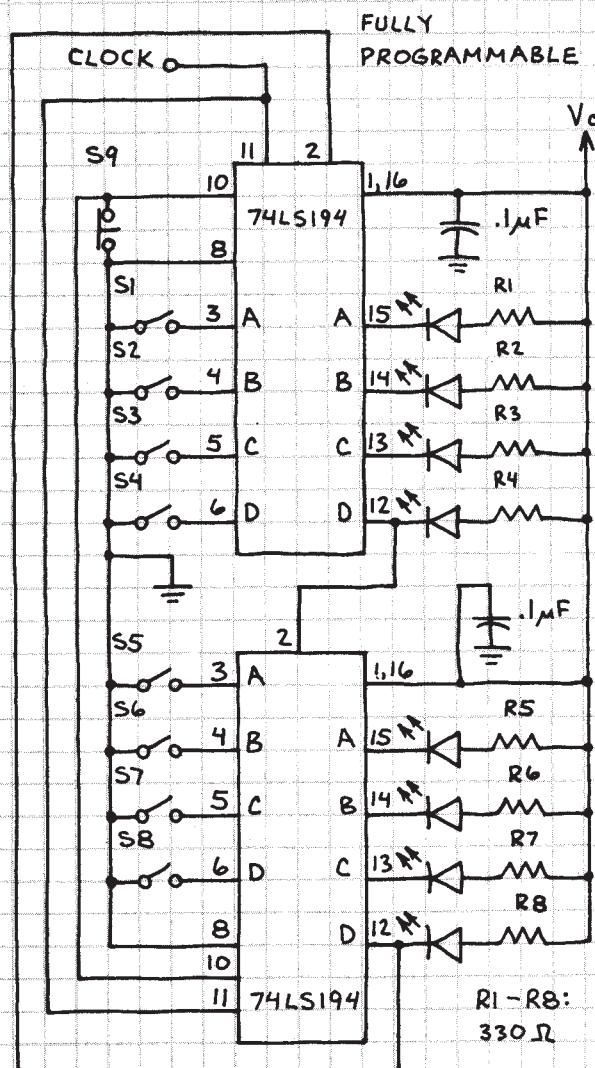

BARGRAPH GENERATOR

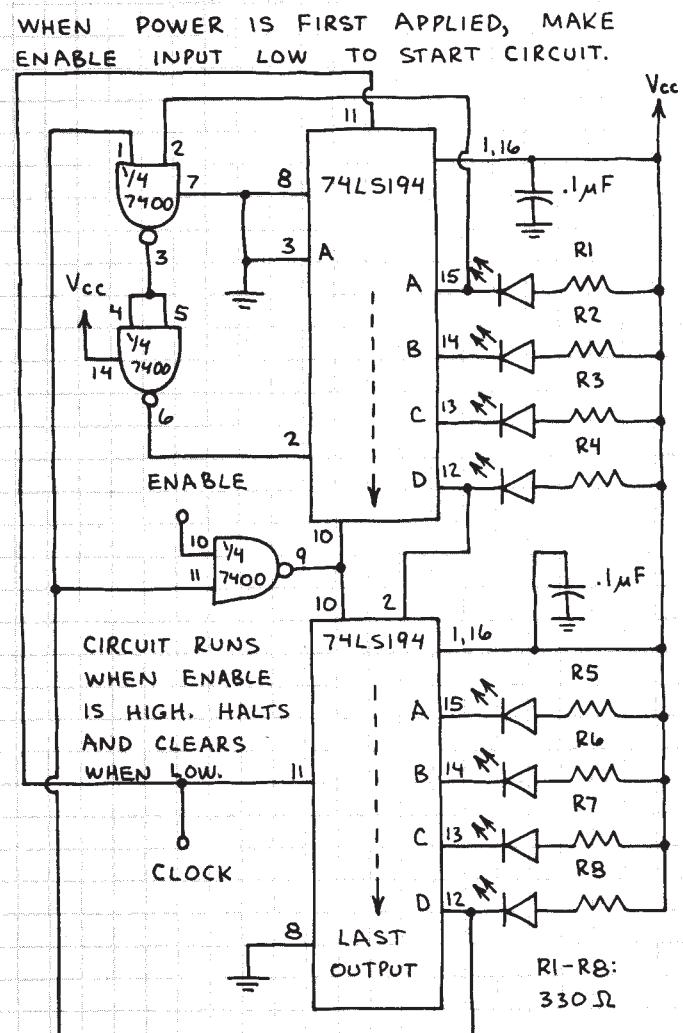


LOAD ANY DESIRED BIT PATTERN INTO SI-S8 (OPEN = HIGH AND CLOSED = LOW). PRESS S9 (NORMALLY CLOSED) TO LOAD. DATA WILL MOVE RIGHT ONE OUTPUT PER CLOCK PULSE. LEDS ARE OPTIONAL.

OUTPUTS GO LOW AND STAY LOW ONE AT A TIME FROM LEFT TO RIGHT ($A \rightarrow D$) IN SEQUENCE WITH CLOCK. WHEN FINAL OUTPUT GOES LOW, ALL OUTPUTS BUT THE FIRST GO HIGH AND RECYCLE.


BCD (DECADE) COUNTER

7490 / 74LS90

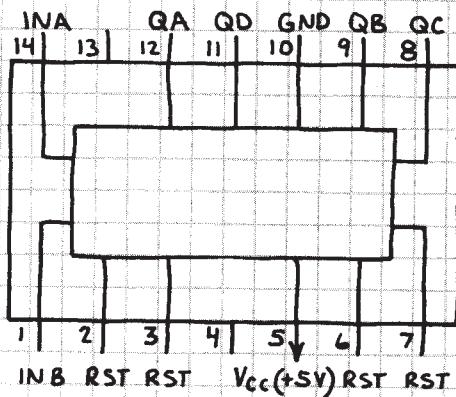
ONE OF THE MOST POPULAR DECADE COUNTERS. EASILY USED FOR DIVIDE-BY-N COUNTERS. LESS EXPENSIVE THAN MORE SOPHISTICATED COUNTERS. RST INDICATES RESET PINS. THIS CHIP IS USUALLY USED IN DECIMAL COUNTING UNITS, BUT CIRCUITS ON THIS PAGE SHOW MANY OTHER POSSIBILITIES.




DIVIDE-BY-5 COUNTER

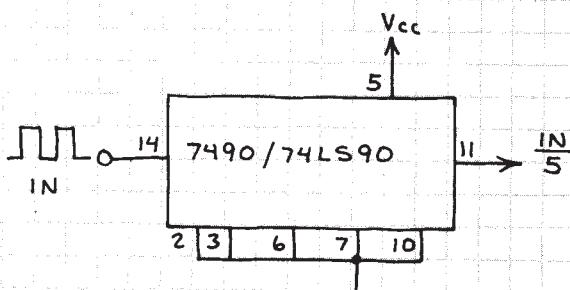


DIVIDE-BY-8 COUNTER

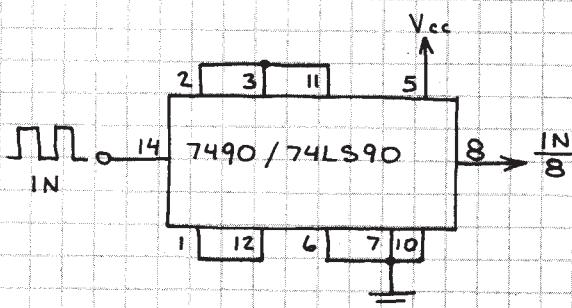


DIVIDE-BY-6 COUNTER

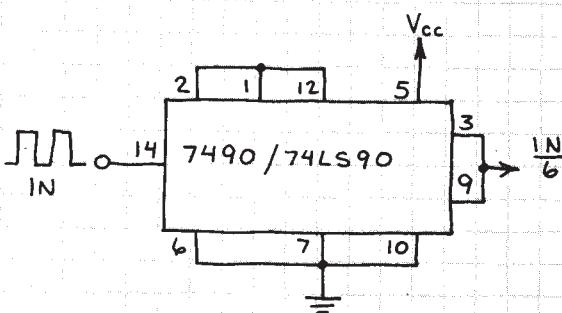


DIVIDE-BY-9 COUNTER

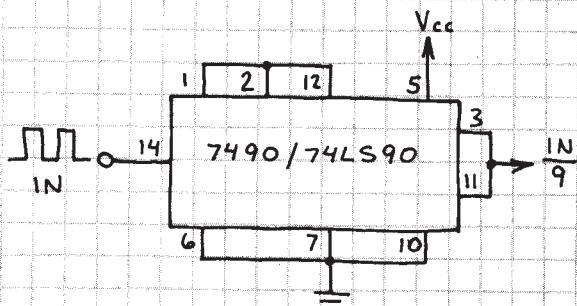

DIVIDE-BY-7 COUNTER

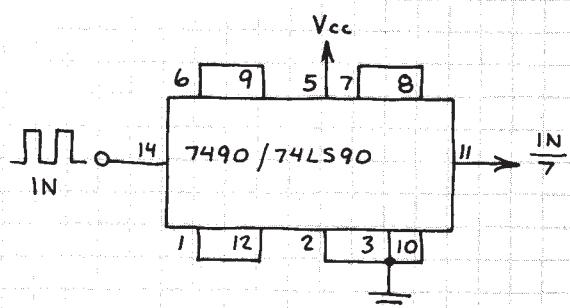


DIVIDE-BY-10 COUNTER

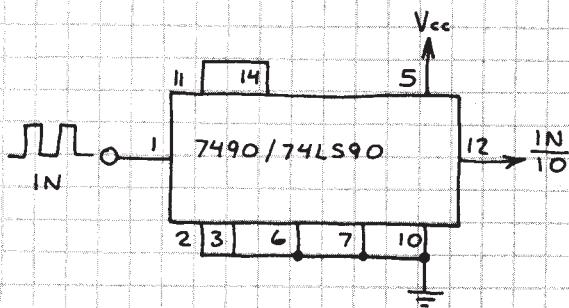


DIVIDE-BY-12 BINARY COUNTER

7492 / 74LS92

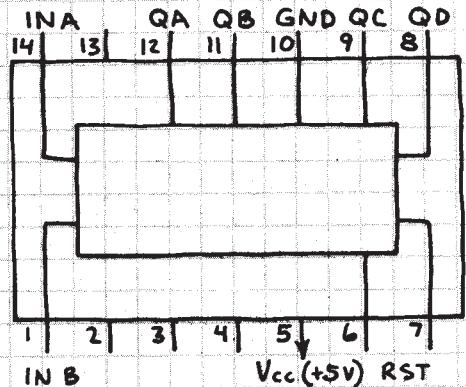
OFTEN USED TO DIVIDE CONDITIONED
60 Hz PULSES FROM AC POWER
LINE INTO 10 Hz PULSES. OTHER
DIVIDER APPLICATIONS ALSO. RST
INDICATES RESET PINS.




DIVIDE-BY-7 COUNTER

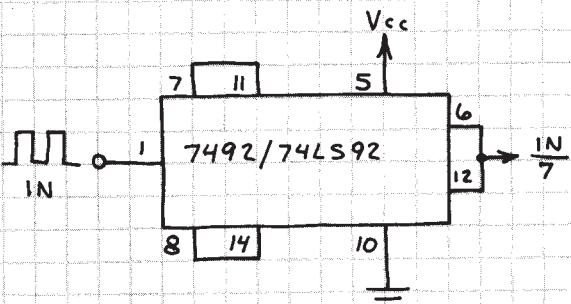


DIVIDE-BY-12 COUNTER

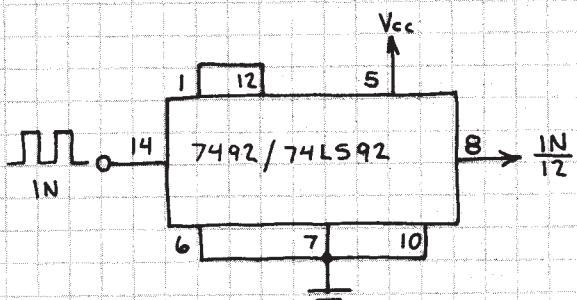



DIVIDE-BY-9 COUNTER

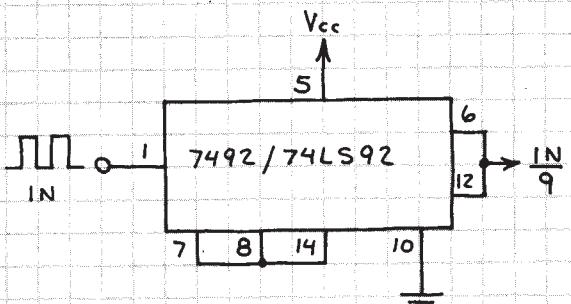

10-HZ PULSE SOURCE

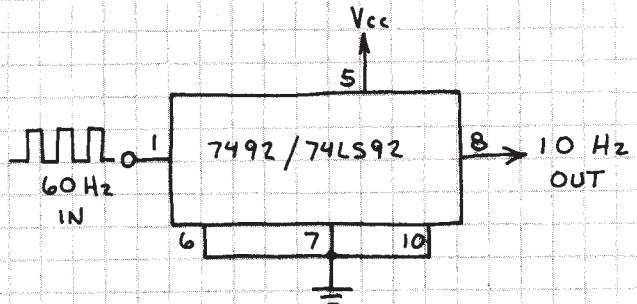

DIVIDE-BY-120 COUNTER

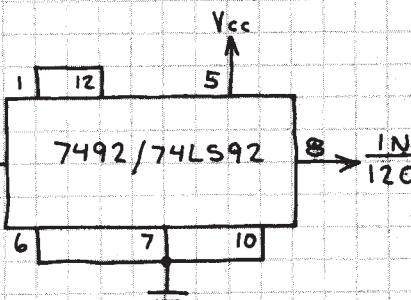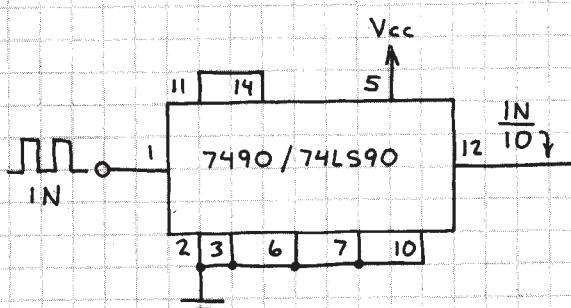


THIS METHOD OF
CASCAADING COUNTERS
CAN BE USED TO
CREATE ANY
DIVIDE-BY-N
COUNTER.


4-BIT (BINARY) COUNTER

7493 / 74LS93

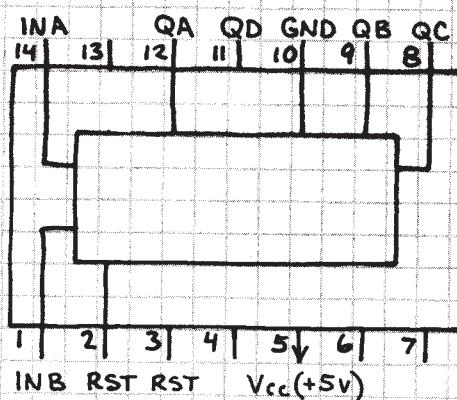
EASY TO USE 4-BIT BINARY COUNTER. LESS EXPENSIVE THAN MORE SOPHISTICATED COUNTERS. RST INDICATES RESET PINS. NOTE UNUSUAL LOCATION OF POWER SUPPLY PINS.




DIVIDE-BY-10 COUNTER

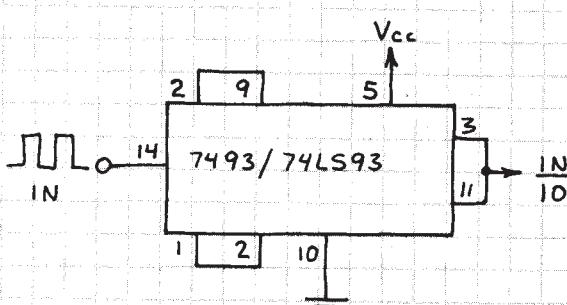


DIVIDE-BY-12 COUNTER

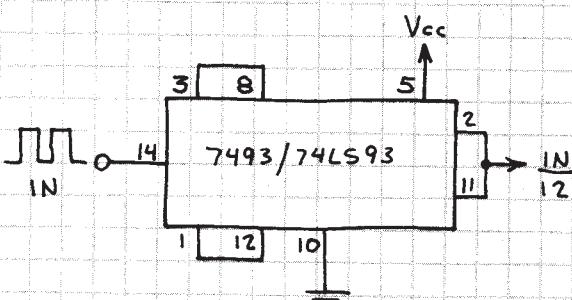


DIVIDE-BY-11 COUNTER

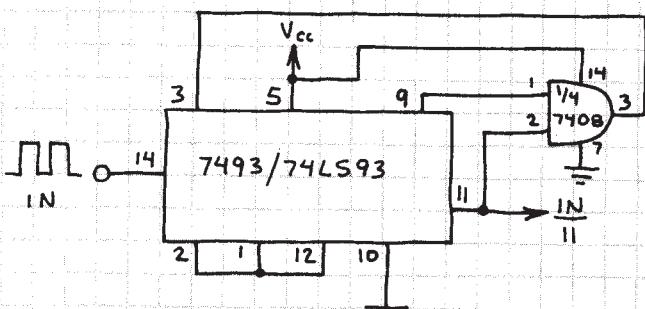

DIVIDE-BY-16 COUNTER

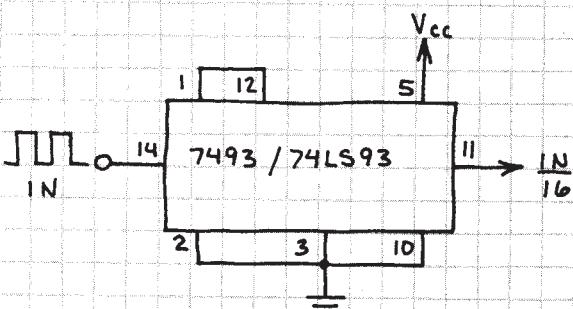

4-BIT BINARY COUNTER

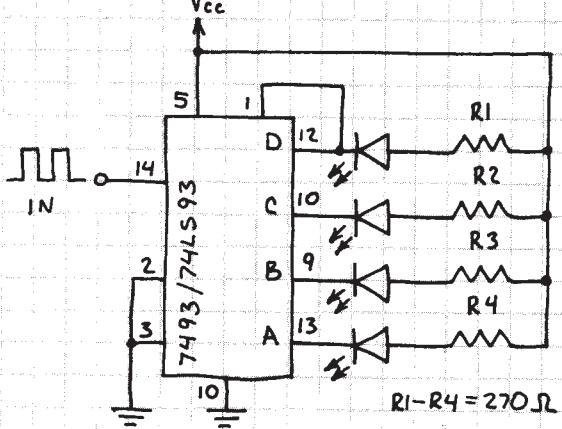

COUNTS FROM 0-15 IN BINARY AND RECYCLES. GLOWING LED = L (0); OFF LED = H (1). 555 TIMER IC MAKES GOOD INPUT CLOCK.


TRUTH TABLE

DCBA	DCBA
LLL L	H L L L
LL L H	H L L H
L L H L	H L H L
L L H H	H L H H
L H L L	H H L L
L H L H	H H L H
L H H L	H H H L
L H H H	H H H H


4-BIT UP COUNTER

74LS161

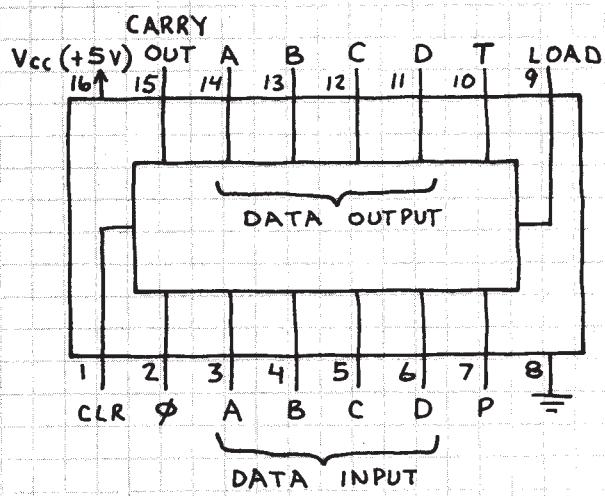GENERAL PURPOSE BINARY COUNTER WITH PROGRAMMABLE INPUTS.
 COUNTER ACCEPTS DATA AT INPUTS WHEN LOAD INPUT GOES LOW.
 A LOW AT THE CLEAR INPUT RESETS THE COUNTER TO LLLL
 UPON THE NEXT CLOCK PULSE.
 P AND T ARE COUNT ENABLE INPUTS. BOTH P AND T MUST BE HIGH TO COUNT. THESE ENABLE INPUTS ARE NOT AVAILABLE WITH THE OTHERWISE MORE ADVANCED 74LS193.




8-BIT COUNTER

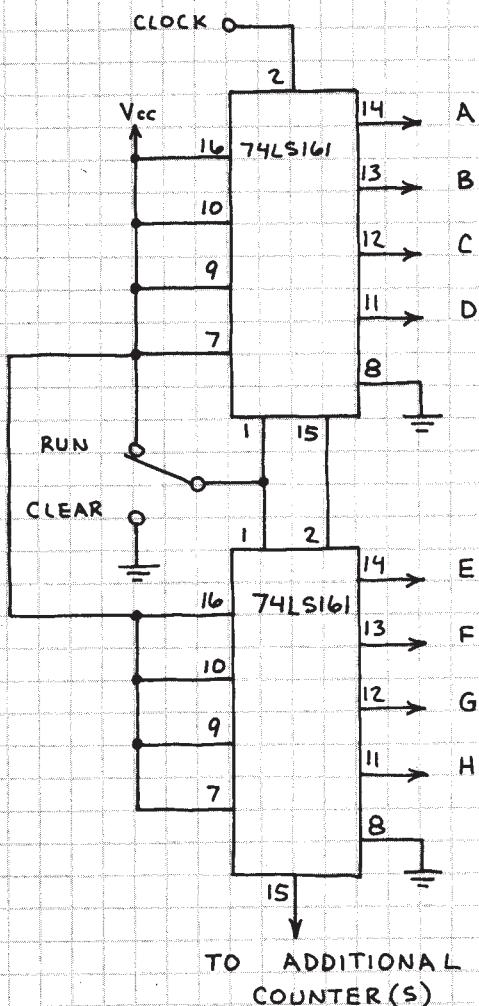

OUTPUT A IS LOWEST ORDER BIT.

RAMP SYNTHESIZER

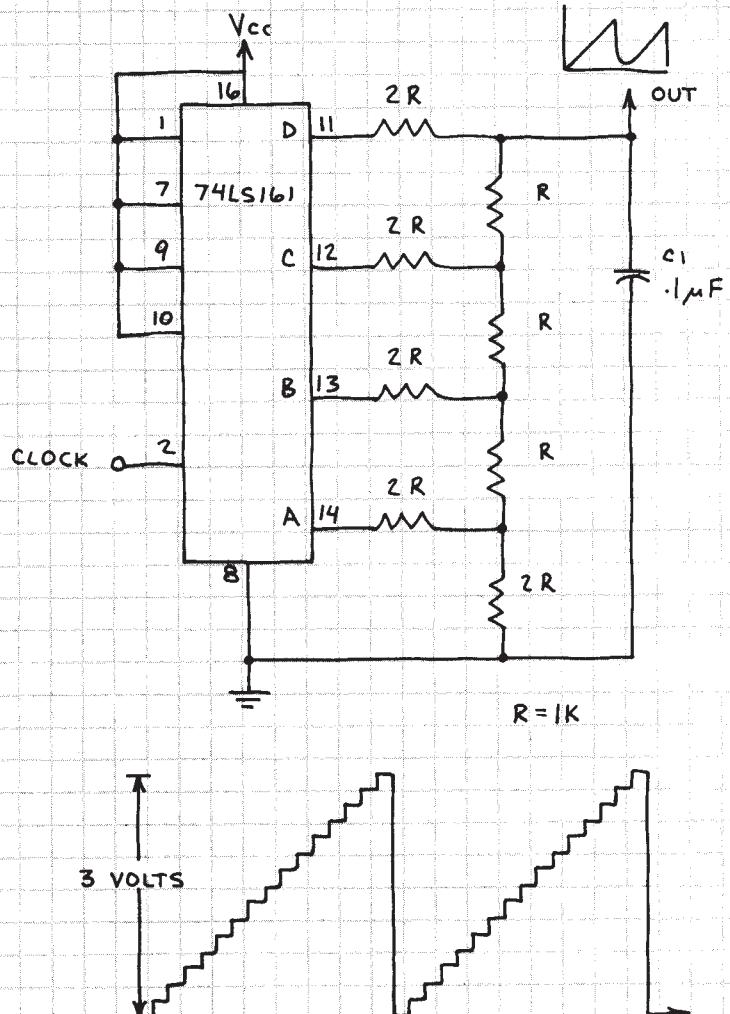


REMOVE C1 TO OBTAIN THIS STAIRCASE.
 FREQUENCY OF RAMP AND STAIRCASE IS 1/16 CLOCK FREQUENCY.


BCD UP-DOWN COUNTER

74192 / 74LS192

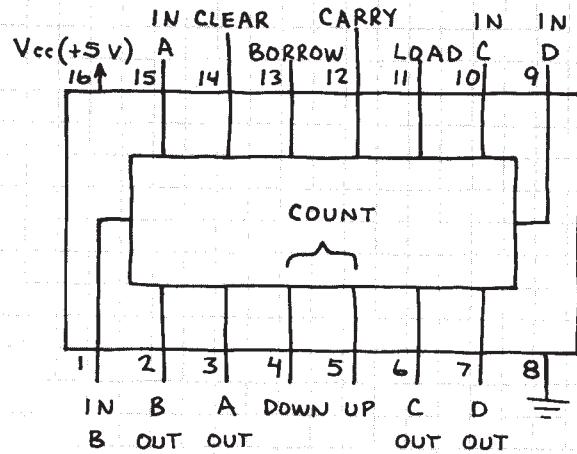
FULLY PROGRAMMABLE BCD COUNTER.
OPERATION IS IDENTICAL TO 74193 /
74LS193 EXCEPT COUNT IS 10-STEP
BCD (LLLL-HLLH) INSTEAD OF
16-STEP BINARY. MANY APPLICATIONS
FOR 74192 / 74LS192 AND 74193 / 74LS193
ARE INTERCHANGEABLE.




CASCADED COUNTERS

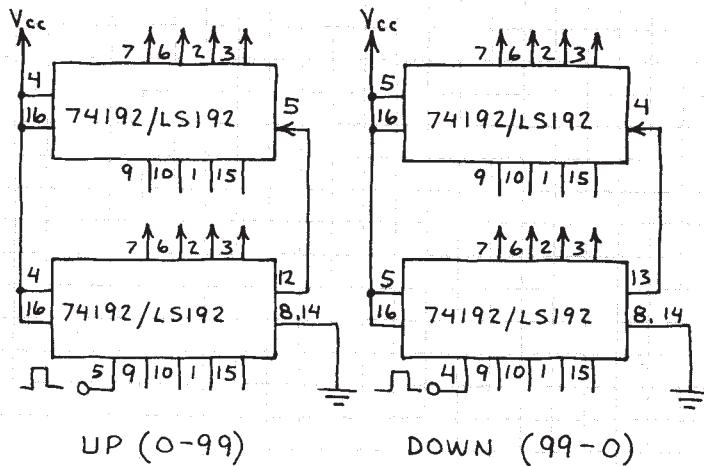

SINGLE UP-DOWN INPUT

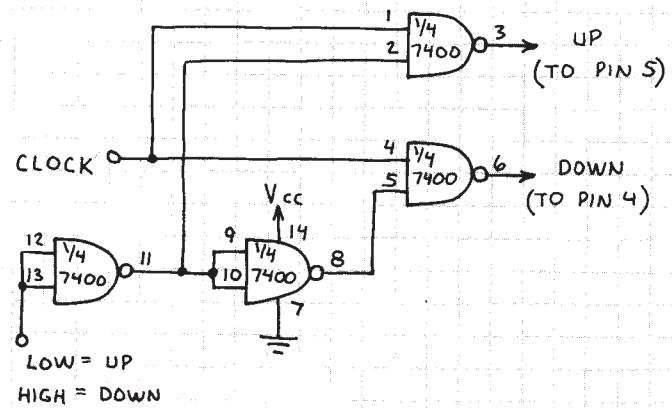

PROGRAMMABLE COUNT DOWN TIMER

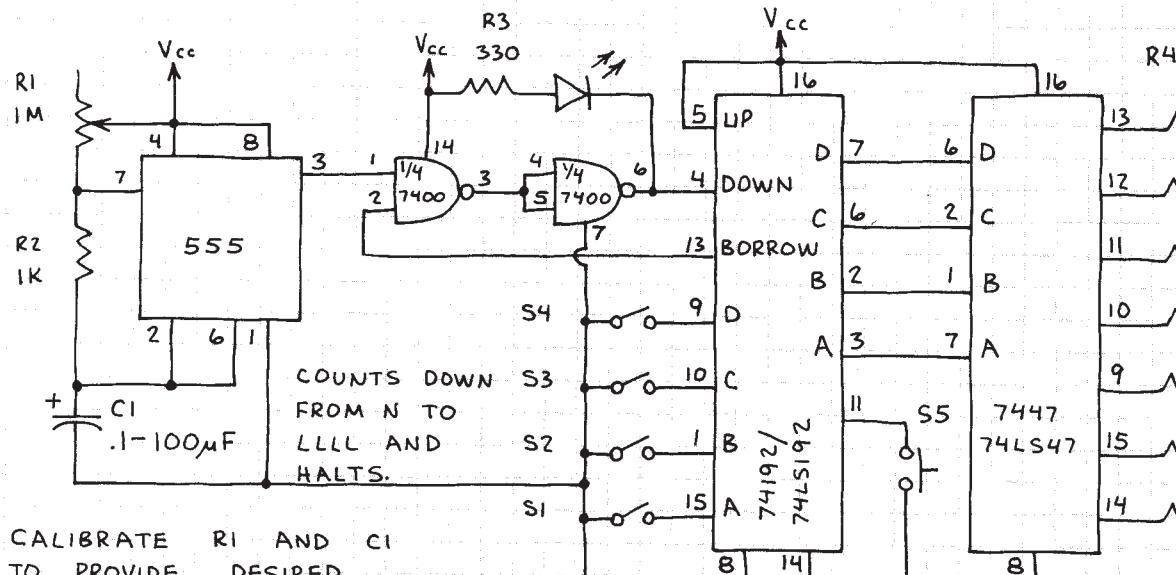


CALIBRATE RI AND CI
TO PROVIDE DESIRED
NUMBER OF CLOCK PULSES

PER MINUTE. SET DESIRED N INTO S1-S4 (CLOSED
SWITCH = LOW AND OPEN SWITCH = HIGH). PRESS S5 TO
LOAD N AND START (OR RESET) COUNT. LED GLOWS AT HALT.


4-BIT UP-DOWN COUNTER

74193/74LS193

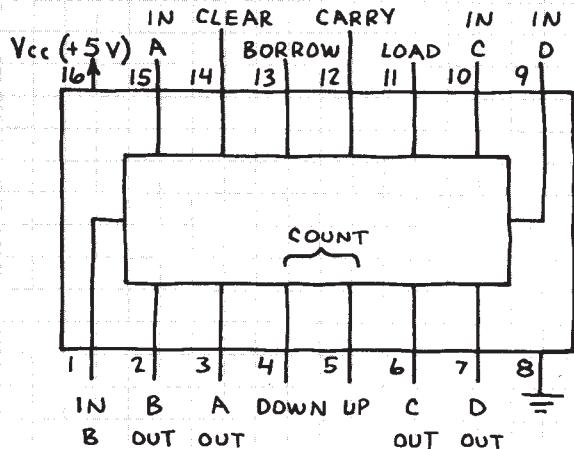VERY VERSATILE 4-BIT COUNTER WITH UP-DOWN CAPABILITY. ANY 4-BIT NUMBER AT THE DCBA INPUTS IS LOADED INTO THE COUNTER WHEN THE LOAD INPUT (PIN 11) IS MADE LOW. THE COUNTER IS CLEARED TO LLLL WHEN THE CLEAR INPUT (PIN 14) IS MADE HIGH. THE BORROW AND CARRY OUTPUTS INDICATE UNDERFLOW OR OVERFLOW BY GOING LOW.




COUNT DOWN FROM N AND RECYCLE

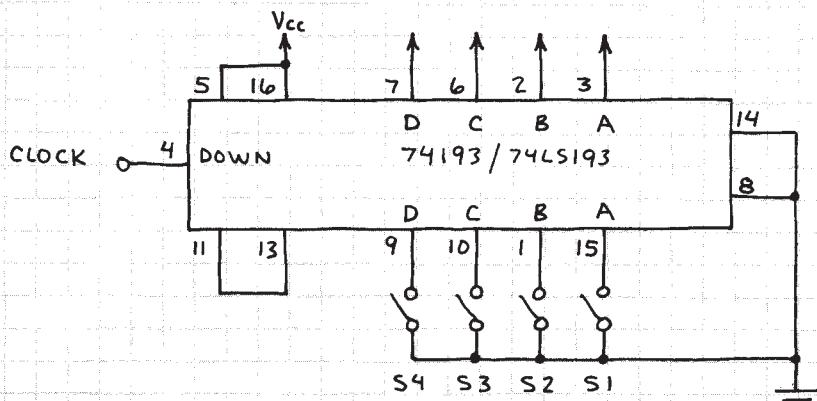


SET DESIRED N INTO S1-S4 (CLOSED SWITCH = LOW AND OPEN SWITCH = HIGH). WHEN COUNT REACHES LLLL AND THEN UNDERFLOWS, THE BORROW PULSE LOADS N AND THE COUNT RECYCLES.

COUNT UP TO N AND HALT

PRESS SI (NORMALLY CLOSED) TO RESET.

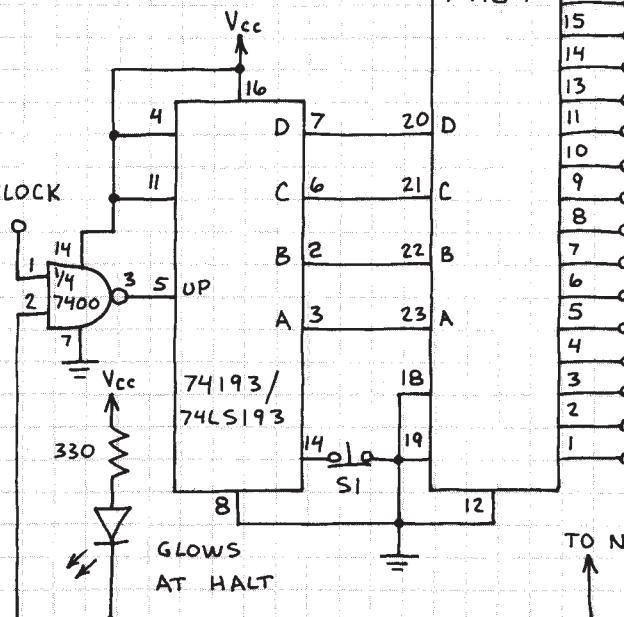


COUNT UP TO N AND RECYCLE

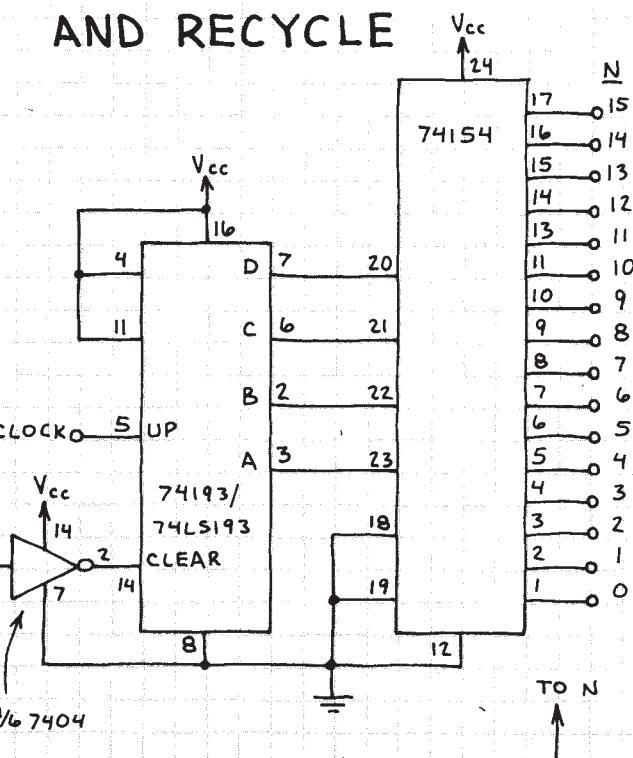


BCD (DECade) COUNTER

74LS196

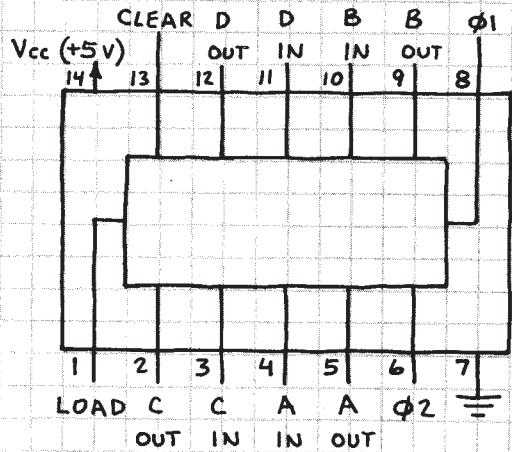
MORE SOPHISTICATED VERSION OF THE POPULAR 7490/74LS90 BCD COUNTER. INCLUDES 4-PRESET INPUTS WHICH PERMIT ANY BCD NUMBER TO BE LOADED WHEN PIN 1 IS MADE LOW. THE COUNTER IS CLEARED TO LLLL WHEN PIN 13 IS MADE LOW. ϕ INDICATES CLOCK INPUT.




DECADE COUNTER

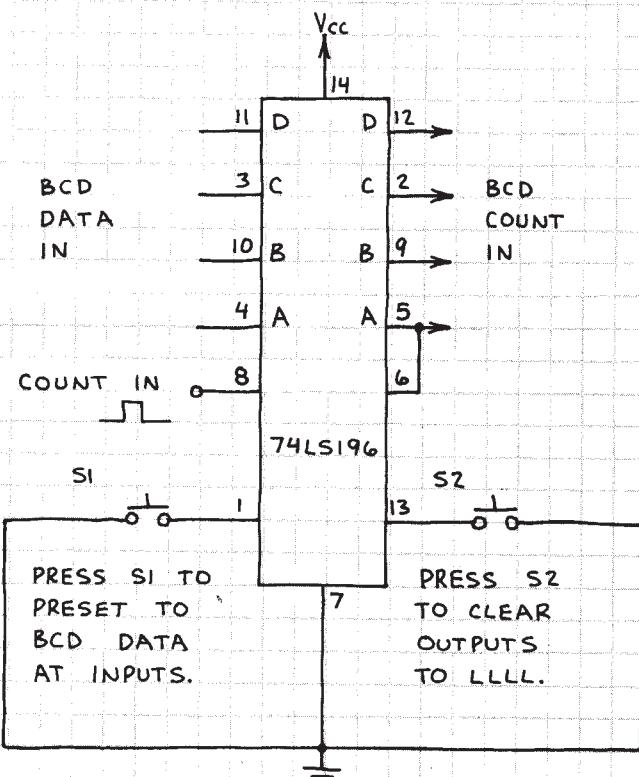


4-BIT LATCH

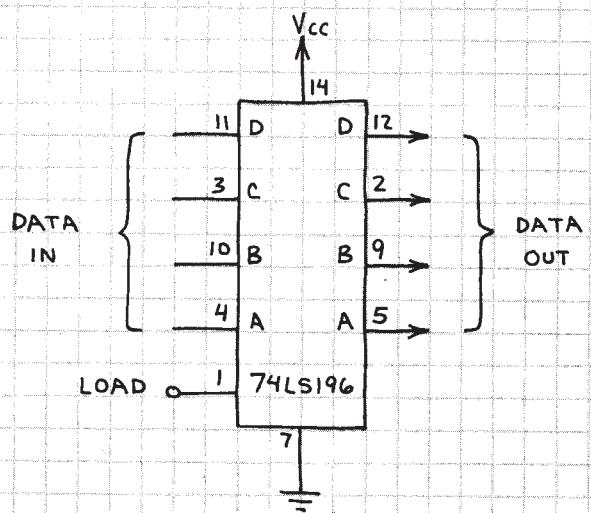

DIVIDE-BY-5 COUNTER

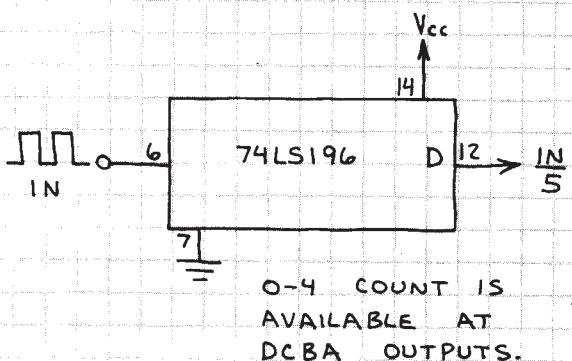

DIVIDE-BY-10 COUNTER

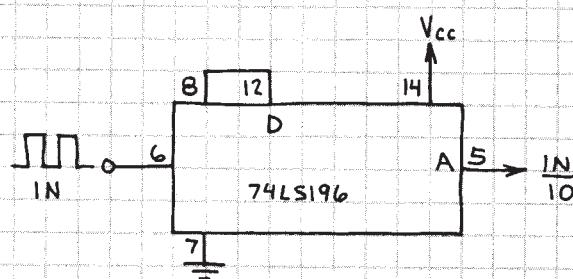


NOTES

NOTES

LINEAR INTEGRATED CIRCUITS

INTRODUCTION

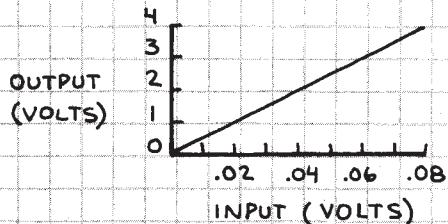THE OUTPUT OF A LINEAR IC IS PROPORTIONAL TO THE SIGNAL AT ITS INPUT. THE CLASSIC LINEAR IC IS THE OPERATIONAL AMPLIFIER. THIS GRAPH SHOWS THE LINEAR INPUT-OUTPUT RELATIONSHIP OF A TYPICAL OP-AMP CIRCUIT:



MANY NON-DIGITAL ICs—INCLUDING OP-AMPS—CAN BE USED IN BOTH LINEAR AND NON-LINEAR MODES. THEY ARE SOMETIMES DESCRIBED AS ANALOG ICs.

LINEAR ICs GENERALLY REQUIRE MORE EXTERNAL COMPONENTS THAN DIGITAL ICs. THIS INCREASES THEIR SUSCEPTABILITY TO EXTERNAL NOISE AND MAKES THEM A LITTLE TRICKIER TO USE. ON THE OTHER HAND, SOME LINEAR ICs CAN DO ESSENTIALLY THE SAME THING AS A NETWORK OF DIGITAL CHIPS.

HERE'S A BRIEF DESCRIPTION OF THE LINEAR CHIPS IN THIS SECTION:

VOLTAGE REGULATORS

PROVIDE A STEADY VOLTAGE, EITHER FIXED OR ADJUSTABLE, THAT IS UNAFFECTED BY CHANGES IN THE SUPPLY VOLTAGE AS LONG AS THE SUPPLY VOLTAGE IS ABOVE THE DESIRED OUTPUT VOLTAGE.

OPERATIONAL AMPLIFIERS

THE IDEAL AMPLIFIER... ALMOST. HIGH INPUT IMPEDANCE AND GAIN. LOW OUTPUT IMPEDANCE. GAIN IS

EASILY CONTROLLED WITH A SINGLE FEEDBACK RESISTOR. FET INPUT OP-AMPS (BIFETS) HAVE A VERY HIGH FREQUENCY RESPONSE. IT'S USUALLY OK TO SUBSTITUTE OP-AMPS IF BOTH ARE NORMALLY POWERED BY A DUAL POLARITY SUPPLY ($\frac{1}{2}$ LF353 FOR 741C, ETC.)... BUT PERFORMANCE WILL IMPROVE OR DECREASE ACCORDING TO THE NEW OP-AMP's SPECIFICATIONS.

COMPARATOR

SAME AS AN OP-AMP WITHOUT A FEEDBACK RESISTOR. ULTRA-HIGH GAIN GIVES A SNAP-LIKE RESPONSE TO AN INPUT VOLTAGE AT ONE INPUT THAT EXCEEDS A REFERENCE VOLTAGE AT THE SECOND INPUT.

TIMERS

USE ALONE OR WITH OTHER ICs FOR NUMEROUS TIMING AND PULSE GENERATION APPLICATIONS.

LED CHIPS

MOST IMPORTANT ARE A FLASHER CHIP AND A DOT-BARGRAPH ANALOG-TO-DIGITAL DISPLAY, VERY EASY TO USE.

OSCILLATORS

A VOLTAGE CONTROLLED OSCILLATOR AND A COMBINED VOLTAGE-TO-FREQUENCY AND FREQUENCY-TO-VOLTAGE CONVERTER. ALSO INCLUDED IS A TONE DECODER THAT CAN BE SET TO INDICATE A SPECIFIC FREQUENCY.

AUDIO AMPLIFIERS

THIS SECTION INCLUDES SEVERAL EASY TO USE POWER AMPLIFIERS THAT ARE IDEAL FOR DO-IT-YOURSELF STEREO, PUBLIC ADDRESS SYSTEMS, INTERCOMS AND OTHER AUDIO APPLICATIONS.

VOLTAGE REGULATORS

7805 (5-VOLTS)

7812 (12-VOLTS)

7815 (15-VOLTS)

FIXED VOLTAGE REGULATORS.

IDEAL FOR STAND-ALONE

POWER SUPPLIES, ON-CARD

REGULATORS, AUTOMOBILE

BATTERY POWERED PROJECTS,

ETC. UP TO 1.5 AMPERES


OUTPUT IF PROPERLY HEAT

SUNK AND SUFFICIENT INPUT

CURRENT AVAILABLE. THERMAL

SHUTDOWN CIRCUIT TURNS OFF

REGULATOR IF HEATSINK TOO SMALL.

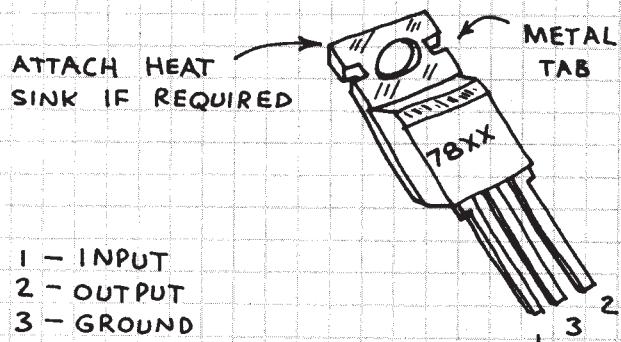


1 - INPUT

2 - OUTPUT

3 - GROUND


5-VOLT LINE POWERED TTL/LS POWER SUPPLY

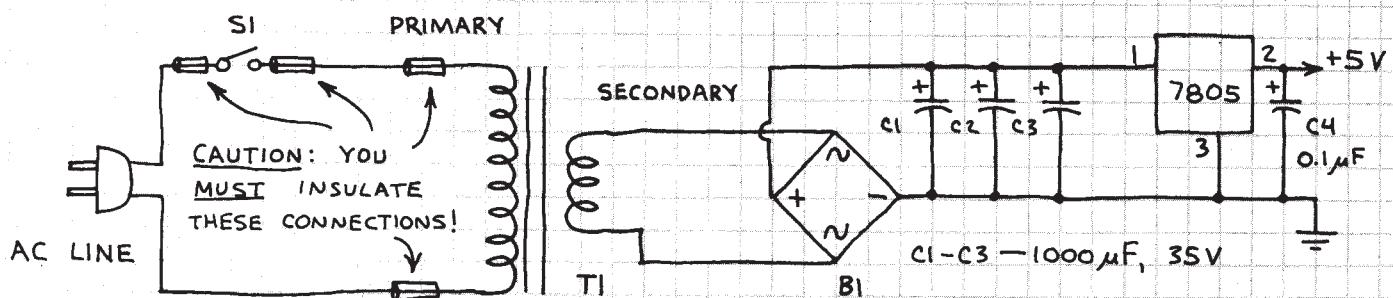

TI - 117-12.6 V, 1.2A OR 3A TRANSFORMER (273-1505 OR 273-1511).

BI - 1A - 4A FULL WAVE BRIDGE RECTIFIER (276-1161, 276-1151 OR 276-1171).
(RADIO SHACK CATALOG NUMBERS IN PARENTHESES.)


VOLTAGE REGULATOR

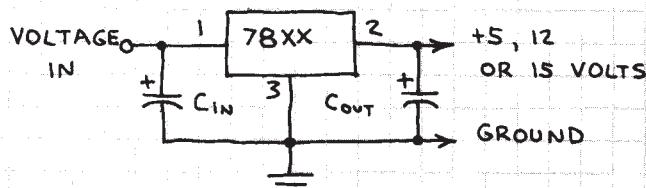

CIN - OPTIONAL; USE 0.33 μF OR SO IF REGULATOR FAR FROM POWER SUPPLY.


COUT - OPTIONAL; USE 0.1 μF OR MORE TO TRAP SPIKES THAT BOTHER LOGIC ICS.

CURRENT REGULATOR

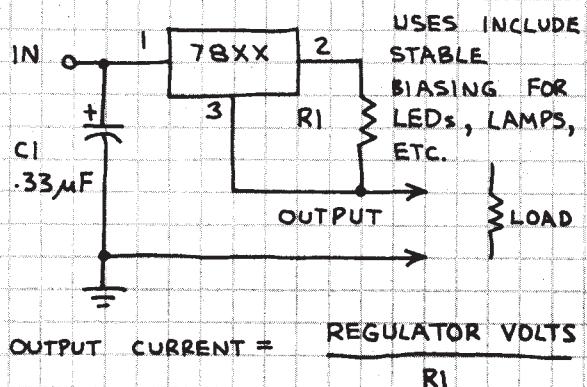


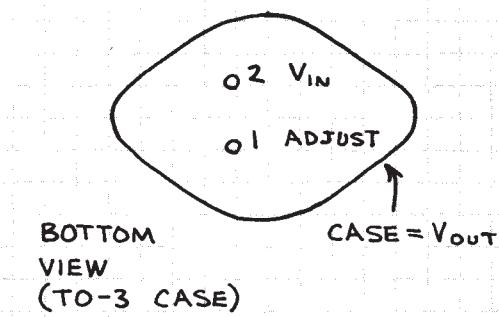1.2-37 VOLT REGULATOR LM317

CAN SUPPLY UP TO 1.5 AMPERES OVER A 1.2-37 VOLT OUTPUT RANGE. NOTE MINIMUM NUMBER OF EXTERNAL COMPONENTS IN BASIC REGULATOR CIRCUIT BELOW. USE HEAT SINK FOR APPLICATIONS REQUIRING FULL POWER OUTPUT. SEE APPROPRIATE DATA BOOK FOR ADDITIONAL INFORMATION:




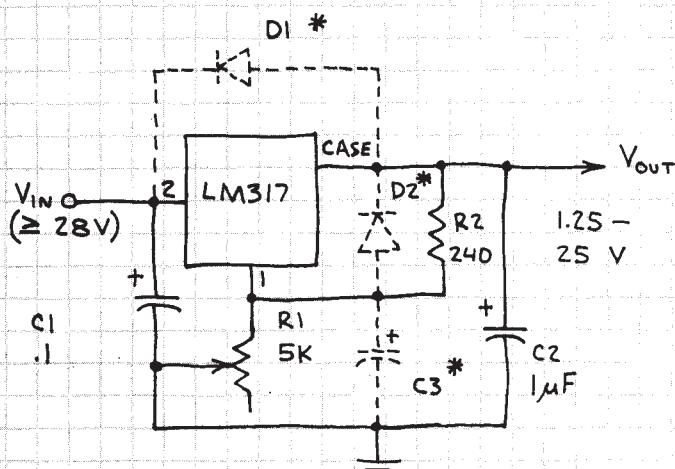1.25-25 VOLT REGULATOR 6-VOLT NICAD CHARGER




V_{IN} SHOULD BE FILTERED. OK TO OMIT C1 IF V_{IN} VERY CLOSE TO LM317.
R1 CONTROLS OUTPUT VOLTAGE.

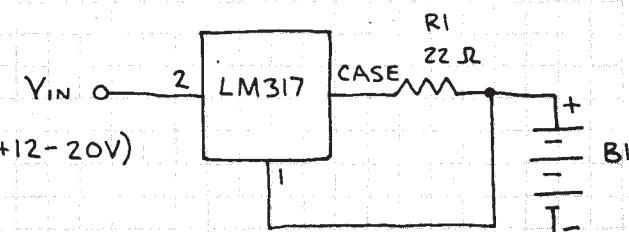* ADD IF OUTPUT $> 25V$ AND C2 $> 25\mu F$.



B1 IS BATTERY OF 4 NICKEL CADMIUM STORAGE CELLS IN SERIES. THIS CIRCUIT CHARGES B1 AT A CURRENT OF 51.2 mA. INCREASE R1 TO REDUCE CURRENT. FOR EXAMPLE, CURRENT IS 43 mA WHEN R1 IS 24 OHMS.


PROGRAMMABLE POWER SUPPLY

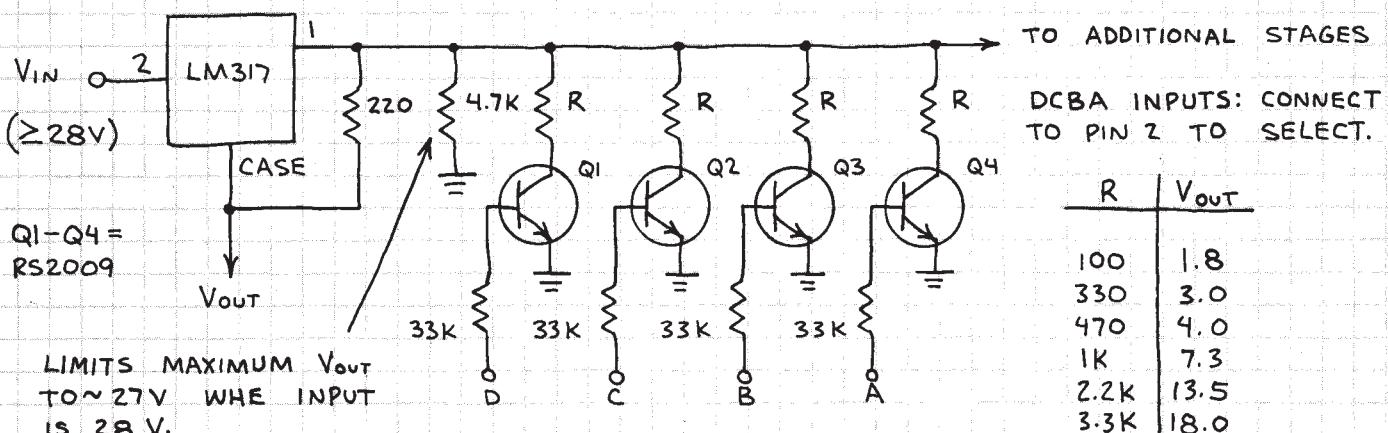

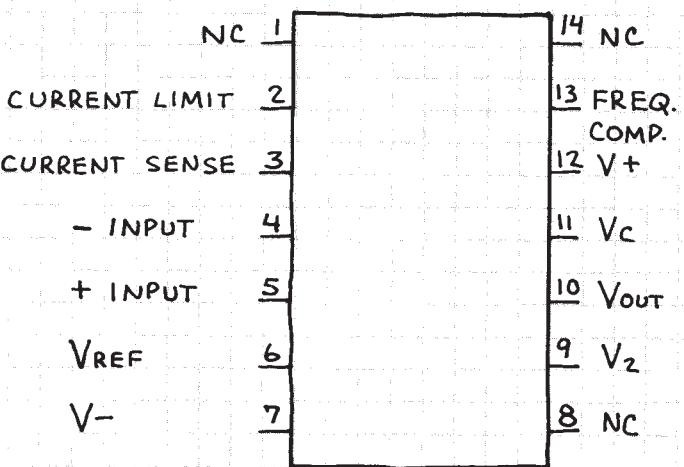
2-37 VOLT REGULATOR

723

VERY VERSATILE SERIES REGULATOR. UP TO 40 VOLTS INPUT AND 2-37 VOLT OUTPUT. MAXIMUM OUTPUT CURRENT OF 150 mA CAN BE EXTENDED TO 10 A BY ADDING EXTERNAL POWER TRANSISTORS. SHOWN BELOW ARE TWO BASIC CIRCUITS. TRY THESE, THEN SEE APPROPRIATE DATA BOOK FOR ADDITIONAL CIRCUITS.



2-7 VOLT REGULATOR

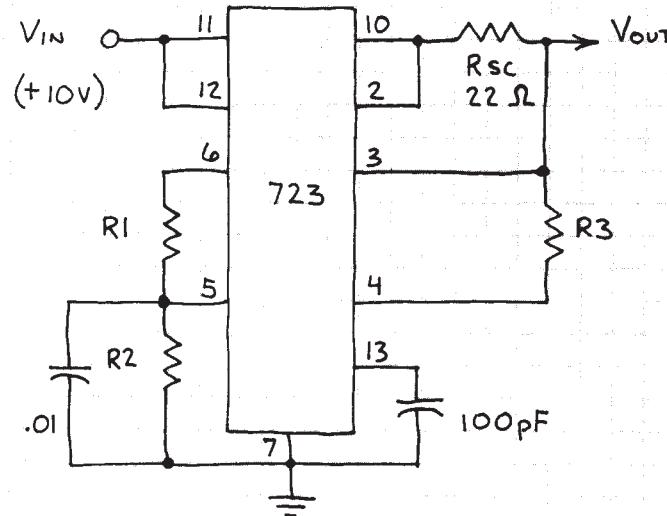

TYPICAL VALUES

Vout	R1	R2	R3
3.0	4.12 K	3.01 K	1.74 K
3.6	3.57 K	3.65 K	1.80K
5.0	2.15 K	4.99 K	1.50K
6.0	1.15 K	6.04 K	966


FOR ANY VOLTAGE BETWEEN 2-7 VOLTS:

$$V_{out} = (V_{ref}^*) \times \left(\frac{R_2}{R_1 + R_2} \right)$$

* $V_{ref} = 6.8 - 7.5$ V (MEASURE AT PIN 6)

$$R_3 = \frac{R_1 \times R_2}{R_1 + R_2}$$

7-37 VOLT REGULATOR

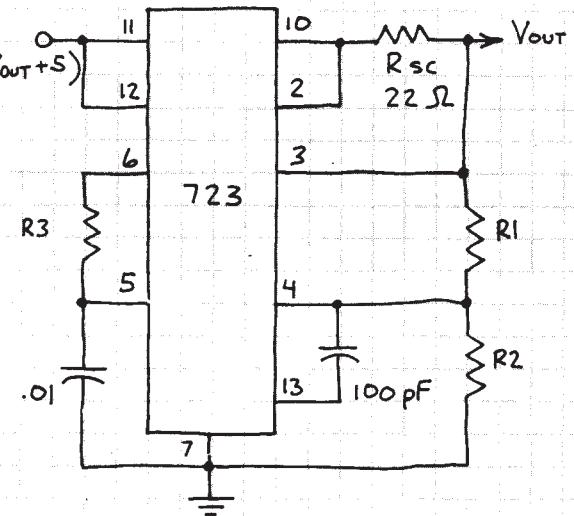

TYPICAL VALUES

Vout	R1	R2	R3
9	1.87 K	7.15 K	.48K
12	4.87 K	7.15 K	2.90K
15	7.87 K	7.15 K	3.75K
28	21.0 K	7.15 K	5.33K

FOR ANY VOLTAGE BETWEEN 7-37 VOLTS:


$$V_{out} = (V_{ref}^*) \times \left(\frac{R_1 + R_2}{R_2} \right)$$

$R_3 = \frac{R_1 \times R_2}{R_1 + R_2}$ (R3, WHICH IS OPTIONAL, GIVES TEMPERATURE STABILITY)



OPERATIONAL AMPLIFIER

741C

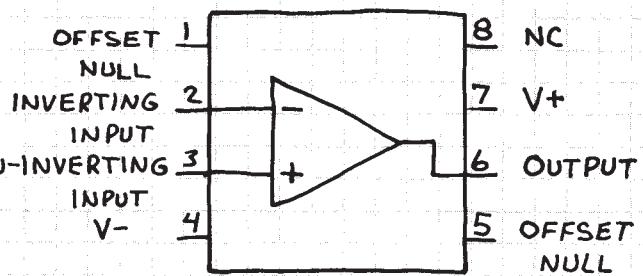
THE MOST POPULAR OP-AMP.
USE FOR ALL GENERAL PURPOSE
APPLICATIONS. (FOR SINGLE
SUPPLY OPERATION AND VERY
HIGH INPUT IMPEDANCE, USE
OTHER OP-AMPS IN THIS NOTEBOOK.)



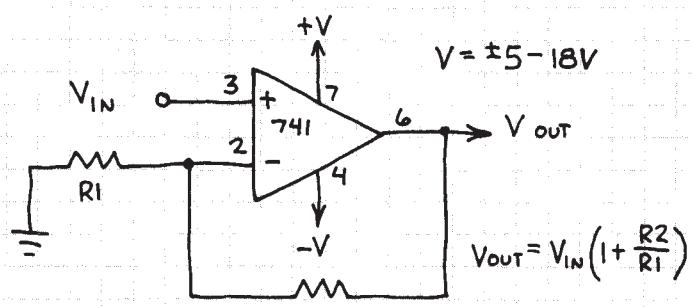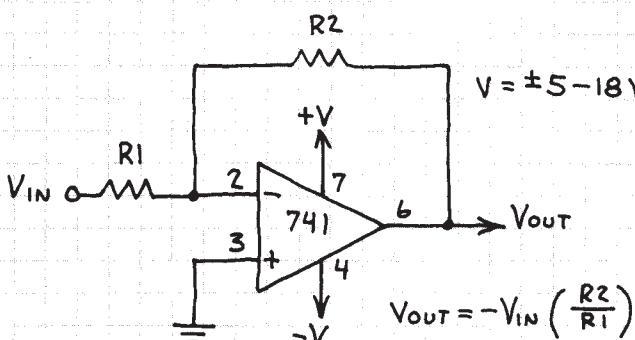
INVERTING AMPLIFIER NON-INVERTING AMPLIFIER



UNITY GAIN FOLLOWER

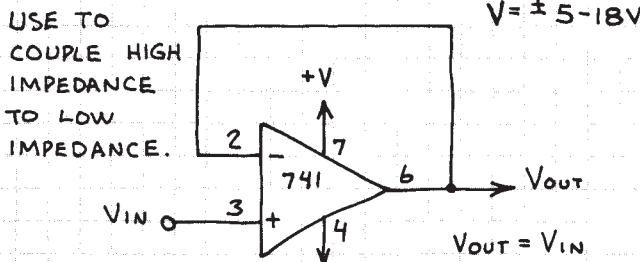


COMPARATOR

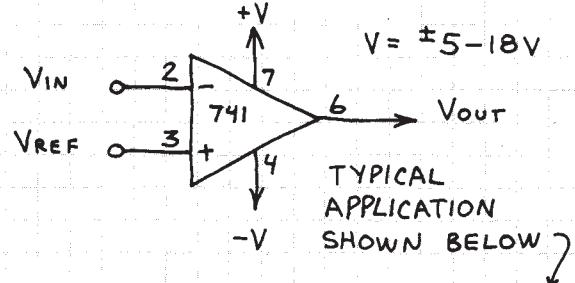


LEVEL DETECTOR

SINGLE POLARITY SUPPLY

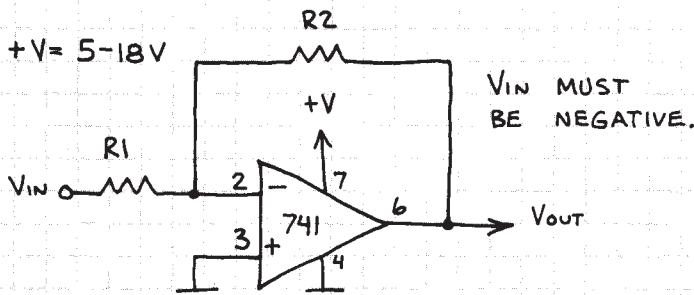

TYPICAL USES:

AMPLIFICATION OF DC VOLTAGE AND PULSES.

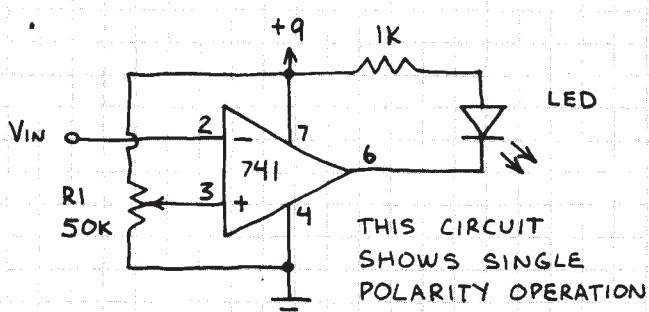


R1 SETS THE VOLTAGE DETECTION THRESHOLD (UP TO +9V). WHEN V_{IN} EXCEEDS THE THRESHOLD (ALSO CALLED THE REFERENCE), THE LED GLOWS.


OPERATIONAL AMPLIFIER (CONTINUED)

741C


BASIC INTEGRATOR

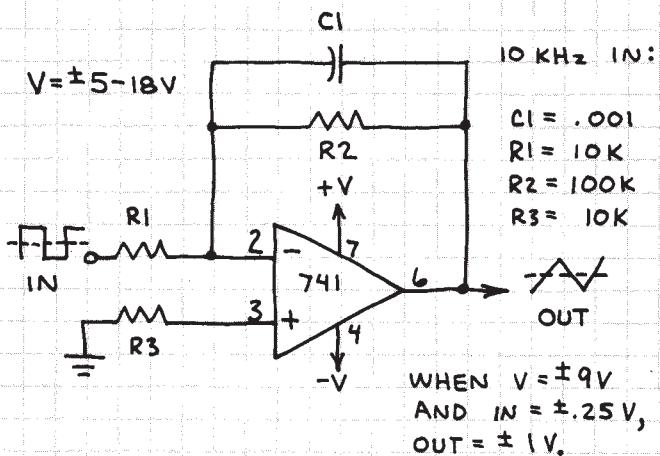


BASIC DIFFERENTIATOR

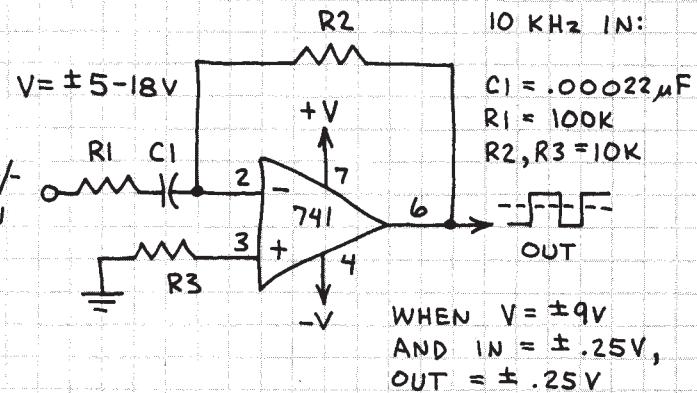


CLIPPING AMPLIFIER

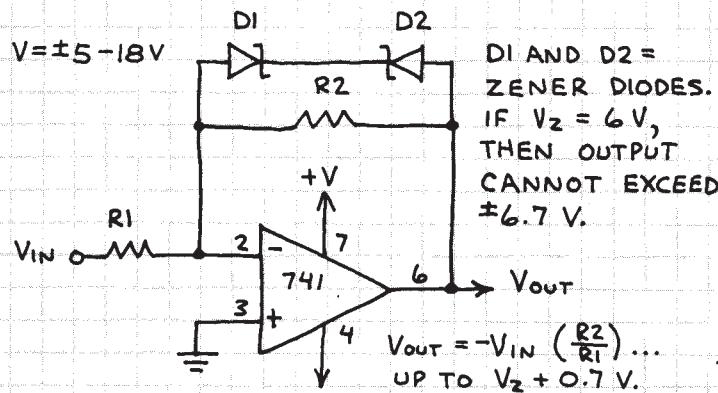

BRIDGE AMPLIFIER

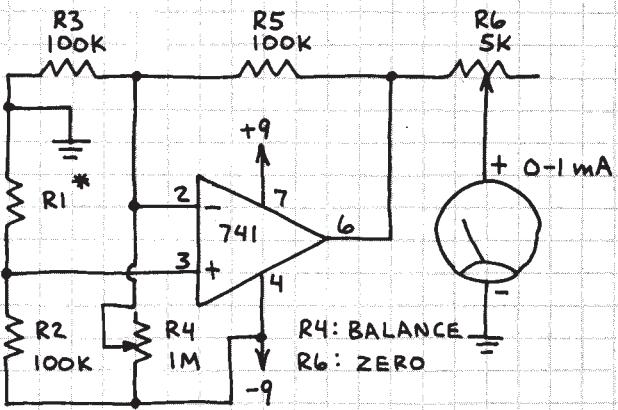


SUMMING AMPLIFIER

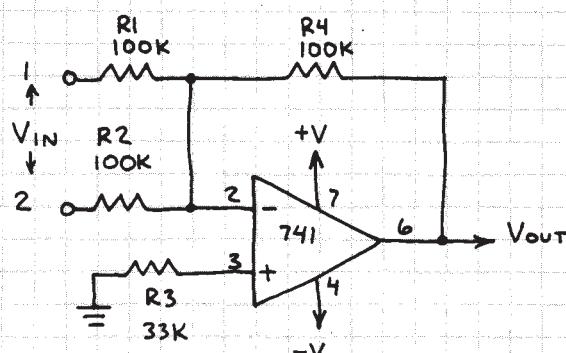

NOTE: V_{OUT} CANNOT EXCEED $\pm V$.


DIFFERENCE AMPLIFIER

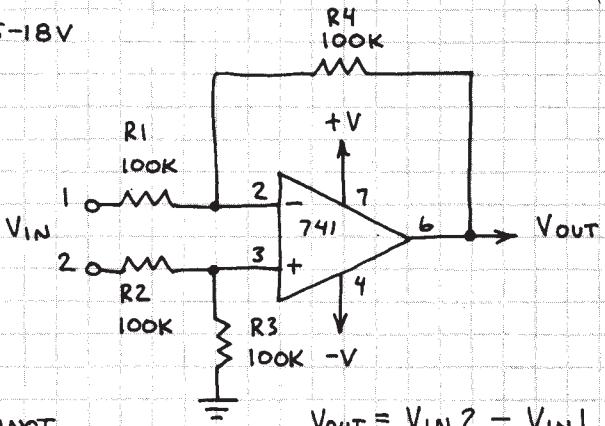

OPERATIONAL AMPLIFIER (CONTINUED)


741C

LIGHT WAVE RECEIVER 60-Hz NOTCH FILTER


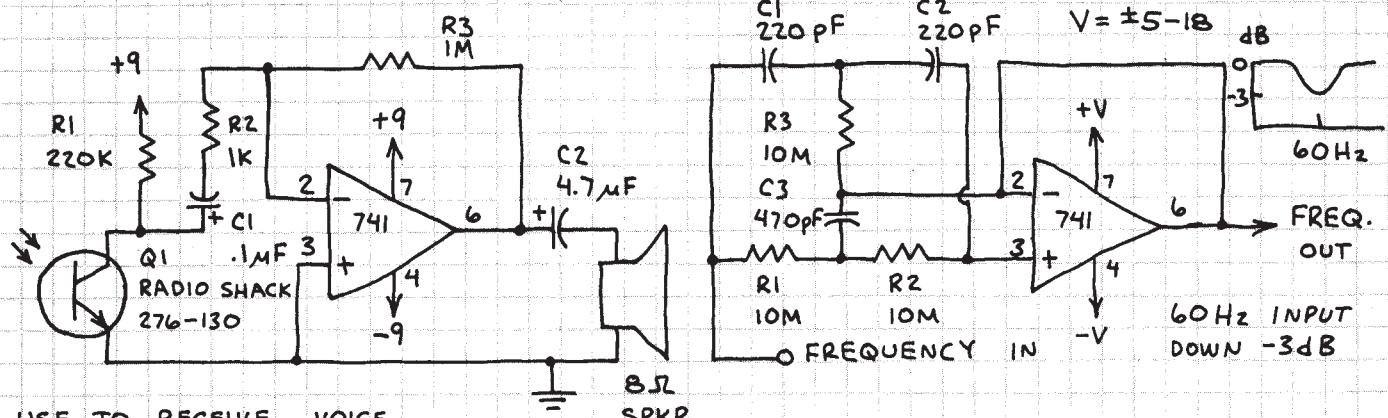


USE TO RECEIVE VOICE MODULATED LIGHT WAVES. OK TO USE SINGLE POLARITY POWER SUPPLY FOR NON-VOICE RECEPTION.

4-BIT D/A CONVERTER

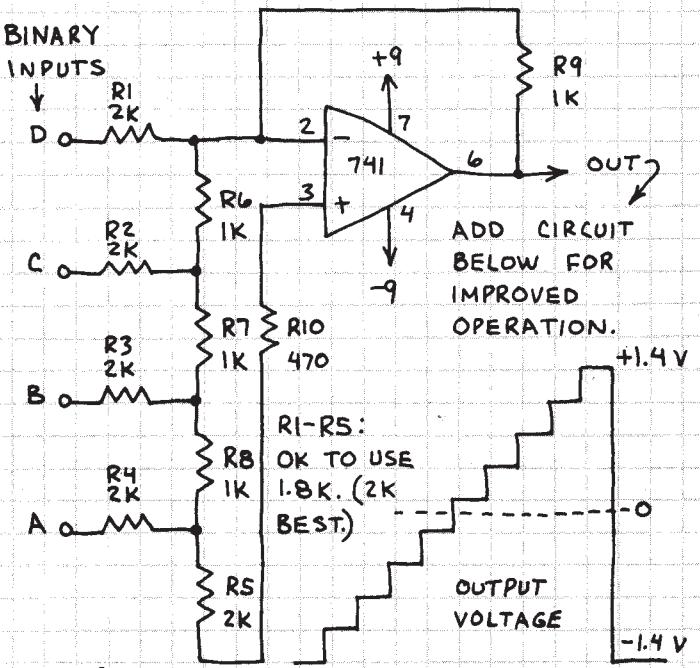


LOW PASS ACTIVE FILTER

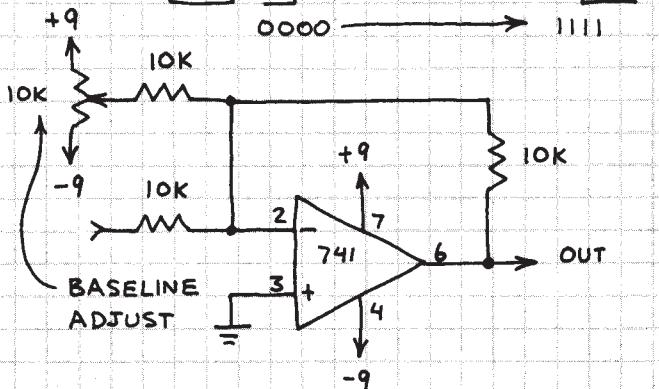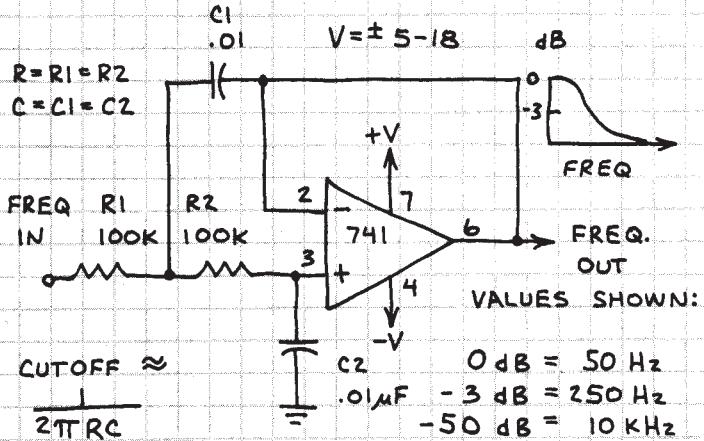


OPERATIONAL AMPLIFIER (CONTINUED)

741C


OPTICAL POWER METER

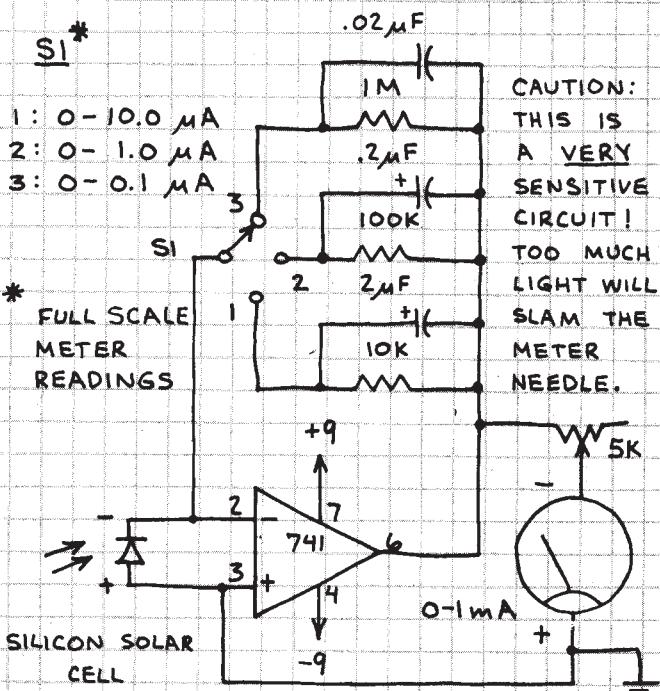


BARGRAPH LIGHT METER

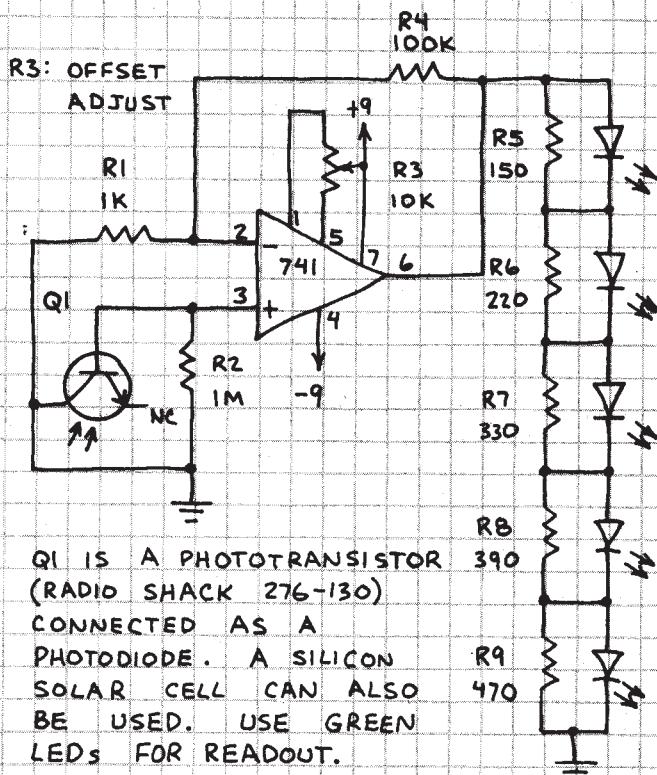

ELECTRONIC BELL

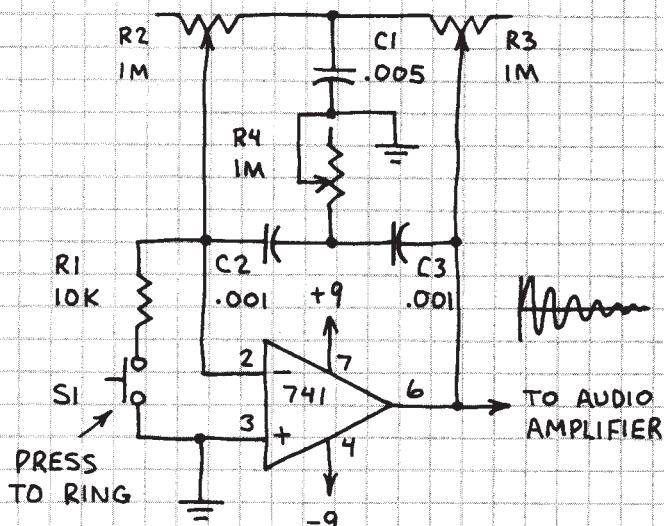


AUDIBLE LIGHT SENSOR

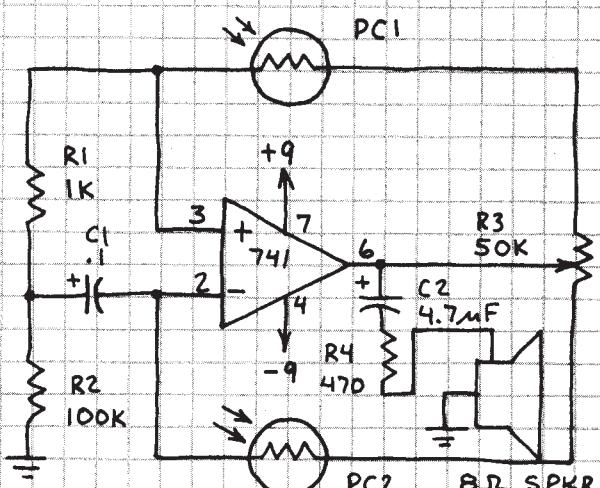


DUAL OPERATIONAL AMPLIFIER

1458

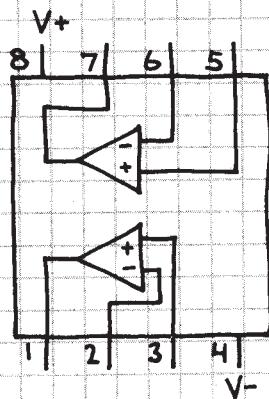TWO 741C OP-AMPS IN A SINGLE 8-PIN MINI-DIP. TRY TO USE THIS CHIP FOR CIRCUITS THAT REQUIRE TWO OR MORE 741'S. YOU'LL SAVE TIME, SPACE AND MONEY.




PEAK DETECTOR

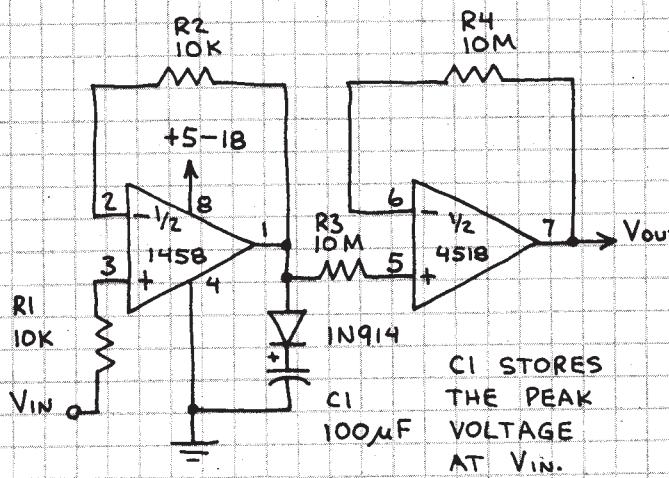

C_1 STORES THE PEAK VOLTAGE AT V_{in} .


APPLICATIONS INCLUDE USE AS ANALOG "MEMORY" THAT STORES PEAK AMPLITUDE OF A FLUCTUATING VOLTAGE.

PULSE GENERATOR

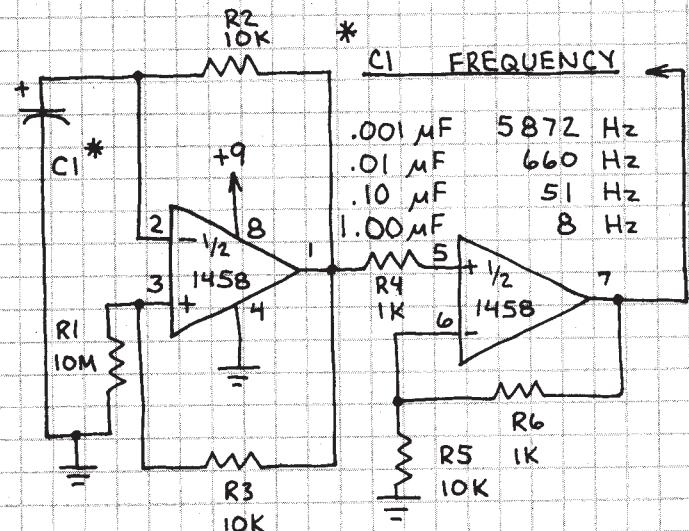

PULSES ARE DC. AMPLITUDE WHEN $C_1 = 0.1 \mu F$ IS 5 VOLTS.


FUNCTION GENERATOR

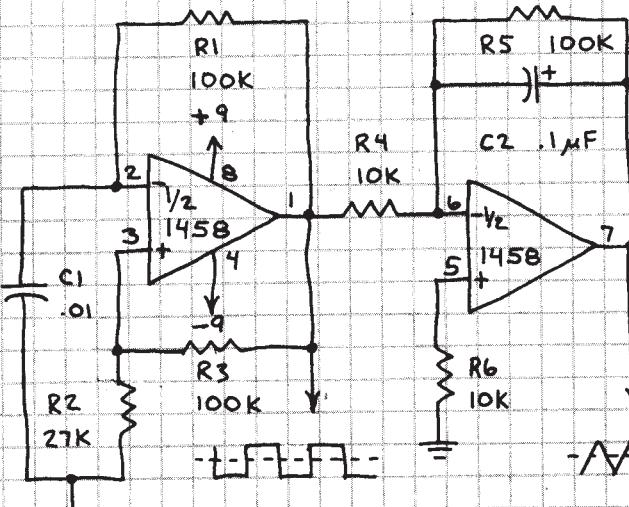

SQUARE: $\pm 7.5V$

TRIANGLE: $\pm 2V$


FREQUENCY = 1 KHz

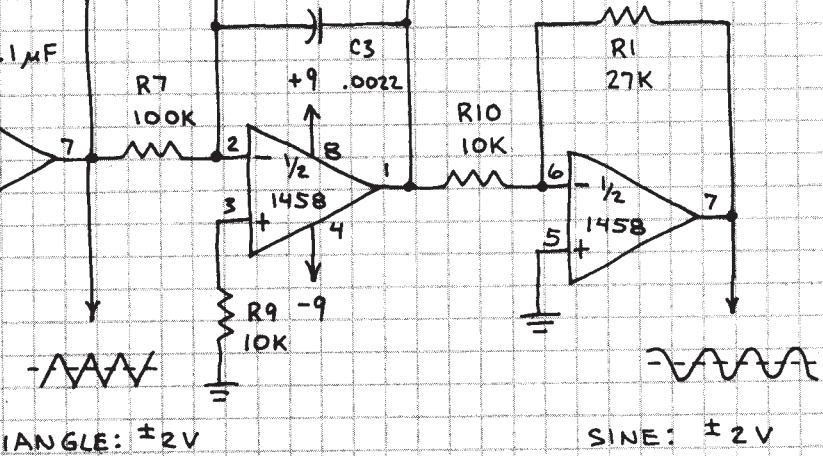


SINE: $\pm 2V$

DUAL OPERATIONAL AMPLIFIER LF353N (JFET INPUT)

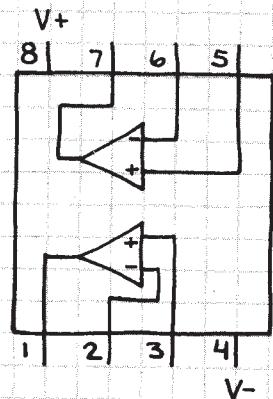
HIGH IMPEDANCE (10^{12} OM) JUNCTION FET INPUTS. OUTPUT SHORT CIRCUIT PROTECTION. HIGH SLEW RATE (13 V/MSEC), LOW NOISE OPERATION. AMPLIFIERS ARE SIMILAR TO THOSE IN THE TL084C. NOTE THAT PIN CONNECTIONS ARE THE SAME AS 1458. THIS OP-AMP, HOWEVER, OFFERS MUCH BETTER PERFORMANCE.




SAMPLE AND HOLD

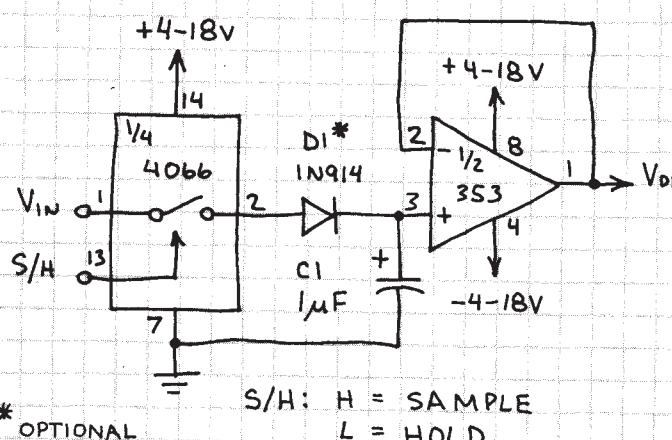

PEAK DETECTOR

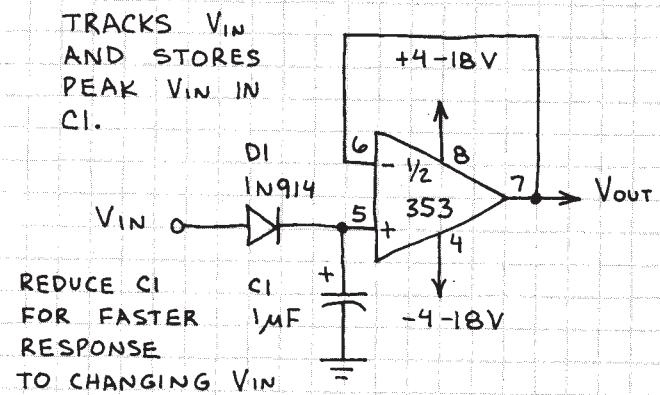


AUDIO MIXER

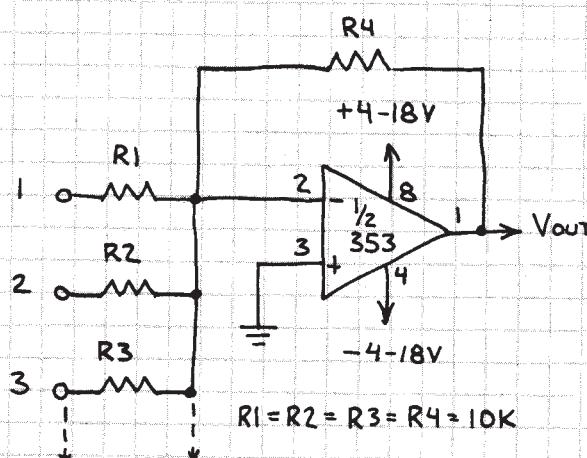


CONNECT OUTPUTS OF PREAMPLIFIERS TO INPUTS 1-3. OK TO ADD MORE CHANNELS. WORKS WELL WITH TL084 MICROPHONE PREAMPLIFIERS.

PROGRAMMABLE GAIN OP-AMP

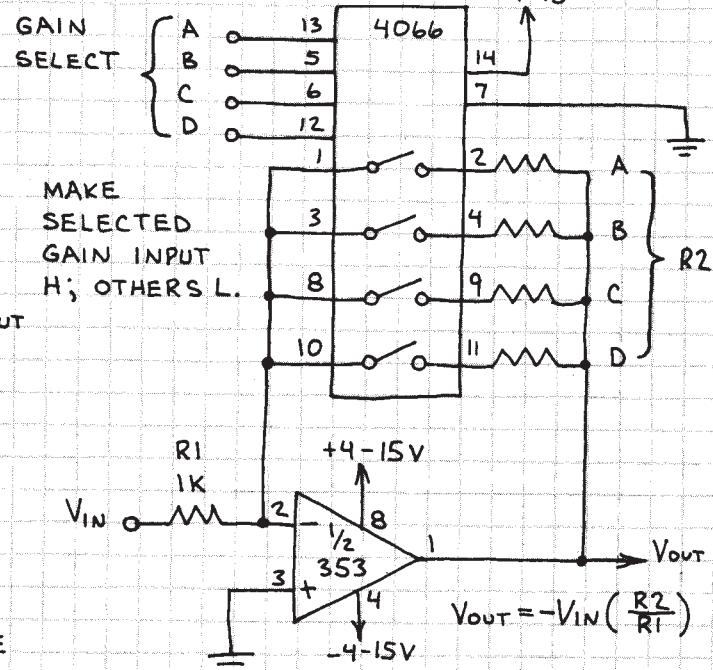


QUAD OPERATIONAL AMPLIFIER TL084C (JFET INPUT)

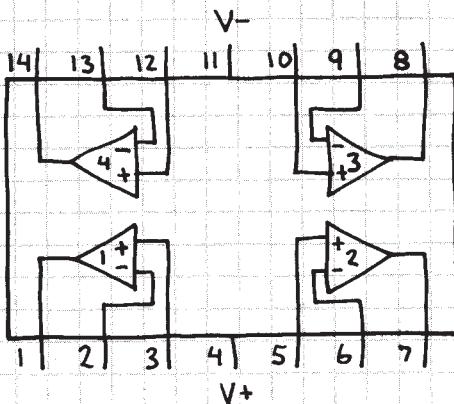HIGH IMPEDANCE (10^{12} OHMS) JUNCTION FET INPUTS. OUTPUT SHORT CIRCUIT PROTECTION. HIGH SLEW RATE (12 V/MSEC) PLUS LOW NOISE OPERATION. PERFORMANCE SIMILAR TO LF353 N. NOTE THAT PIN CONNECTIONS ARE SAME AS LM324.





MICROPHONE PREAMPLIFIER

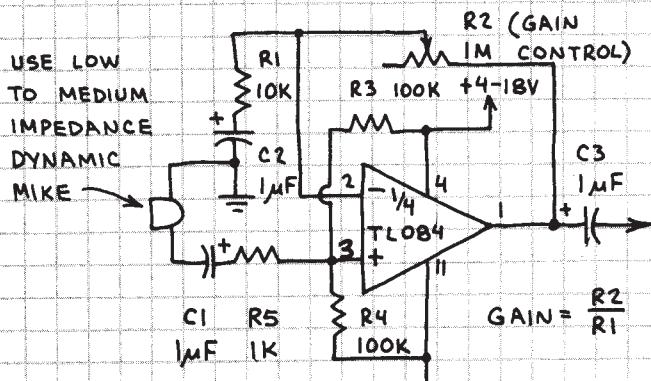


NOTE SINGLE POLARITY POWER SUPPLY (THANKS TO R3 AND R4) AND AC COUPLING.


LOW-Z PREAMPLIFIER

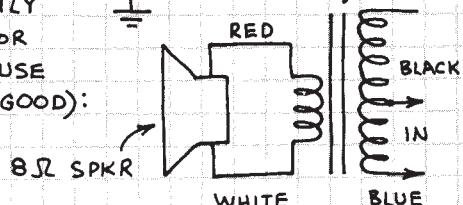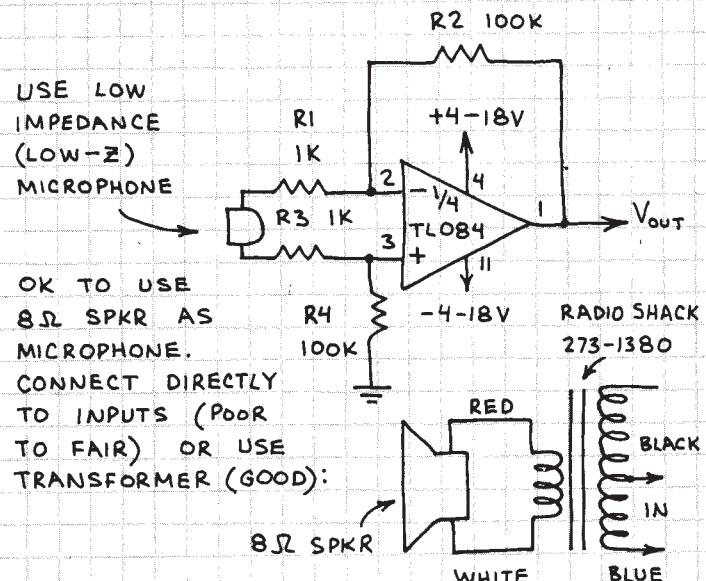

INFRARED VOICE COMMUNICATOR

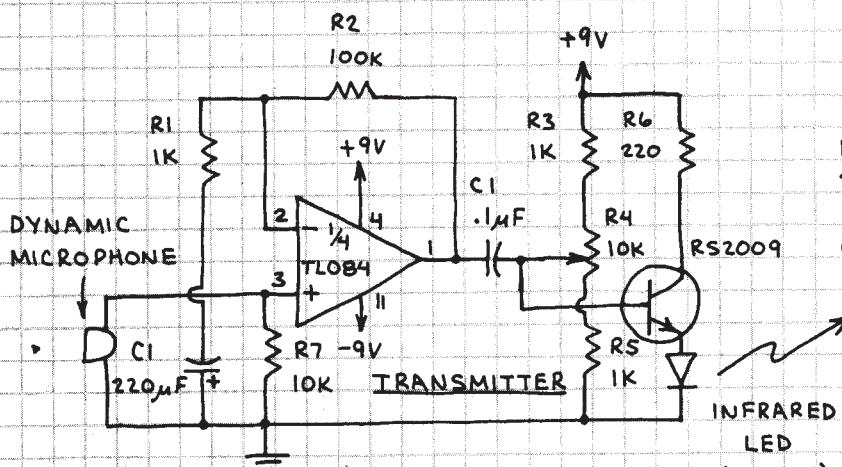

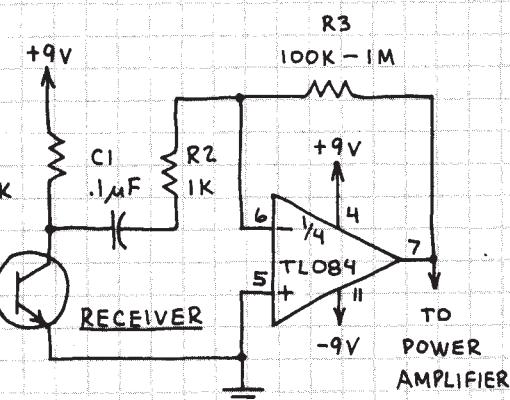
POINT THE LED AT Q1 AND ADJUST R4 UNTIL BEST VOICE QUALITY IS OBTAINED. (R4 APPLIES PREBIAS TO LED.) R6 LIMITS MAXIMUM LED CURRENT TO A SAFE 40 mA.




USE RADIO SHACK 276-130 PHOTOTRANSISTOR FOR Q1. MAXIMUM RANGE: HUNDREDS OF FEET AT NIGHT WITH LENSES AT Q1 AND LED. POWER AMP: SEE LM386.

QUAD OPERATIONAL AMPLIFIER LM324N

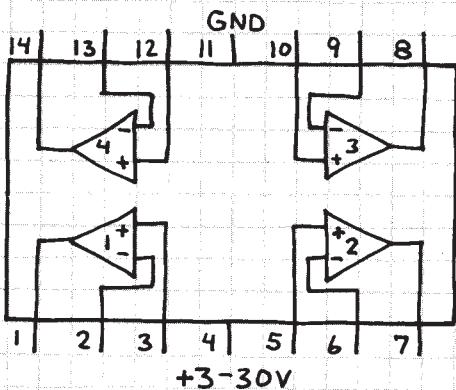
OPERATES FROM SINGLE POLARITY POWER SUPPLY. MORE GAIN (100 dB) BUT LESS BANDWIDTH (1 MHz WHEN GAIN IS 1) THAN THE LM3900 QUAD OP-AMP. NOTE UNUSUAL LOCATION OF POWER SUPPLY PINS. CAUTION: SHORTING THE OUTPUTS DIRECTLY TO V₊ OR GND OR REVERSING THE POWER SUPPLY MAY DAMAGE THIS CHIP.




BANDPASS FILTER

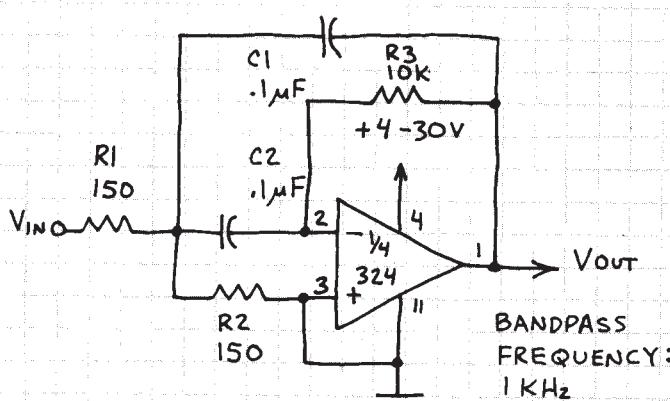


INFRARED TRANSMITTER

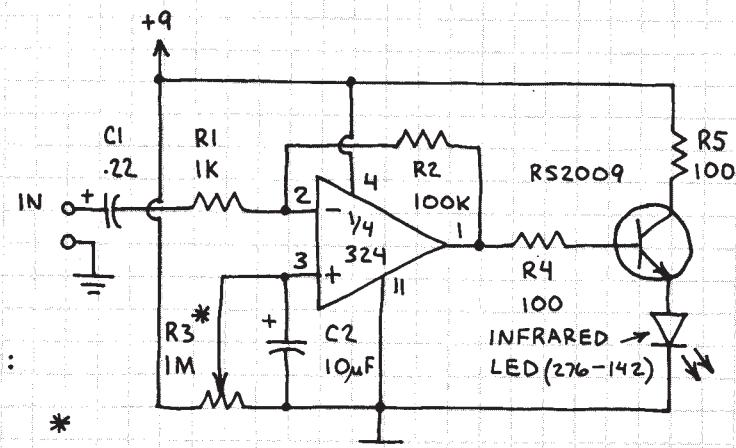

PULSE GENERATOR

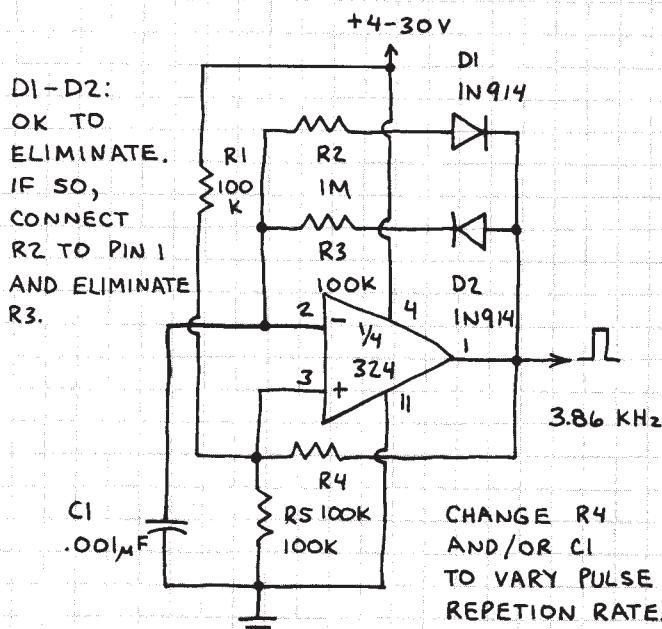


INTERFACE CIRCUITS

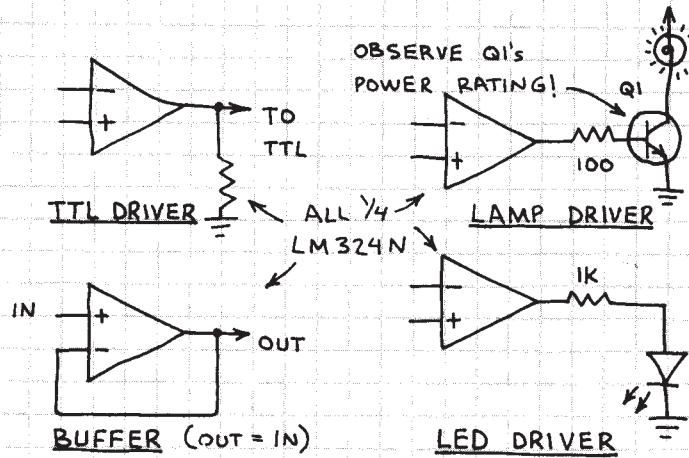

QUAD OPERATIONAL AMPLIFIER

LM3900N

+4-36V


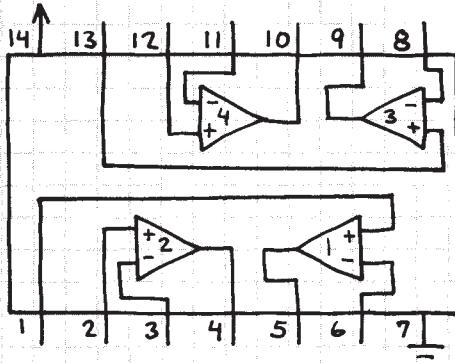


OPERATES FROM SINGLE POLARITY POWER SUPPLY. LESS GAIN (70 dB) BUT WIDER BANDWIDTH (25 MHz AT GAIN OF 1) THAN THE LM324 QUAD OP-AMP. NOTE STANDARD POWER SUPPLY PIN LOCATIONS. CAUTION: SHORTING THE OUTPUTS DIRECTLY TO V_T OR GROUND OR REVERSED POWER CONNECTIONS MAY DAMAGE THIS CHIP.


NOTE: DO NOT SUBSTITUTE LM3900 FOR OTHER OP-AMPS

ASTABLE MULTIVIBRATOR


TOGGLE FLIP-FLOP

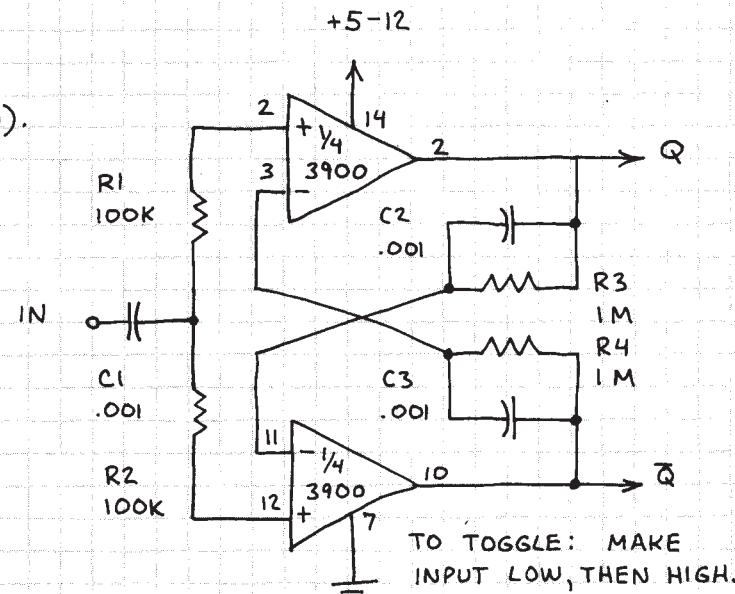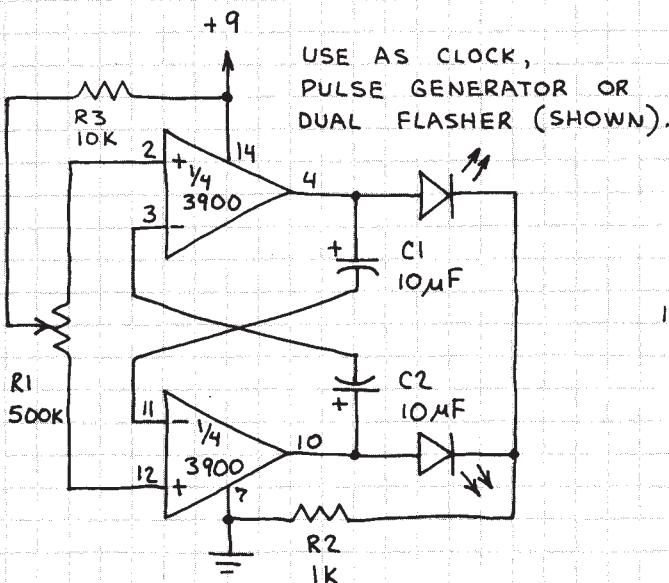

FUNCTION GENERATOR

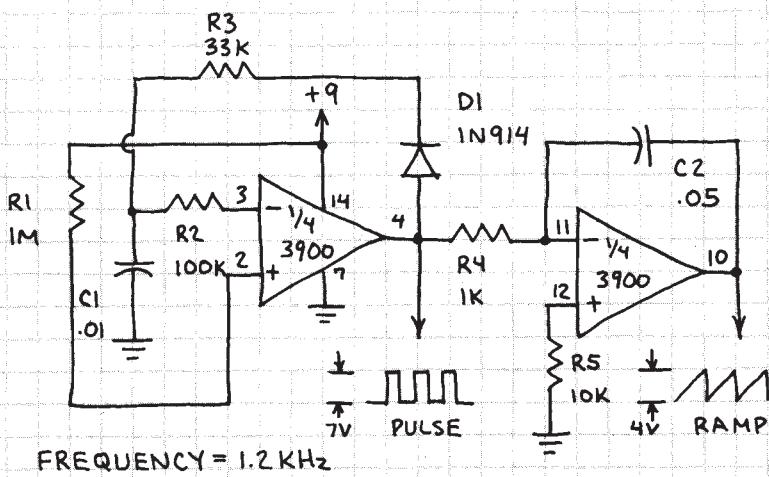


X10 AMPLIFIER

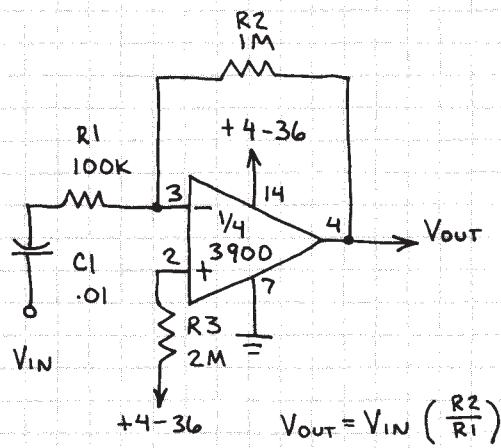


QUAD COMPARATOR LM339 (276-1712)

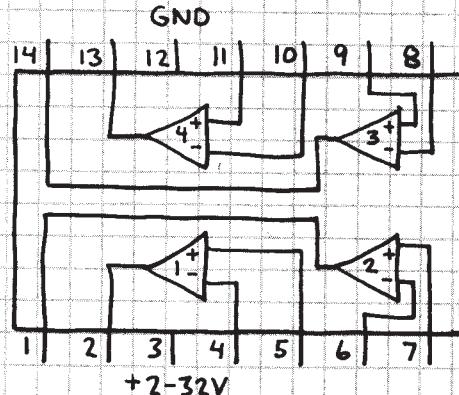FOUR INDEPENDENT VOLTAGE COMPARATORS IN A SINGLE PACKAGE. NOTE THAT A SINGLE POLARITY POWER SUPPLY IS REQUIRED. (MOST COMPARATORS ARE DESIGNED PRIMARILY FOR DUAL SUPPLY OPERATION.) NOTE UNUSUAL LOCATION OF THE SUPPLY PINS. COMPARATORS MAY OSCILLATE IF OUTPUT LEAD IS TOO CLOSE TO INPUT LEADS. GROUND ALL PINS OF UNUSED COMPARATORS.




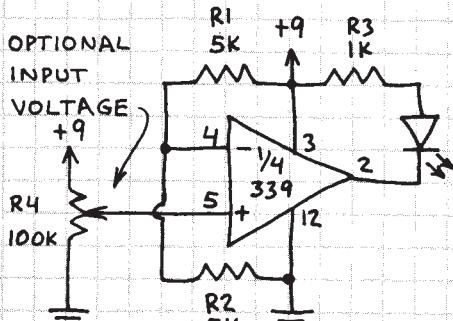NON-INVERTING COMPARATOR INVERTING COMPARATOR




R₁-R₂
DETERMINE
REFERENCE
VOLTAGE
(4.5 V AS SHOWN).

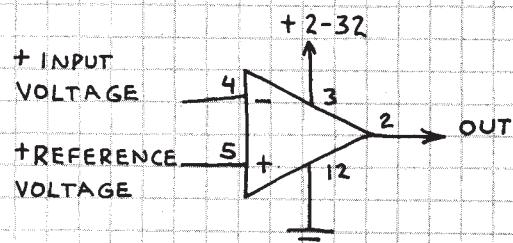LED GLOWS WHEN INPUT VOLTAGE (PIN 5) FALLS BELOW REFERENCE VOLTAGE (PIN 4).



INVERTING COMPARATOR WITH HYSTERESIS


NON-INVERTING COMPARATOR WITH HYSTERESIS

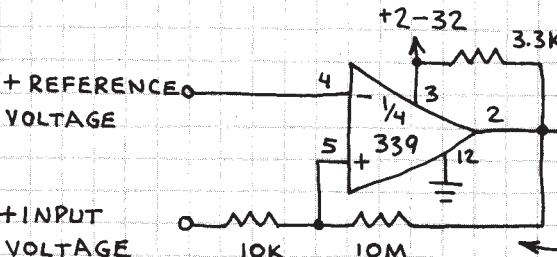

+ INPUT
VOLTAGE




+ REFERENCE
VOLTAGE

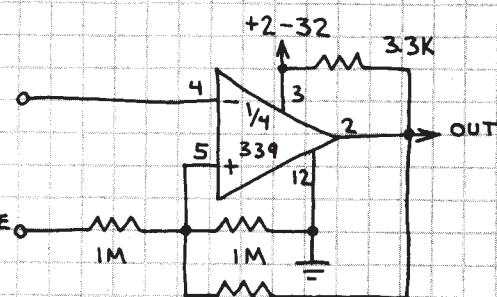NOTE: HYSTERESIS PROVIDED
BY FEEDBACK RESISTOR STOPS
OSCILLATION.



3-STATE OUTPUT


TTL DRIVER CMOS DRIVER

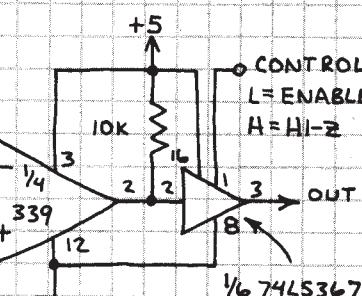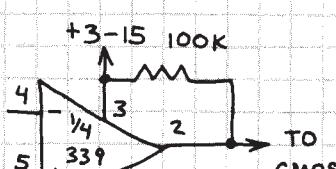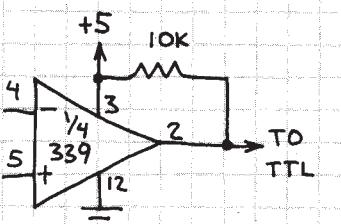


QUAD COMPARATOR (CONTINUED)

LM339

LED BARGRAPH READOUT


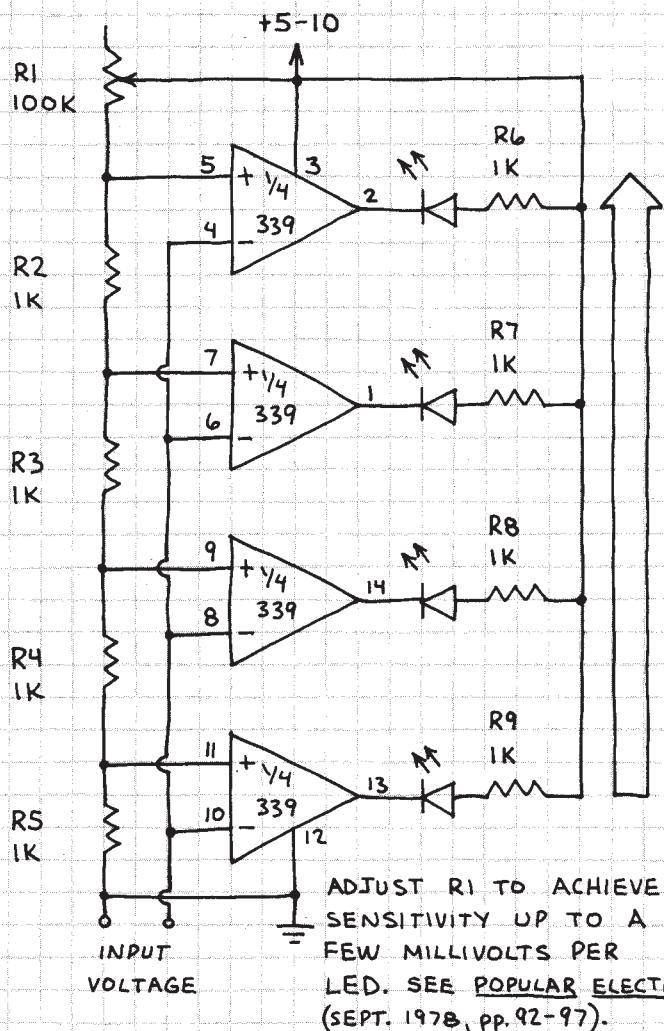


WINDOW COMPARATOR

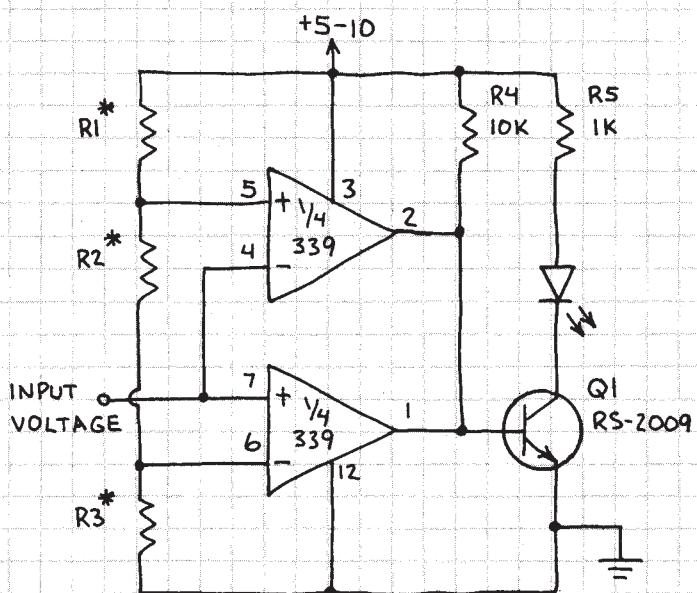

PROGRAMMABLE LIGHT METER


SQUAREWAVE OSCILLATOR

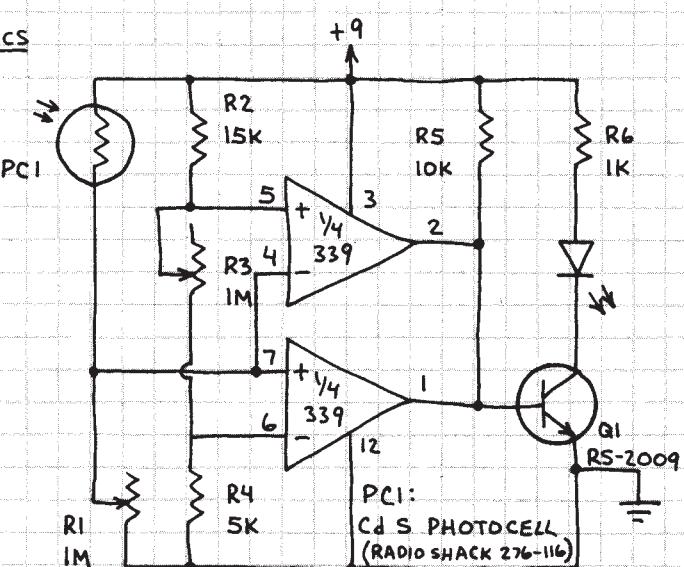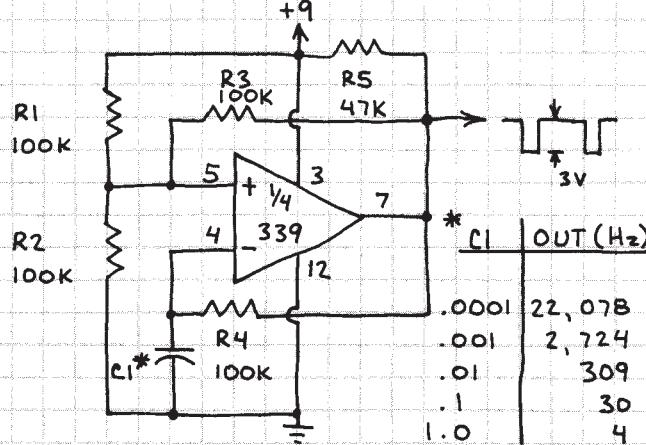


LED FLASHER / OSCILLATOR

3909

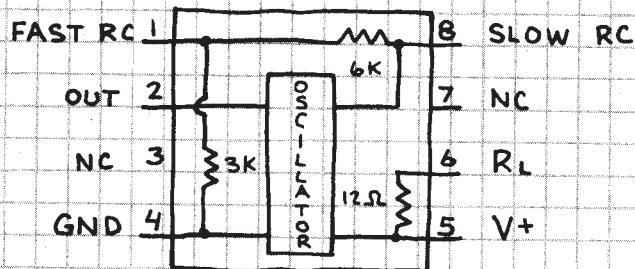
EASIEST TO USE IC IN THIS NOTEBOOK. FLASHES LEDs OR CAN BE USED AS TONE SOURCE. WILL DRIVE SPEAKER DIRECTLY. WILL FLASH A RED LED WHEN V_T IS ONLY 1.3 VOLTS.



LED FLASHER

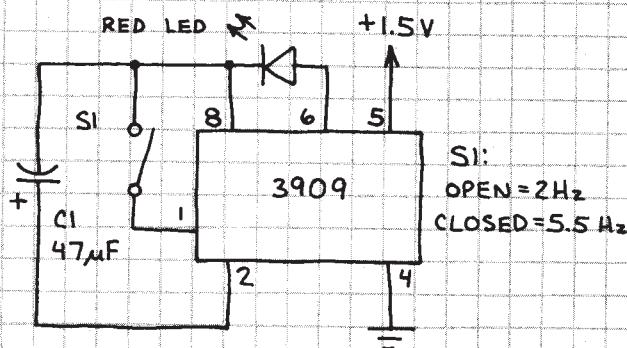

POWER FLASHER

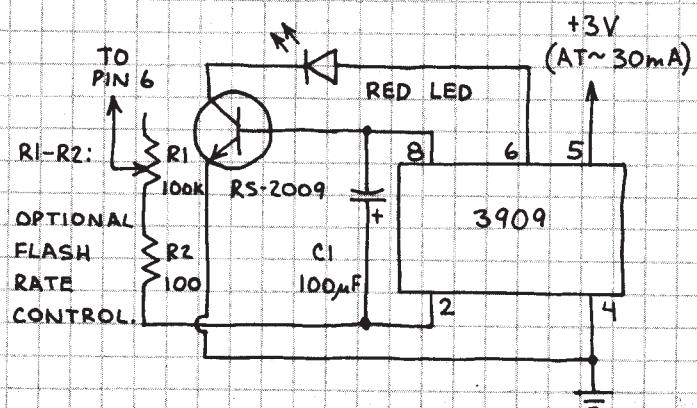


INFRARED TRANSMITTERS

TRANSMITS


STEADY IR LED
1 KHz
(276-142)

IN914 +1.5V

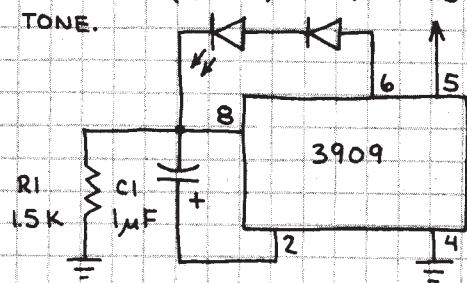


TRANSMITS
DISTINCTIVE
WARBLE TONE


IR LED
(276-142) IN914 +1.5V

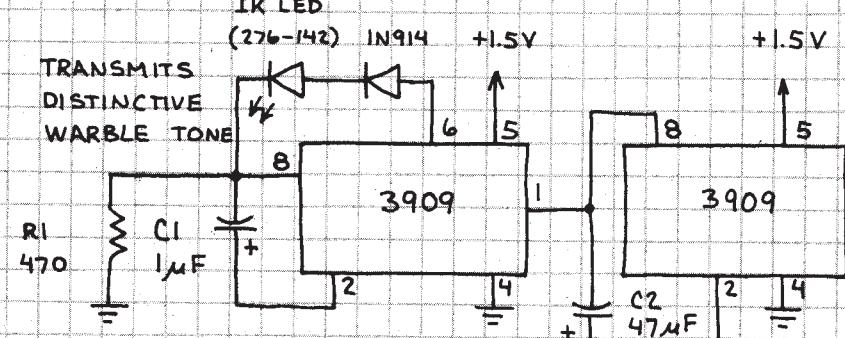

LIGHT CONTROLLED TONE

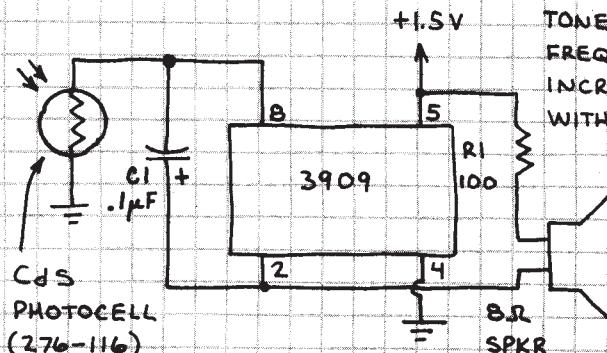


LAMP FLASHER

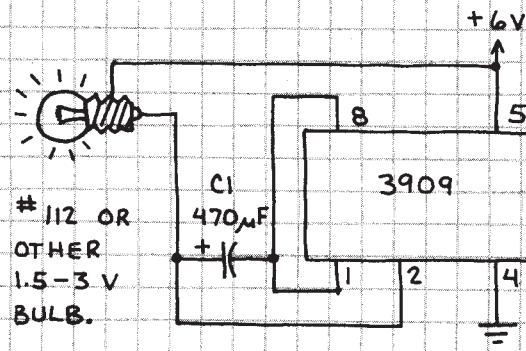


LED FLASHER / OSCILLATOR (CONTINUED)

3909


WHOOPER

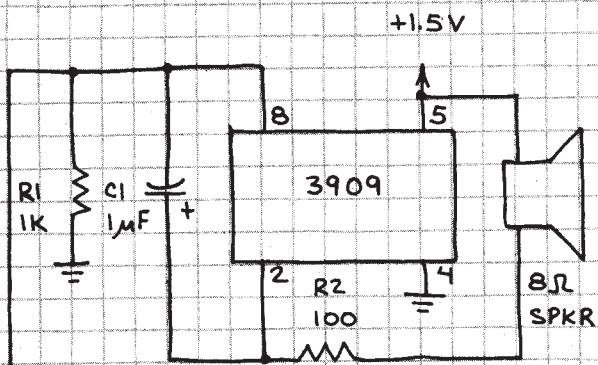


CHIRPER

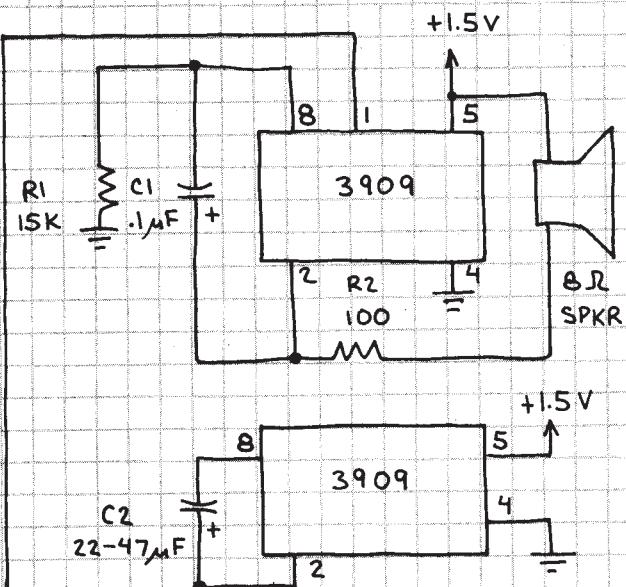


SUN POWERED OSCILLATOR

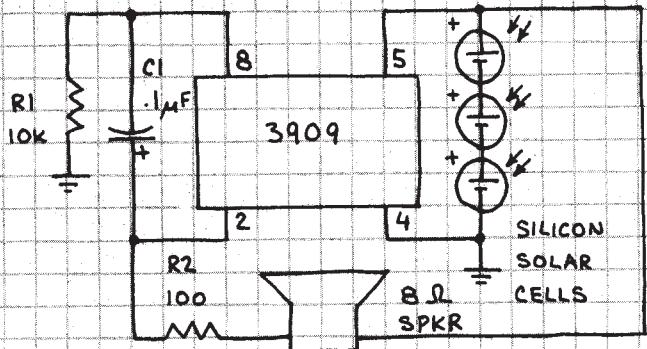


TOY ORGAN

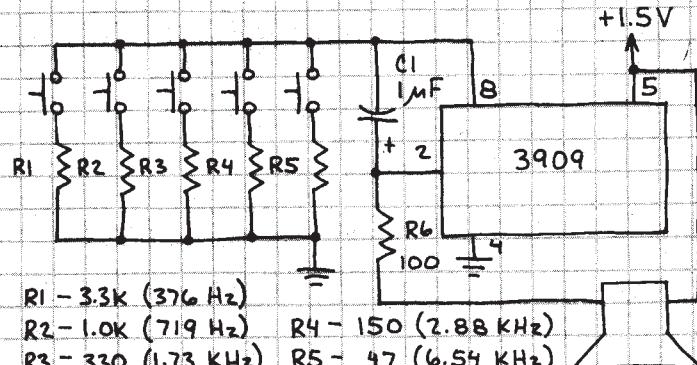

TTL CONTROLLED 3909

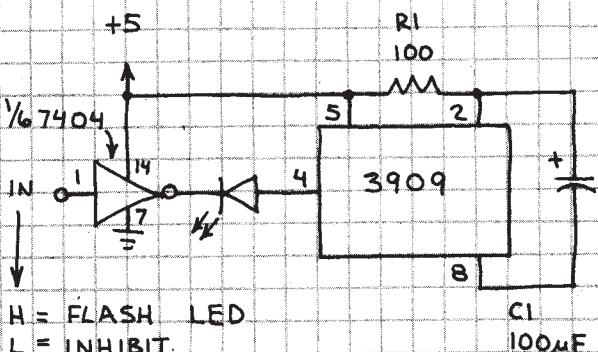

H = FLASH LED
L = INHIBIT

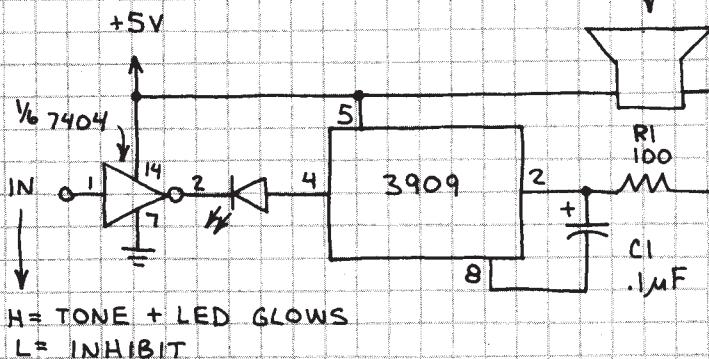


H = TONE + LED GLOWS
L = INHIBIT


DOT/BAR DISPLAY DRIVER

LM3914N

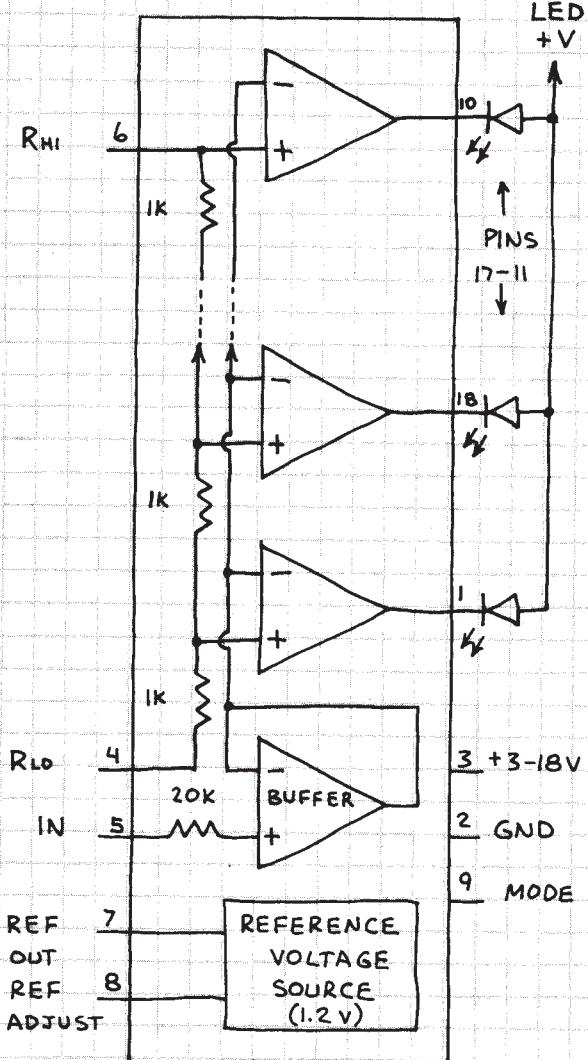
ONE OF THE MOST IMPORTANT CHIPS IN THIS NOTEBOOK. LIGHTS UP TO 10 LEDs (BAR MODE) OR 1-OF-10 LEDs (DOT MODE) IN RESPONSE TO AN INPUT VOLTAGE. CHIP CONTAINS A VOLTAGE DIVIDER AND 10 COMPARATORS THAT TURN ON IN SEQUENCE AS THE INPUT VOLTAGE RISES. HERE'S A SIMPLIFIED VERSION OF THE CIRCUIT:



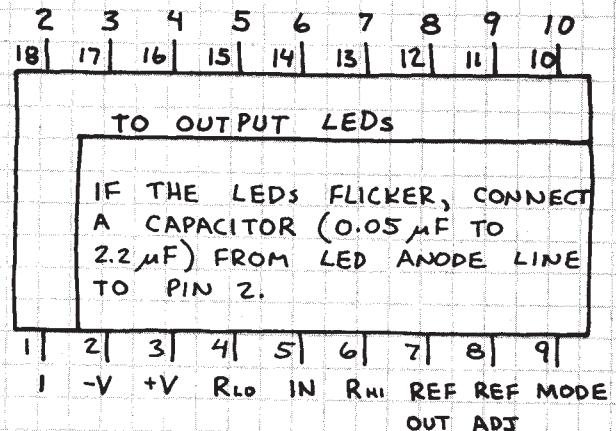R_{H1} AND R_{LO} ARE THE ENDS OF THE DIVIDER CHAIN. THE REFERENCE VOLTAGE OUTPUT (REF OUT) IS 1.2-1.3 VOLTS. CONNECT PIN 9 TO PIN 11 FOR DOT MODE OR +V FOR BAR MODE.



DOT/BAR DISPLAY

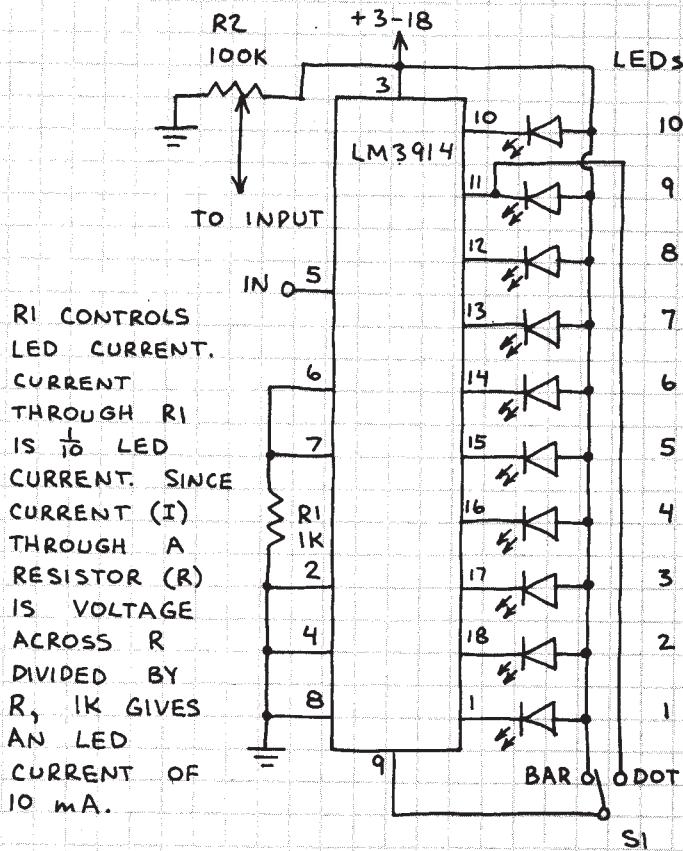


WHEN +V = +3-18 VOLTS, THE READOUT RANGE IS 0.13 - 1.30 VOLTS. TO CHANGE RANGE TO 0.1-1.0 VOLT (0.1 VOLT PER LED), INSERT A 5K POTENTIOMETER BETWEEN PINS 6 AND 7. CONNECT VOLTMETER ACROSS PINS 5 AND 8 AND ADJUST R2 FOR 1 VOLT AT PIN 5. THEN ADJUST 1K POT UNTIL LED 10 GLOWS. REPEAT THIS PROCEDURE FOR 0.1 VOLT AT PIN 5 AND LED 1. OK TO REPLACE THE 1K POT WITH A FIXED RESISTOR OF THE PROPER VALUE.

DOT/BAR DISPLAY DRIVER (CONTINUED)

LM3914N


20-ELEMENT READOUT

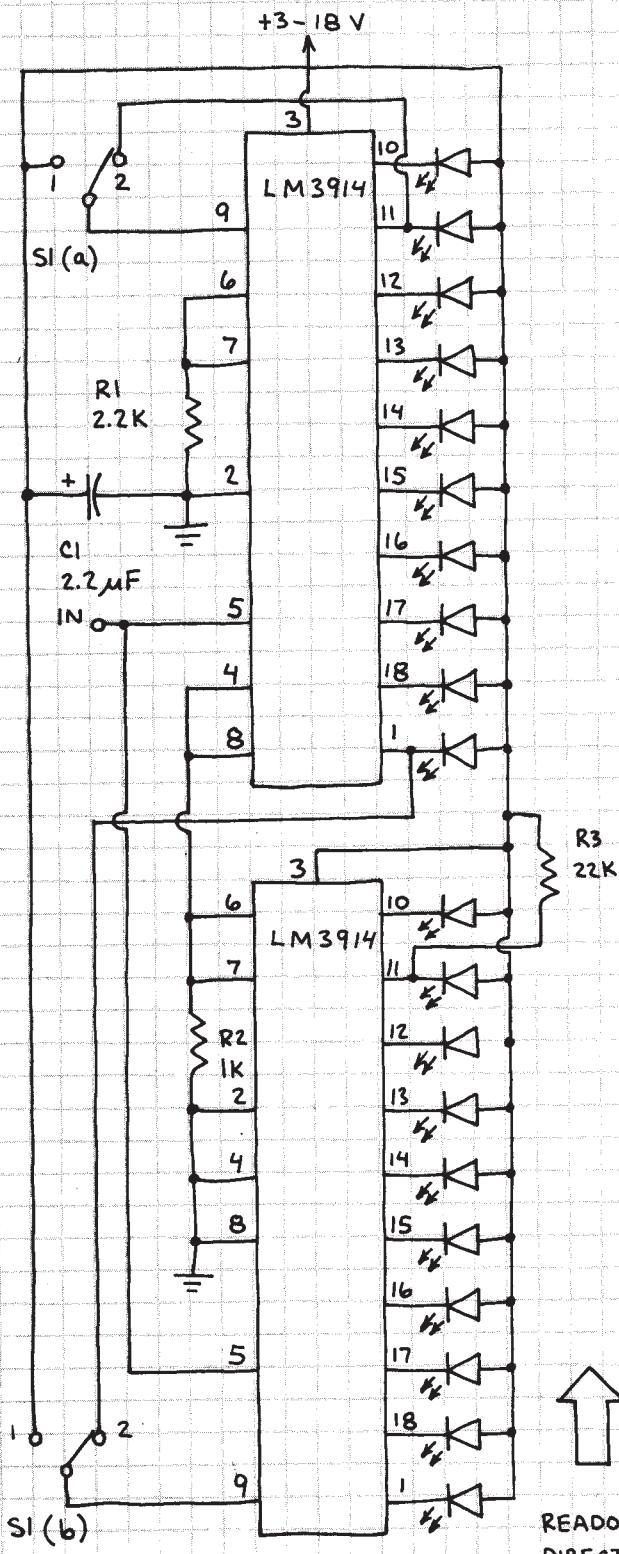

THIS CIRCUIT SHOWS HOW TO CASCADE 2 OR MORE LM3914'S. WHEN $+V = 5$ VOLTS, THE READOUT RANGE IS 0.14 V TO 2.7 V. HIGHEST ORDER LED STAYS ON DURING OVERRANGE. AVOID SUBSTITUTIONS FOR R₁, R₂ AND R₃.

S₁ IS THE MODE SWITCH. USE A DPDT TOGGLE. POSITION 1 SELECTS BAR AND POSITION 2 SELECTS DOT. OMIT S₁ IF ONLY ONE MODE IS REQUIRED. SIMPLY WIRE IN THE CORRECT CONNECTIONS.

FLASHING BAR READOUT

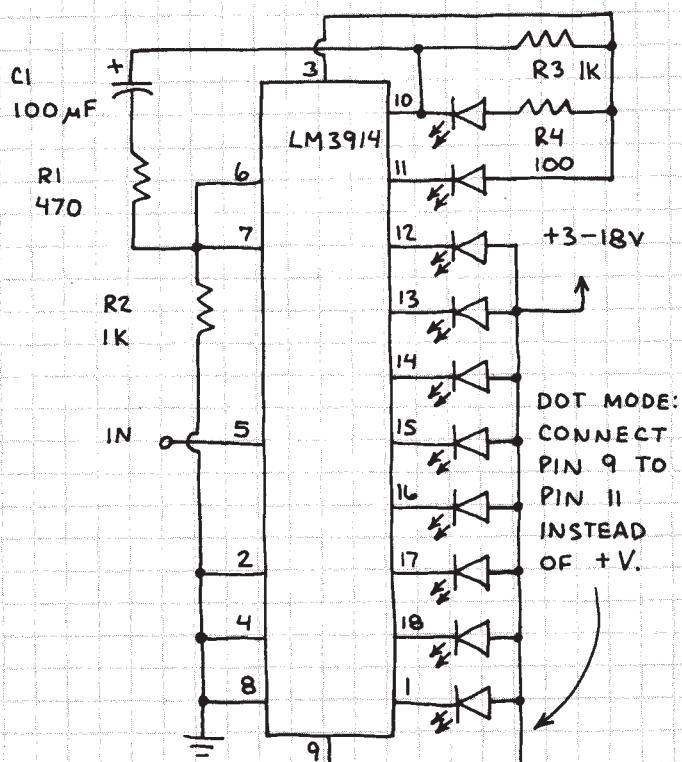

DOT MODE:
CONNECT PIN 9 TO PIN 11
INSTEAD OF $+V$.


THE CIRCUITS ON THIS PAGE ARE ADAPTED FROM NATIONAL SEMICONDUCTOR'S LM3914 LITERATURE. BOTH WORK WELL.

WHEN ALL 10 LEDs ARE ON THE DISPLAY FLASHES. OTHERWISE THE LEDs DO NOT FLASH. INCREASE C₁ TO SLOW FLASH RATE.

DOT/BAR DISPLAY DRIVER (CONTINUED)

LM3914N


SOLID-STATE OSCILLOSCOPE

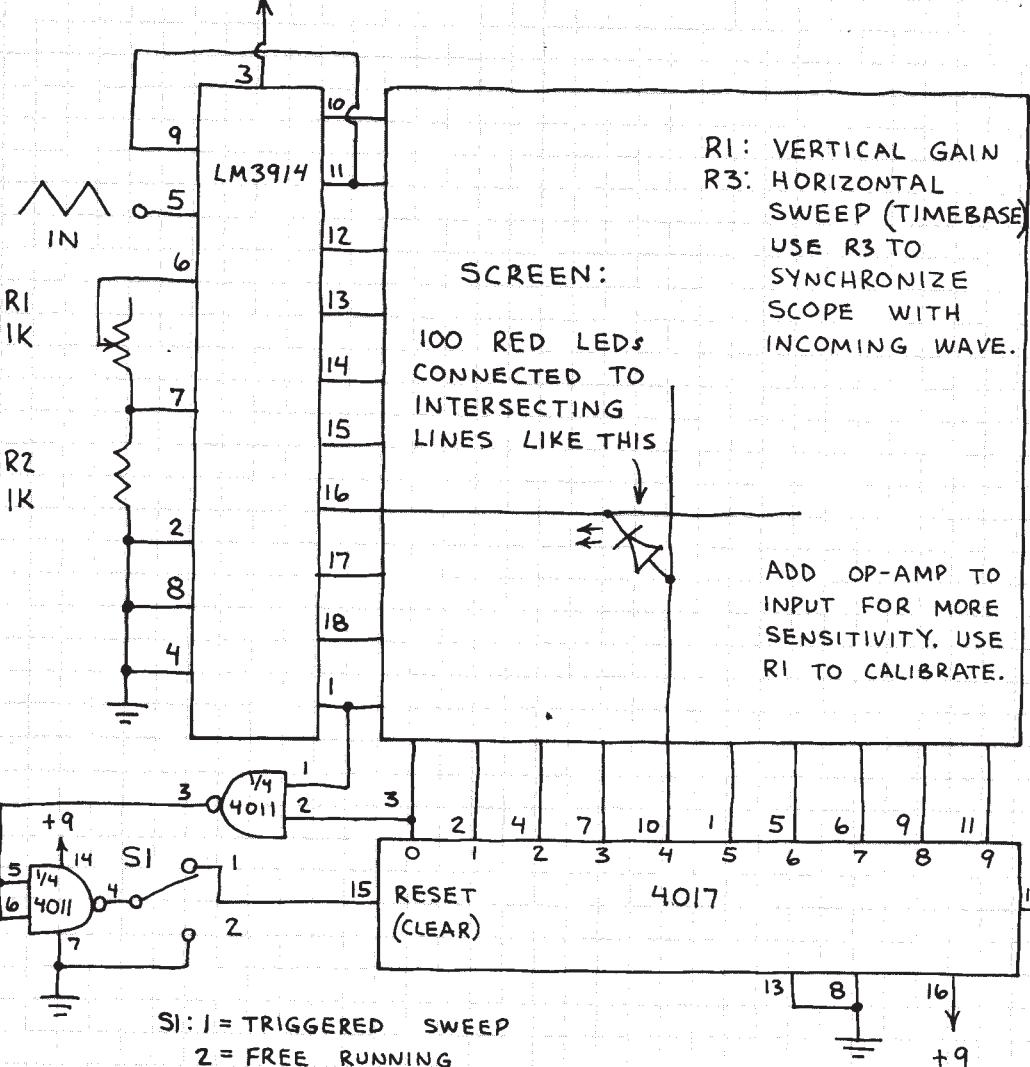

THIS IS AN EXPERIMENTAL SOLID-STATE SCOPE THAT WILL FIT IN A POCKET SIZE HOUSING. THE RESOLUTION IS POOR, BUT VARIOUS WAVEFORMS CAN BE VISUALIZED. EXPAND BOTH THE VERTICAL AND HORIZONTAL CIRCUITS FOR MORE RESOLUTION. FOR MORE INFORMATION SEE POPULAR ELECTRONICS, AUGUST 1979 (PP. 78-79).


USING THE LM3914 AS A CONTROLLER:

RELAY

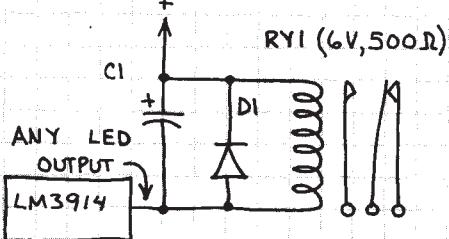

C1 - 47μF (PREVENTS CHATTER)
DI - IN914
RY1 - RADIO SHACK 275-004

OPTICAL COUPLING

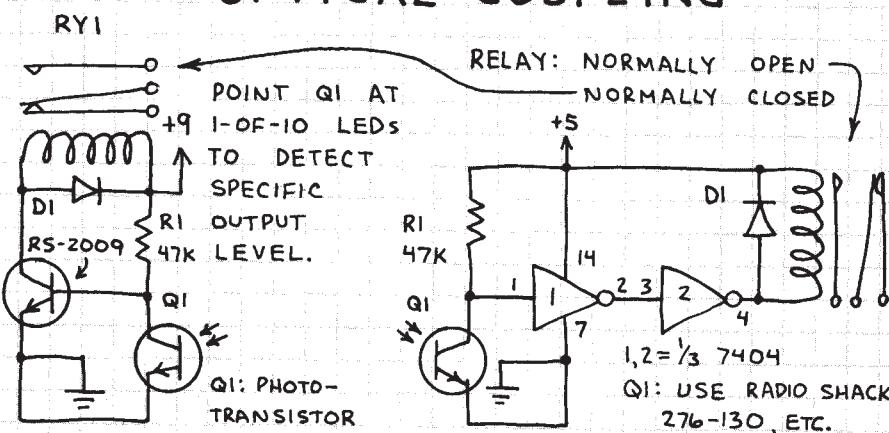

DOT/BAR DISPLAY DRIVER

LM3915N

LOGARITHMIC VERSION OF THE LM3914 N. THE LM3915 N USES A STRING OF 1K RESISTORS AS A VOLTAGE DIVIDER WITH LINEARLY SCALED DIVISIONS.

THE VOLTAGE DIVIDER RESISTORS OF THE LM3915N ARE SCALED TO GIVE A -3dB INTERVAL FOR EACH OUTPUT. THIS CHIP IS IDEAL FOR VISUALLY MONITORING THE AMPLITUDE OF AUDIO SIGNALS.

2 3 4 5 6 7 8 9 10
18 17 16 15 14 13 12 11 10


TO OUTPUT LEDs

IF THE LEDS FLICKER, CONNECT A CAPACITOR ($0.05 \mu\text{F}$ - $2.2 \mu\text{F}$) FROM LED ANODE LINE TO PIN 2.

1 2 3 4 5 6 7 8 9
1 -V +V R_{LO} IN R_{H1} REF REF MODE
OUT ADJ

SEE LM3914N FOR EXPLANATION OF PIN FUNCTIONS.

0 TO -27 dB DOT/BAR DISPLAY

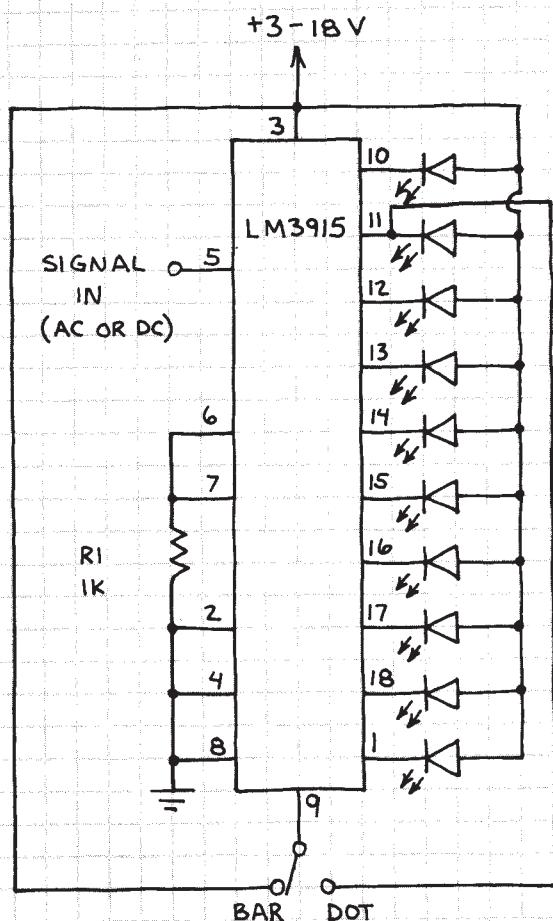

LED DISPLAY

* BAR MODE


0 dB (FULLSCALE OR FS)	● ● ● ● ● ● ● ●
-3 dB (.707 FS)	● ● ● ● ● ● ○ ○
-6 dB (.500 FS)	● ● ● ● ● ○ ○ ○
-9 dB (.354 FS)	● ● ● ● ○ ○ ○ ○
-12 dB (.250 FS)	● ● ● ○ ○ ○ ○ ○
-15 dB (.177 FS)	● ● ○ ○ ○ ○ ○ ○
-18 dB (.125 FS)	● ○ ○ ○ ○ ○ ○ ○
-21 dB (.088 FS)	○ ○ ○ ○ ○ ○ ○ ○
-24 dB (.062 FS)	○ ○ ○ ○ ○ ○ ○ ○
-27 dB (.044 FS)	○ ○ ○ ○ ○ ○ ○ ○

* OK TO USE DOT MODE.


THE INPUT SIGNAL CAN BE CONNECTED DIRECTLY TO PIN 5 WITHOUT RECTIFICATION, LIMITING OR AC COUPLING. SEE THE LM3914 N FOR MORE IDEAS AND TIPS.

TIMER 555

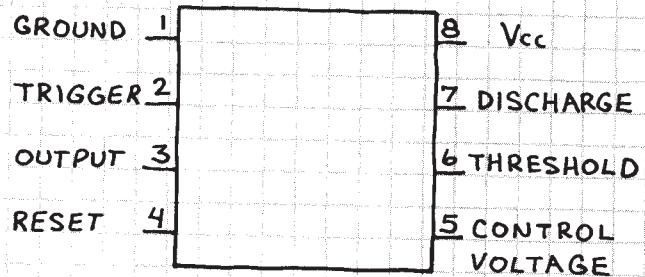THE FIRST AND STILL THE MOST POPULAR IC TIMER CHIP. OPERATES AS A ONE-SHOT TIMER OR AN ASTABLE MULTIVIBRATOR. THE 556 IS TWO 555 CIRCUITS ON ONE CHIP.




555 EQUIVALENT CIRCUIT

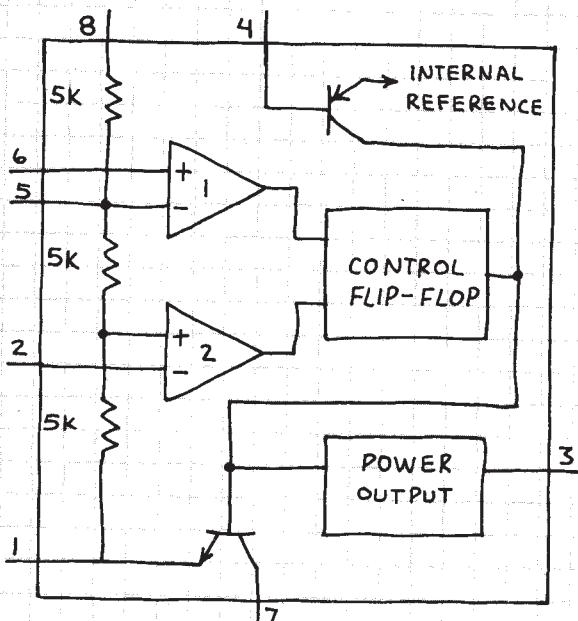


1 AND 2 ARE COMPARATORS. CIRCUIT CAN BE MADE FROM INDIVIDUAL PARTS AS SHOWN... BUT 555 IS MUCH SIMPLER.


ONE-SHOT TIMER

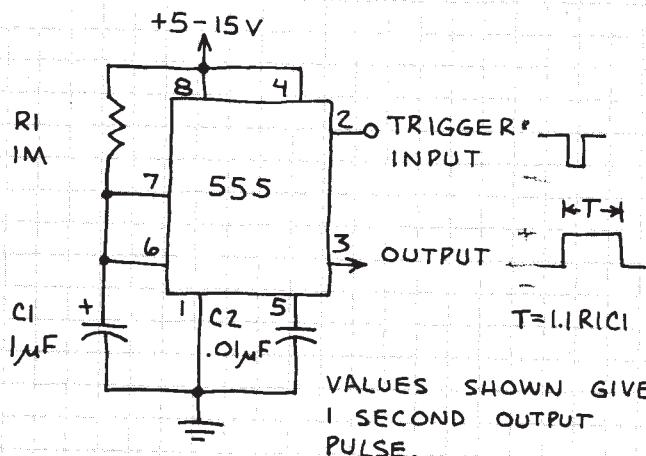

BOUNCELESS SWITCH

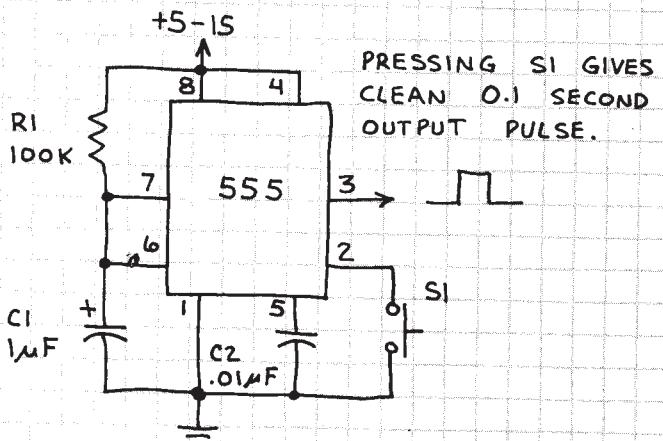

TIMER PLUS RELAY

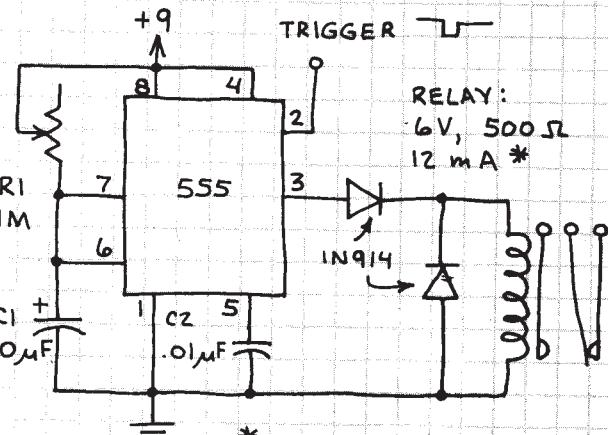


VALUES OF R1 AND C1 SHOWN WILL PULL RELAY IN FOR UP TO ABOUT 11 SECONDS. USE POINTER KNOB AND PAPER SCALE TO HELP CALIBRATE CIRCUIT. USES INCLUDE DARKROOM TIMING. CIRCUIT CAN BE TRIGGERED BY A NEGATIVE PULSE OR WITH A PUSHBUTTON SWITCH ACROSS PINS 1 AND 2.


TIMER (CONTINUED)

555


TOY ORGAN

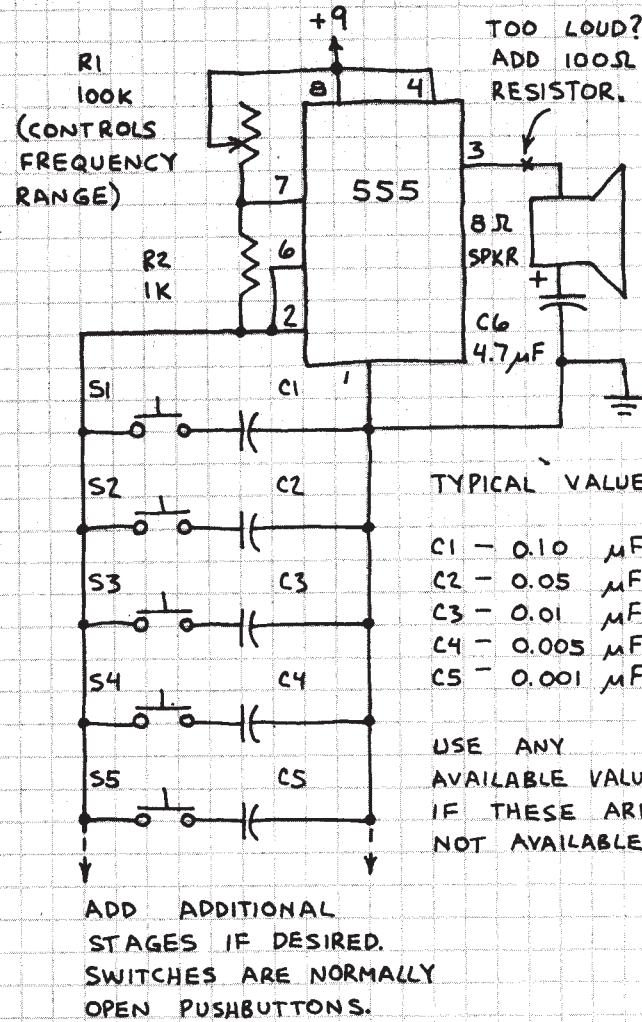


LED TRANSMITTER

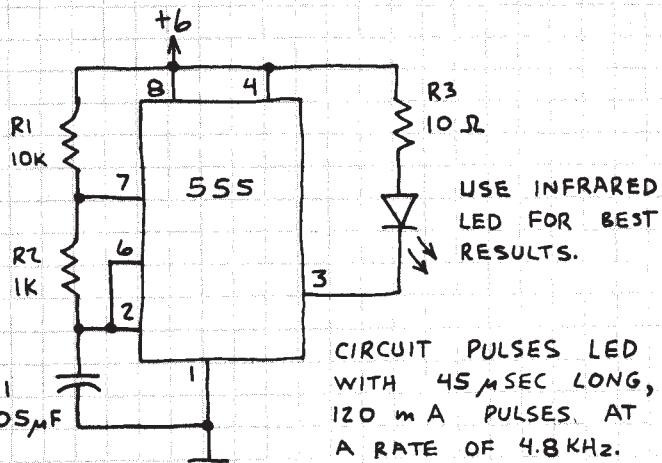

PULSE GENERATOR

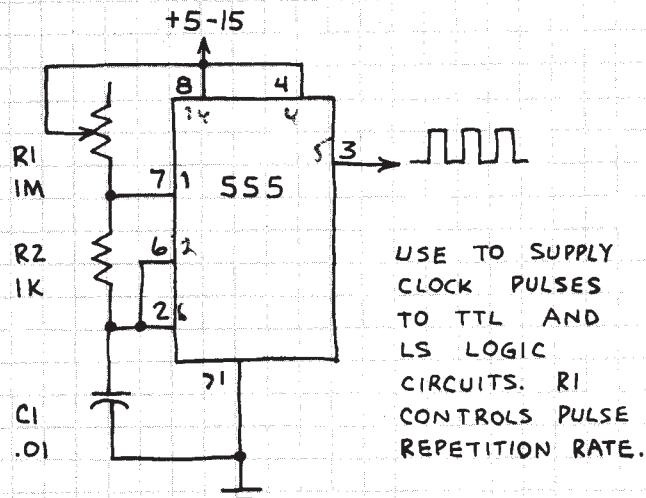

MISSING PULSE DETECTOR

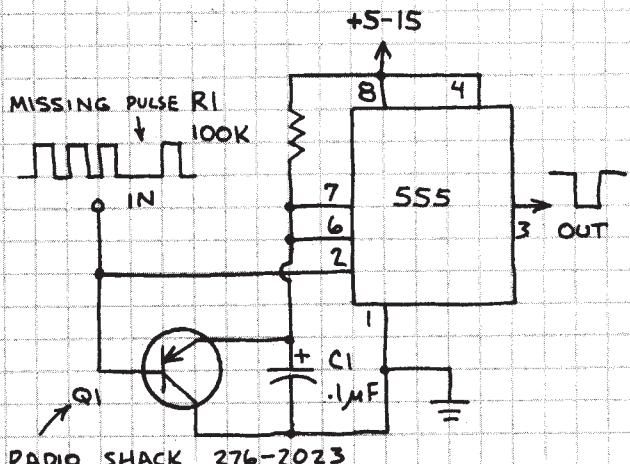


THIS CIRCUIT IS A ONE-SHOT THAT IS CONTINUALLY RETRIGGERED BY INCOMING PULSES. A MISSING OR DELAYED PULSE THAT PREVENTS RETRIGGERING BEFORE A TIMING CYCLE IS COMPLETE CAUSES PIN 3 TO GO LOW UNTIL A NEW INPUT PULSE ARRIVES. R1 AND C1 CONTROL RESPONSE TIME. USE IN SECURITY ALARMS, CONTINUITY TESTERS, ETC.

TIMER (CONTINUED)


555

ULTRA-LONG TIME DELAY

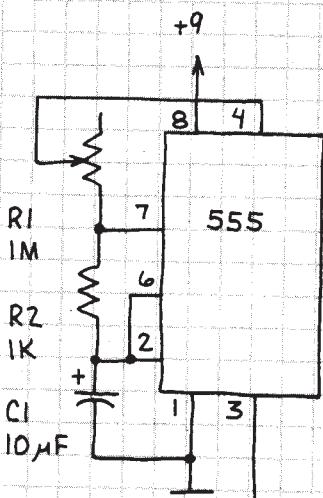


R1
1M
R2
1K
C1
10 μ F

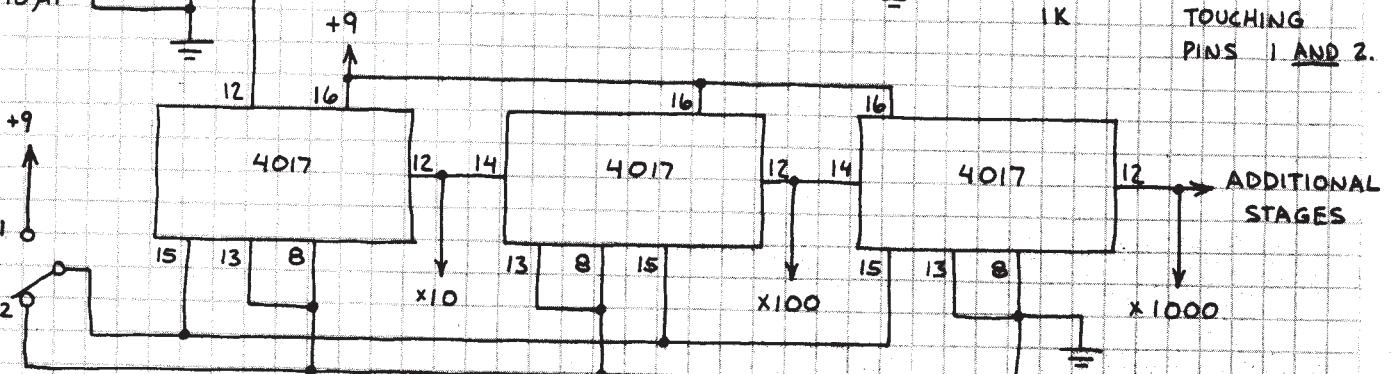RI CONTROLS PULSE RATE FROM 555. THIS RATE IS DIVIDED BY THE 4017'S TO GIVE $\times 10$, $\times 100$ AND $\times 1000$ DELAYS.



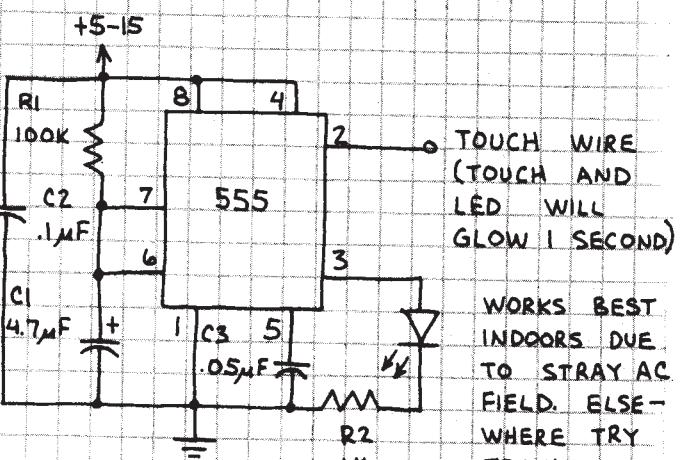
1 = RESET TYPICAL OUTPUT: 555 (PIN 3)
2 = RUN 4017 ($\times 10$ OUTPUT)



+5-15
TOUCH WIRE (TOUCH AND LED WILL GLOW 1 SECOND)


WORKS BEST INDOORS DUE TO STRAY AC FIELD. ELSEWHERE TRY TOUCHING PINS 1 AND 2.

LIGHT DETECTOR

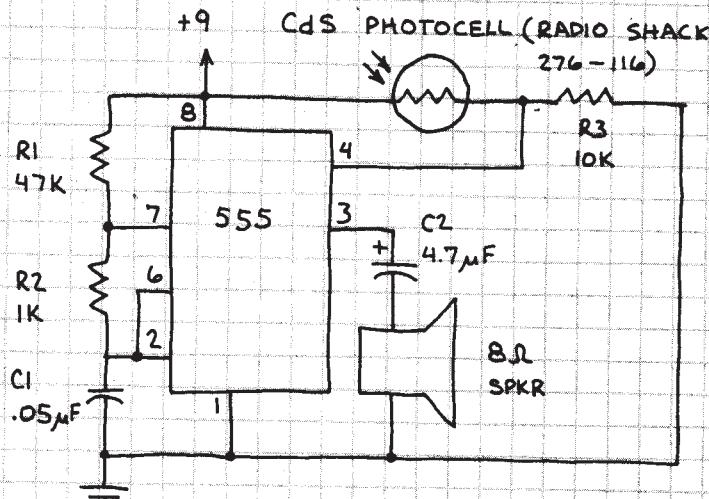

PRODUCES WARNING TONE WHEN LIGHT STRIKES PHOTOCELL. MAKES A GOOD OPEN DOOR ALARM FOR REFRIGERATOR OR FREEZER.

DARK DETECTOR


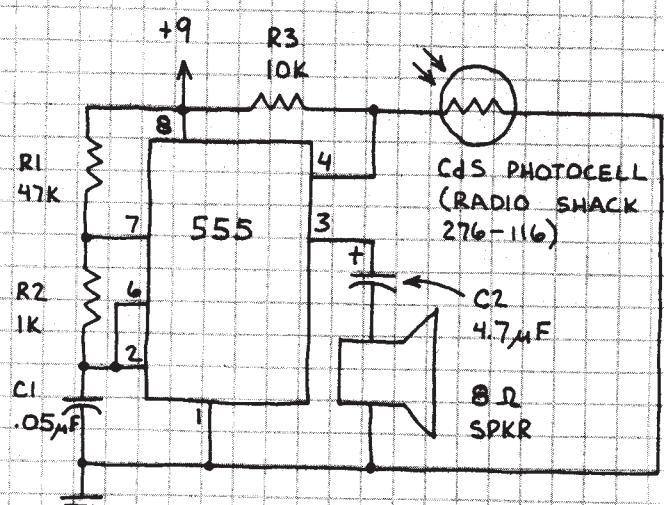


SILENT WHEN LIGHT STRIKES PHOTOCELL. REMOVE LIGHT AND TONE SOUNDS. FASTER RESPONSE THAN ADJACENT CIRCUIT.

TIMER (CONTINUED)


555

NEON LAMP POWER SOURCE FREQUENCY DIVIDER

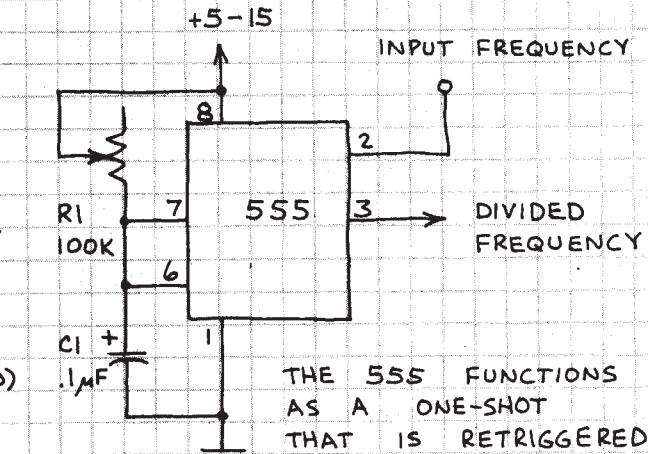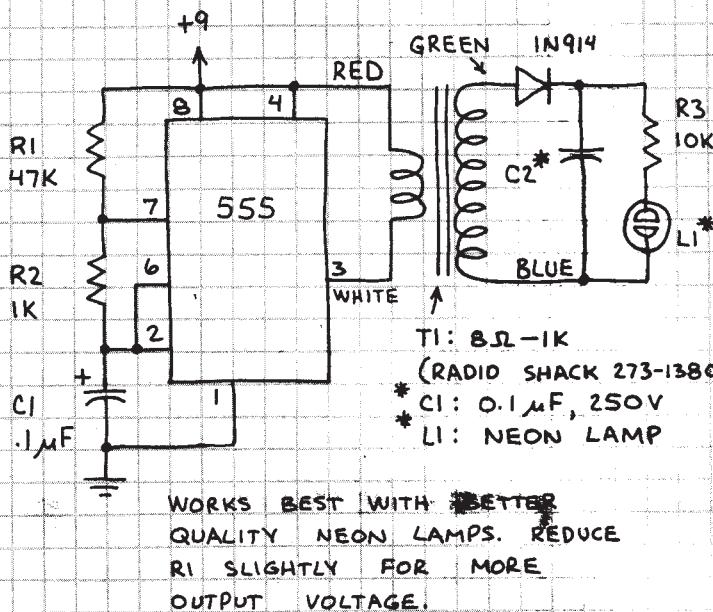


THE 555 FUNCTIONS AS A ONE-SHOT THAT IS RETRIGGERED BY THE INPUT WAVE. WAVES ARRIVING DURING THE TIMING CYCLE ARE IGNORED.

TRIANGLE WAVE GENERATOR

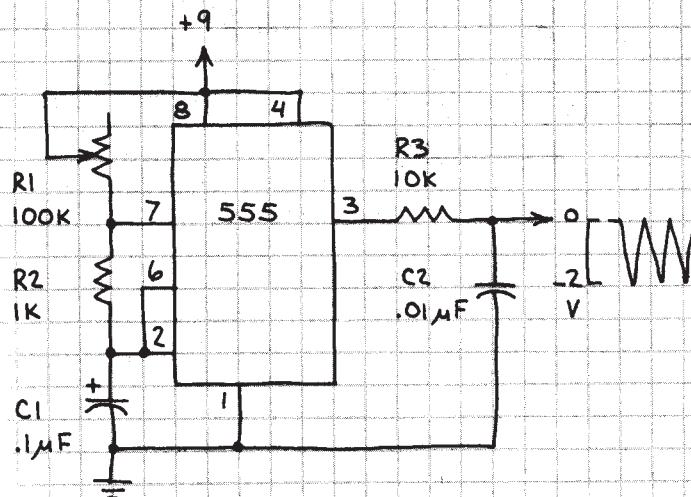

ADJUST R1 TO PROVIDE UP TO 10 kHz. OUTPUT FREQUENCY THIS HIGH PRODUCES CLOSELY SPACED TRIANGLE WAVES. THE WAVES ARE SEPARATED AT SLOWER FREQUENCIES (VVVV).

ONE-SHOT TONE BURST

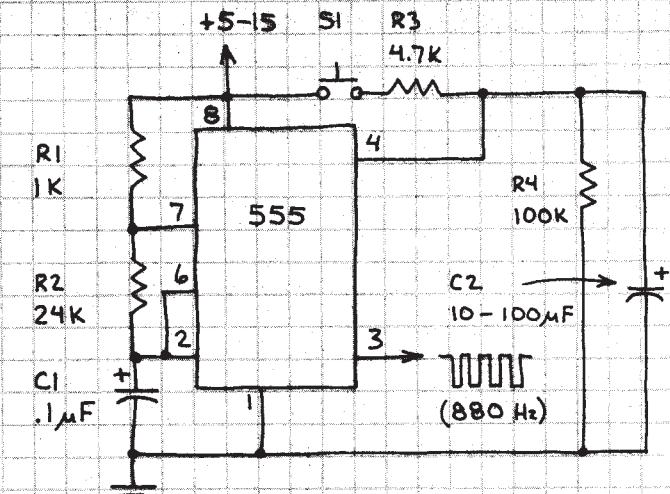


PRESS S1 AND STEADY OUTPUT FREQUENCY APPEARS AT PIN 3. RELEASE S1 AND OUTPUT FREQUENCY CONTINUES UNTIL C2 IS DISCHARGED BY R4. INCREASE C2 (OR R4) TO INCREASE LENGTH OF THE BURST. CHANGE FREQUENCY OF TONE BURST VIA R2 OR C1.

DUAL TIMER


556

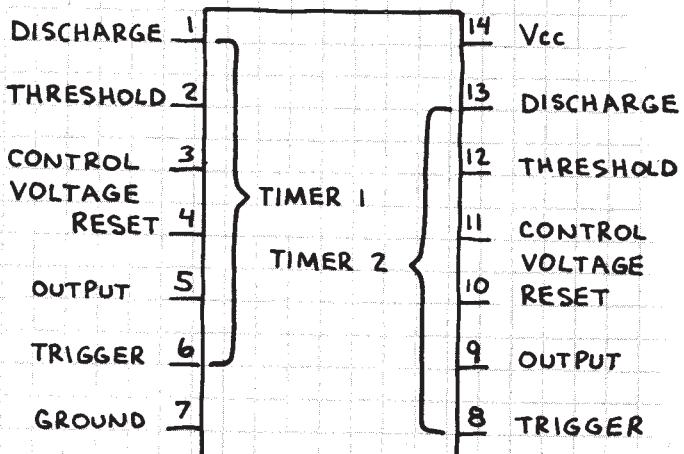CONTAINS TWO INDEPENDENT TIMERS ON A SINGLE CHIP. BOTH TIMERS ARE IDENTICAL TO THE 555. ALL THE APPLICATION CIRCUITS CAN ALSO BE BUILT WITH TWO 555's. THIS PIN CROSS REFERENCE WILL SIMPLIFY SUBSTITUTING TWO 555's FOR A 556 OR HALF A 556 FOR A 555:




FUNCTION	555	556(1)	556(2)
GROUND	1	7	7
TRIGGER	2	6	8
OUTPUT	3	5	9
RESET	4	4	10
CONTROL V.	5	3	11
THRESHOLD	6	2	12
DISCHARGE	7	1	13
Vcc	8	14	14

INTERVAL TIMER

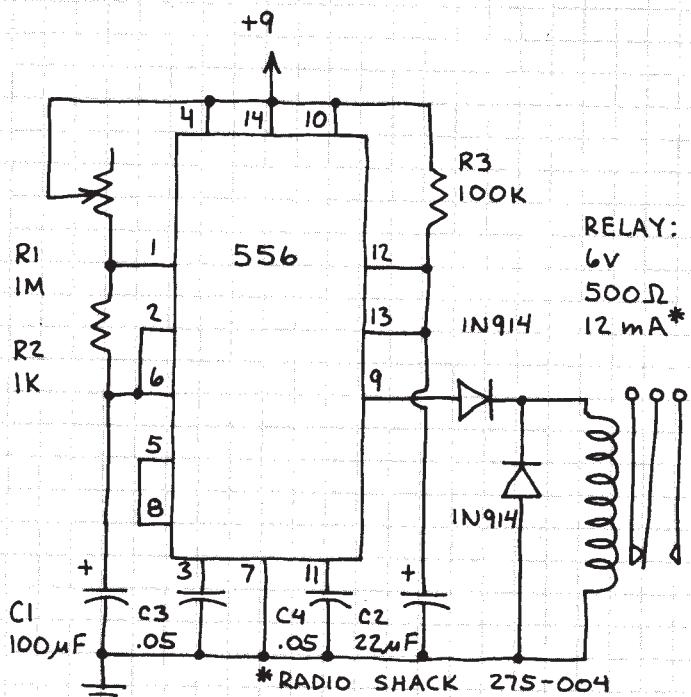


TIMER 1 IS CONNECTED AS ASTABLE OSCILLATOR. TIMER 2 IS A ONE-SHOT RELAY DRIVER. 1 FIRES 2 ONCE EACH CYCLE. 2 PULLS RELAY IN FOR 3-5 SECONDS.

3-STATE TONE SOURCE

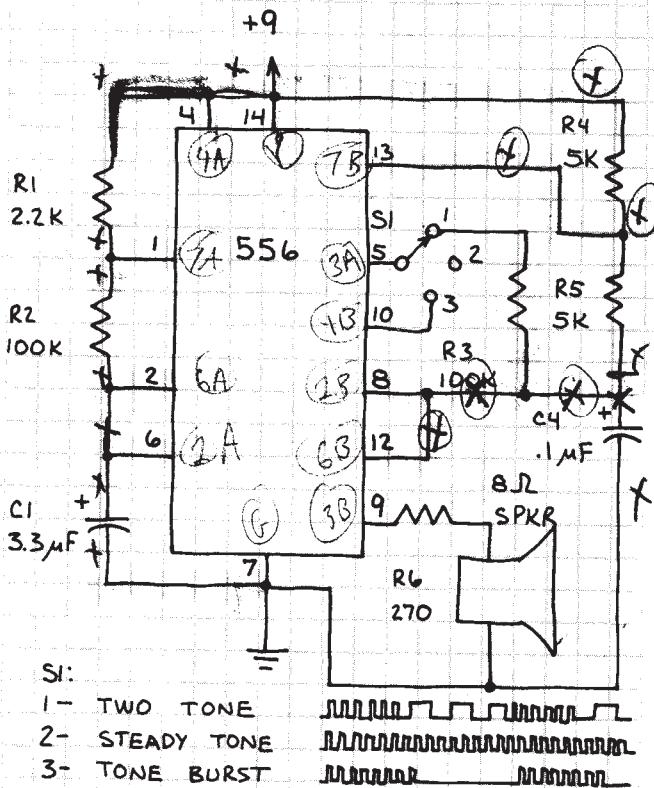


555/556 SCR OUTPUT

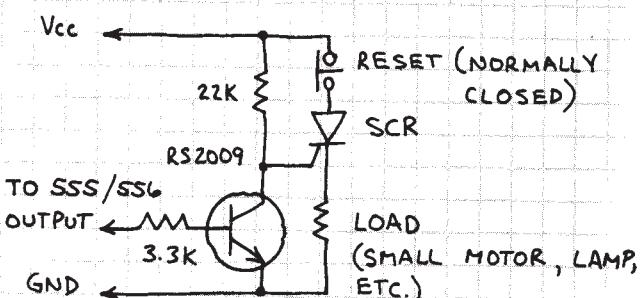

DUAL TIMER (CONTINUED)


556

SOUND SYNTHESIZER

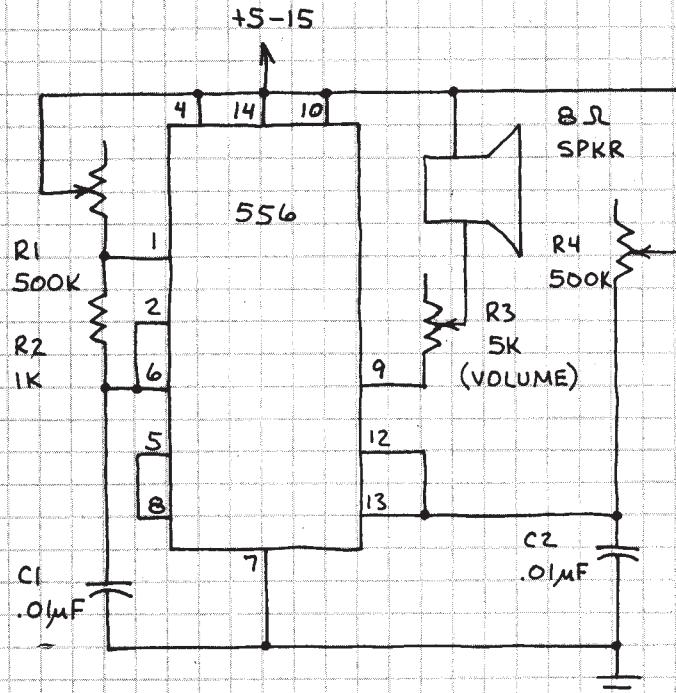


THIS CIRCUIT IS AN OSCILLATOR FOLLOWED BY A FREQUENCY DIVIDER. ADJUST R1 AND R4 FOR VERY UNUSUAL SOUND EFFECTS.

TWO-STAGE TIMER

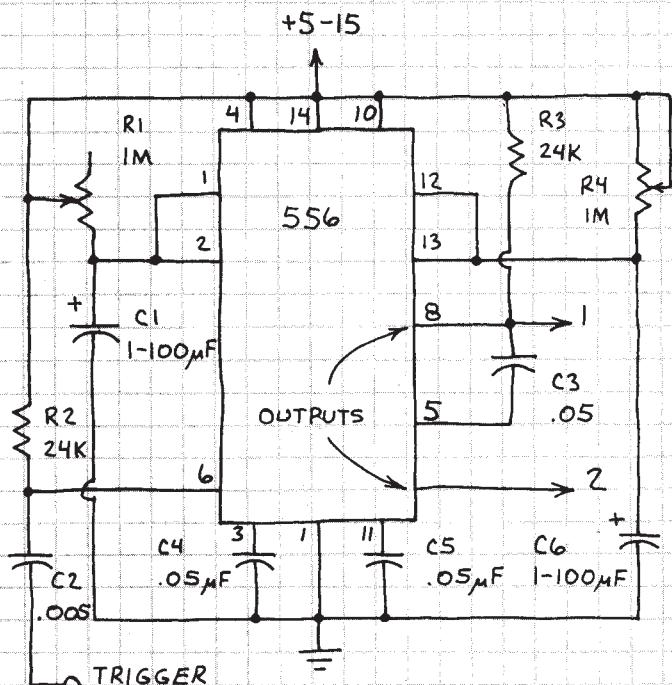

BOTH TIMERS ARE IN ONE-SHOT MODE. GROUNDING THE TRIGGER INPUT INITIATES THE FIRST TIMER'S CYCLE TIME. THE SECOND TIMER'S CYCLE BEGINS AFTER THE FIRST IS COMPLETE.


PROGRAMMABLE 4-STATE TONE GENERATOR

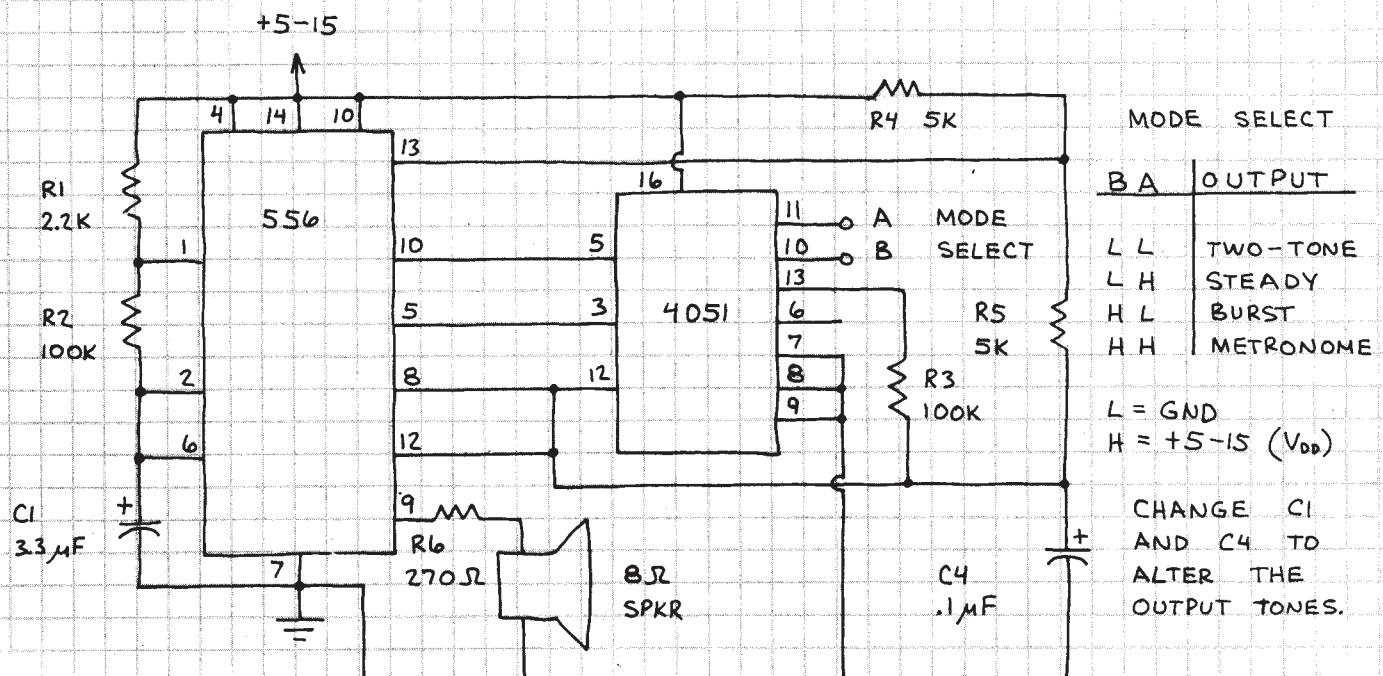

TONE DECODER


567

CONTAINS A PHASE-LOCKED LOOP. PIN 8 GOES LOW WHEN THE INPUT FREQUENCY MATCHES THE CHIP'S CENTER FREQUENCY (f_0). THE LATTER FREQUENCY IS SET BY THE TIMING RESISTOR AND CAPACITOR (R AND C) AND IS $(1.1) \div (RC)$. R SHOULD BE BETWEEN 2K-20K. THE 567 CAN BE ADJUSTED TO DETECT ANY INPUT BETWEEN 0.01 Hz TO 500kHz. NOTE: 1 SECOND OR MORE MAY BE REQUIRED FOR THE 567 TO LOCK ON TO LOW FREQUENCY INPUTS! SEE THIS CHIP'S SPECIFICATIONS FOR MORE INFORMATION.

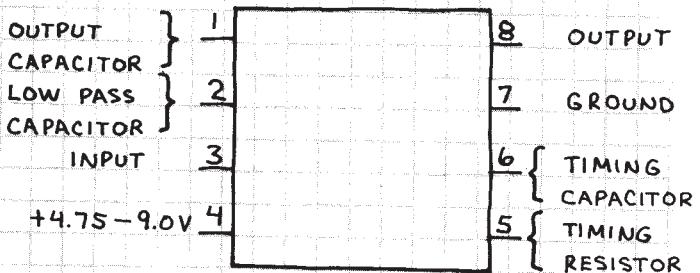


THE VALUE IN MICROFARADS OF THE LOW PASS CAPACITOR SHOULD BE n/f_0 WHERE n RANGES BETWEEN 1300 (FOR UP TO 14% f_0 DETECTION BANDWIDTH) TO 62,000 (UP TO 2% f_0 DETECTION BANDWIDTH). THE OUTPUT CAPACITOR SHOULD HAVE ABOUT TWICE THE CAPACITANCE OF THE LOW PASS FILTER CAPACITOR.

BASIC TONE DETECTOR CIRCUIT

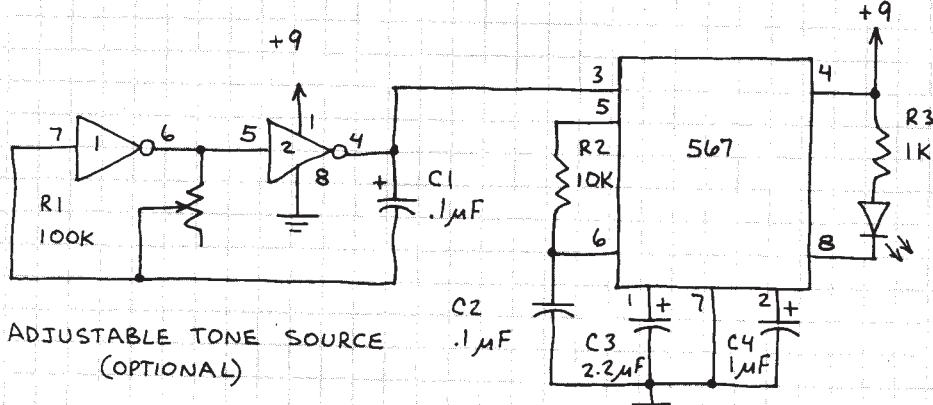

THIS CIRCUIT IS HANDY FOR LEARNING TONE DECODER BASICS. THE 567 PORTION CAN BE USED IN MANY DIFFERENT APPLICATIONS (SEE BELOW). THE PREDICTED f_0 IS 1.1 kHz. THE TEST CIRCUIT f_0 WAS 1.3 kHz.

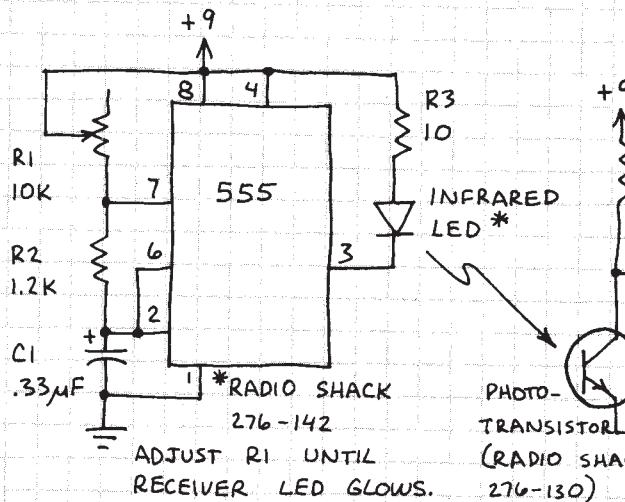INFRARED REMOTE CONTROL SYSTEM TRANSMITTER



ADJUST RI UNTIL RECEIVER LED GLOWS.

(*RADIO SHACK 276-130)

RANGE: SEVERAL INCHES.
USE LENSES TO INCREASE.

OK TO USE 6V RELAY.



120

120

TONE DECODER (CONTINUED)



567

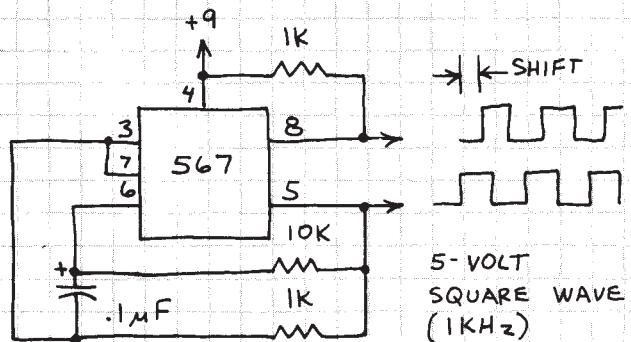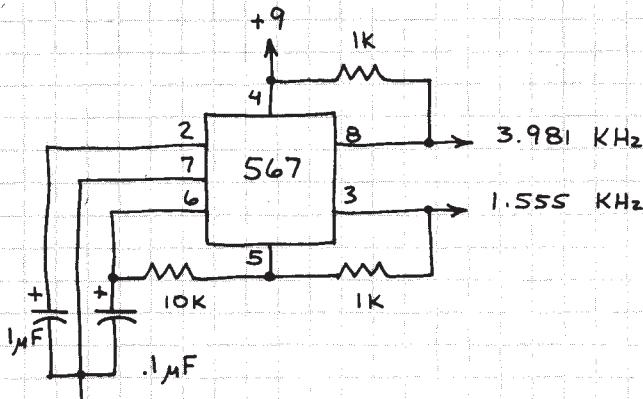2-FREQUENCY OSCILLATOR 2-PHASE OSCILLATOR




LATCHING THE 567 OUTPUT *

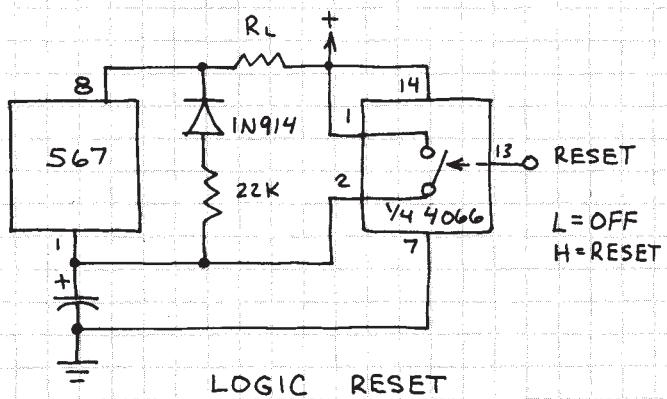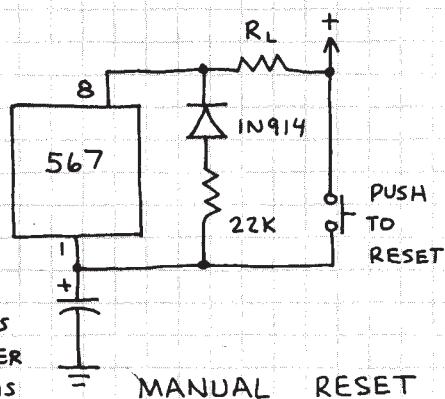BOTH CIRCUITS
SHOW ONLY
THE LATCH
COMPONENTS.
RL IS THE
LOAD (LED,
RELAY, ETC.).




NARROW BAND FREQUENCY DETECTOR

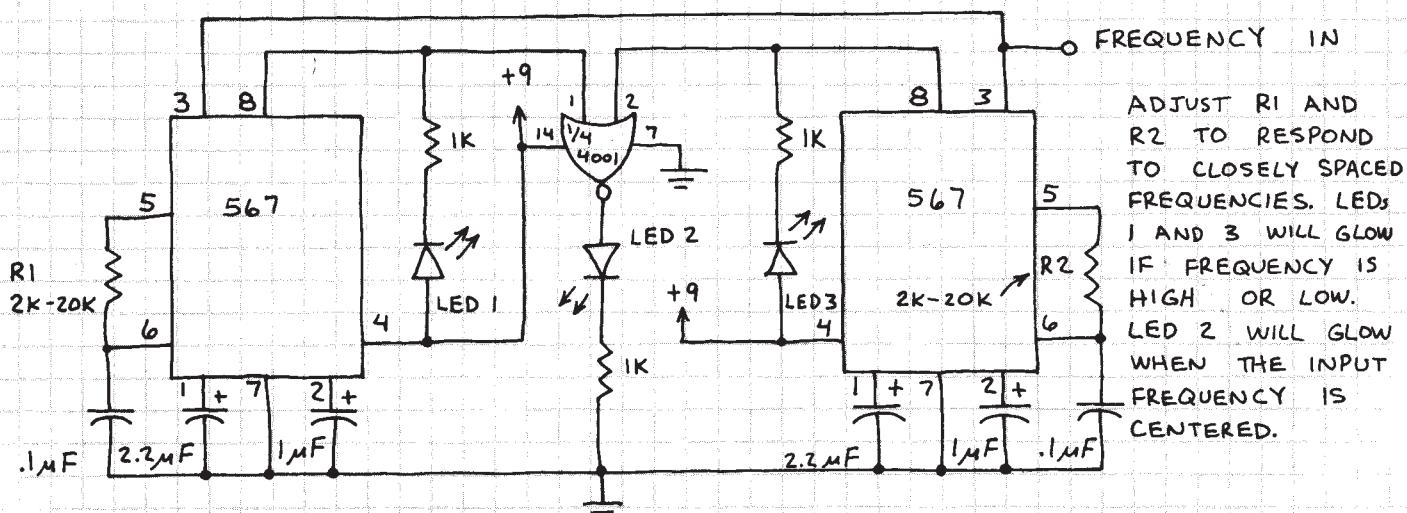



VOLTAGE-TO-FREQUENCY FREQUENCY-TO-VOLTAGE CONVERTER 9400 (276-1790)

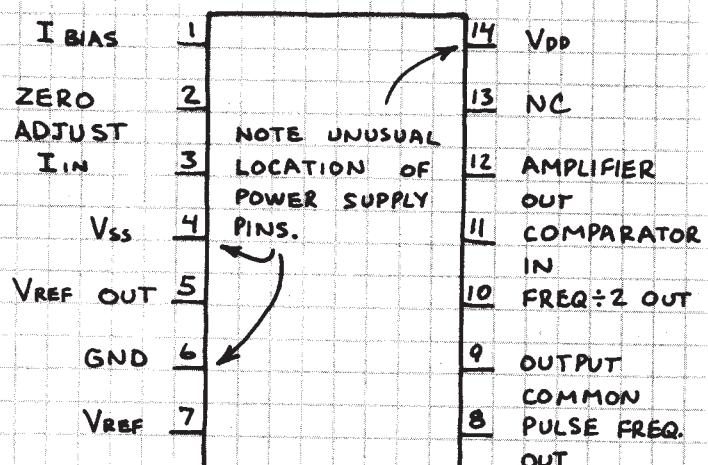IN VOLTAGE-TO-FREQUENCY (V-F) MODE, AN INPUT VOLTAGE WHICH HAS BEEN CONVERTED INTO A CURRENT BY A RESISTOR AT PIN 3 IS TRANSFORMED INTO A PROPORTIONAL FREQUENCY. IN FREQUENCY-TO-VOLTAGE MODE A FREQUENCY AT PIN 11 IS CONVERTED INTO A PROPORTIONAL VOLTAGE. THIS CHIP CAN BE OPERATED FROM A SINGLE OR DUAL POLARITY POWER SUPPLY.



CAUTION: THIS CHIP INCORPORATES BOTH BIPOLAR AND CMOS CIRCUITRY. THEREFORE CMOS HANDLING PRECAUTIONS MUST BE FOLLOWED TO AVOID PERMANENT DAMAGE.

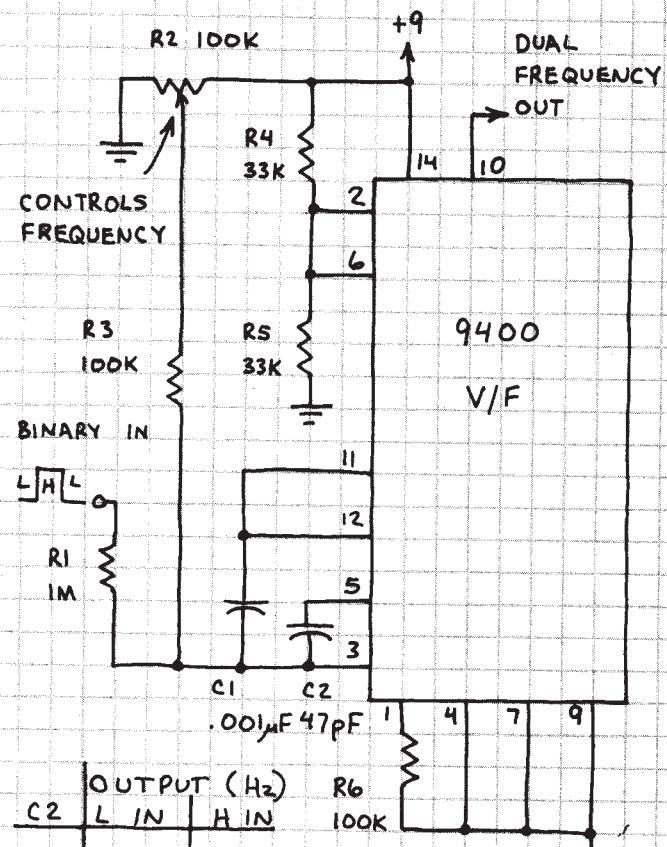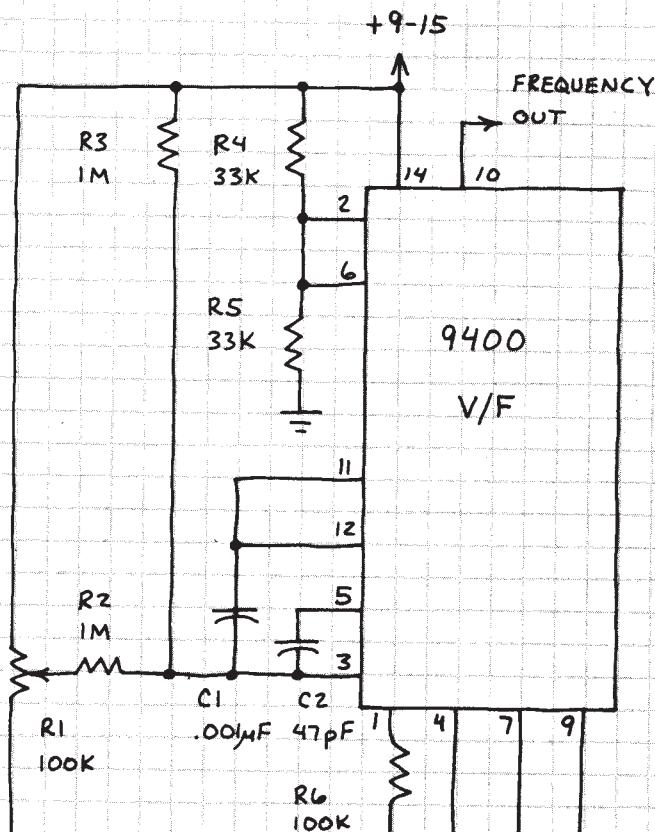
BASIC V/F CONVERTER FSK* DATA TRANSMITTER




VOLTAGE-TO-FREQUENCY FREQUENCY-TO-VOLTAGE CONVERTER 9400

AUDIO FREQUENCY METER

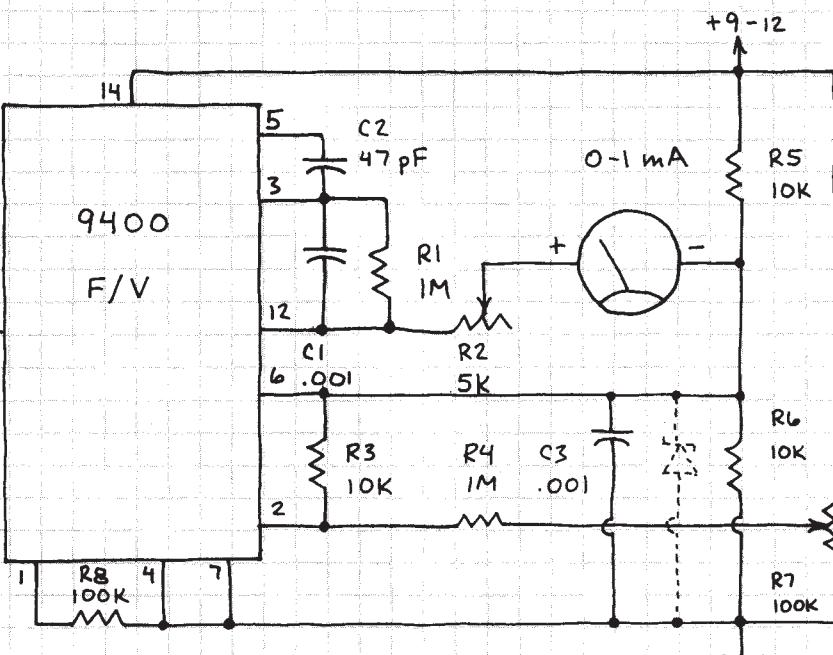INPUT FREQUENCY MUST CROSS 0 VOLT. WORKS UP TO 25 KHz. R7 IS ZERO. ADJUST FOR METER. ADJUST RS TO GIVE MAXIMUM READING AT 25 KHz IN. FOR MORE STABILITY, CHANGE R6 TO 6-V ZENER DIODE.



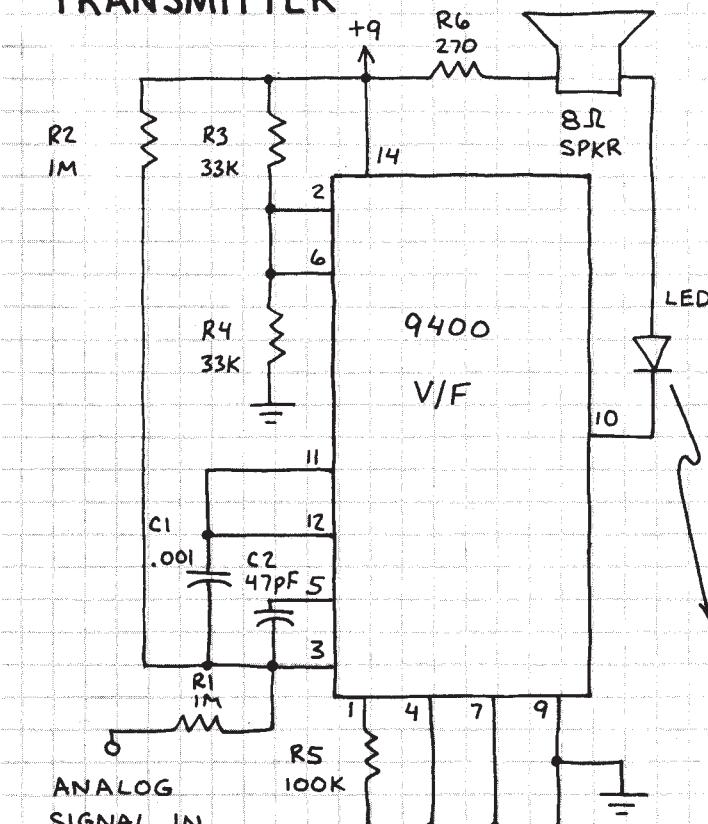ANALOG DATA TRANSMISSION SYSTEM* TRANSMITTER




THE SPKR IS OPTIONAL BUT MAY PROVE HELPFUL DURING INITIAL TESTING. USE AN INFRARED LED (RADIO SHACK 276-142). Q1 CAN BE THE PHOTOTRANSISTOR SUPPLIED WITH THE LED OR RADIO SHACK 276-130. R7 IN THE RECEIVER IS ZERO ADJUST.

VOLTAGE CONTROLLED OSCILLATOR (VCO)

566


VERY STABLE, EASY TO USE TRIANGLE AND SQUARE WAVE OUTPUTS. R_1 AND C_1 CONTROL CENTER FREQUENCY. VOLTAGE AT PIN 5 VARIES FREQUENCY.

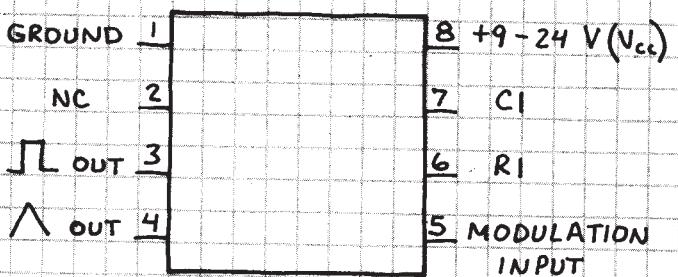IMPORTANT: OUTPUT WAVE DOES NOT FALL TO 0 VOLT! AT 12 VOLTS (PIN 8), FOR EXAMPLE, TRIANGLE OUTPUT CYCLES BETWEEN +4 AND +6 VOLTS. SQUARE OUTPUT CYCLES BETWEEN +6 AND +11.5 VOLTS.




$$\text{CENTER FREQUENCY} = \frac{2(V_{cc} - \text{INPUT VOLTS})}{R_1 C_1 V_{cc}}$$

FUNCTION GENERATOR

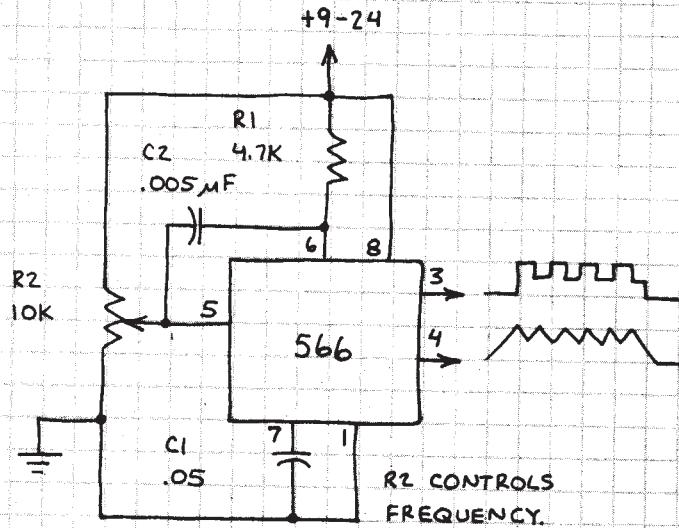

FSK GENERATOR *

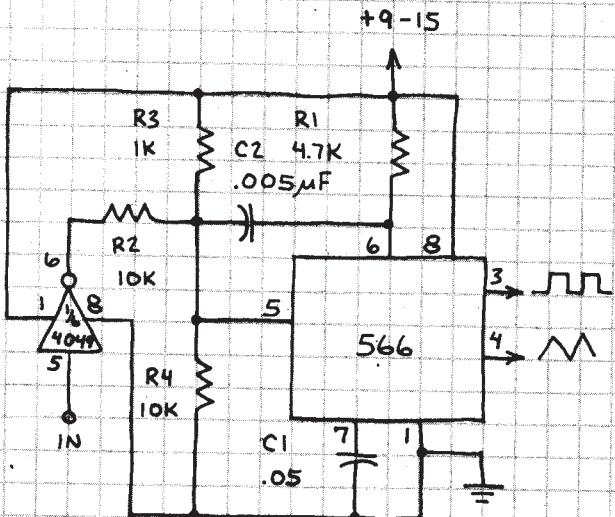

* FSK MEANS FREQUENCY SHIFT KEYING.

IN	OUTPUT
L	1.5 KHz
H	3.0 KHz



USE TO TRANSMIT BINARY DATA OVER TELEPHONE LINES OR STORE BINARY DATA ON MAGNETIC TAPE.
 $V_{cc} = 9$ VOLTS.

TWO-TONE WARBLER

R_1 CONTROLS WARBLE RATE.

R_3 CONTROLS TONE FREQUENCY.


$$1,2 = \frac{1}{3} 4049$$

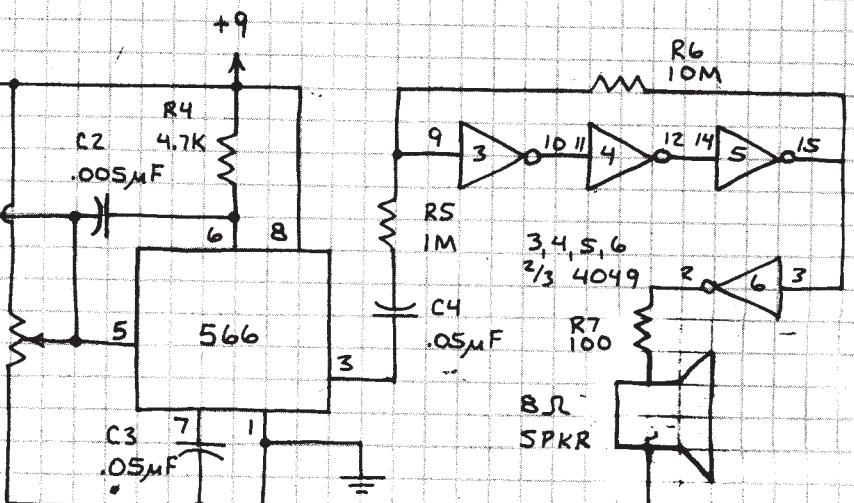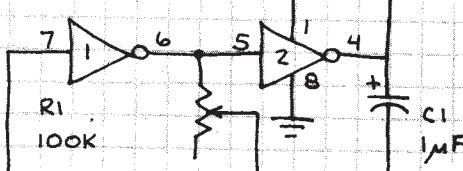


POWER AMPLIFIER

LM386

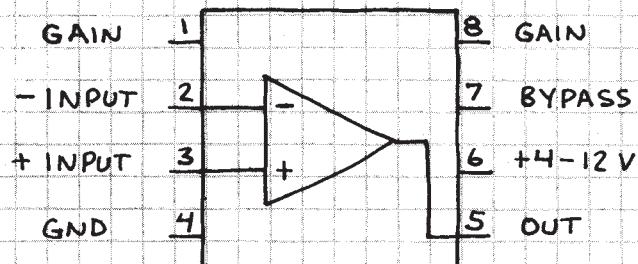DESIGNED MAINLY FOR LOW VOLTAGE AMPLIFICATION. WILL DRIVE DIRECTLY AN 8-OHM SPEAKER. GAIN FIXED AT 20 BUT CAN BE INCREASED TO ANY VALUE UP TO 200.




X20 AMPLIFIER

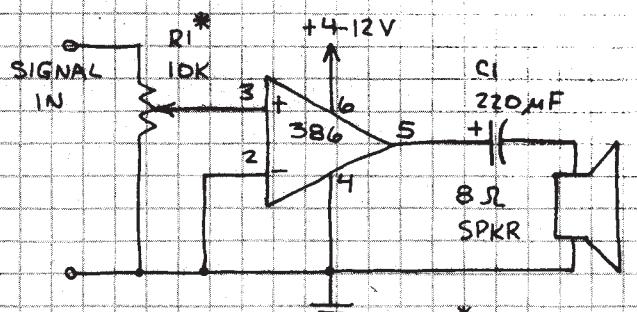


* R1 CONTROLS INPUT SIGNAL LEVEL.


X200 AMPLIFIER

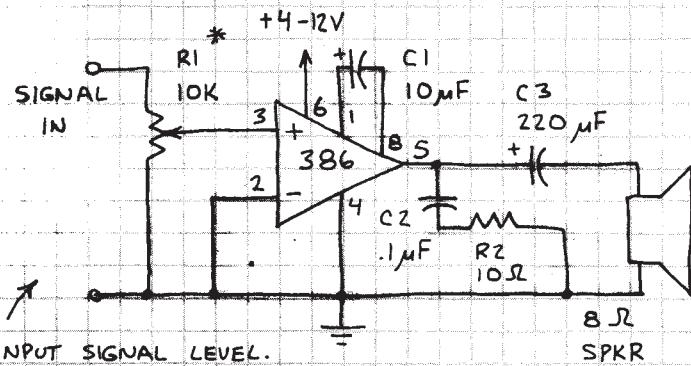

BASS BOOSTER

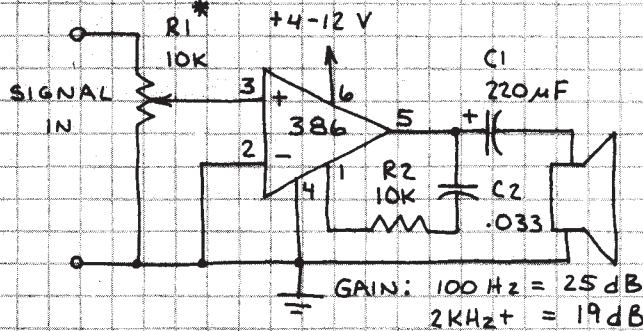


AUDIBLE ALARM

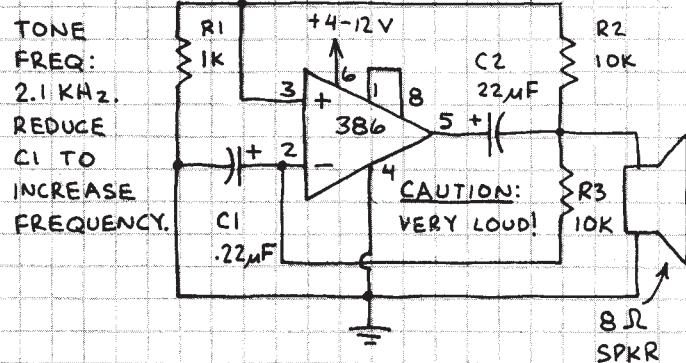

HIGH GAIN POWER AMPLIFIER

CIRCUIT SHOWN IS VERY SENSITIVE LIGHT WAVE RECEIVER. OK TO USE OTHER OP-AMPS FOR THE TL084.

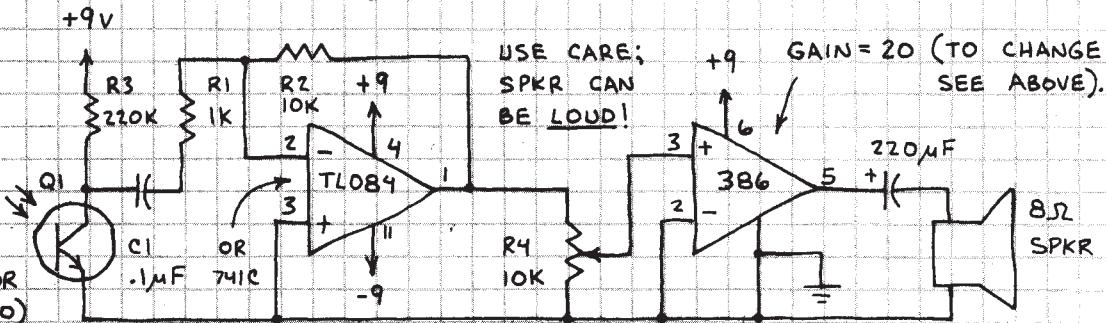
Q1 - PHOTOTRANSISTOR (RADIO SHACK 276-130)




8-WATT POWER AMPLIFIER

LM383 / TDA2002

POWER AMPLIFIER DESIGNED SPECIFICALLY FOR AUTOMOTIVE APPLICATIONS — BUT IDEAL FOR ANY AUDIO AMPLIFICATION SYSTEM. DESIGNED TO DRIVE A 4-OHM LOAD (EQUIVALENT TO A SINGLE 4-OHM SPEAKER OR TWO 8-OHM SPEAKERS IN PARALLEL). THIS CHIP CONTAINS THERMAL SHUTDOWN CIRCUITRY TO PROTECT ITSELF FROM EXCESSIVE LOADING. THIS WILL CAUSE SEVERE DISTORTION DURING OVERLOAD CONDITIONS. YOU MUST USE AN APPROPRIATE HEAT SINK (e.g. RADIO SHACK 276-1363). SPREAD SOME HEAT SINK COMPOUND (276-1372) ON THE LM383 TAB BEFORE ATTACHING THE HEAT SINK.

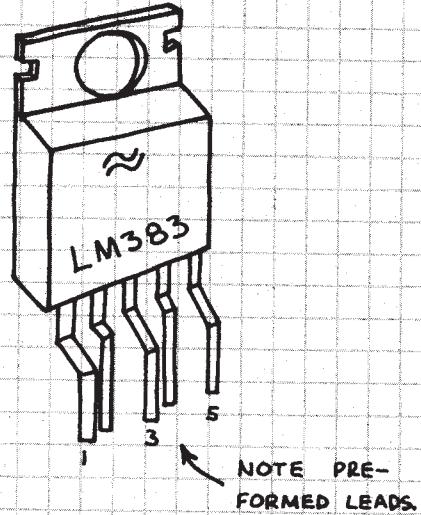


8-WATT AMPLIFIER

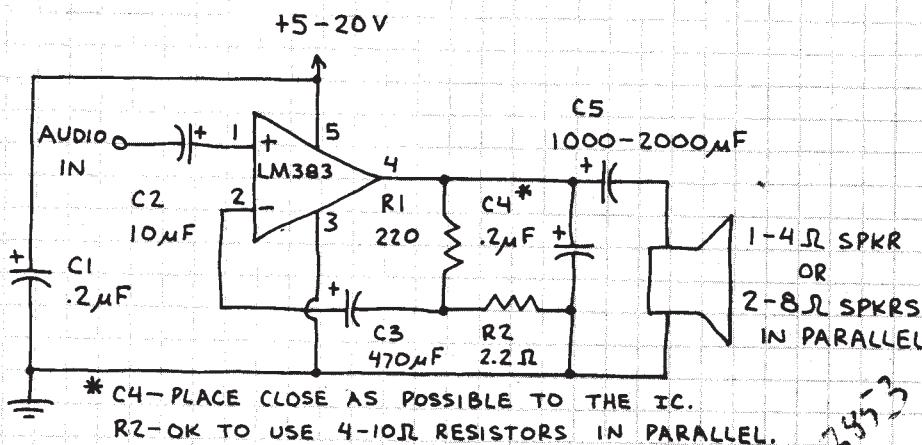

OPERATION:


1. USE HEAT SINK.
2. REDUCE POWER SUPPLY VOLTAGE TO 6-9 VOLTS (AS IN CIRCUIT BELOW) IF SEVERE DISTORTION OCCURS.
3. DON'T APPLY EXCESSIVE INPUT SIGNAL.

16-WATT BRIDGE AMPLIFIER

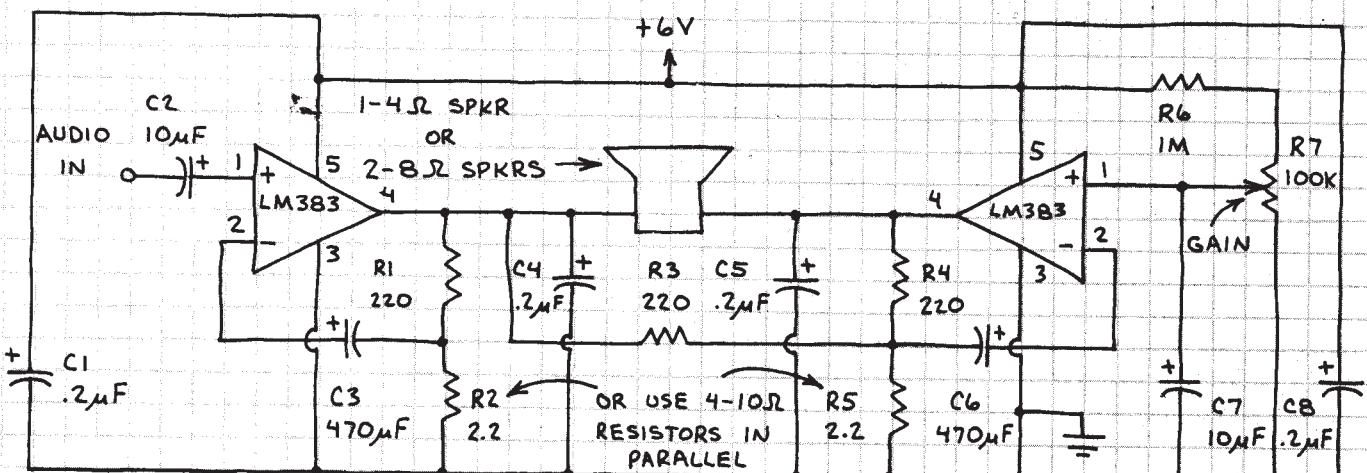


DUAL 2-WATT AMPLIFIER LM1877/LM377

HIGH QUALITY, EASY TO USE POWER AMPLIFIER. IDEAL FOR DO-IT-YOURSELF STEREO, P.A. SYSTEMS, INTERCOMS, ETC. AUTOMATIC THERMAL SHUTDOWN PROTECTS AGAINST OVERHEATING. 70dB CHANNEL SEPARATION MEANS VIRTUALLY NO CROSSTALK. ONLY 3 MICROVOLTS NOISE INPUT. HEATSINKING: UNNECESSARY IN MANY APPLICATIONS SINCE AVERAGE POWER IS USUALLY WELL BELOW BRIEF PEAKS. IN ANY CASE, PINS 3, 4, 5, 10, 11 AND 12 SHOULD BE CONNECTED TOGETHER. IF LOAD EXCEEDS DEVICE RATING, THERMAL SHUTDOWN WILL OCCUR.... AND WILL CAUSE SEVERE DISTORTION. USE HEATSINK (UP TO 10 SQUARE INCHES OF COPPER FOIL ON PC BOARD OR METAL FIN) IF THIS OCCURS.

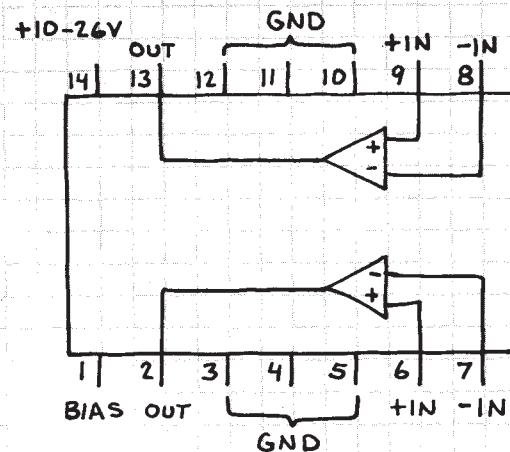


NOTE: GND PINS SHOULD BE HEAT SUNK FOR MAXIMUM POWER.


STEREO AMPLIFIER

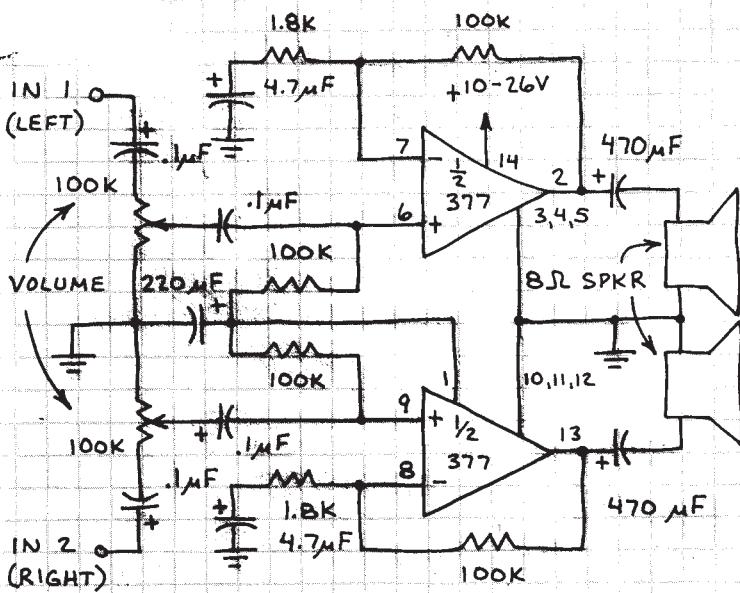

4-WATT AMPLIFIER

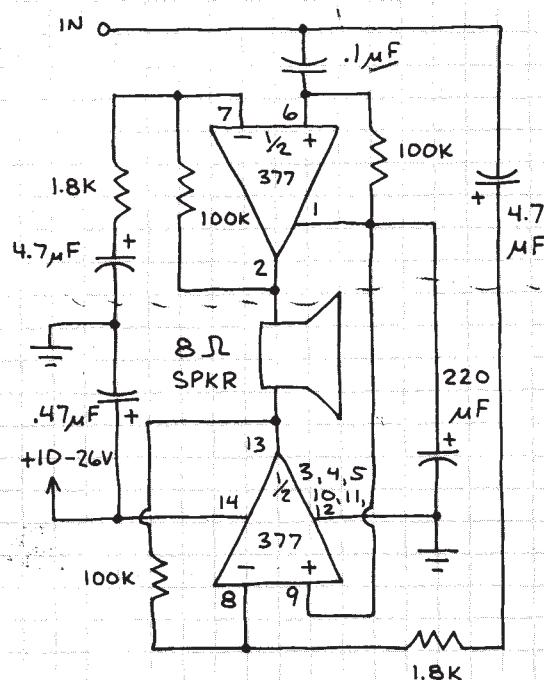

PUBLIC ADDRESS SYSTEM

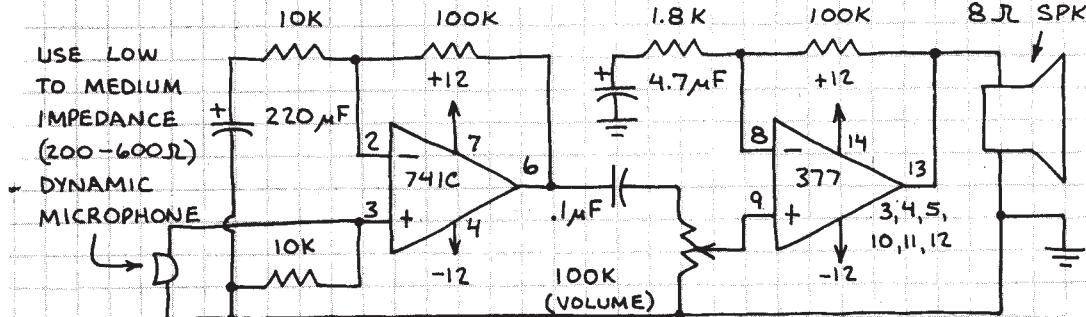

THIS CIRCUIT WORKS WELL.
NOTE FEWER PARTS IN
LM1877 / LM377
STAGE... THANKS
TO SPLIT POWER
SUPPLY.

TEMPERATURE SENSOR AND ADJUSTABLE CURRENT SOURCE


LM334 (276-1734)

VERSATILE 3-LEAD COMPONENT THAT LOOKS MORE LIKE A TRANSISTOR THAN AN IC. CAN BE USED AS A TEMPERATURE SENSOR, CURRENT SOURCE FOR LEDs AND OTHER COMPONENTS OR CIRCUITS, VOLTAGE REFERENCE, ETC.




1 = R
2 = +V
3 = -V (GND)


BASIC THERMOMETERS BASIC CURRENT SOURCE

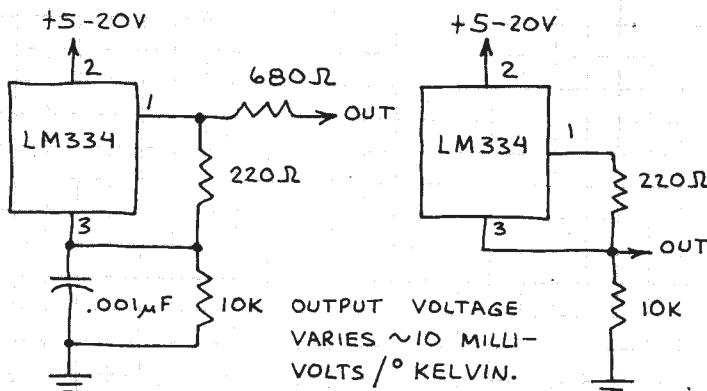


I_{SET} =
CURRENT
INTO PIN 2.

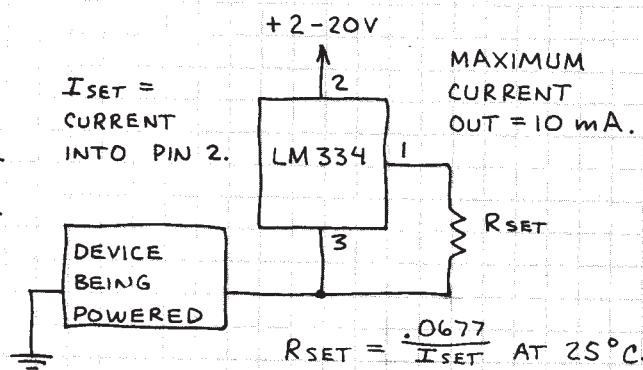


VOLTAGE REFERENCE

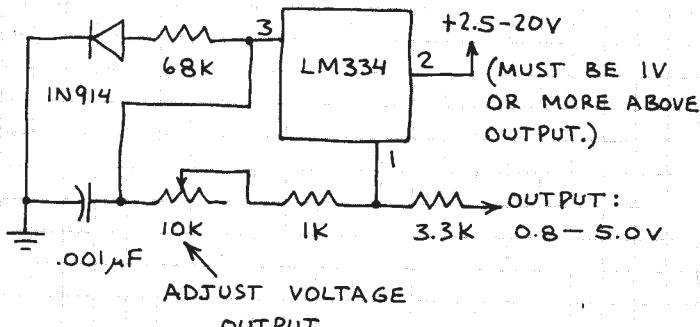


CALIBRATED LED

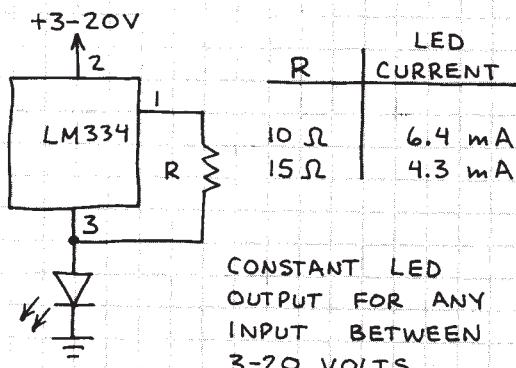

RAMP GENERATOR

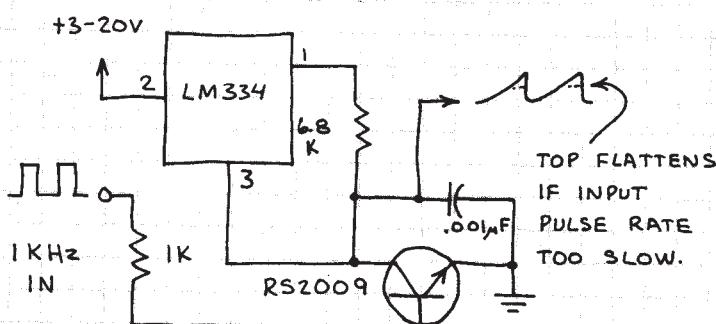

LIGHT METER

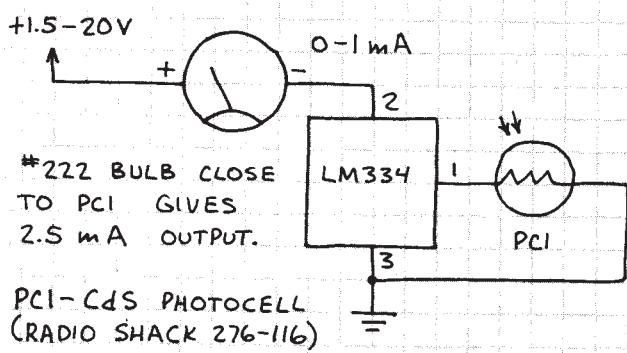

RADIO SHACK  A DIVISION OF TANDY CORPORATION

U.S.A.: FORT WORTH, TEXAS 76102
CANADA: BARRIE, ONTARIO, CANADA L4M 4W5

TANDY CORPORATION

AUSTRALIA

280-316 VICTORIA ROAD
RYDALMERE, N.S.W. 2116

BELGIUM

PARC INDUSTRIEL DE NANINNE
5140 NANINNE

U.K.

BILSTON ROAD
WEDNESBURY, STAFFS WS10 7JN

PRINTED IN U.S.A.